 


## Major Combinational Automatic Test-Pattern Generation Algorithms

- Definitions
- D-Algorithm (Roth) -- 1966
  - *D-cubes*
  - Bridging faults
  - Logic gate function change faults
- PODEM (Goel) -- 1981
  - *X-Path-Check*
  - *Backtracing*
- Summary

## Forward Implication




- Results in logic gate inputs that are significantly labeled so that output is uniquely determined
- AND gate forward implication table:

	$\bar{D}$	0	1	X	$\bar{D}$	$\bar{D}$
$\bar{D}$	0	0	0	0	0	0
1	0	1	X	$\bar{D}$	$\bar{D}$	
X	0	X	X	X	X	
$\bar{D}$	0	$\bar{D}$	X	$\bar{D}$	0	
$\bar{D}$	0	$\bar{D}$	X	0	$\bar{D}$	

 
## Backward Implication

- Unique determination of all gate inputs when the gate output and some of the inputs are given


 
## Implication Stack


- Push-down stack. Records:
  - Each signal set in circuit by ATPG
  - Whether alternate signal value already tried
  - Portion of binary search tree already searched



## Implication Stack after Backtrack


Signal	Value	Alternative tried
E	1	NO
B	0	YES
F	0	YES

 - ..... Unexplored
- Present Assignment
- Searched and Infeasible


 
## Objectives and Backtracing of ATPG Algorithm

- **Objective** – desired signal value goal for ATPG
  - Guides it away from Infeasible/hard solutions
- **Backtrace** – Determines which primary input and value to set to achieve objective
  - Use testability measures



## Branch-and-Bound Search

- Efficiently searches binary search tree
- **Branching** – At each tree level, selects which input variable to set to what value
- **Bounding** – Avoids exploring large tree portions by artificially restricting search decision choices
  - Complete exploration is impractical
  - Uses *heuristics*

## D-Algorithm -- Roth IBM (1966)

- Fundamental concepts invented:
  - First complete ATPG algorithm
  - *D-Cube*
  - *D-Calculus*
  - *Implications* – forward and backward
  - *Implication stack*
  - *Backtrack*
  - Test Search Space

## Singular Cover Example

- Minimal set of logic signal assignments to show *essential prime Implicants* of *Karnaugh map*



Gate	Inputs	Output	Gate	Inputs	Output
AND	A B	d	NOR	d e	F
1	0 X	0	1	1 X	0
2	X 0	0	2	X 1	0
3	1 1	1	3	0 0	1

## D-Cube

- Collapsed truth table entry to characterize logic
- Use Roth's 5-valued algebra
- Can change all *D*'s to  $\overline{D}$ 's and  $\overline{D}$ 's to *D*'s (do both)
- AND gate:

	A	B	d
Rows 1 & 3	D	1	D
Reverse inputs	1	D	D
And two cubes	$\overline{D}$	$\overline{D}$	$\overline{D}$
Interchange D and $\overline{D}$	D	D	$\overline{D}$
	1	D	$\overline{D}$
	$\overline{D}$	1	$\overline{D}$

## D-Cube Operation of D-Intersection

- $\psi$  - undefined (same as  $\phi$ )
- $\mu$  or  $\lambda$  - requires inversion of *D* and  $\overline{D}$
- D-Intersection:**
  - $0 \cap 0 = 0 \cap X = X \cap 0 = 0$
  - $1 \cap 1 = 1 \cap X = X \cap 1 = 1$
  - $X \cap X = X$

$\cap$	0	1	X	D	$\overline{D}$
0	0	$\phi$	0	$\psi$	$\psi$
1	$\phi$	1	1	$\psi$	$\psi$
X	0	1	X	D	$\overline{D}$
$\overline{D}$	$\psi$	$\psi$	$\overline{D}$	$\mu$	$\lambda$
D	$\psi$	$\psi$	D	$\lambda$	$\mu$

- D-containment** - Cube *a* contains Cube *b* if *b* is a subset of *a*


## Primitive D-Cube of Failure

- Models circuit faults:
  - Stuck-at-0*
  - Stuck-at-1*
  - Bridging fault* (short circuit)
  - Arbitrary change in logic function
- AND Output sa0: "1 1  $\overline{D}$ "
- AND Output sa1: "0 X  $\overline{D}$ "  
"X 0  $\overline{D}$ "
- Wire sa0: "D"
- Propagation D-cube** - models conditions under which fault effect propagates through gate

## Implication Procedure

1. Model fault with appropriate *primitive D-cube of failure* (PDF)
2. Select *propagation D-cubes* to propagate fault effect to a circuit output (*D-drive* procedure)
3. Select *singular cover* cubes to justify internal circuit signals (*Consistency* procedure)
  - Put signal assignments in *test cube*
  - Regrettably, cubes are selected very arbitrarily by D-ALG

## Bridging Fault Circuit

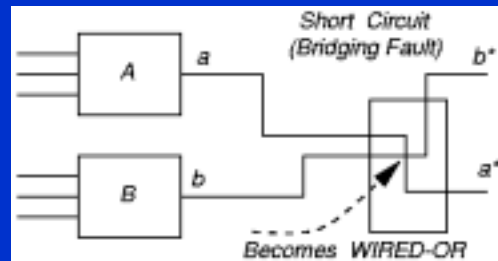


## Construction of Primitive D-Cubes of Failure

1. Make cube set  $\alpha 1$  when good machine output is 1 and set  $\alpha 0$  when good machine output is 0
2. Make cube set  $\beta 1$  when failing machine output is 1 and  $\beta 0$  when it is 0
3. Change  $\alpha 1$  outputs to 0 and D-Intersect each cube with every  $\beta 0$ . If intersection works, change output of cube to D
4. Change  $\alpha 0$  outputs to 1 and D-Intersect each cube with every  $\beta 1$ . If intersection works, change output of cube to D

## Bridging Fault D-Cubes of Failure

Cube-set	<i>a</i>	<i>b</i>	<i>a*</i>	<i>b*</i>	Cube-set	<i>a</i>	<i>b</i>	<i>a*</i>	<i>b*</i>
$\alpha 0$	0	X	0	X	PDFs for Bridging fault	1	0	<u>1</u>	<u>D</u>
	X	0	X	0		0	1	D	1
$\alpha 1$	1	X	1	X					
	X	1	X	1					
$\beta 0$	0	0	0	0					
$\beta 1$	X	1	1	1					
	1	X	1	1					
 
## Gate Function Change D-Cube of Failure



Cube-set	a	b	c	Cube-set	a	b	c
$\alpha 0$	0	X	0	PDFs for AND changing to OR	0	1	$\overline{D}$
	X	0	0				$\overline{D}$
$\alpha 1$	1	1	1				$\overline{D}$
$\beta 0$	0	0	0				$\overline{D}$
$\beta 1$	1	X	1				
	X	1	1				

## D-Algorithm – Top Level

1. Number all circuit lines in increasing level order from PIs to POs;
2. Select a primitive D-cube of the fault to be the *test cube*;
  - Put logic outputs with inputs labeled as  $D$  ( $\overline{D}$ ) onto the *D-frontier*;
3. *D-drive* ();
4. *Consistency* ();
5. return ();

## D-Algorithm – D-drive

```

while (untried fault effects on D-frontier)
  select next untried D-frontier gate for propagation;
  while (untried fault effect fanouts exist)
    select next untried fault effect fanout;
    generate next untried propagation D-cube;
    D-Intersect selected cube with test cube;
    if (Intersection fails or is undefined) continue;
    if (all propagation D-cubes tried & failed) break;
    if (Intersection succeeded)
      add propagation D-cube to test cube -- recreate D-frontier;
      Find all forward & backward implications of assignment;
      save D-frontier, algorithm state, test cube, fanouts, fault;
      break;
    else if (Intersection fails &  $D$  and  $\overline{D}$  in test cube) Backtrack ();
    else if (Intersection fails) break;
  if (all fault effects unpropagatable) Backtrack ();
    
```

## D-Algorithm -- Consistency


```

g = coordinates of test cube with 1's & 0's;
if (g is only PIs) fault testable & stop;
for (each unjustified signal in g)
  Select highest # unjustified signal z in g, not a PI;
  if (inputs to gate z are both D and  $\overline{D}$ ) break;
  while (untried singular covers of gate z)
    select next untried singular cover;
    if (no more singular covers)
      if (no more stack choices) fault untestable & stop;
      else if (untried alternatives in Consistency)
        pop implication stack -- try alternate assignment;
      else
        Backtrack ();
        D-drive ();
    if (singular cover D-Intersects with z) delete z from g, add
    inputs to singular cover to g, find all forward and
    backward implications of new assignment, and break;
  if (Intersection fails) mark singular cover as failed;
    
```

## Backtrack

if (PO exists with fault effect) *Consistency* ();  
 else pop prior implication stack setting to try  
 alternate assignment;  
 If (no untried choices in Implication stack)  
   *fault untestable & stop;*  
 else return;

## Circuit Example 7.1 and Truth Table

 

Inputs			Output
a	b	c	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

## Singular Cover & D-Cubes

A	B	C	d	e	F
1	1		1		
0			0		
	0	1		1	
	1	0		1	
			1	1	1
			0	1	0
D	D		D		
1	D		D		
D	D	1	D		
D	D	D	D		
D	D	D	D	1	1
D	D	D	D	0	0
D	D	D	D	D	D

■ *Singular cover* – Used for justifying lines


■ *Propagation D-cubes* – Conditions under which difference between good/faulting machines propagates

## Steps for Fault *d* sa0

Step	A	B	C	d	e	F	Cube type
1	1	1		D			PDF of AND gate
2				D	0	$\overline{D}$	Prop. D-cube for NOR
3	1	1		0			Sing. Cover of NAND


## Example 7.2 Fault A sa0

- Step 1 - *D-Drive* - Set  $A = 1$

 


## Step 2 -- Example 7.2

- Step 2 - *D-Drive* - Set  $f = 0$

 


## Step 3 -- Example 7.2

- Step 3 - *D-Drive* - Set  $k = 1$

 


## Step 4 -- Example 7.2

- Step 4 - *Consistency* - Set  $g = 1$

 

 
## Step 5 -- Example 7.2

- Step 5 - *Consistency* -  $f = 0$  Already set



 
## Step 6 -- Example 7.2

- Step 6 - *Consistency* - Set  $c = 0$ , Set  $e = 0$


 
## D-Chain Dies -- Example 7.2


- Step 7 - *Consistency* - Set  $B = 0$
- D-Chain* dies



- Test cube:  $A, B, C, D, e, f, g, h, k, L$

## Example 7.3 - Fault sa1


- Primitive D-cube of Failure

 




### Example 7.3 – Step 2 s sa1

- Propagation D-cube for  $v$

 


### Example 7.3 – Step 2 s sa1

- Forward & Backward Implications

 

 
### Example 7.3 – Step 3 s sa1

- Propagation D-cube for  $Z$  – test found!




### Example 7.3 – Fault u sa1

- Primitive D-cube of Failure

 


## Example 7.3 – Step 2 $u sa1$

- Propagation D-cube for  $v$

 

## Example 7.3 – Step 2 $u sa1$

- Forward and backward Implications

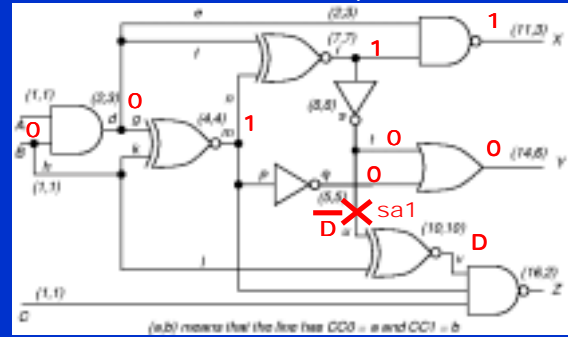


## Inconsistent

- $d = 0$  and  $m = 1$  cannot justify  $r = 1$  (equivalence)
  - Backtrack
  - Remove  $B = 0$  assignment

 
## Example 7.3 – Backtrack

- Need alternate propagation D-cube for  $v$




### Example 7.3 – Step 3 $u\ sa1$

- Propagation D-cube for  $v$

 


### Example 7.3 – Step 4 $u\ sa1$

- Propagation D-cube for  $Z$

 
 
### Example 7.3 – Step 4 $u\ sa1$

- Propagation D-cube for  $Z$  and implications



## PODEM -- Goel IBM (1981)

- New concepts introduced:
  - Expand binary decision tree only around primary inputs
  - Use *X-PATH-CHECK* to test whether *D-frontier* still there
  - *Objectives* -- bring ATPG closer to propagating  $D$  ( $\bar{D}$ ) to PO
  - *Backtracing*

## Motivation


- IBM introduced semiconductor DRAM memory into its mainframes – late 1970's
- Memory had error correction and translation circuits – improved reliability
  - D-ALG unable to test these circuits
    - Search too undirected
    - Large XOR-gate trees
    - Must set all external inputs to define output
  - Needed a better ATPG tool

## PODEM High-Level Flow

1. Assign binary value to unassigned PI
2. Determine Implications of all PIs
3. Test Generated? If so, **done**.
4. Test possible with more assigned PIs? If maybe, go to **Step 1**
5. Is there untried combination of values on assigned PIs? If not, **exit: untestable fault**
6. Set untried combination of values on assigned PIs using objectives and backtrace. Then, go to **Step 2**

 
## Example 7.3 Again

- Select path **s - Y** for fault propagation



 
## Example 7.3 -- Step 2 s sa1

- Initial objective: Set **r** to 1 to sensitize fault




### Example 7.3 -- Step 3 s sa1

- Backtrace from  $r$

 


### Example 7.3 -- Step 4 s sa1

- Set  $A = 0$  in Implication stack

 


### Example 7.3 -- Step 5 s sa1

- Forward Implications:  $d = 0, X = 1$

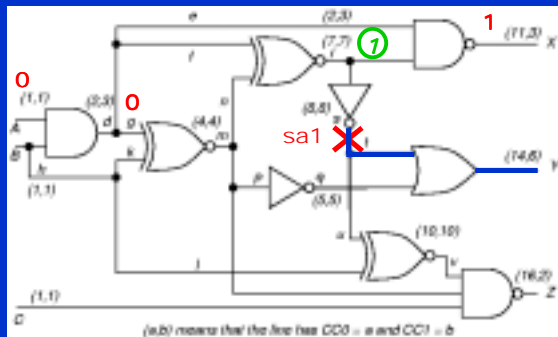


### Example 7.3 -- Step 6 s sa1

- Initial objective: set  $r$  to 1

 


### Example 7.3 -- Step 7 s sa1

- Backtrace from  $r$  again

 

 
### Example 7.3 -- Step 8 s sa1

- Set  $B$  to 1. Implications in stack:  $A = 0, B = 1$



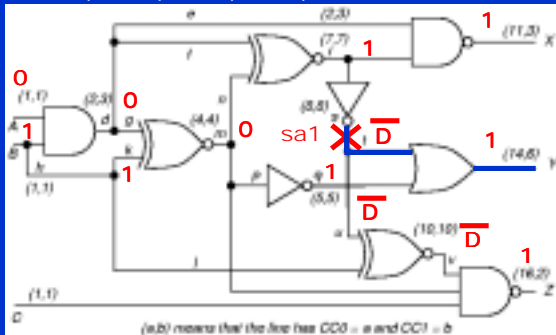
### Example 7.3 -- Step 9 s sa1

- Forward Implications:  $k = 1, m = 0, r = 1, q = 1, Y = 1, s = \bar{D}, u = \bar{D}, v = \bar{D}, Z = 1$



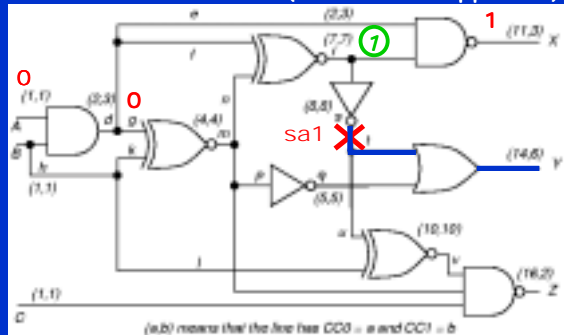
### Backtrack -- Step 10 s sa1

- $X$ -PATH-CHECK shows paths  $s - Y$  and  $s - u - v - Z$  blocked ( $D$ -frontier disappeared)




## Step 11 -- s sa1

- Set  $B = 0$  (alternate assignment)

 

 
## Backtrack -- s sa1

- Forward implications:  $d = 0, X = 1, m = 1, r = 0, s = 1, q = 0, Y = 1, v = 0, Z = 1$ . Fault not sensitized.




## Step 13 -- s sa1

- Set  $A = 1$  (alternate assignment)

 


## Step 14 -- s sa1

- Backtrace from  $r$  again

 

 
## Step 15 -- s sa1

- Set  $B = 0$ . Implications in stack:  $A = 1, B = 0$



 
## Backtrack -- s sa1

- Forward Implications:  $d = 0, X = 1, m = 1, r = 0$ . Conflict: fault not sensitized. Backtrack




## Step 17 -- s sa1

- Set  $B = 1$  (alternate assignment)

 
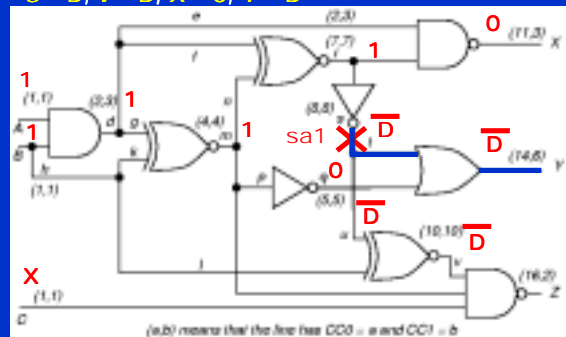
## Fault Tested -- Step 18 s sa1

- Forward Implications:  $d = 1, m = 1, r = 1, q = 0, s = D, v = D, X = 0, Y = D$





## Backtrace ( $s, v_s$ ) Pseudo-Code

```

 $v = v_s$ ;
while ( $s$  is a gate output)
  if ( $s$  is NAND or INVERTER or NOR)  $v = \overline{v}$ ;
  if (objective requires setting all inputs)
    select unassigned input  $a$  of  $s$  with
      hardest controllability to value  $v$ ;
  else
    select unassigned input  $a$  of  $s$  with
      easiest controllability to value  $v$ ;
   $s = a$ ;
return ( $s, v$ ) /* Gate and value to be assigned */;

```

## Objective Selection Code

```

if (gate  $g$  is unassigned) return ( $g, \overline{v}$ );
select a gate  $P$  from the D-frontier;
select an unassigned input  $I$  of  $P$ ;
if (gate  $g$  has controlling value)
   $c =$  controlling input value of  $g$ ;
else if (0 value easier to get at input of
  XOR/EQUIV gate)
   $c = 1$ ;
else  $c = 0$ ;
return ( $I, \overline{c}$ );

```

## PODEM Algorithm

```

while (no fault effect at POs)
  if ( $xpathcheck$  (D-frontier))
    ( $I, v_I$ ) =  $Objective$  ( $fault, v_{fault}$ );
    ( $pI, v_{pI}$ ) =  $Backtrace$  ( $I, v_I$ );
     $Imply$  ( $pI, v_{pI}$ );
    if ( $PODEM$  ( $fault, v_{fault}$ ) == SUCCESS) return (SUCCESS);
    ( $pI, v_{pI}$ ) =  $Backtrack$  ();
     $Imply$  ( $pI, v_{pI}$ );
    if ( $PODEM$  ( $fault, v_{fault}$ ) == SUCCESS) return
      (SUCCESS);
     $Imply$  ( $pI, *X*$ );
    return (FAILURE);
  else if (implication stack exhausted)
    return (FAILURE);
  else  $Backtrack$  ();
return (SUCCESS);

```

## Summary

- D-ALG – First complete ATPG algorithm
  - *D-Cube*
  - *D-Calculus*
  - *Implications* – forward and backward
  - *Implication stack*
  - *Backup*
- PODEM
  - Expand decision tree only around PIs
  - Use *X-PATH-CHECK* to see if *D-frontier* exists
  - *Objectives* -- bring ATPG closer to getting  $D(\overline{D})$  to PO
  - *Backtracing*