

1. In a lab, we are measuring a periodic voltage signal with period 0.1ms.

But: 60 Hz interference from wiring in the lab walls is causing problems.

Q: Can we reduce interference by 99% using a 1-capacitor filter? How?

Specs: Source: Thevenin resistance=0; **Load:** input resistance=100Ω.

A: Reduce by 99% $\Leftrightarrow 40dB \Leftrightarrow 2$ decades. $H(j\omega) = \frac{R}{\frac{1}{j\omega C} + R} = \frac{j\omega RC}{1 + j\omega RC}$.

Zero at origin \leftrightarrow initial slope 20 dB/decade; **Pole** at $\omega = 1/(RC)$.

Use: -40 dB at 60Hz \rightarrow corner freq=6kHz=1/(2π(100Ω)C) $\rightarrow C = 0.27\mu F$.

Insert: C between source and load; measure output across load resistance.

Then: Fundamental and harmonics of periodic signal are hardly affected.

2. **Tuning AM radio:** Tune in 800 kHz, reject 750 kHz by 90%.

Antenna: Antenna current=(50μA) cos(2π800t) + (50μA) cos(2π750t) (t in ms).

Radio: Parallel RLC: L = 39.6μH (loopstick antenna); C=variable; R=load.

RLC: Parallel RLC admittance: $Y = G + j\omega C + \frac{1}{j\omega L} = G + j(\omega C - \frac{1}{\omega L})$.

800 kHz: Parallel RLC *resonating*: $Y = G$. **750 kHz:** Off resonant peak.

Tune: $2\pi(800kHz) = 1/\sqrt{(39.6\mu H)C} \rightarrow C=1$ nF. Adjust variable C to 1 nF.

750 kHz: Set $|Y| = \sqrt{G^2 + (\omega C - \frac{1}{\omega L})^2} = 10G$ (down 90%) at $\omega = 2\pi(750kHz)$.

since: Larger Y \rightarrow smaller voltage across load R for the given antenna current.

Soln: L = 39.6μH given; C varied to 1 nF to tune in 800 kHz. Get R = 15kΩ.

So: Radio amplifier should have input resistance of 15kΩ (is reasonable).

3. Series RLC has gain shown. **Plot is 3 lines through these points:**

3a. What is the form of $H(j\omega)$? (**0 db@w=0.1**); (**0 db@w=1**);

3b. What element(s) are tapped? (**-20 db@w=10**); (**-60 db@w=100**);

3c. R = 11Ω. What are L and C? (**-100 db@w=1000**); etc.

3a. $H(j\omega) = 10/[(j\omega + 1)(j\omega + 10)]$ since: DC gain=1; Poles at $\omega = 1; 10$.

3b. DC gain=1 \rightarrow must tap C; Hi-frequency gain $\simeq \frac{1}{\omega^2} \rightarrow$ must tap *only* C.

3c. $H(j\omega) = \frac{1/(j\omega C)}{R + j\omega L + \frac{1}{j\omega C}} = \frac{1}{(j\omega)^2(LC) + j\omega(RC) + 1} = \frac{1}{(j\omega)^2(0.1) + j\omega(1.1) + 1}$.

These must be equal. So we can equate coefficients of powers of $j\omega$:

$\omega^2 \rightarrow LC = 0.1; \omega \rightarrow RC = 1.1 \rightarrow L = 1H; C = 0.1F$ since R = 11Ω.

Note: We can ignore phase response here, since we know we have series RLC.

Phase is important in identifying unknowns in more complex problems.

Given: *Non-ideal* (finite gain) op-amp connected as an *inverting amplifier*.

Goal: Show (gain)(bandwidth)=constant (general property of amplifiers).

Note: *Lab Book* notes this in Lab Expt 4, p.9 (Post-Lab) and Unit 4, p.1.

Fact: Amplifiers tend to have a *midband* range of freqs in which gain=constant.

But: Gain rolls off for frequencies below and above this midband range.

See: *Additional Course Notes* Fig. 1.10 on p.15 and *Lab Book* Unit 3, p.9.

DEF: At *Half-power=3 dB* frequencies, gain is down 3 dB from midband gain.

Recall: For op-amp with finite open-loop gain A , inverting amplifier gain is:

$$\frac{V_O}{V_I} = -\frac{R_F}{R_I} \frac{1}{1 + \frac{1}{A}(1 + \frac{R_F}{R_I})} \simeq -\frac{R_F}{R_I} j$$
 as $A \rightarrow \infty$ (see *Op-Amps* handout).

Specs: Open-loop low-frequency gain:106 dB= 2×10^5 . Pole frequency:8 Hz.

Model: Transfer function= $A(jf) = \frac{1.6 \times 10^6}{jf+8}$. Note $A(0) = \frac{1.6 \times 10^6}{0+8} = 2 \times 10^5$.

Plug: $\frac{V_O}{V_I}(f) = -\frac{R_F}{R_I} / [1 + \frac{jf+8}{1.6 \times 10^6} (1 + \frac{R_F}{R_I})] \approx -\frac{1.6 \times 10^6}{jf + 1.6 \times 10^6 \frac{R_I}{R_F}}$ (1-pole filter).

Using: $\frac{R_F/R_I}{1+R_F/R_I} \approx 1 \Leftrightarrow R_F/R_I \gg 1$ and $1.6 \times 10^6 \frac{R_I}{R_F} \gg 8$ (reasonable).

Then: Closed-loop low-frequency gain= $-\frac{1.6 \times 10^6}{0 + 1.6 \times 10^6 \frac{R_I}{R_F}} = -\frac{R_F}{R_I}$ as expected.

And: Pole frequency=3 dB frequency=bandwidth= $1.6 \times 10^6 \frac{R_I}{R_F}$ in Hertz.

So: (Gain)(Bandwidth)=($\frac{R_F}{R_I}$)($1.6 \times 10^6 \frac{R_I}{R_F}$) = 1.6×10^6 =constant.

Means: We can trade gain for bandwidth; consider filtering of, e.g.,square wave.

ACTIVE FILTERS (OP-AMP FILTER CIRCUITS)

Why?: Can *combine* the two circuits below to produce *new* and *better* filters:

Like: Lowpass+highpass=bandpass; lowpass+lowpass=higher-order lowpass.

Also: Load at op-amp output does not affect filter; isolate input if needed.

Low-pass filter (note $\omega \rightarrow 0$)

High-pass filter (note $\omega \rightarrow \infty$)

$$H(j\omega) = -\frac{R_2}{R_1} \frac{1}{j\omega R_2 C + 1}$$

$$H(j\omega) = -\frac{R_2}{R_1} \frac{j\omega R_1 C}{j\omega R_1 C + 1}$$