

Networks or Circuits Themselves: Need KVL and KCL

DEF: A *circuit* or *network* is an interconnection of *devices*.

Each device has a *voltage across* it and a *current through* it.

KCL: Kirchhoff's Current Law: Conservation of charge →

$$\sum \text{currents flowing into a point} = \sum \text{currents flowing out of that point.}$$

KVL: Kirchhoff's Voltage Law: Conservation of energy →

$$\sum \text{voltages around any closed path in a circuit or network} = 0.$$

Why? Move a charge q around the loop. Think of a car on a rollercoaster:

Going "up" a voltage v_1 , the charge *gains* potential energy qv_1 .

Going "down" voltage v_2 , the charge *loses* potential energy qv_2 .

Charge returns to starting point → $\sum \text{energy} = \sum qv_i = q \sum v_i = 0$.


KVL: $v_1 - v_2 - v_3 = 0$ (left loop)

KVL: $v_3 + v_2 - v_4 - v_5 = 0$ (right)

KVL: $v_1 - v_4 - v_5 = 0$ (outer loop)

KCL: $i_1 = i_2 + i_3$ (at both points)

Note: 1 KVL and 1 KCL redundant.

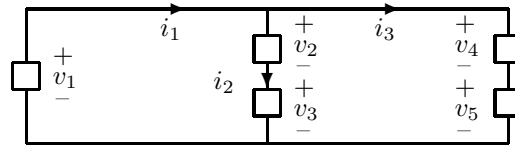

Devices in a Network or Circuit: Need i-v Characteristic

DEF: Any device can be described by rule $i = \text{function}(v)$,


where $i = \text{current through it}$ and $v = \text{voltage across it}$.

using the **standard reference directions** shown:

- (Ideal) **current source:** $i = \text{constant}$. EX: ideal solar cell.
- (Ideal) **voltage source:** $v = \text{constant}$. EX: ideal battery.
- (Ideal) **Resistor:** $v = iR$ (Ohm's law). Units: volts=(ohms)(amps).
- (Ideal) **Conductance:** $i = Gv$ where $G = 1/R$. amps=(mhos)(volts).
- (Ideal) **Short circuit:** (wire) $R = 0 \Leftrightarrow G \rightarrow \infty$.
- (Ideal) **Open circuit:** (gap) $G = 0 \Leftrightarrow R \rightarrow \infty$.

KVL: $12 - 6i - 2(i + 2) = 0 \rightarrow i = 1 A$
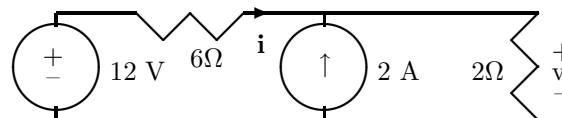
$$\rightarrow v = 12 - 6(1) = 2(1 + 2) = 6 V$$



Power: Dissipated: $2\Omega : (6)(1+2) = 18W$; $6\Omega : (6)(1) = 6W$; Total: $24W$.

Power: Supplied: $2A : (6)(-2) = -12W$; $12V : (12)(-1) = -12W$; Total: $-24W$.

Check: Power dissipated = power supplied (Tellegen's law) where power = vi .

- **Voltage sources in series add:** Apply KVL
- **Current sources in parallel add:** Apply KCL
- **Resistors in series add:** $v = iR_1 + \dots + iR_n = i(R_1 + \dots + R_n) = iR_{eq}$
- **Conductances in parallel add:** $i = G_1v \dots G_nv = (G_1 \dots G_n)v$
- **Resistors in parallel:** add $1/R$'s (*conductances* in parallel add)
- **Voltage sources in parallel blow up!** KVL: $\sum v_i \neq 0 \rightarrow$ Can't be!
- **Current sources in series blow up!** KCL: $\sum i_j \neq 0 \rightarrow$ Can't be!
- **Inductors in series add:** $v = L_1 \frac{di}{dt} + \dots + L_n \frac{di}{dt} = (L_1 + \dots + L_n) \frac{di}{dt}$
- **Capacitors in parallel add:** $i = C_1 \frac{dv}{dt} + \dots + C_n \frac{dv}{dt} = (C_1 + \dots + C_n) \frac{dv}{dt}$
- **Capacitors in series:** add $1/C$'s (see later)
- **Inductors in parallel:** add $1/L$'s (see later)

EX#1: $30\Omega, 60\Omega, 20\Omega$ resistors connected in series. Compute R_{eq} .

Soln: $R_{eq} = 30 + 60 + 20 = 110\Omega$.

EX#2: $30\Omega, 60\Omega, 20\Omega$ resistors connected in parallel. Compute R_{eq} .

Soln: $G_{eq} = 1/30 + 1/60 + 1/20 = 1/10$ Mhos $\rightarrow R_{eq} = 1/G_{eq} = 10\Omega$.

EX#3: N resistors of $R\Omega$ each are connected in parallel. Compute R_{eq} .

Soln: $G_{eq} = \frac{1}{R} + \dots + \frac{1}{R} = \frac{N}{R} \rightarrow R_{eq} = \frac{R}{N}\Omega$. Parallel current paths.

Note: For **two** resistors in parallel: $R_{eq} = R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2}$.

BUT: This does **not** work for more than two resistors in parallel!

$R_{eq} \neq \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}$! Look at units: This *must* be wrong!

VOLTAGE AND CURRENT DIVIDERS


CURRENT DIVIDER

$$i_1 = i_s \frac{G_1}{G_1 + G_2} = i_s \frac{R_2}{R_1 + R_2}$$

$$i_2 = i_s \frac{G_2}{G_1 + G_2} = i_s \frac{R_1}{R_1 + R_2}$$

i_s divided between G_1, G_2

same voltage across both

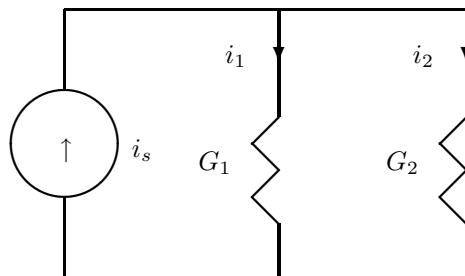

VOLTAGE DIVIDER

$$v_1 = v_s \frac{R_1}{R_1 + R_2} \quad \text{EXS: rheostat,}$$

$$v_2 = v_s \frac{R_2}{R_1 + R_2} \quad \text{volume control}$$

v_s divided between R_1, R_2

same current through both

