

DEF: In EECS 210 a **capacitor** is a device with i-v characteristic $i = C \frac{dv}{dt}$.

Energy: $\frac{\text{stored}}{\text{energy}} = \int_0^t i(\tau)v(\tau)d\tau = \int_0^t Cv(\tau)\frac{dv}{d\tau}d\tau = \int_0^{v(t)} Cv dv = \frac{1}{2}Cv(t)^2$.

Series: Capacitors in series: $\frac{1}{C_{EQ}} = \frac{1}{C_1} + \dots + \frac{1}{C_N}$. **N=2:** $C_{EQ} = \frac{C_1C_2}{C_1+C_2}$.

Parallel: Capacitors in parallel: $C_{EQ} = C_1 + \dots + C_N$ (EX: parallel plates).

Derive: $v(t) = v(0) + \frac{1}{C} \int_0^t i(\tau)d\tau$; $i(t) = i(0) + \frac{1}{L} \int_0^t v(\tau)d\tau$. Also useful.

Note: Short capacitor: $-\frac{dv}{dt}$ huge $\rightarrow -i(t)$ huge \rightarrow **spark**. EX: camera flash.

Thus: Capacitors tend to retard sharp voltage changes. EX: auto ignition.

Sinusoid: $v(t) = \cos(\omega t) \rightarrow i(t) = -\omega C \sin(\omega t)$. Gain= ωC ; Phase= 90° .

$i(t) = \cos(\omega t) \rightarrow v(t) = \frac{1}{\omega C} \sin(\omega t)$. Gain= $\frac{1}{\omega C}$; Phase= -90° .

Physics: A capacitor stores **separated** charge; its *net* charge is zero. $q = Cv$.
More stored charge \rightarrow bigger electric field \rightarrow bigger potential difference.
Time-varying voltage \rightarrow time-varying charge \rightarrow current flow.

If voltage and current **constant** in time, capacitor=**open** circuit.

EX: Parallel-plate: $C = \frac{A\epsilon}{d}$ (ϵ =permittivity, A=area, d=separation).

Units: Farads=coulombs/volts; Joules=(coulombs)(volts)=(farads)(volts)².

DEF: In EECS 210 an **inductor** is a device with i-v characteristic $v = L \frac{di}{dt}$.

Energy: $\frac{\text{stored}}{\text{energy}} = \int_0^t i(\tau)v(\tau)d\tau = \int_0^t Li(\tau)\frac{di}{d\tau}d\tau = \int_0^{i(t)} Li di = \frac{1}{2}Li(t)^2$.

Parallel: Inductors in parallel: $\frac{1}{L_{EQ}} = \frac{1}{L_1} + \dots + \frac{1}{L_N}$. **N=2:** $L_{EQ} = \frac{L_1L_2}{L_1+L_2}$.

Series: Inductors in series: $L_{EQ} = L_1 + \dots + L_N$ (EX: longer coil (more turns)).

Note: Open inductor: $-\frac{di}{dt}$ huge $\rightarrow -v(t)$ huge \rightarrow **spark**. EX: spark plug.

Thus: Inductors tend to retard sharp current changes. EX: "choke" coils.

Sinusoid: $i(t) = \cos(\omega t) \rightarrow v(t) = -\omega L \sin(\omega t)$. Gain= ωL ; Phase= 90° .

$v(t) = \cos(\omega t) \rightarrow i(t) = \frac{1}{\omega L} \sin(\omega t)$. Gain= $\frac{1}{\omega L}$; Phase= -90° .

Physics: An inductor stores *magnetic flux*=(magnetic field)(area). $\Phi = Li$.

More magnetic flux \rightarrow bigger magnetic field \rightarrow bigger current flow.

Time-varying current \rightarrow time-varying flux \rightarrow emf \leftrightarrow voltage (Faraday).

If voltage and current **constant** in time, inductor=**short** circuit.

EX: Coil: $L = N^2 \frac{A\mu}{d}$ (μ =permeability, A=area, d=length, N=#turns).

Units: Henrys=(Ohms)(sec.); Farads=(Mhos)(sec.); Joules=(henrys)(amps)².

Given: A circuit in which a switch is opened or closed at $t = 0$.

Where: The circuit includes: inductors; capacitors; resistors; DC sources.

Goal: What are the currents and voltages at $t = 0^-$; $t = 0^+$; $t \rightarrow \infty$?

$t = 0^+$: Use following to link voltages and currents at $t = 0^-$ to $t = 0^+$:

1. Inductor *current can't jump*: Otherwise $V = L \frac{di}{dt} \rightarrow \infty!$
2. Capacitor *voltage can't jump*: Otherwise $I = C \frac{dv}{dt} \rightarrow \infty!$

$t \rightarrow \infty$: Use following to compute voltages and currents as $t \rightarrow \infty$:

1. Circuit contains only DC (constant) sources \rightarrow inductor = short circuit.
 2. Circuit contains only DC (constant) sources \rightarrow capacitor = open circuit.
-

EX: Electromagnet modelled
by $10H$ in series with 4Ω
(models coil resistance).
After being closed awhile,
switch is opened at $t = 0$.
Compute $V_s(t)$ and $I_L(t)$.

$t = 0^-$: Inductor = short $\rightarrow V_s = (200A)(16\Omega || 4\Omega) = 640V$.
Current divider $\rightarrow I_L = (200A) \frac{16\Omega}{16+4\Omega} = 160A$.

$t = 0^+$: Impossible! Inductor voltage $\rightarrow \infty!$ Let $I_L(t) = (160A)e^{-t/1ms}, t > 0$.

Models: Switch is opened over a *finite time*; the current falls rapidly to zero.

Then: $V_s(t) = (10H) \frac{d}{dt} (160A)e^{-t/1ms} = -(10H)(160A) \frac{1}{0.001s} e^{-t/1ms}, t > 0$.

Note: Maximum voltage: $V_s(0) = -1.6$ million volts! Not ∞ , but large!

$t \rightarrow \infty$: $V_s = 0$ across inductor; $V_s = (200A)(16\Omega) = 3200V$ across source.

Also: Energy dissipated: $\frac{1}{2}LI_L^2 = \frac{1}{2}(10H)(160A)^2 = 128kJ$ (128,000 Joules!)

COMPLEX NUMBER MANIPULATIONS

Euler: $z = Me^{j\theta} = M \cos \theta + jM \sin \theta = R + jX$; $R = \text{Re}[z]$; $X = \text{Im}[z]$.

Note: $j = \sqrt{-1}$ (in EE, i =current!). Imaginary part is **not** itself imaginary!

Add: Add and subtract in rectangular form: $(3 + j4) + (5 + j12) = (8 + j16)$.

Mult: Multiply & divide in polar form: $3 + j4 = 5e^{j53^\circ}$; $5 + j12 = 13e^{j67^\circ}$.

$(3 + j4)(5 + j12) = (3 \cdot 5 - 4 \cdot 12) + j(4 \cdot 5 + 3 \cdot 12) = -33 + j56$ (hard).

$(3 + j4)(5 + j12) = 5e^{j53^\circ} 13e^{j67^\circ} = 65e^{j120^\circ}$ (easy). Division easy too.

$$\frac{(a+jb)(c+jd)}{(e+jf)(g+jh)} = \sqrt{\frac{(a^2+b^2)(c^2+d^2)}{(e^2+f^2)(g^2+h^2)}} \exp j[\tan^{-1} \frac{b}{a} + \tan^{-1} \frac{d}{c} - \tan^{-1} \frac{f}{e} - \tan^{-1} \frac{h}{g}]$$