

1a. Let $Z = R_L || \frac{1}{j\omega C} = \frac{R_L/(j\omega C)}{R_L + 1/(j\omega C)} = R_L/(1 + j\omega R_L C)$.

$H(j\omega) = \frac{V_O}{V_I} = \frac{Z}{Z+R} = R_L/(R_L + R(1 + j\omega R_L C)) = \frac{1}{RC}/(j\omega + \frac{R+R_L}{RR_L C})$. 1-pole filter.

1b,c. Maximum $|H(j\omega)| = \frac{R_L}{R+R_L}$ at DC ($\omega = 0$). Check: Capacitor=open circuit at DC.

1d. $|H(j\omega)|$ down by $\frac{1}{\sqrt{2}}=3$ dB at pole frequency $\omega_c = \frac{R+R_L}{RR_L C}$.

2a,b. (a) $f = \frac{160,000}{2\pi} = 25.46\text{kHz}$. (b) $160,000 = \frac{1}{RC} \rightarrow R = 250\Omega$.

2c. Using 1d, $\omega_c = \frac{R+R_L}{RR_L C} = \frac{1.08}{RC} \rightarrow \frac{R+R_L}{R_L} = 1.08 \rightarrow R_L = \frac{R}{0.08} = 3125\Omega$.

2d. Using 1c, $H(j0) = \frac{R_L}{R+R_L} = \frac{1}{1.08} = 0.926$. Note we don't need values of R or R_L .

3a. $\omega_o = \frac{1}{\sqrt{LC}} = \sqrt{\frac{10^3 \cdot 10^{12}}{312 \cdot 1.25}} = 1.6 \times 10^6 \frac{\text{rad}}{\text{sec}}$. $f_o = \frac{\omega_o}{2\pi} = 254.8\text{kHz}$.

3b,e. $Q = \frac{\omega_o L}{R} = \frac{1.6 \cdot 312 \cdot 1000}{(50 + 12.5)k\Omega} = 8$. Bandwidth $= \beta = \frac{\omega_o}{Q} = \frac{1.6 \times 10^6}{8} = 200k \frac{\text{rad}}{\text{sec}} = 31.83\text{kHz}$.

3c,d. $f_{c1} = f_o - \frac{\beta}{2} = 254.8 - \frac{31.83}{2} = 238.9\text{kHz}$. $f_{c2} = f_o + \frac{\beta}{2} = 254.8 + \frac{31.83}{2} = 270.7\text{kHz}$.

NOTE: Using formulae on p. 720-722, get 239.2kHz and 271.0kHz (close despite low Q).

4a. $2\pi(20\text{kHz}) = \omega_o = \frac{1}{\sqrt{LC}} \rightarrow L = \frac{10^9/10^6}{20(2\pi(20))^2} = 3.17\text{mH}$.

4a. $5 = Q = \frac{\omega_o L}{R} = \frac{40\pi \cdot 3.17}{R} \rightarrow R = \frac{40\pi \cdot 3.17}{5} = 79.58\Omega$.

4d. Bandwidth $= \beta = \frac{f_o}{Q} = \frac{20}{5} = 4\text{kHz}$. Note Q is dimensionless, so use Hz throughout.

4b,c. $f_{c1} = f_o - \frac{\beta}{2} = 20 - \frac{4}{2} = 18\text{kHz}$. $f_{c2} = f_o + \frac{\beta}{2} = 20 + \frac{4}{2} = 22\text{kHz}$.

NOTE: Using formulae on p. 720-722 (ugh), get 18.1kHz and 22.1kHz (close despite low Q).

5. Bode magnitude plot starts off level, so no zero at DC ($\omega = 0$).

Up 3 dB (from 1 to 4 dB) at $\omega = 1$, so this is a zero frequency.

Levels off at 20 dB, and is down 3 dB (at 17 dB) at $\omega = 10 \rightarrow$ pole frequency.

Down 3 dB (at 17 dB) at $\omega = 100 \rightarrow$ pole frequency. No further slope changes.

$H(j\omega) = K \frac{j\omega+1}{(j\omega+10)(j\omega+100)}$. $H(j0) = 1 = K \frac{1}{(10)(100)} \rightarrow K = 1000$.

6a. *High-pass* filter $\rightarrow H(j0) = 0, H(j\infty) = 1$. See what circuit looks like at these.

$\omega = 0$: L \rightarrow short, C \rightarrow open circuit. But circuit $\rightarrow \times$, so *can't tell* (yet).

$\omega \rightarrow \infty$: L \rightarrow open, C \rightarrow short. Now circuit $\rightarrow ||$, so *input=top, output=bottom* (or vice-versa).

6b. Taking the top half of the circuit, and taking Thevenin equivalent of its left half, get

$H(j\omega) = (j\omega)^3 / [(j\omega + \frac{R}{L})(-2\omega^2 + j\omega \frac{1}{RC} + \frac{1}{LC})]$ for arbitrary R,L,C.


Plugging in $\rightarrow H(j\omega) = \frac{(j\omega)^3/2}{(j\omega+a)(-\omega^2+j\omega a+a^2)}$ where $a = 3.456 \times 10^8 = 55\text{MHz}$.

Zeros: 3 at origin. **Poles:** $-a, -a \frac{1 \pm \sqrt{3}}{2}$. See overleaf for more details.

NOTE: BELOW I USE $s = j\omega$ (MAKES THINGS A LITTLE NEATER)

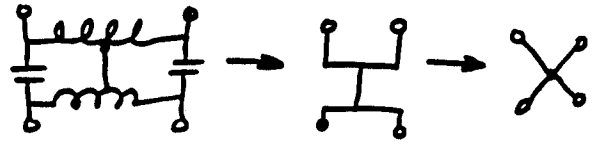
(a) KNOW FROM DESCRIPTION IT'S A HIGH-PASS FILTER, SO
 TRANSFER FUNCTION $\rightarrow 0$ AT LOW FREQS. AND $\rightarrow 1$ AT HIGH FREQS.

AT LOW FREQS: $L \rightarrow$ SHORT
 $C \rightarrow$ OPEN




SO XFER FUNCTION IS 0, FOR ANY ORIENTATION!

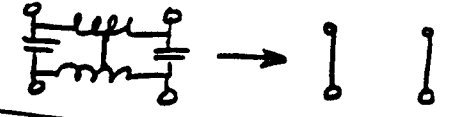AT HIGH FREQS: $L \rightarrow$ OPEN
 $C \rightarrow$ SHORT




WANT XFER FUNCTION TO BE 1. OBVIOUSLY INPUT = TOP OUTPUT = BOTTOM (OR VICE-VERSA)

(b) TAKE TOP HALF OF CIRCUIT:

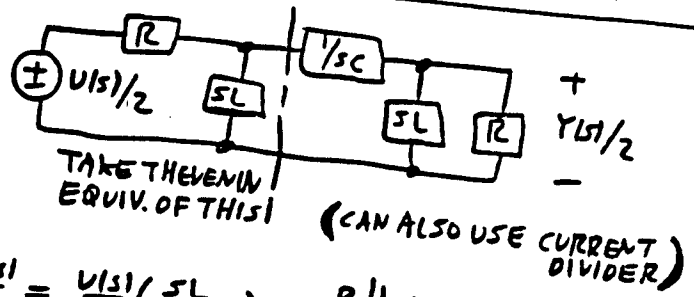

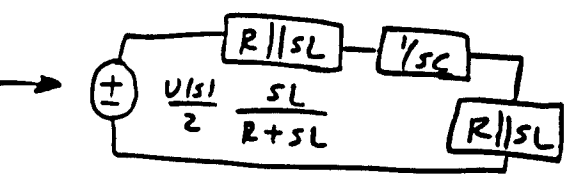TAKE THEVENIN EQUIV. OF THIS! (CAN ALSO USE CURRENT DIVIDER)



$$\frac{Y(s)}{U(s)} = \frac{s^3}{(s + R/L)(2s^2 + s \frac{1}{RC} + \frac{1}{LC})}$$


CHECKS:

- (1) UMTS $R/L, 1/RC, 1/LC$ ALL OK
- (2) HIGH-FREQ. BEHAVIOR: $\frac{Y(s)}{U(s)}|_{s \rightarrow \infty} = \frac{1}{2}$ (SPLIT BETWEEN THE RS)
- (3) $L \rightarrow \infty$: $L =$ OPEN CIRCUIT. $\frac{Y(s)}{U(s)}|_{L \rightarrow \infty} = \frac{R}{2R + 1/sC} = \frac{s}{2s + 1/R}$

NOT REQUIRED, BUT A GOOD IDEA!

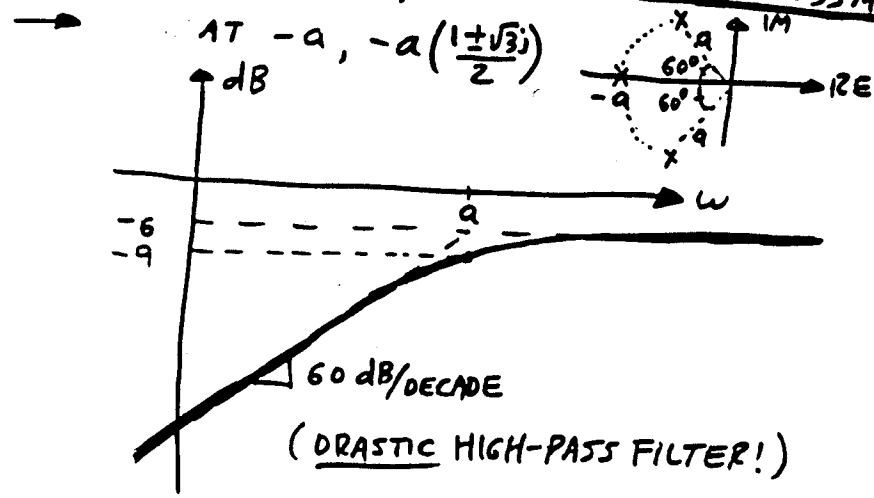(c) $R = 150, L = 0.434 \times 10^{-6}, C = 9.65 \times 10^{-12}$

$$\frac{(s + 3.456 \times 10^8)(2s^2 + 6.91 \times 10^8 s + 2.388 \times 10^{17})}{s^3}$$



LOW-FREQ ASYMPTOTE:

- $s \rightarrow 0$ GIVES $H(s) \approx s^3 / 2a^3$
- AT $\omega = a, |H(j\omega)| = 1/2 = -6$ dB.
- TRIPLE ZERO AT ORIGIN $\rightarrow 60$ dB/DECADE

HIGH FREQ ASYMPTOTE:

- $s \rightarrow \infty$ GIVES $H(s) \approx 1/2 = -6$ dB
- AT $\omega = a$: POLE AT $-a \rightarrow$ DOWN 3 dB.
- COMPLEX POLES $-a(1 \pm j\sqrt{3}) \rightarrow$ RESONANCE PEAK HEIGHT $20 \log_{10}(\frac{1}{2} \sec 60^\circ) = 0$ dB
- SUM: DOWN 3 dB.
- CHECK: $\frac{s^3}{2(s+a)(s^2+as+a^2)}|_{s=j\omega} = \frac{1}{2\sqrt{2}} = -9$ dB