

- 1a. $\omega \rightarrow 0$: $L \rightarrow$ short so gain=1. $\omega \rightarrow \infty$: $C \rightarrow$ short so gain=1. Passes low & high freqs.
 $0 < \omega < \infty$: $L||C$ can only get larger, so gain < 1. Gain has a minimum somewhere.
- 1b. Let $Z = j\omega L || \frac{1}{j\omega C} = \frac{(j\omega L)/(j\omega C)}{j\omega L + 1/(j\omega C)} = \frac{j\omega L}{1 - \omega^2 LC}$.
 $H(j\omega) = \frac{V_O}{V_I} = \frac{R}{R+Z} = \frac{R(1-\omega^2 LC)}{R(1-\omega^2 LC) + j\omega L} = \frac{(j\omega)^2 + \frac{1}{LC}}{(j\omega)^2 + j\omega \frac{1}{RC} + \frac{1}{LC}}$.
- 1c. $|H(j\omega)| = 0$ (can't get smaller than that) at $\omega_o = 1/\sqrt{LC}$ (same as series RLC).
- 1d. $|H(j0)| = |H(j\infty)| = 1$ so $|H(j\omega)| = 1/\sqrt{2}$ at cutoff frequencies ω_{c1}, ω_{c2} .
 $|H(j\omega)| = 1/\sqrt{2}$ when $\pm \omega \frac{1}{RC} = \frac{1}{LC} - \omega^2 \rightarrow \omega_{c1}, \omega_{c2} = \pm \frac{1}{2RC} + \sqrt{\frac{1}{(2RC)^2} + \frac{1}{LC}}$.
- 1e. Bandwidth = $\omega_{c2} - \omega_{c1} = \frac{1}{RC}$. As before, $\omega_{c1} \approx \omega_o - \frac{1}{2RC}$; $\omega_{c2} \approx \omega_o + \frac{1}{2RC}$.
- 1f. $Q = \frac{\text{resonant freq}}{\text{bandwidth}} = \omega_o RC$ (same as parallel RLC circuit).

- 2a. $2\pi(50kHz) = \frac{1}{\sqrt{LC}} \rightarrow L = 1/[(100,000\pi)^2(0.1 \times 10^{-6})] = 101.3\mu H$.
- 2a. $8 = Q = \omega_o RC = 100,000\pi(0.1 \times 10^{-6})R \rightarrow R = \frac{800}{\pi} = 254.6\Omega$.
- 2c. $Q = \frac{\text{resonant freq}}{\text{bandwidth}} \rightarrow \text{Bandwidth} = \frac{50kHz}{8} = 6.25kHz$.
- 2b. $f_{c1} = 50 - \frac{6.25}{2} = 46.9kHz$. $f_{c2} = 50 + \frac{6.25}{2} = 53.1kHz$.

These differ from the exact answers using the square root by only 0.1kHz.

- 3a. $\frac{V_O}{V_I} = -\frac{Z_F}{Z_I}$ where $Z_I = R_1 + \frac{1}{j\omega C_1} = \frac{j\omega R_1 C_1 + 1}{j\omega C_1}$ and $Z_F = R_2 || \frac{1}{j\omega C_2} = \frac{R_2}{j\omega R_2 C_2 + 1}$.
- 3a. $H(j\omega) = -\frac{j\omega/(R_1 C_2)}{(j\omega + \frac{1}{R_1 C_1})(j\omega + \frac{1}{R_2 C_2})}$. **Zero:** origin. **Poles:** $\frac{1}{R_2 C_2}$; $\frac{1}{R_1 C_1}$.
- 3b. $H(j0) = 0$. Makes sense: $C_2 \rightarrow$ open vanishes; $C_1 \rightarrow$ open \rightarrow gain=0.
- 3c. $H(j\infty) = 0$. Makes sense: $C_1 \rightarrow$ short vanishes; $C_2 \rightarrow$ short \rightarrow gain=0.

Bode: Zero: origin. **Poles:** $\frac{1}{R_2 C_2} = 10^3$; $\frac{1}{R_1 C_1} = 10^5$. $\omega \rightarrow 0$: $|H(j\omega)| \simeq \left| \frac{-10^5 j\omega}{10^3 10^5} \right| = \frac{\omega}{10^3}$.

4. $Q = \frac{\text{resonant freq}}{\text{bandwidth}} = \frac{100kr/s}{4r/s} = 25 = \frac{(100kr/s)L}{1000\Omega} \rightarrow L = 0.25H$
 $100,000 = \frac{1}{\sqrt{LC}} \rightarrow C = 10^{-10}/0.25 = 400pF$. At resonance, impedance=R=1000 Ω

- 5a. $V_I(t) = 12.54 - 25.08 \sum_{n=1}^{\infty} \frac{\cos(754nt)}{4n^2 - 1}$ where $\frac{2(19.7)}{\pi} = 12.54$ (from inside back cover).
- 5b. **Pole:** $\frac{1}{RC} = \frac{1}{2(0.00663)} = 75.4 \frac{rad}{sec} = 12Hz$. Gain = $\frac{1}{\sqrt{1 + (\frac{f}{12})^2}}$. Phase = $-\tan^{-1} \frac{f}{12}$.
- 5c. $V_O(t) = 12.54 - 25.08 \sum_{n=1}^{\infty} \frac{\cos[754nt - \tan^{-1}(10n)]}{(4n^2 - 1)\sqrt{1 + 100n^2}}$ using $f = 120n \rightarrow \omega RC = \frac{120n}{12} = 10n$.

