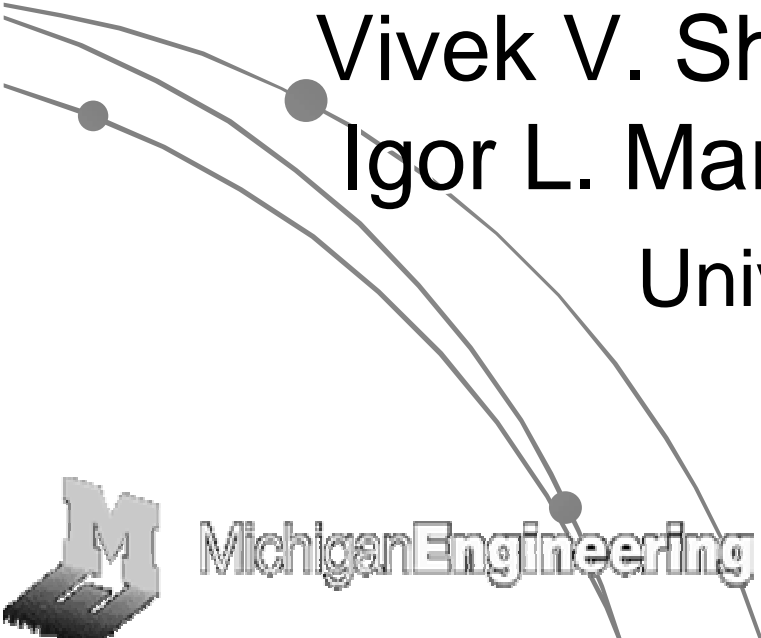




# Reversible Logic Circuit Synthesis



Vivek V. Shende, Aditya K. Prasad,  
Igor L. Markov and John P. Hayes  
University of Michigan



MichiganEngineering

# Outline

- Motivation
  - Real-world Applications
  - Theoretical Advantages
  - Links to Quantum Computation
- Background
- Theoretical Results
- Synthesis of Optimal Circuits
- An Application to Quantum Computing

# Real-world Applications

- Many inherently reversible applications
- Info. is re-coded, but none is lost or added
  - Digital signal processing
  - Cryptography
  - Communications
  - Computer graphics
  - Network congestion modeling

# Theoretical Advantages

- Information conservation laws in physics
  - Thermodynamics ties irreversibility to dissipated heat: every lost bit causes an energy loss
  - C. Bennett, 1973, *IBM J. of R & D*
- Energy-lossless circuits ( $Time \rightarrow \infty$ )
  - must be information-lossless
  - have been built: S. Younis and T. Knight, 1994, *Workshop on Low Power Design*

# Links to Quantum Computation

- Quantum operations are all reversible
  - M. Nielsen and I. Chuang, **Quantum Computation and Quantum Information**, *Cambridge Univ. Press* 2000
- Every (classical) reversible circuit may be implemented in quantum technology, with overhead
- “Pseudo-classical” subroutines of quantum algos
  - Can be implemented in classical reversible logic circuits
  - S. Betteli, L. Serafini, and T. Calarco, 2001, <http://xxx.lanl.gov/abs/cs.PL/0103009>



# Outline

- Motivation
- Background
  - Reversibility
  - Permutations
  - Known Facts
- Theoretical Results
- Synthesis of Optimal Circuits
- An Application to Quantum Computing
  
# Reversibility in Logic Gates



- Definition: reversible logic gate

- #input wires = #output wires
- Permutes the set of input values



  
- Examples

- Inverter
- 2-input, 2-output SWAP (S) gate



- $k$ -CNOT gate

 - $(k+1)$ -inputs and  $(k+1)$ -outputs
- Values on the first  $k$  wires are unchanged
- The last value is flipped if the first  $k$  were all 1



# Reversibility in Logic Circuits

- Definition:

A combinational logic circuit is reversible iff

- It contains only reversible gates
- It has no fan-out
- It is acyclic (as a directed multi-graph)

- Theorem:

A reversible circuit must


- Have as many input wires as output wires
- Permute the set of input values



# Example:


## A Reversible Circuit and Truth Table

a	b	c	a'	b'	c'
0	0	0	0	0	1
0	0	1	0	0	0
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	1	0	1
1	0	1	1	0	0
1	1	0	1	1	1
1	1	1	1	1	0

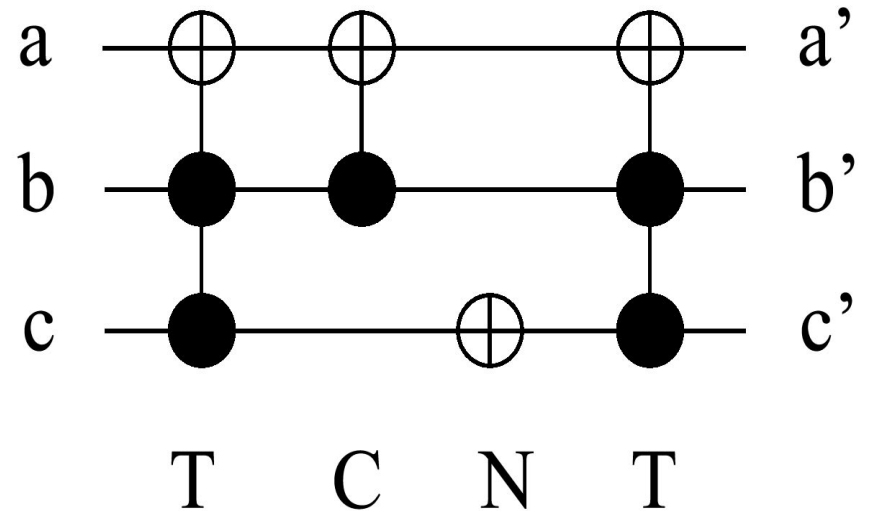

Equivalent to a NOT gate on wire c

# Circuit Equivalences

 

**Figure 2: Two reversible circuit equivalences.**  $T(1,2;3) \cdot N(1) \cdot T(1,2;3) \cdot N(1) = C(2;3)$ , and  $C(3;2) \cdot C(2;3) \cdot C(3;2) = S(2,3)$



- Circuit equivalences: useful in synthesis
- More will be shown later

# Reversible Circuits & Permutations

- A reversible gate (or circuit) with  $n$  inputs and  $n$  outputs has
  - $2^n$  possible input values
  - $2^n$  possible output values
- The function it computes on this set must, by definition, be a permutation
- The set of such permutations is called  $S_{2^n}$
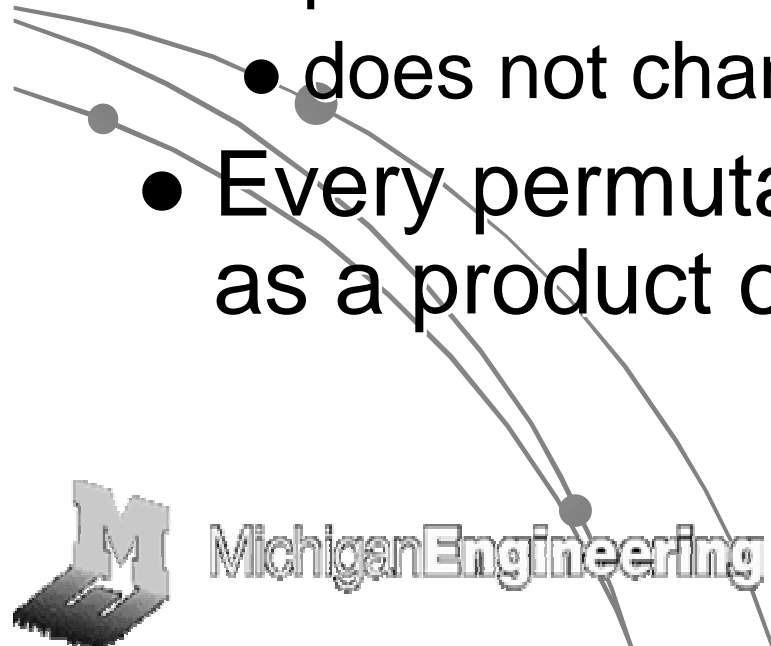 
# Basic Facts About Permutations

- Permutations are multiplied by first applying one, then the other
  - example:  $(1,2) \circ (2,3) = (1,3,2)$
- A transposition
  - permutes exactly two elements
  - does not change any others
- Every permutation can be written as a product of transpositions




# Even Permutations

- Consider all possible decompositions of a permutation into transpositions
- Theorem: The parity of the number of transpositions is constant
- Definition: Even permutations are those for which the number of transpositions is even

# Known Facts

- Fact 1: Consider a reversible circuit
  - $n+1$  inputs and  $n+1$  outputs
  - Built from gates which have at most  $n$  inputs and  $n$  outputs
  - Must compute an even permutation
- Fact 2: A universal gate library
  - CNOT, NOT, and TOFFOLI (“CNT”)
  - Temporary storage may be required

# Temporary Storage

 

**Figure 3: A reversible circuit with  $n-k$  wires of temp. storage.**

# Outline

- Motivation
- Background
- Theoretical Results
  - Zero-storage Circuits
  - Reversible De Morgan's Laws
- Synthesis of Optimal Circuits
- An Application to Quantum Computing



# Minimizing Temporary Storage

- Consider CNT circuits
  - Theorem: even permutations computable by circuits without temporary storage
  - Theorem: odd permutations computable *with one line of temporary storage*
- Same holds for NT and CNTS circuits
- The proof is constructive and may be used as a synthesis heuristic

# Outline of Proof

- Explicitly construct a circuit to compute an arbitrary pair of disjoint transpositions  $(A, B) (C, D)$  is okay;  $(A, B) (B, C)$  is not
- Pick an even permutation
- Decompose it into transpositions
  - Will have an even number of transpositions
- Pair these up, guaranteeing disjointness
- Apply above construction to each pair


# Reversible De Morgan's Laws (1)

- De Morgan's Laws
  - Apply to AND/OR/NOT circuits
  - Allow pushing all inverters to the inputs
- Reversible De Morgan's Laws
  - Applied to reversible CNT circuits
  - Allow pushing all inverters to the inputs
- Pictures follow


# Reversible De Morgan's Laws (2)

- Similar rules exist for interchanging TOFFOLI and CNOT gates
- However, it is not always possible to push all CNOT gates to the inputs
- Oddly enough, all CNOT gates can be pushed to the “middle” of the circuit

# Reversible De Morgan's Laws (3)

 

# Reversible De Morgan's Laws (4)

 

# Outline

- Motivation
- Background
- Theoretical Results
- Synthesis of Optimal Circuits
  - Optimality
  - IDA\* Search Algorithm
  - Circuit Libraries
- An Application to Quantum Computing


# Optimality

- The cost of a circuit is its gate count
  - Other cost functions can be considered
- Definition: optimal reversible circuit
  - no circuit with fewer gates computes the same permutation
- Theorem: a sub-circuit of an optimal circuit is optimal
  - Proof: otherwise, can improve the sub-circuit


 
# IDA\* Search

- Checks all possible circuits of cost 1, then all possible circuits of cost 2, etc...
- Avoids the memory blowup of BFS
- Still finds optimal solutions (unlike DFS)
- Checking circuits of cost less than  $n$ 
  - Is much faster than processing cost- $n$  circuits



# Dynamic Prog + Circuit Libraries

- IDA\* search requires a subroutine to check all circuits of cost  $n$ , for arbitrary  $n$ 
  - Called iteratively for  $1 \dots n$
- Only need to check locally optimal circuits
- Build optimal circuit library bottom up by DP
  - Index optimal circuits by computed permutation
  - In practice use hash\_map datastruct from STL

# Synthesis Algorithm (1)

```
CIRCUIT synthesize(PERM)
{
  if (PERM==IDENTITY) return EMPTY_CCT;
  // otherwise, use IDA* to find a circuit.
  for(DEPTH ← 1, DEPTH < MAX_DEPTH; DEPTH++)
  {
    CIRCUIT ← find_circ(DEPTH, PERM, EMPTY_CCT);
    if (CIRCUIT != NIL) return CIRCUIT;
  }
}
```

# Synthesis Algorithm (2)


```
CIRCUIT find_circ(COST, PERM, CURR_CCT)
{
  if (COST  $\leq$  k)
    // if PERM can be computed by a circuit
    // with fewer at most k gates,
    // such a circuit must be in the library
    return CURR_CCT + LIB[DEPTH].find(PERM);
  else
    // The goal circuit must have >k gates;
    // Try constructing it from k-gate circuits
    for each C in LIB[k]
      {
        // divide PERM by permutation computed by C
        PERM2  $\leftarrow$  PERM * INVERSE(C.perm)
        // and try to synthesize the result
        TEMP_CCT  $\leftarrow$  find_circ(depth-k, PERM2);
        if (TEMP_CCT  $\neq$  NIL) return TEMP_CCT;
      }
}
```

# Empirical Circuit Synthesis

- Consider all reversible functions on 3 wires  
( $8! = 40,320$  functions)
- For each gate library from N, C, T, NC, CT, NT, CNT, CNTS
  - Is it universal?
  - How many functions can it synthesize?
  - What are largest optimal circuits?
  - How long does it take to synthesize circuits?

# Optimal Circuit Sizes

Size	N	C	T	NC	CT	NT	CNT	CNTS
12	0	0	0	0	0	47	0	0
11	0	0	0	0	0	1690	0	0
10	0	0	0	0	0	8363	0	0
9	0	0	0	0	0	12237	0	0
8	0	0	0	0	6	9339	577	32
7	0	0	0	14	386	5097	10253	6817
6	0	2	0	215	1688	2262	17049	17531
5	0	24	0	474	1784	870	8921	11194
4	0	60	5	393	845	296	2780	3752
3	1	51	9	187	261	88	625	844
2	3	24	6	51	60	24	102	<u>135</u>
1	3	6	3	9	9	6	12	15
0	1	1	1	1	1	1	1	1
<b>Total</b>	<b>8</b>	<b>168</b>	<b>24</b>	<b>1344</b>	<b>5040</b>	<b>40320</b>	<b>40320</b>	<b>40320</b>
<b>Time, s</b>	<b>0</b>	<b>0</b>	<b>0</b>	<b>30</b>	<b>215</b>	<b>97</b>	<b>40</b>	<b>15</b>

 

# Outline

- Motivation
- Background
- Theoretical Results
- Synthesis of Optimal Circuits
- An Application to Quantum Computing
  - Grover's Search
  - Pseudo-classical Synthesis

# Grover's Search

- A quantum algorithm for associative search (input is not sorted)
  - Search criterion: a classical one-output function  $f$
  - L. K. Grover, "A Framework For Fast Quantum Mechanical Algorithms", *STOC* 1998
  - M. Nielsen and I. Chuang, 2000
- Runs in time  $O(\sqrt{N})$ 
  - any classical algorithm provably requires  $\Omega(N)$  time
- Requires a subroutine (oracle) that
  - changes the phase (sign) of all basis states (bit-strings) that match the search criterion  $f$



# Pseudo-classical Synthesis

- We focus on circuits for Grover oracles
- To change the sign of a bit-string
  - Initialize a qubit to  $|0\rangle - |1\rangle$
  - Compute the classical one-output function  $f$
  - XOR the qubit with  $f$
  - Whenever  $f=1$ , the sign (phase) will change
- Thus, the design of Grover search circuits for a given  $f$ 
  - Is reduced to reversible synthesis
  - Can be solved optimally by our methods

# ROM-based Circuits

- Desired circuits must alter phase of basis states
  - All bits except one must be restored to input values
- Previous work studied ROM-based circuits
  - Constraint: ROM qubits can never change
  - B. Travaglione et al., 2001,  
<http://xxx.lanl.gov/abs/quant-ph/0109016>
  - Theorems + heuristic synthesis algorithms
- Our work: synthesis of pseudo-classical circuits
  - 3 read-only “ROM” wires that can never change
  - 1 wire that can be changed during computation, but must be restored by end
  - 1 wire on which function is computed

# Synthesis Algorithms Compared

- Heuristic synthesis of ROM-based circuits
  - Proposed by Travaglione et al, 2001
  - Based on EXOR-sum decomposition (“EXOR”) (Our code uses Mishchenko’s EXORCISM-4)
  - Imposed a restriction: at most one control bit per gate can be on a ROM bit
- Optimal synthesis (as described earlier)
  - with restriction from Travaglione (“Opt T”)
  - without this restriction (“Opt”)

# Sizes of 3+2 ROM-circuits

Size	0	1	2	3	4	5	6	7	8	9	10	11	12
EXOR	<u>1</u>	4	<u>6</u>	<u>4</u>	<u>4</u>	<u>12</u>	<u>18</u>	<u>12</u>	<u>6</u>	<u>12</u>	<u>19</u>	<u>16</u>	<u>10</u>
OptT	1	4	<u>6</u>	4	4	12	21	24	29	33	44	46	22
Opt	1	7	21	35	36	28	28	36	35	21	7	1	0

Size	13	14	15	16	17	18	19	20	21	22	23	24	25	26
EXOR	<u>8</u>	<u>10</u>	<u>16</u>	<u>19</u>	<u>12</u>	<u>6</u>	<u>12</u>	<u>18</u>	<u>12</u>	<u>4</u>	<u>4</u>	<u>6</u>	<u>4</u>	<u>1</u>
OptT	5	1	0	0	0	0	0	0	0	0	0	0	0	0
Opt	0	0	0	0	0	0	0	0	0	0	0	0	0	0


# Discussion of Empirical Results

- The EXOR-SUM heuristic is sub-optimal
- All methods able to synthesize all 256 fns
  - “Opt T” able to synthesize as many as “Opt”:  
B. Travaglione et al., 2001
- “Opt” results symmetrical about 5-6 gates
  - Function  $x$  requires one fewer gate than  $256-x$
  - Explanation yet to be found
- “Exor” results symmetrical about 13 gates

# Conclusions

- Classical reversible circuits as special-case quantum circuits
- Existence theorems
- Reversible De Morgan's laws
  - Future research on optimization heuristics
- Algorithm for synthesis of optimal circuits
  - Applicable to Grover's search

# Thank You For Your Attention

 

IWLS 2002