

Optimal Synthesis of Linear Reversible Circuits

Ketan Patel, Igor Markov, and John Hayes



*University of Michigan
Electrical Engineering & Computer Science*



Outline

- Motivation
- Background
- Lower Bound
- Synthesis Algorithm
- Application: [Quantum] Stabilizer Circuits
- Future work

Motivation

Reversible Computation


- “Energy-free” computation
- Reversible applications: **cryptology, DSP, etc.**

Quantum Computation

- Application to important quantum circuits: **stabilizer circuits**

C-NOT Gate

Input	Output
00	00
01	01
10	11
11	10

 

First input (**control**) passes through unchanged

Second input (**target**) inverted if control=1


C-NOT is **linear** (under bitwise XOR operation \oplus)

i.e.

$$f(x_1 \oplus x_2) = f(x_1) \oplus f(x_2) \quad \text{for all } x_1, x_2 \in \{0,1\}^n$$

C-NOT Circuits

 Compute linear transformation over $\{0,1\}^n$



$$|0000\rangle \rightarrow |0000\rangle$$

Mapping of $|0001\rangle, |0010\rangle, |0100\rangle, |1000\rangle$ determine full mapping

Example:

$$f(|1100\rangle) = f(|1000\rangle) \oplus f(|0100\rangle)$$

Matrix Representation


Can use matrix representation

Example:

$$\left\{ \begin{array}{l} |100\rangle \rightarrow |001\rangle \\ |010\rangle \rightarrow |011\rangle \\ |001\rangle \rightarrow |101\rangle \end{array} \right\} \Leftrightarrow \begin{bmatrix} 0 & 0 & 1 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \end{bmatrix} \quad |110\rangle \rightarrow \begin{bmatrix} 0 & 0 & 1 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \end{bmatrix} \cdot \begin{bmatrix} 1 \\ 1 \\ 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 1 \\ 1 \end{bmatrix}$$

C-NOT action corresponds to multiplication by **elementary matrix**

 
$$\text{row (target)} \rightarrow \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & \mathbf{1} & 1 \end{bmatrix} \Leftrightarrow \begin{matrix} \text{column (control)} \uparrow \end{matrix}$$



Matrix Representation (cont.)

Concatenation of C-NOT's corresponds to matrix multiplication

Example:

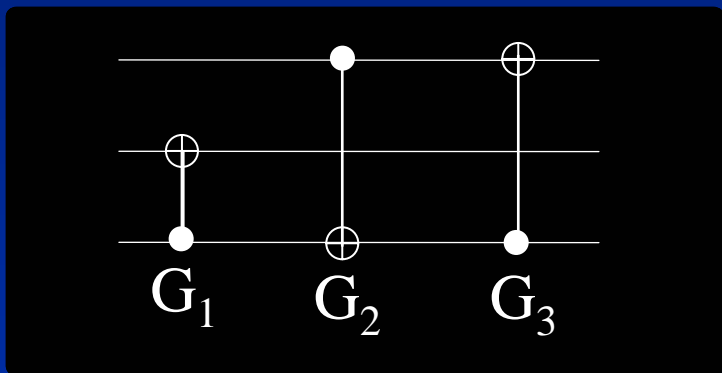

$$\Rightarrow \begin{bmatrix} 0 & 0 & 1 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \end{bmatrix} = \underbrace{\begin{bmatrix} 1 & 0 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}}_{G_3} \cdot \underbrace{\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 1 & 0 & 1 \end{bmatrix}}_{G_2} \cdot \underbrace{\begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 1 \\ 0 & 0 & 1 \end{bmatrix}}_{G_1}$$

Matrix row reduction \Rightarrow decomposition into elementary matrices
(recall Gaussian elimination)

C-NOT Synthesis


C-NOT Synthesis \longleftrightarrow binary matrix row reduction

of gates = # of row operations

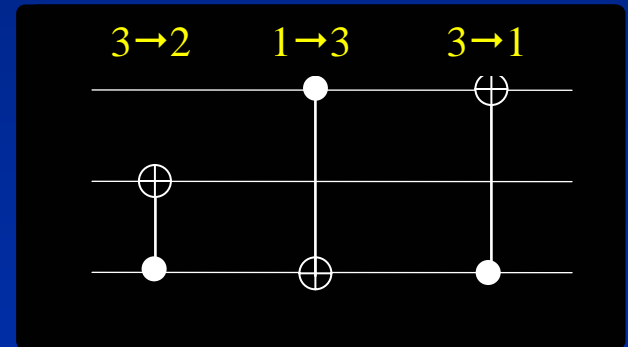Example:

$$\begin{bmatrix} 0 & 0 & 1 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \end{bmatrix} \xrightarrow{3 \rightarrow 1} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \end{bmatrix} \xrightarrow{1 \rightarrow 3} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 1 \\ 0 & 0 & 1 \end{bmatrix} \xrightarrow{3 \rightarrow 2} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 0 & 0 & 1 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \cdot \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 1 & 0 & 1 \end{bmatrix} \cdot \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 1 \\ 0 & 0 & 1 \end{bmatrix}$$



Gaussian Elimination Requires $O(n^2)$ row ops (gates)

Lower Bound

Number of n -wire linear reversible transformations

$$\prod_{i=0}^{n-1} (2^n - 2^i)$$


If all transformations require $\leq d$ gates,
then the number of d -gate circuits must be no smaller

$$\prod_{i=0}^{n-1} (2^n - 2^i) \leq (n(n-1) + 1)^d$$

$$\Rightarrow \boxed{c n^2 / \log n \leq d} \quad \text{for some } c > 0$$

Conclusion: need at least $c n^2 / \log n$ gates

Our Synthesis Algorithm (intuition)

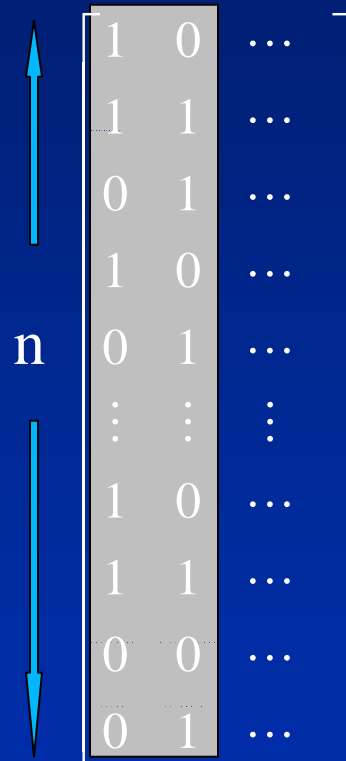

A vertical double-headed arrow on the left side of the matrix is labeled with the letter 'n'. The matrix is enclosed in large square brackets and contains the following rows:

$$\begin{bmatrix} 1 & 0 & \cdots \\ 1 & 1 & \cdots \\ 0 & 1 & \cdots \\ 1 & 0 & \cdots \\ 0 & 1 & \cdots \\ \vdots & \vdots & \vdots \\ 1 & 0 & \cdots \\ 1 & 1 & \cdots \\ 0 & 0 & \cdots \\ 0 & 1 & \cdots \end{bmatrix}$$

Assume n is large

- Use $\leq n$ row ops to eliminate duplicate sub-rows
- Leave no more than 3 non-zero sub-rows
relatively few operations necessary to clear

Reduces number of ops by factor ~ 2

Synthesis Algorithm

- Group columns into sections of size $\leq \alpha \log n$ with $\alpha < 1$
- Eliminate duplicate sub-rows in each column section
row ops = $O(n)$ • # sections = $O(n^2/\log n)$
- Place 1s on the diagonal
row ops = $O(n)$
- Eliminate (relatively few) remaining off-diagonal 1s
row ops = $O(2^{\alpha \log n})$ • # sections
= $O(n^\alpha) \cdot n/(\alpha \log n) = O(n^{1+\alpha}/\log n)$

Total # of row operations: $O(n^2/\log n)$

Execution Time

Execution time dominated by row ops


$$\Rightarrow O(n^3/\log n)$$

Execution time for Gaussian Elimination

$$\Rightarrow O(n^3)$$


...but how soon do the asymptotics kick in?

Empirical Results

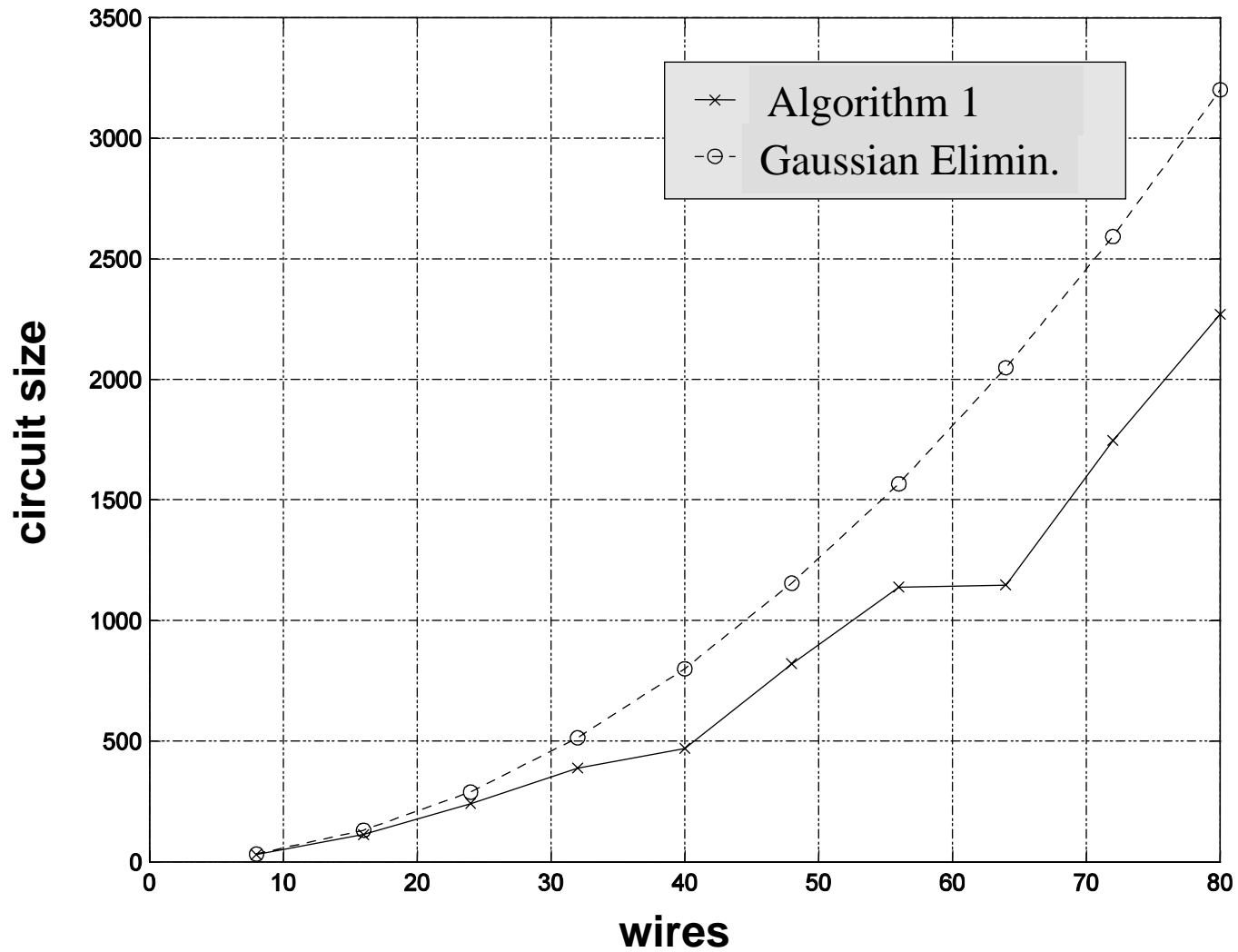

Application: Stabilizer Circuits

 - Important class of quantum circuits
- Composed of Hadamard, Phase, and C-NOT gates
- Can use blocks of H, P & C gates to synthesize
(Aaronson & Gottesman)



Circuit size dominated by size of C-blocks

Related Topics

- Optimal column partitioning
- Synthesis of general reversible circuits
 - T-C-N-T decomposition
- Applications to synthesis of quantum circuits
 - E.g., via the Gottesman-Knill theorem
- Reducing circuit depth rather than size

Thank you