

Combinational Logic Design Techniques

Introduction to Digital Systems

Lecture #5

Prepared by
Pinaki Mazumder
Professor of Computer Science & Engineering
University of Michigan

Copyrighted Materials © Prof. Pinaki Mazumder

Today's Lecture Addresses

1. How to design a digital system when the design specs are given in plain English
2. Other Representations - Equation, Truth Table, & Input-Output Waveforms
3. Minterm Expansion, Maxterm Expansion, Canonical SOP, Canonical POS, Self-Duality
4. Verilog Modeling and Design using Verilog

Reading Assignment: Lecture Slides, Textbook Chapter 2, Sec. 2.6-2.8; pp. 61-83; Chapter 9, Sec. 9.2-9.4; pp. 489-511.

Digital System Design Principles

1. Problem Statement
2. Canonical Implementation
3. Minimization by Boolean Algebra
4. Scaling of Problem Size

Copyrighted Materials © Prof. Pinaki Mazumder

Objectives of Today's Lecture

Given a Problem in English Statement

1. How to assign Boolean variables
2. How to obtain Truth Table
3. How to write the
 - canonical sum of products (SOP)
 - canonical product of sums (POS)
4. How to minimize logic expressions using Boolean algebra

Copyrighted Materials © Prof. Pinaki Mazumder

Objectives of Today's Lecture

5. How to Implement SOP in AND-OR, NAND-NAND, OR-NAND, NOR-OR Gates
6. How to Implement POS in OR-AND, NOR-NOR, AND-NOR, NAND-AND Gates

Altogether EIGHT (4 SOP and 4 POS) 2-level logic gate implementations can be done

Copyrighted Materials © Prof. Pinaki Mazumder


Step #1: ASSIGN BOOLEAN VARIABLES AND DEFINE THEIR VALUES with respect to the PROBLEM

Let L be the Boolean variable denoting the lamp, and A , B , and C are switches on the *first*, the *second* and the *third* floors, respectively.

Let each switch, $X \in \{A, B, C\}$ has two positions – Up and Down.

Let $X = 1 \rightarrow$ switch X is in Up position
 $X = 0 \rightarrow$ switch X is in Down position

 Let $L = 0 \rightarrow$ lamp L is Off
 $L = 1 \rightarrow$ lamp L is On



Copyrighted Materials © Prof. Pinaki Mazumder

PROBLEM STATEMENT



In a 3-story building, there is a lamp to illuminate a stairwell.

The lamp can be *independently* turned **ON** and **OFF** from each floor by flipping an electrical switch on that floor. Design the logic circuit for the problem.

Copyrighted Materials © Prof. Pinaki Mazumder

Note that Lamp can be either **On** or **Off**
But Switches can be either **Up** or **Down**. By flipping switches **Up** or **Down**, the Lamp can be turned **On** or **Off**.

Step #2: WRITE THE TRUTH TABLE

The **TRUTH TABLE** Shows the Input-Output Relationships between Boolean variables.

- Input Boolean Variables: A , B , and C
- Output Boolean Variable: L
- Boolean Function: $L(A,B,C)$

Number of Input Variables = 3 \rightarrow
Number of Rows = 8.

Copyrighted Materials © Prof. Pinaki Mazumder

Switch and Lamp States	Switch A	Switch B	Switch C	Lamp L
A=B=C=DOWN, L is OFF	0	0	0	0
C=UP, A=B=DOWN, L is ON	0	0	1	1
A=C=DOWN, B=UP, L is ON	0	1	0	1
B=C=UP, A=DOWN, L is OFF	0	1	1	0
B=C=DOWN, A=UP, L is ON	1	0	0	1
A=C=UP, B=DOWN, L is OFF	1	0	1	0
C=DOWN, A=B=UP, L is OFF	1	1	0	0
A=B=C=UP, L is ON	1	1	1	1

All 3 switches DOWN, Lamp is OFF.

↓ 001, 010, 100

2 switches DOWN, 1 UP, Lamp is ON.

↓ 011, 101, 110

1 switch DOWN, 2 UP, Lamp is OFF.

↓ 111

All 3 switches UP, Lamp is ON.

Therefore, L is ON (1) iff (A is DOWN (0) & B is DOWN (0) & C is UP (1)) OR (A is DOWN (0) & B is UP (1) & C is DOWN (0)) OR (A is in UP (1) & B is DOWN (0) & C is DOWN (0)) OR (A is UP (1) & B is UP (1) & C is UP (1))

Copyrighted Materials © Prof. Pinaki Mazumder

Step #4: DIRECT IMPLEMENTATION OF THE CANONICAL SOP EXPRESSION

Cost of Implementation

No. of Gates = Gate cost = 4 X 3-input AND + 1 X 4-input OR

No. of Literals = Literal Cost = 3 X 4 = 12 (3 literals per gate)

No. of Transistors = 4 x (6+2) + (8+2) = 32 + 10 = 42

Rule: In standard CMOS technology logic gates generally have negated outputs. In order to implement an N-input NAND or NOR gate, 2N transistors are required. In order to implement an AND or OR gate, an additional NOT gate using 2 transistors is needed. Hence, NAND and NOR gates are more commonly used (instead of AND and OR gates) in CMOS implementation of Boolean functions.

Copyrighted Materials © Prof. Pinaki Mazumder

Hence, $L=1$ iff $(A=B=0, C=1)$ OR $(A=C=0, B=1)$ OR $(A=1, B=C=0)$ OR $(A=B=C=1)$

Step #3: WRITE CANONICAL SUM OF PRODUCTS (STANDARD SOP) FOR THE OUTPUT BOOLEAN VARIABLE(S)

$L(A, B, C) = A'B'C + A'BC' + AB'C' + ABC$

Note that each Product term has all three inputs in True or Complement form. These inputs are called Literals, and each product term is called a Minterm. The output function can be written as a sum of minterms, $L(A,B,C) = \Sigma(1,2,4,7)$ which is called the Minterm Expansion for L(A,B,C).

Copyrighted Materials © Prof. Pinaki Mazumder

Step #5: MINIMIZATION OF THE CANONICAL SOP

Use Boolean Algebra to Simplify the Canonical Expression

$$\begin{aligned}
 L(A, B, C) &= AB'C' + A'BC' + A'B'C + ABC \\
 &= (AB' + A'B).C' + (A'B' + AB).C \quad (\text{Law of Distribution}) \\
 &= (A \oplus B).C' + (A \oplus B).C \quad (\text{Def. of Ex-Or Equivalence}) \\
 &= (A \oplus B) \oplus C = A \oplus B \oplus C.
 \end{aligned}$$

Cost of Implementation

Gate cost = 2 X 2-input Ex-OR

Literal Cost = 3

No of Transistors = 6 x 2 = 12

Copyrighted Materials © Prof. Pinaki Mazumder

Savings due to Minimization

Gate Cost = $(5-2)/5 = 60\%$
Literal Cost = $(12-3)/12 = 9/12 = 75\%$
No. of Transistors = $(42-12)/42 = 30/42 = 75\%$



**How many Minterms appear in the Expression?
(Exponential Growth of the Output Expression)**

For $n = 3$, # of minterms or product terms = 4
For $n = 11$, # of minterms or product terms = 1024.

Copyrighted Materials © Prof. Pinaki Mazumder

Combinational Logic Design Techniques

Introduction to Digital Systems

Lecture #5 contd.

Prepared by
Pinaki Mazumder
Professor of Computer Science & Engineering
University of Michigan

Copyrighted Materials © Prof. Pinaki Mazumder



Exclusive OR and Exclusive NOR (or Equivalence) gates are used in such pathological cases when the minterms cannot be combined to yield smaller product terms.

GENERAL SOLUTION:
For an n -story building,
the Lamp equation will be given by:

$$L(S_0, S_1, S_2, \dots, S_{n-1}) = S_0 \oplus S_1 \oplus S_2 \oplus \dots \oplus S_{n-1}$$

Copyrighted Materials © Prof. Pinaki Mazumder

Digital System Design

1. Majority Gate
2. Canonical SOP Implementation
3. Minimization of SOP by Boolean Algebra
4. Canonical POS Implementation
5. Minimization of POS by Boolean Algebra
6. Self-Duality of Majority Function

Copyrighted Materials © Prof. Pinaki Mazumder

DESIGN OF A MAJORITY GATE



An n -input Majority Gate has an output $Z = 1$ iff at least $\lfloor n/2 \rfloor + 1$ inputs are 1. Otherwise, $Z = 0$.

For a 3-input (A , B , and C) Majority Gate, at least 2 inputs must be 1 in order that output $Z(A,B,C) = 1$.

Step #1: IDENTIFY BOOLEAN VARIABLES

Input Variables = A, B, C
Output Variable = Z

Copyrighted Materials © Prof. Pinaki Mazumder

Therefore, Z is ON (1) iff $(A=0 \ \& \ B=1 \ \& \ C=1)$ OR $(A=1 \ \& \ B=0 \ \& \ C=1)$ OR $(A=1 \ \& \ B=1 \ \& \ C=0)$ OR $(A=1 \ \& \ B=1 \ \& \ C=1)$

Step #3: WRITE CANONICAL SUM OF PRODUCTS (STANDARD SOP) OR MINTERM EXPANSION FOR THE OUTPUT BOOLEAN VARIABLE

$$Z(A, B, C) = A'BC + AB'C + ABC' + ABC = \sum m(3,5,6,7)$$

Note that each **Product term** has all three inputs in **true** or **complement** form. These inputs are called **literals**, and each product term is called a **Minterm**. The expression $\sum m(3,5,6,7)$ is called the **Minterm Expansion for $Z(A, B, C)$**

Copyrighted Materials © Prof. Pinaki Mazumder

Step #2: WRITE THE TRUTH TABLE

The TRUTH TABLE shows the Input-Output relationships between Boolean variables.


Input Boolean Variables: A, B , and C ;

Output Boolean Variable: Z

Minterm and Maxterm	A	B	C	Z
$m_0 = A'B'C'$ $M_0 = A+B+C$	0	0	0	0
$m_1 = A'B'C$ $M_1 = A+B+C'$	0	0	1	0
$m_2 = A'BC'$ $M_2 = A+B'+C$	0	1	0	0
$m_3 = A'BC$ $M_3 = A+B'+C'$	0	1	1	1
$m_4 = AB'C'$ $M_4 = A'+B+C$	1	0	0	0
$m_5 = AB'C$ $M_5 = A'+B+C'$	1	0	1	1
$m_6 = ABC'$ $M_6 = A'+B'+C$	1	1	0	1
$m_7 = ABC$ $M_7 = A'+B'+C'$	1	1	1	1

Copyrighted Materials © Prof. Pinaki Mazumder

 Step #4: DIRECT IMPLEMENTATION OF THE CANONICAL SOP EXPRESSION



Implementation Cost:
No. of gates = 5
No. of literals = $4 \times 3 = 12$
No. of transistors = $4 \times [3 \times 2 \text{ (NAND)} + 2 \text{ (NOT)}] + 1 \times [4 \times 2 \text{ (NOR)} + 2 \text{ (NOT)}] = 42$


Rule: In standard CMOS technology logic gates generally have negated outputs. In order to implement an N -input NAND or NOR gate, $2N$ transistors are required. In order to implement an AND or OR gate, an additional NOT gate using 2 transistors is needed. Hence, NAND and NOR gates are more commonly used (instead of AND and OR gates) in CMOS implementation of Boolean functions.

Copyrighted Materials © Prof. Pinaki Mazumder

MINIMIZATION OF THE CANONICAL SOP

Use Boolean Algebra to Simplify the Canonical Expression
 
$$\begin{aligned} Z(A, B, C) &= A'BC + AB'C + ABC + ABC \\ &= A'BC + ABC + AB'C + ABC + ABC + ABC \text{ (Idempotent Laws)} \\ &= (A+A)BC + A(B+B')C + AB(C+C) \text{ (Distributive Laws)} \\ &= 1.BC + A.1.C + AB.1 \text{ (Laws of Complementarity)} \\ &= BC + CA + AB \text{ (since, } Y.1 = Y \text{; Commutative Laws)} \end{aligned}$$




Implementation Cost:

$$\begin{aligned} \text{No. of gates} &= 4 \text{ (Savings = 20\%)} \\ \text{No. of literals} &= 3 \times 2 = 6 \text{ (Savings = 50\%)} \\ \text{No. of transistors} &= \\ &= 3 \times [2 \times 2 \text{ (NAND)} + 2 \text{ (NOT)}] \\ &+ 1 \times [3 \times 2 \text{ (NOR)} + 2 \text{ (NOT)}] \\ &= 26 \text{ (Savings = 16\%)} \end{aligned}$$

Copyrighted Materials © Prof. Pinaki Mazumder

The above expression for $Z(A,B,C)$ is called **CANONICAL PRODUCT OF SUMS, or PRODUCT OF MAXTERMS, or MAXTERM EXPANSION FORM.**
Note that $Z(A,B,C) = \Sigma m(3,5,6,7) = \Pi M(0,1,2,4)$
Hence, the SOP and POS implementations are functionally equivalent.

 Step #4: DIRECT IMPLEMENTATION OF THE CANONICAL POS EXPRESSION



Copyrighted Materials © Prof. Pinaki Mazumder

ALTERNATIVE IMPLEMENTATION

CANONICAL PRODUCT OF SUMS OR MAXTERM EXPANSION

Alternatively, Z is OFF (0), i.e., Z' is ON (1) iff $(A=0 \& B=0 \& C=0)$ OR $(A=0 \& B=0 \& C=1)$ OR $(A=0 \& B=1 \& C=0)$ OR $(A=1 \& B=0 \& C=0)$

$$Z'(A, B, C) = A'B'C' + A'B'C + A'BC' + AB'C' = \Sigma m(0,1,2,4)$$

$$\rightarrow Z(A, B, C) = [A'B'C' + A'B'C + A'BC' + AB'C']'$$

$$\rightarrow Z(A, B, C) = (A'B'C')' \cdot (A'B'C)' \cdot (A'BC')' \cdot (AB'C')'$$

(applying De Morgan's Laws)

$$\rightarrow Z(A, B, C) = (A+B+C) \cdot (A+B+C') \cdot (A+B'+C) \cdot (A'+B+C)$$

$$\rightarrow Z(A, B, C) = M_0.M_1.M_2.M_4 = \Pi M(0,1,2,4)$$

Copyrighted Materials © Prof. Pinaki Mazumder

Step #5: MINIMIZATION OF THE CANONICAL POS

Canonical POS expression for $Z(A,B,C)$ is given by:

$$\begin{aligned} Z(A, B, C) &= (A+B+C) \cdot (A+B+C') \cdot (A+B'+C) \cdot (A'+B+C) \\ Z(A, B, C) &= [(A+B+C) \cdot (A+B+C')] \cdot [(A+B'+C) \cdot (A'+B+C)] \\ &= [X = X \cdot X, \text{ Laws of Idempotence}] \end{aligned}$$

$$Z(A, B, C) = (A+B) \cdot (A+C) \cdot (B+C) \text{ [Laws of Complementarity, } (X+Y) \cdot (X+Y') = X]$$

Dual of POS = $Z_D(A, B, C) = A \cdot B + B \cdot C + C \cdot A = Z(A, B, C)$ of SOP
 \rightarrow Majority Function (Z) is Self-Dual.

Copyrighted Materials © Prof. Pinaki Mazumder

2-LEVEL LOGIC IMPLEMENTATION STYLES

Sum of Products (SOP)

1. AND-OR: $Z = AB + BC + CA$

2. NAND-NAND: $Z = \overline{\overline{AB + BC + CA}}$
 $= \overline{\overline{AB} \cdot \overline{BC} \cdot \overline{CA}}$

Inverted Inputs

3. OR-NAND: $Z = \overline{(A+B) \cdot (B+C) \cdot (C+A)}$

4. NOR-OR: $Z = \overline{(A+B)' + (B+C)' + (C+A)'}$

Copyrighted Materials © Prof. Pinaki Mazumder

Large Circuit Diagram Becomes Messy



9.1

- A drawing of a circuit, or *schematic*, contains graphical information about a design

- Inverter is above the OR gate, AND gate is to the right, etc.

- Such graphical information may not be useful for large designs

- Can use textual language instead

  

Digital Design 2e
Copyright © 2010
Frank Vahid

Note: Slides with animation are denoted with a small red "a" near the animated items.

27

Product of Sums (POS)

1. OR-AND $Z = (A+B)(B+C)(C+A)$

2. NOR-NOR $Z = \overline{\overline{(A+B)(B+C)(C+A)}}$

Inverted Inputs $= \overline{[(A+B)' + (B+C)' + (C+A)']}$

3. AND-NOR $Z = \overline{(A'B)' + (B'C)' + (C'A)'}$

4. NAND-AND $Z = \overline{\overline{AB} \cdot \overline{BC} \cdot \overline{CA}}$


Therefore, given a Boolean expression, you can implement the expression in 8 different styles.

Copyrighted Materials © Prof. Pinaki Mazumder

- A drawing of a circuit, or *schematic*, contains graphical information about a design

- Such graphical information may not be useful for large designs

- Can use textual language instead

 

28

Computer-Readable Textual Language for Describing Hardware Circuits: HDLs

- **Hardware description language (HDL)**
 - Intended to describe circuits textually, for a computer to read
 - Evolved starting in the 1970s and 1980s
- **Popular languages today include:**
 - VHDL –Defined in 1980s by U.S. military; Ada-like language
 - Verilog –Defined in 1980s by a company; C-like language
 - SystemC –Defined in 2000s by several companies; consists of libraries in C++



29

```
/usr/caen/ius-8.2/tools/bin/ncverilog probs.v
```

```
ncsim> source /usr/caen/ius-8.2/tools/inca/files/ncsimrc
ncsim> run
```

```
A:0 B:0 C:0 majority:0 lamp:0
A:0 B:0 C:1 majority:0 lamp:1
A:0 B:1 C:0 majority:0 lamp:1
A:0 B:1 C:1 majority:1 lamp:0
A:1 B:0 C:0 majority:0 lamp:1
A:1 B:0 C:1 majority:1 lamp:0
A:1 B:1 C:0 majority:1 lamp:0
A:1 B:1 C:1 majority:1 lamp:1
```

Majority = 1, if at least 2 inputs are 1.

Lamp = 1, if odd number of inputs are 1.

```
Simulation complete via $finish(1) at time 39 NS + 0
./probs.v:46 $finish;
```

```
ncsim> exit
```


Copyrighted Materials © Prof. Pinaki Mazumder

```
VERILOG CODE
timescale 1ns/1ps
module probs(majority, lamp_on);
  output reg majority; output reg lamp_on;
  reg A; reg B; reg C;
  always
    #5 C <= ~C;
  end
  always
    #10 B <= ~B;
  end
  always
    #20 A <= ~A;
  end
  always @(A or B or C)
  begin
    if ((B && C) || (A && C) || (A && B))
      majority = 1'b1;
    else
      majority = 1'b0;
    end
    if (~A && (~B && C) || (B && ~C)) || (A && (~B && ~C) || (B && C))
      lamp_on = 1'b1;
    else
      lamp_on = 1'b0;
    end
  end
  initial
  begin
    $monitor("A:%b B:%b C:%b majority:%b lamp:%b ", A, B, C, majority, lamp_on);
    A <= 0; B <= 0; C <= 0; #39; $finish;
  end
endmodule
```

Copyrighted Materials © Prof. Pinaki Mazumder

Hardware Description Language

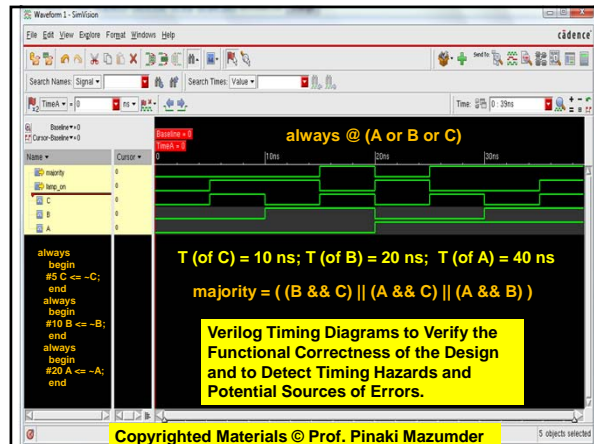VERILOG Simulation Codes are written for Designing Large Digital Systems and are Verified for Functional and Timing Correctness before Hardware Implementation is Made using FPGA or Discrete Chips.



Copyrighted Materials © Prof. Pinaki Mazumder

ANOTHER EXAMPLE


Before Digital Gates

- FULL ADDER that consists of

3 inputs (A, B, Ci) and two outputs (S, Co)

$$S = A \oplus B \oplus Ci$$


$$Co = AB + BCi + CiA$$

 

A → Addend
B → Augend
Ci → Carry In

S → Sum
Co → Carry Out

 Copyrighted Materials © Prof. Pinaki Mazumder




Describing a Full-Adder in Verilog

- Module

- Declares inputs/outputs
- Described behaviorally (could have been described structurally)
- "always" procedure
 - Sensitive to inputs
- Computes expressions, sets outputs

$$s = a \text{ xor } b \text{ xor } ci$$

$$co = bc + ac + ab$$

 

Chapter 9 of Vahid





```
module FullAdder(a, b, ci, s, co);
    input a, b, ci;
    output s, co;
    reg s, co;

    always @(a or b or ci)
    begin
        s <= a ^ b ^ ci;
        co <= (b & ci) | (a & ci) | (a & b);
    end
endmodule
```

Hierarchical Design of a 4-bit Ripple Carry Adder (RCA)

$$A[0:3] + B[0:3] = S[0:3], Co$$

  


Hierarchical Design Method Allows the Digital System to Scale up Easily and Reduces the Design Complexity

Copyrighted Materials © Prof. Pinaki Mazumder

Describing a Carry-Ripple Adder in Verilog

- Module

 - Declares inputs/outputs
- Uses vectors for 4-bit inputs/outputs
- Described structurally by composing four full-adders (could have been described behaviorally instead)
- Instantiates four full-adders, connects
 - Note use of three internal wires for connecting carry-out of one stage to carry-in of next stage




```
module CarryRippleAdder4(a, b, ci, s, co);
    input [3:0] a;
    input [3:0] b;
    input ci;
    output [3:0] s;
    output co;

    wire co1, co2, co3;

    FullAdder FullAdder1(a[0], b[0], ci, s[0], co1);
    FullAdder FullAdder2(a[1], b[1], co1, s[1], co2);
    FullAdder FullAdder3(a[2], b[2], co2, s[2], co3);
    FullAdder FullAdder4(a[3], b[3], co3, s[3], co);
endmodule
```



Chapter 9 of Vahid

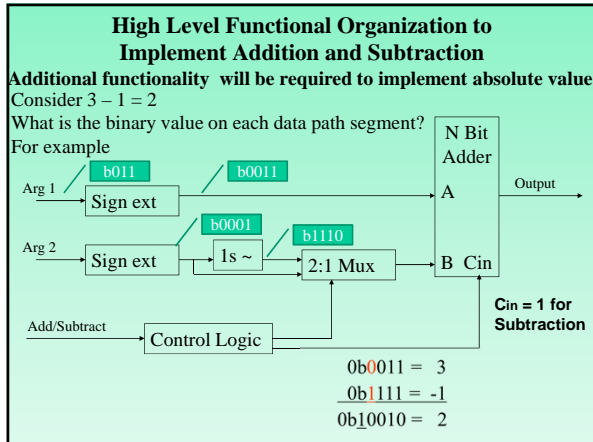

- ### Today's Lecture Addresses
1. How to design a digital system when the design specs are given in plain English
 2. Other Representations - Equation, Truth Table, & Input-Output Waveforms
 3. Minterm Expansion, Maxterm Expansion, Canonical SOP, Canonical POS, Self-Duality
 4. Verilog Modeling and Design using Verilog
- Reading Assignment: Lecture Slides, Textbook Chapter 2, Sec. 2.6-2.8; pp. 61-83; Chapter 9, Sec. 9.2-9.4; pp. 489-511.