

Built-In Self-Testing Pattern Generation and Response Compaction

- Motivation and economics
- Definitions
- *Built-in self-testing (BIST)* process
- *BIST pattern generation (PG)*
- *BIST response compaction (RC)*
- *Aliasing probability*
- Example
- Summary

BIST Motivation

- Useful for field test and diagnosis (less expensive than a local automatic test equipment)
- Software tests for field test and diagnosis:
 - Low hardware fault coverage
 - Low diagnostic resolution
 - Slow to operate
- Hardware BIST benefits:
 - Lower system test effort
 - Improved system maintenance and repair
 - Improved component repair
 - Better diagnosis

Costly Test Problems Alleviated by BIST

- Increasing chip logic-to-pin ratio – harder observability
- Increasingly dense devices and faster clocks
- Increasing test generation and application times
- Increasing size of test vectors stored in ATE
- Expensive ATE needed for 1 GHz clocking chips
- Hard testability insertion – designers unfamiliar with gate-level logic, since they design at behavioral level
- *In-circuit testing* no longer technically feasible
- Shortage of test engineers
- Circuit testing cannot be easily partitioned

Typical Quality Requirements

- 98% single stuck-at fault coverage
- 100% interconnect fault coverage
- Reject ratio – 1 in 100,000

Benefits and Costs of BIST with DFT

Level	Design and test	Fabri- cation	Manuf. Test	Maintenance test	Diagnosis and repair	Service interruption
Chips	+ / -	+	-			
Boards	+ / -	+	-			
System	+ / -	+	-	-	-	-

- + Cost increase
- Cost saving
- +/- Cost increase may balance cost reduction

Economics – BIST Costs

- Chip area overhead for:
 - Test controller
 - Hardware pattern generator
 - Hardware response compacter
 - Testing of BIST hardware
- Pin overhead – At least 1 pin needed to activate BIST operation
- Performance overhead – extra path delays due to BIST
- Yield loss – due to increased chip area or more chips in system because of BIST
- Reliability reduction – due to increased area
- Increased BIST hardware complexity – happens when BIST hardware is made testable

BIST Benefits

- **Faults tested:**
 - Single combinational / sequential stuck-at faults
 - Delay faults
 - Single stuck-at faults in BIST hardware
- **BIST benefits**
 - Reduced testing and maintenance cost
 - Lower test generation cost
 - Reduced storage / maintenance of test patterns
 - Simpler and less expensive ATE
 - Can test many units in parallel
 - Shorter test application times
 - Can test at functional system speed


Definitions

- **BILBO** – *Built-in logic block observer*, extra hardware added to flip-flops so they can be reconfigured as an LFSR pattern generator or response compacter, a scan chain, or as flip-flops
- **Concurrent testing** – Testing process that detects faults during normal system operation
- **CUT** – *Circuit-under-test*
- **Exhaustive testing** – Apply all possible 2^n patterns to a circuit with n inputs
- **Irreducible polynomial** – Boolean polynomial that cannot be factored
- **LFSR** – *Linear feedback shift register*, hardware that generates pseudo-random pattern sequence

More Definitions


- **Primitive polynomial** – Boolean polynomial $p(x)$ that can be used to compute increasing powers n of x^n modulo $p(x)$ to obtain all possible non-zero polynomials of degree less than $p(x)$
- **Pseudo-exhaustive testing** – Break circuit into small, overlapping blocks and test each exhaustively
- **Pseudo-random testing** – Algorithmic pattern generator that produces a subset of all possible tests with most of the properties of randomly-generated patterns
- **Signature** – Any statistical circuit property distinguishing between bad and good circuits
- **TPG** – *Hardware test pattern generator*

BIST Process

 


- **Test controller** – Hardware that activates self-test simultaneously on all PCBs
- Each board controller activates parallel chip BIST
- Diagnosis effective only if very high fault coverage

BIST Architecture

 


- **Note:** BIST cannot test wires and transistors:
 - From PI pins to Input MUX
 - From POs to output pins

BILBO – Works as Both a PG and a RC

 


- **Built-in Logic Block Observer (BILBO)** – 4 modes:
 1. Flip-flop
 2. LFSR pattern generator
 3. LFSR response compacter
 4. Scan chain for flip-flops

Complex BIST Architecture

 

- Testing epoch I:
 - LFSR1 generates tests for CUT1 and CUT2
 - BILBO2 (LFSR3) compacts CUT1 (CUT2)
- Testing epoch II:
 - BILBO2 generates test patterns for CUT3
 - LFSR3 compacts CUT3 response

Bus-Based BIST Architecture

 


- Self-test control broadcasts patterns to each CUT over bus – parallel pattern generation
- Awaits bus transactions showing CUT's responses to the patterns: serialized compaction

Pattern Generation

- Store in ROM – too expensive
- Exhaustive
- Pseudo-exhaustive
- Pseudo-random (LFSR) – Preferred method
- Binary counters – use more hardware than LFSR
- Modified counters
- Test pattern augmentation
 - LFSR combined with a few patterns in ROM
 - Hardware diffracter – generates pattern cluster in neighborhood of pattern stored in ROM

Exhaustive Pattern Generation

 


- Shows that every state and transition works
- For n -input circuits, requires all 2^n vectors
- Impractical for $n > 20$

Pseudo-Exhaustive Method


- Partition large circuit into fanin cones
 - Backtrace from each PO to PIs influencing it
 - Test fanin cones in parallel!
- Reduced # of tests from $2^8 = 256$ to $2^5 \times 2 = 64$
 - Incomplete fault coverage

Pseudo-Exhaustive Pattern Generation

 


Random Pattern Testing

 Bottom:
Random-
Pattern
Resistant
circuit



Pseudo-Random Pattern Generation

 

- **Standard Linear Feedback Shift Register (LFSR)**
 - Produces patterns algorithmically - repeatable
 - Has most of desirable random # properties
- **Need not cover all 2^n input combinations**
- **Long sequences needed for good fault coverage**

Matrix Equation for Standard LFSR


$$\begin{bmatrix} X_0(t+1) \\ X_1(t+1) \\ \vdots \\ X_{n-3}(t+1) \\ X_{n-2}(t+1) \\ X_{n-1}(t+1) \end{bmatrix} = \begin{bmatrix} 0 & 1 & 0 & \dots & 0 & 0 \\ 0 & 0 & 1 & \dots & 0 & 0 \\ \vdots & \vdots & \vdots & \ddots & \vdots & \vdots \\ 0 & 0 & 0 & \dots & 1 & 0 \\ 0 & 0 & 0 & \dots & 0 & 1 \\ 1 & h_1 & h_2 & \dots & h_{n-2} & h_{n-1} \end{bmatrix} \begin{bmatrix} X_0(t) \\ X_1(t) \\ \vdots \\ X_{n-3}(t) \\ X_{n-2}(t) \\ X_{n-1}(t) \end{bmatrix}$$

$$X(t+1) = T_S X(t) \quad (T_S \text{ is companion matrix})$$

LFSR Implements a Galois Field

- **Galois field (mathematical system):**
 - Multiplication by x same as right shift of LFSR
 - Addition operator is XOR (\oplus)
- **T_S companion matrix:**
 - 1st column 0, except n th element which is always 1 (X_0 always feeds X_{n-1})
 - Rest of row n - feedback coefficients h_i
 - Rest is identity matrix I - means a right shift
- **Near-exhaustive (maximal length) LFSR**
 - Cycles through $2^n - 1$ states (excluding all-0)
 - 1 pattern of n 1's, one of $n-1$ consecutive 0's

Standard n -Stage LFSR Implementation

 

- **Autocorrelation** - any shifted sequence same as original in $2^{n-1} - 1$ bits, differs in 2^{n-1} bits
- If $h_i = 0$, that XOR gate is deleted

LFSR Theory

- Cannot initialize to all 0's - hangs
- If X is initial state, progresses through states $X, T_S X, T_S^2 X, T_S^3 X, \dots$
- **Matrix period:**
 - Smallest k such that $T_S^k = I$
 - $k \equiv$ LFSR cycle length
- Described by characteristic polynomial:


$$f(x) = |T_S - I X|$$

$$= 1 + h_1 x + h_2 x^2 + \dots + h_{n-1} x^{n-1} + x^n$$

Modular LFSR Matrix

$$\begin{bmatrix} X_0(t+1) \\ X_1(t+1) \\ X_2(t+1) \\ \vdots \\ X_{n-3}(t+1) \\ X_{n-2}(t+1) \\ X_{n-1}(t+1) \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & \dots & 0 & 0 & 1 \\ 1 & 0 & 0 & \dots & 0 & 0 & h_1 \\ 0 & 1 & 0 & \dots & 0 & 0 & h_2 \\ \vdots & \vdots & \vdots & \ddots & \vdots & \vdots & \vdots \\ 0 & 0 & 0 & \dots & 0 & 0 & h_{n-3} \\ 0 & 0 & 0 & \dots & 1 & 0 & h_{n-2} \\ 0 & 0 & 0 & \dots & 0 & 1 & h_{n-1} \end{bmatrix} \begin{bmatrix} X_0(t) \\ X_1(t) \\ X_2(t) \\ \vdots \\ X_{n-3}(t) \\ X_{n-2}(t) \\ X_{n-1}(t) \end{bmatrix}$$

Example Modular LFSR

 

- $f(x) = 1 + x^2 + x^7 + x^8$
- Read LFSR tap coefficients from left to right

Primitive Polynomials

- Want LFSR to generate all possible $2^n - 1$ patterns (except the all-0 pattern)
- Conditions for this - must have a *primitive polynomial*:
 - *Monic* - coefficient of x^n term must be 1
 - Modular LFSR - all D FF's must right shift through XOR's from X_0 through X_1, \dots , through X_{n-1} , which must feed back directly to X_0
 - Standard LFSR - all D FF's must right shift directly from X_{n-1} through X_{n-2}, \dots , through X_0 , which must feed back into X_{n-1} through XORing feedback network

Primitive Polynomials (continued)

- Characteristic polynomial must divide the polynomial $1 + x^k$ for $k = 2^n - 1$, but not for any smaller k value
- See Appendix B of book for tables of primitive polynomials
- If $p(\text{error}) = 0.5$, no difference between behavior of primitive & non-primitive polynomial
- But $p(\text{error})$ is rarely = 0.5 In that case, non-primitive polynomial LFSR takes much longer to stabilize with random properties than primitive polynomial LFSR

Weighted Pseudo-Random Pattern Generation




- If $p(1)$ at all PIs is 0.5, $p_F(1) = 0.5^8 = \frac{1}{256}$
- $p_F(0) = 1 - \frac{1}{256} = \frac{255}{256}$
- Will need enormous # of random patterns to test a stuck-at 0 fault on F -- LFSR $p(1) = 0.5$
 - We must not use an ordinary LFSR to test this
- IBM - holds patents on weighted pseudo-random pattern generator in ATE

Weighted Pseudo-Random Pattern Generator

- LFSR $p(1) = 0.5$
- Solution: Add programmable weight selection and complement LFSR bits to get $p(1)$'s other than 0.5
- Need 2-3 weight sets for a typical circuit
- Weighted pattern generator drastically shortens pattern length for pseudo-random patterns

Weighted Pattern Gen.

 

w_1	w_2	Inv.	p (output)	w_1	w_2	Inv.	p (output)
0	0	0	$\frac{1}{2}$	1	0	0	$\frac{1}{8}$
0	0	1	$\frac{1}{2}$	1	0	1	$\frac{7}{8}$
0	1	0	$\frac{1}{4}$	1	1	0	$\frac{1}{16}$
0	1	1	$\frac{3}{4}$	1	1	1	$\frac{15}{16}$

Cellular Automata (CA)


- Superior to LFSR – even “more” random
 - No shift-induced bit value correlation
 - Can make LFSR more random with linear phase shifter
- Regular connections – each cell only connects to local neighbors

	$x_{c-1}(t) \ x_c(t) \ x_{c+1}(t)$ Gives CA cell connections							
	111	110	101	100	011	010	001	000
● $x_c(t+1)$	0	1	0	1	1	0	1	0

$$2^6 + 2^4 + 2^3 + 2^1 = 90 \text{ Called Rule 90}$$

- $x_c(t+1) = x_{c-1}(t) \oplus x_{c+1}(t)$

Cellular Automaton

 

- Five-stage hybrid cellular automaton
- Rule 150: $x_c(t+1) = x_{c-1}(t) \oplus x_c(t) \oplus x_{c+1}(t)$
- Alternate Rule 90 and Rule 150 CA

Test Pattern Augmentation

- Secondary ROM – to get LFSR to 100% SAF coverage
 - Add a small ROM with missing test patterns
 - Add extra circuit mode to Input MUX – shift to ROM patterns after LFSR done
 - Important to compact extra test patterns
- Use diffracter:
 - Generates cluster of patterns in neighborhood of stored ROM pattern
- Transform LFSR patterns into new vector set
- Put LFSR and transformation hardware in full-scan chain


Response Compaction

- Severe amounts of data in CUT response to LFSR patterns – example:
 - Generate 5 million random patterns
 - CUT has 200 outputs
 - Leads to: **5 million x 200 = 1 billion bits** response
- Uneconomical to store and check all of these responses on chip
- Responses must be compacted

Definitions

- **Aliasing** – Due to information loss, signatures of good and some bad machines match
- **Compaction** – Drastically reduce # bits in original circuit response – lose information
- **Compression** – Reduce # bits in original circuit response – no information loss – fully invertible (can get back original response)
- **Signature analysis** – Compact good machine response into *good machine signature*. Actual signature generated during testing, and compared with good machine signature
- **Transition Count Response Compaction** – Count # transitions from 0 \rightarrow 1 and 1 \rightarrow 0 as a signature

Transition Counting

 

Transition Counting Details

- Transition count:

$$C(R) = \sum_{i=1}^m (r_i \oplus r_{i-1}) \text{ for all } m \text{ primary outputs}$$


- To maximize fault coverage:

- Make $C(R0)$ - good machine transition count - as large or as small as possible

LFSR for Response Compaction

- Use *cyclic redundancy check code (CRCC) generator (LFSR)* for response compacter
- Treat data bits from circuit POs to be compacted as a decreasing order coefficient polynomial
- CRCC divides the PO polynomial by its characteristic polynomial
 - Leaves remainder of division in LFSR
 - Must initialize LFSR to *seed value* (usually 0) before testing
- After testing - compare signature in LFSR to known good machine signature
- Critical: Must compute good machine signature

Example Modular LFSR Response Compacter

 

Polynomial Division

Inputs	x^0	x^1	x^2	x^3	x^4
Initial State	0	0	0	0	0
Logic	1	1	0	0	0
Simulation:	0	0	1	0	0
	0	0	0	1	0
	0	0	0	0	1
	1	1	0	0	0
	0	1	0	0	1
	1	1	1	0	0
	0	1	0	1	0
	0	1	0	1	0

Logic simulation: **Remainder** = $1 + x^2 + x^3$

0 1 0 1 0 0 0 1

$0 \cdot x^0 + 1 \cdot x^1 + 0 \cdot x^2 + 1 \cdot x^3 + 0 \cdot x^4 + 0 \cdot x^5 + 0 \cdot x^6 + 1 \cdot x^7$

Symbolic Polynomial Division

$$\begin{array}{r}
 x^2 + 1 \\
 x^5 + x^3 + x + 1 \overline{) x^7 + x^5 + x^3 + x^2 + x} \\
 \underline{x^7 + x^5 + x^3 + x^2} \\
 x^5 + x^3 + x + 1 \\
 \underline{x^5 + x^3} + x + 1 \\
 \text{remainder} \rightarrow x^3 + x^2 + 1
 \end{array}$$

Remainder matches that from logic simulation of the response compacter!

Multiple-Input Signature Register (MISR)


- Problem with ordinary LFSR response compacter:
 - Too much hardware if one of these is put on each primary output (PO)
- Solution: MISR – compacts all outputs into one LFSR
 - Works because LFSR is linear – obeys *superposition principle*
 - Superimpose all responses in one LFSR – final remainder is XOR sum of remainders of polynomial divisions of each PO by the characteristic polynomial

MISR Matrix Equation

- $d_i(t)$ – output response on PO_i at time t

$$\begin{bmatrix} X_0(t+1) \\ X_1(t+1) \\ \vdots \\ X_{n-3}(t+1) \\ X_{n-2}(t+1) \\ X_{n-1}(t+1) \end{bmatrix} = \begin{bmatrix} 0 & 1 & \dots & 0 & 0 \\ 0 & 0 & \dots & 0 & 0 \\ \vdots & \vdots & \ddots & \vdots & \vdots \\ 0 & 0 & \dots & 1 & 0 \\ 0 & 0 & \dots & 0 & 1 \\ 1 & h_1 & \dots & h_{n-2} & h_{n-1} \end{bmatrix} \begin{bmatrix} X_0(t) \\ X_1(t) \\ \vdots \\ X_{n-3}(t) \\ X_{n-2}(t) \\ X_{n-1}(t) \end{bmatrix} + \begin{bmatrix} d_0(t) \\ d_1(t) \\ \vdots \\ d_{n-3}(t) \\ d_{n-2}(t) \\ d_{n-1}(t) \end{bmatrix}$$

Modular MISR Example

 

$$\begin{bmatrix} X_0(t+1) \\ X_1(t+1) \\ X_2(t+1) \end{bmatrix} = \begin{bmatrix} 0 & 0 & 1 \\ 1 & 0 & 1 \\ 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} X_0(t) \\ X_1(t) \\ X_2(t) \end{bmatrix} + \begin{bmatrix} d_0(t) \\ d_1(t) \\ d_2(t) \end{bmatrix}$$


Multiple Signature Checking

- Use 2 different testing epochs:
 - 1st with MISR with 1 polynomial
 - 2nd with MISR with different polynomial
- Reduces probability of aliasing –
 - Very unlikely that both polynomials will alias for the same fault
- Low hardware cost:
 - A few XOR gates for the 2nd MISR polynomial
 - A 2-1 MUX to select between two feedback polynomials

Aliasing Probability

- Aliasing – when bad machine signature equals good machine signature
- Consider error vector $e(n)$ at POs
 - Set to a 1 when good and faulty machines differ at the PO at time t
- $P_{al} \equiv$ aliasing probability
- $p \equiv$ probability of 1 in $e(n)$
- Aliasing limits:
 - $0 < p \leq 1/2$, $p^k \leq P_{al} \leq (1-p)^k$
 - $1/2 \leq p \leq 1$, $(1-p)^k \leq P_{al} \leq p^k$

Aliasing Probability Graph

 


Additional MISR Aliasing

- MISR has more aliasing than LFSR on single PO
 - Error in CUT output d_j at t_i , followed by error in output d_{j+tr} at t_{i+tr} eliminates any signature error if no feedback tap in MISR between bits Q_j and Q_{j+tr}

Aliasing Theorems

- Theorem 15.1:** Assuming that each circuit PO d_{ij} has probability p of being in error, and that all outputs d_{ij} are independent, in a k -bit MISR, $P_{al} = 1/(2^k)$, regardless of initial condition of MISR. Not exactly true – true in practice.
- Theorem 15.2:** Assuming that each PO d_{ij} has probability p_j of being in error, where the p_j probabilities are independent, and that all outputs d_{ij} are independent, in a k -bit MISR, $P_{al} = 1/(2^k)$, regardless of the initial condition.

Experiment Hardware

 

- 3 bit exhaustive binary counter for pattern generator

Transition Counting vs. LFSR

- LFSR aliases for $f\ sa1$, transition counter for $a\ sa1$

Pattern <i>abc</i>	Responses			
	Good	<i>a sa1</i>	<i>f sa1</i>	<i>b sa1</i>
000	0	0	1	0
001	1	1	1	0
010	0	1	1	0
011	0	1	1	0
100	0	0	1	1
101	1	1	1	1
110	1	1	1	1
111	1	1	1	1
Signatures				
Transition Count	3	3	0	1
LFSR	001	101	001	010

Summary

- LFSR pattern generator and MISR response compacter – preferred BIST methods
- BIST has overheads: test controller, extra circuit delay, Input MUX, pattern generator, response compacter, DFT to initialize circuit & test the test hardware
- BIST benefits:
 - At-speed testing for delay & stuck-at faults
 - Drastic ATE cost reduction
 - Field test capability
 - Faster diagnosis during system test
 - Less effort to design testing process
 - Shorter test application times