

EECS 230  
*ENGINEERING ELECTROMAGNETICS*  
*Leland Pierce*

Transmission Lines 2

# Chapter 2 Overview

## What is a transmission line?

Why study transmission lines?

model

diffeq

solve diffeq

wave propagation

lossless transmission line

microstrip lines

reflections

standing waves

impedance




short, open

matching



power flow

smith chart



transients

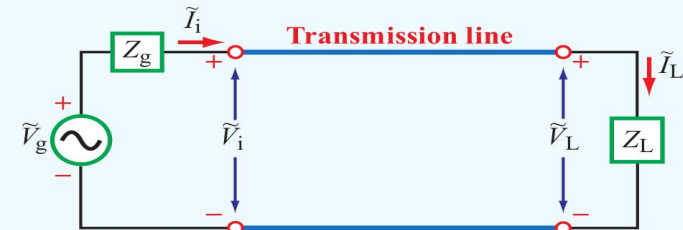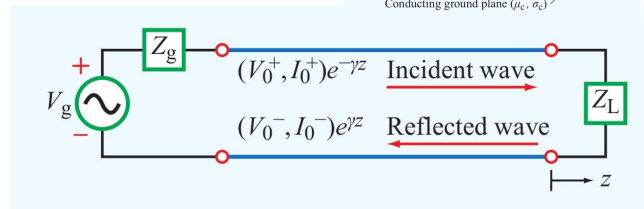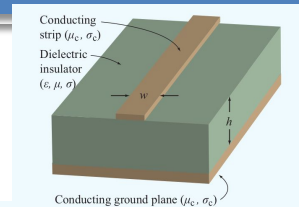

Typical High-Frequency Circuit

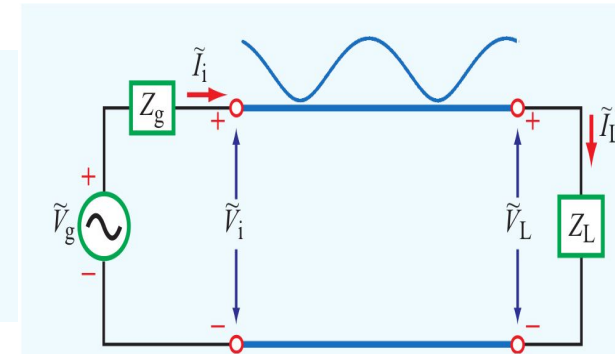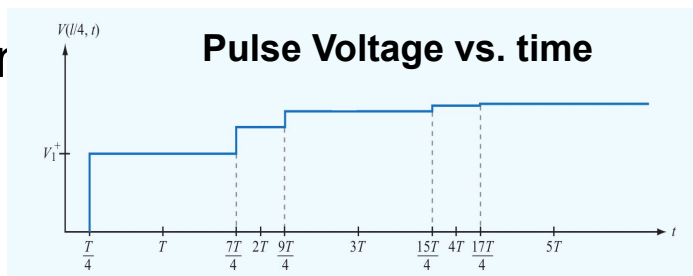

Waves on line: old methods don't work

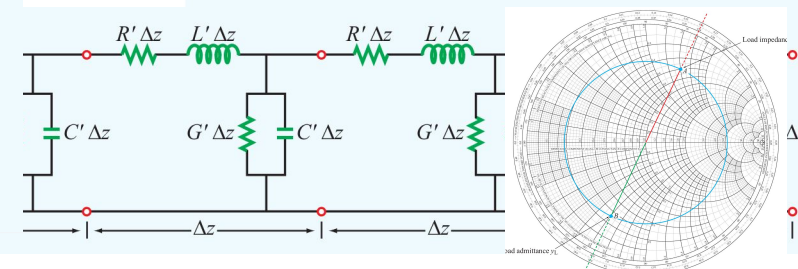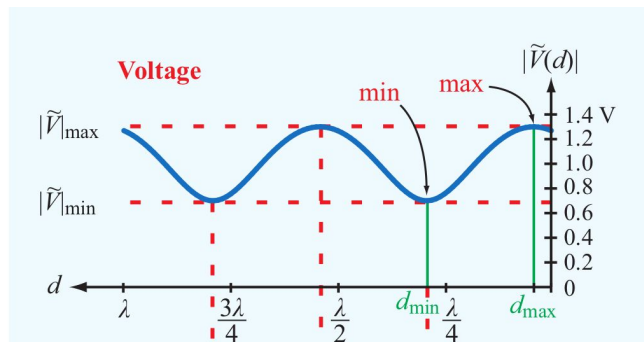

# Chapter 2 Applications

---

**Radios:** cell phones, internet, broadcast radio/tv, GPS

**Radar:** civilian aeronautical, military, vehicle collision sensors, weather, remote sensing

**Heating:** Microwave Ovens, Cancer Treatment

# Today's Lecture Coverage

## **Review Sections 2-1 and 2-2 of the book:**

**2-1:** What is a transmission line?  
Why study transmission lines?

**2-2:** Lumped-Element Model

## **Sections 2-3 through 2-5 of the book:**

**2-3:** Governing Differential Eqns

**2-4:** Solve the Differential Equations

Properties of the solution: wave propagation

**2-5:** Lossless Microstrip Line


# Chapter 2 Review

- A transmission line connects a **generator** to a **load**.


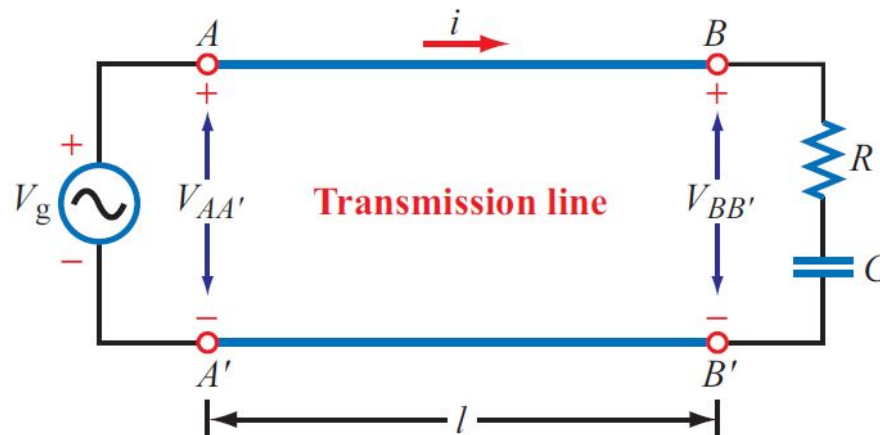
# Chapter 2 Review

Phase Delay due to length of transmission line:




$$\phi_0 = \frac{\omega l}{c} = \frac{2\pi f l}{c} = 2\pi \frac{l}{\lambda} \text{ radians.}$$

$l/\lambda \lesssim 0.01$ : Can ignore transmission-line effects


$l/\lambda \gtrsim 0.01$ : Must deal with phase shift, and other effects...
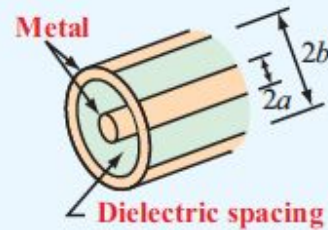
# Chapter 2 Review


Different geometries for transmission lines




(a) Coaxial line

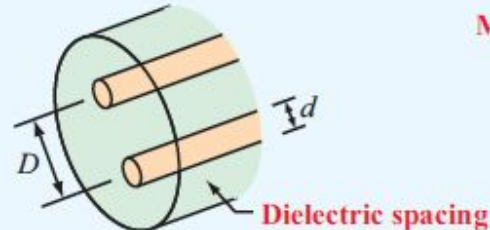


(b) Two-wire line

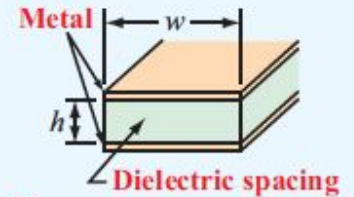


(c) Parallel-plate line

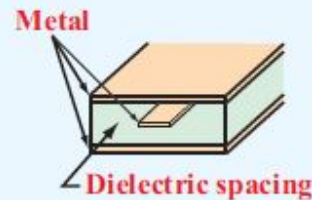

(d) Strip line

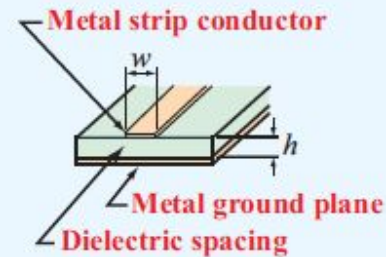


(e) Microstrip line

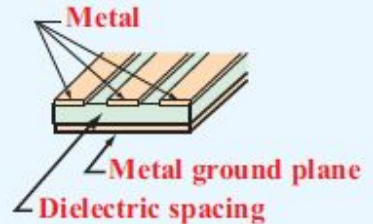


(f) Coplanar waveguide

## TEM Transmission Lines

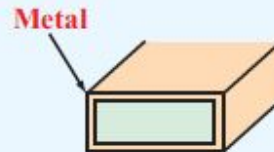

(g) Rectangular waveguide

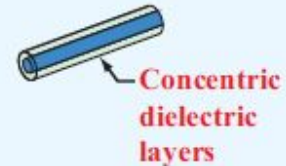


(h) Optical fiber

## Higher-Order Transmission Lines

# Chapter 2 Review

## Lumped-Element Model:

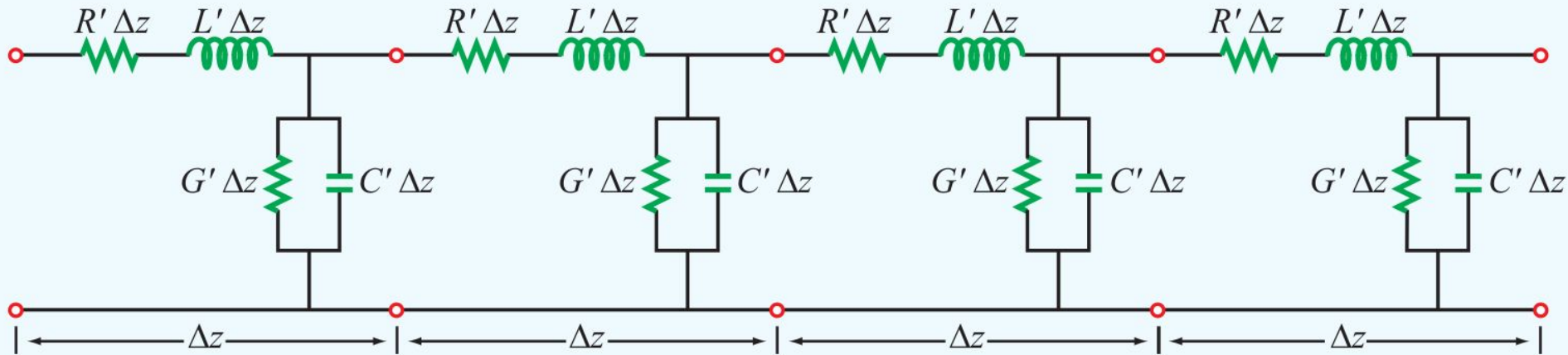

**All parameters are "per unit length":**

**R': Combined Resistance of BOTH conductors:  $\square/m$**

**L': Combined Inductance of BOTH conductors, H/m**

**G': Conductance of insulation**

between inner and outer conductor, S/m

**C': Capacitance**

between inner and outer conductors, F/m

# Chapter 2 Review

## Lumped-Element Values: geometry/materials/freq

**Table 2-1** Transmission-line parameters  $R'$ ,  $L'$ ,  $G'$ , and  $C'$  for three types of lines.

Parameter	Coaxial	Two-Wire	Parallel-Plate	Unit
$R'$	$\frac{R_s}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right)$	$\frac{2R_s}{\pi d}$	$\frac{2R_s}{w}$	$\Omega/\text{m}$
$L'$	$\frac{\mu}{2\pi} \ln(b/a)$	$\frac{\mu}{\pi} \ln \left[ (D/d) + \sqrt{(D/d)^2 - 1} \right]$	$\frac{\mu h}{w}$	$\text{H}/\text{m}$
$G'$	$\frac{2\pi\sigma}{\ln(b/a)}$	$\frac{\pi\sigma}{\ln \left[ (D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\sigma w}{h}$	$\text{S}/\text{m}$
$C'$	$\frac{2\pi\epsilon}{\ln(b/a)}$	$\frac{\pi\epsilon}{\ln \left[ (D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\epsilon w}{h}$	$\text{F}/\text{m}$

$$R_s = \sqrt{\pi f \mu_c / \sigma_c}$$

# Chapter 2 Review

Lumped-Element Values: geometry/materials/freq

Notice that for a coax:

$$L'C' = \left[ \frac{\mu}{2\pi} \ln(b/a) \right] \left[ \frac{2\pi\epsilon}{\ln(b/a)} \right]$$

$$L'C' = \mu\epsilon$$

This turns out to be true for all the transmission-lines we study.

# Chapter 2 Review

Lumped-Element Values: geometry/materials/freq

Also notice that for a coax:


$$\frac{G'}{C'} = \frac{\left[ \frac{2\pi\sigma}{\ln(b/a)} \right]}{\left[ \frac{2\pi\epsilon}{\ln(b/a)} \right]}$$

$$\frac{G'}{C'} = \frac{\sigma}{\epsilon}$$

This also turns out to be true for all the transmission-lines we study.


# 2-3 Transmission-Line Equations

Using our model:

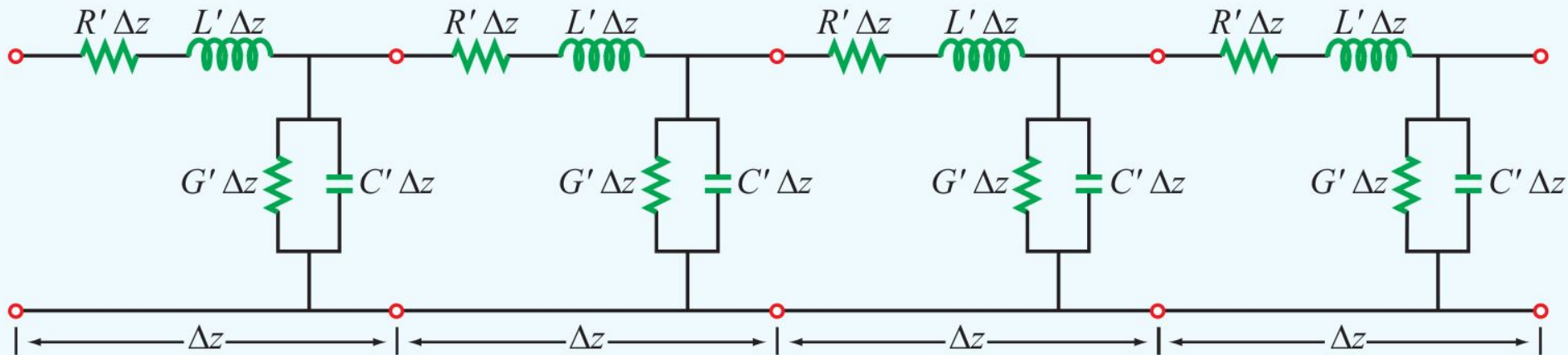

Let's derive the governing differential equations for the transmission line.

## 2-3 Transmission-Line Equations

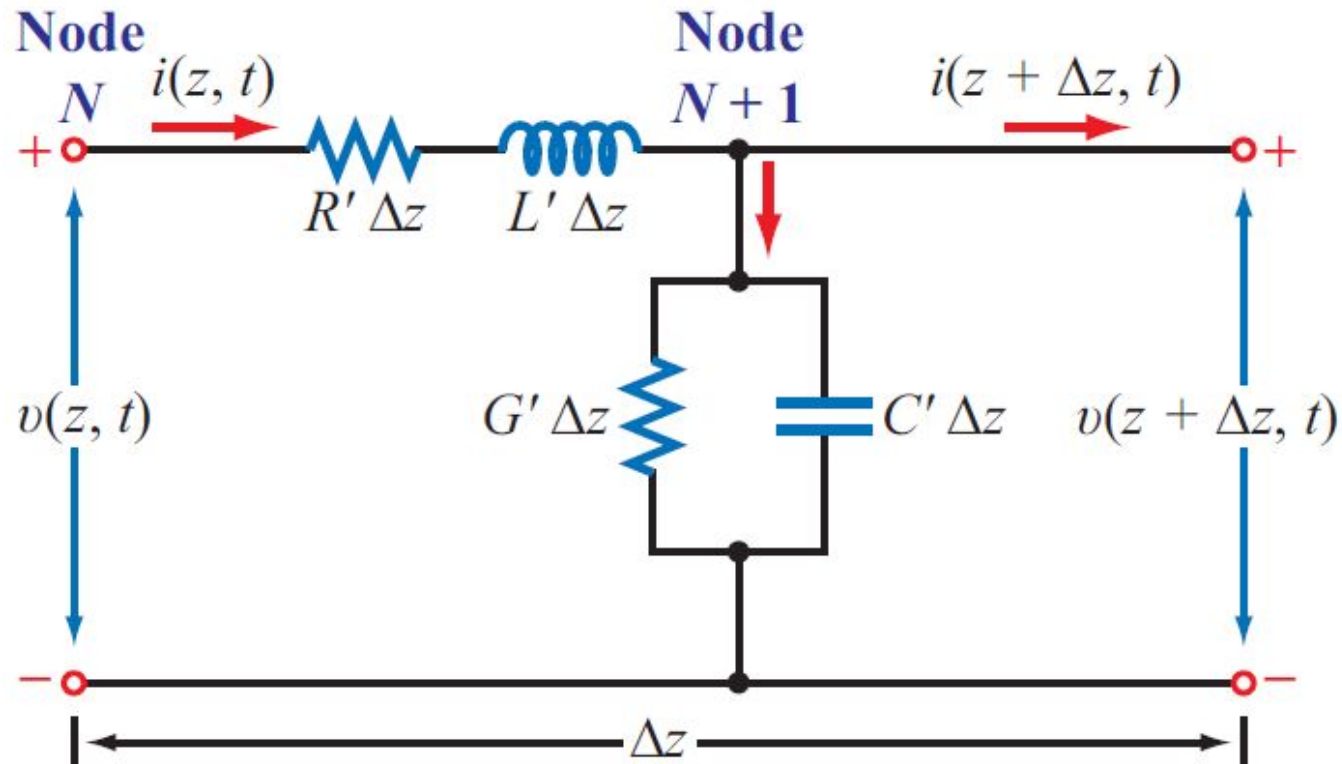

**Apply KVL clockwise around outer loop:**

$$-v(z, t) + R' \Delta z i(z, t) + L' \Delta z \frac{\partial i(z, t)}{\partial t} + v(z + \Delta z, t) = 0$$

## 2-3 Transmission-Line Equations

$$-v(z, t) + R' \Delta z i(z, t) + L' \Delta z \frac{\partial i(z, t)}{\partial t} + v(z + \Delta z, t) = 0$$

Divide by  $\Delta z$  and rearrange:


$$-\left[ \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} \right] = R' i(z, t) + L' \frac{\partial i(z, t)}{\partial t}$$

Take the limit,  $\Delta z \rightarrow 0$ :

$$-\frac{\partial v(z, t)}{\partial z} = R' i(z, t) + L' \frac{\partial i(z, t)}{\partial t} \quad (1)$$

Since we have 2 unknowns,  $v$  and  $i$ , we need another equation.

## 2-3 Transmission-Line Equations

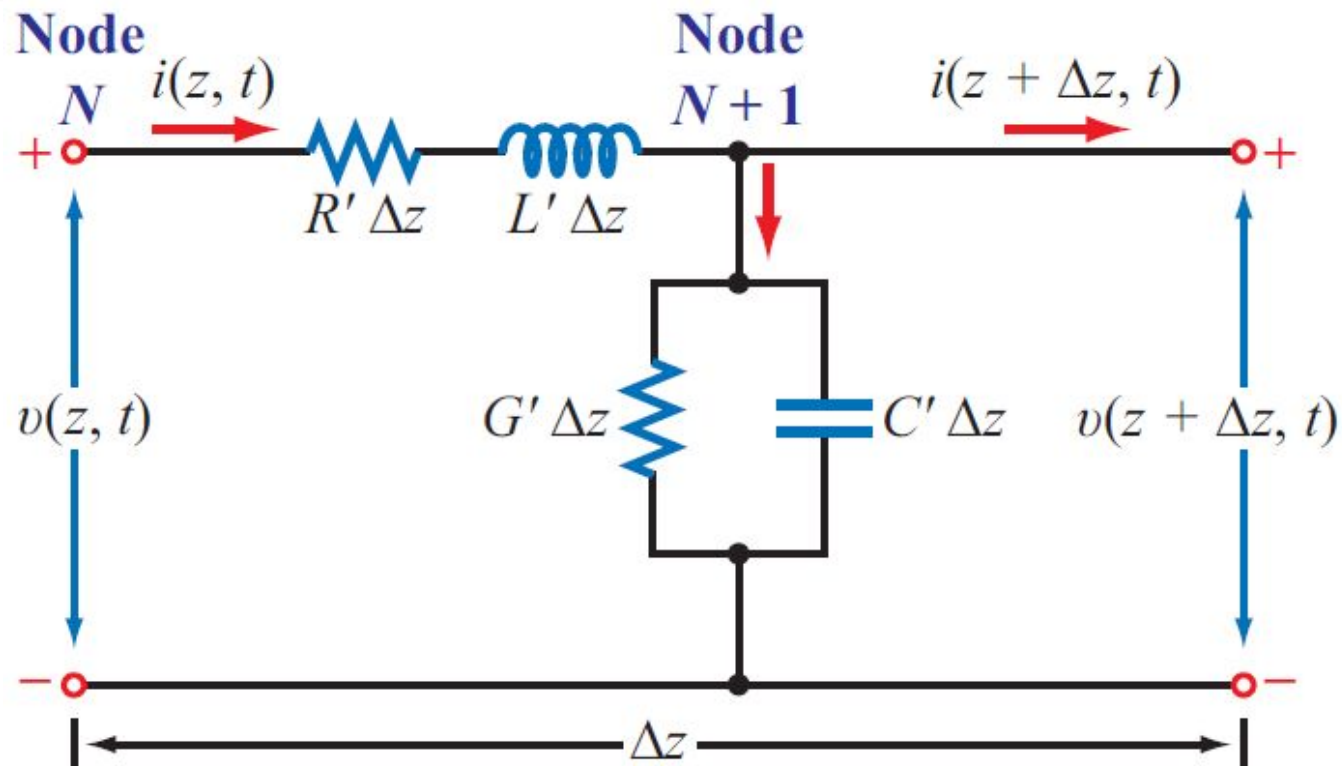

**Apply KCL at node N+1: "sum of the current into the node = 0"**

$$i(z, t) - G' \Delta z v(z + \Delta z, t) - C' \Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0$$

## 2-3 Transmission-Line Equations

$$i(z, t) - G' \Delta z v(z + \Delta z, t) - C' \Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0$$

Divide by  $\Delta z$  and rearrange, and take the limit,  $\Delta z \rightarrow 0$ :

$$-\frac{\partial i(z, t)}{\partial z} = G' v(z, t) + C' \frac{\partial v(z, t)}{\partial t} \quad (2)$$

For sinusoidal signals, convert to phasor notation, using:

$$v(z, t) = \Re[\tilde{V}(z) e^{j\omega t}],$$

$$i(z, t) = \Re[\tilde{I}(z) e^{j\omega t}],$$

## 2-3 Transmission-Line Equations

These are the governing differential equations for a transmission line in phasor form:

$$-\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L') \tilde{I}(z),$$
$$-\frac{d\tilde{I}(z)}{dz} = (G' + j\omega C') \tilde{V}(z).$$

**(telegrapher's equations in phasor form)**

## 2-4 Transmission-Line Solutions

To solve these coupled differential equations, take the  $z$ -derivative of the first:

$$-\frac{d^2\tilde{V}(z)}{dz^2} = (R' + j\omega L') \frac{d\tilde{I}(z)}{dz}$$

Substitute in the equation for the derivative of the current:

$$-\frac{d^2\tilde{V}(z)}{dz^2} = (R' + j\omega L') \left[ -(G' + j\omega C') \tilde{V}(z) \right]$$

$$\frac{d^2\tilde{V}(z)}{dz^2} = (R' + j\omega L') (G' + j\omega C') \tilde{V}(z)$$

$$\frac{d^2\tilde{V}(z)}{dz^2} - (R' + j\omega L') (G' + j\omega C') \tilde{V}(z) = 0$$

## 2-4 Transmission-Line Solutions

Simplify:

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0,$$

**(wave equation for  $\tilde{V}(z)$ )**

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}.$$

**(propagation constant)**

## 2-4 Transmission-Line Solutions

Going through the same process for the current:

$$\frac{d^2 \tilde{I}(z)}{dz^2} - \gamma^2 \tilde{I}(z) = 0.$$

**(wave equation for  $\tilde{I}(z)$ )**

# 2-4 Transmission-Line Solutions

Complex propagation constant:

$$\gamma = \alpha + j\beta$$

Where:

$\gamma$ : Units of 1/m

$\alpha$ : Attenuation constant, units of Np/m (>0 in this class)

$\beta$ : Phase constant, units of rad/m

Np and radians are both "dimensionless", and are the conventional "units" for these parameters.

## 2-4 Transmission-Line Solutions

A solution to the wave equation is:

$$\tilde{V} = Ae^{-\gamma z}$$

To show this: plug into original equation:

$$\frac{d\tilde{V}}{dz} - \gamma^2\tilde{V} = 0$$

$$\frac{d^2}{dz^2} (Ae^{-\gamma z}) - \gamma^2 Ae^{-\gamma z} = 0$$

$$\frac{d}{dz} (-\gamma Ae^{-\gamma z}) - \gamma^2 Ae^{-\gamma z} = 0$$

$$\gamma^2 Ae^{-\gamma z} - \gamma^2 Ae^{-\gamma z} = 0$$

## 2-4 Transmission-Line Solutions

Another solution is:

$$\tilde{V} = Be^{+\gamma z}$$

which means that:

$$\tilde{V} = Ae^{-\gamma z} + Be^{+\gamma z}$$

is also a solution.

## 2-4 Transmission-Line Solutions

So, the solutions of these wave equations are:

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$

These represent the sum of waves traveling in both directions on the line.

Need to solve for the **4 unknowns**.

## 2-4 Transmission-Line Solutions

Let's find a relationship between the voltages and currents. We know:

$$-\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L') \tilde{I}(z),$$

and:

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

which has z-derivative of:

$$\frac{d\tilde{V}(z)}{dz} = -\gamma V_0^+ e^{-\gamma z} + \gamma V_0^- e^{\gamma z}$$

## 2-4 Transmission-Line Solutions

Plug into first equation:

$$\gamma V_0^+ e^{-\gamma z} - \gamma V_0^- e^{\gamma z} = (R' + j\omega L') \tilde{I}(z)$$

Solve for the current:

$$\tilde{I}(z) = \frac{\gamma}{R' + j\omega L'} [V_0^+ e^{-\gamma z} - V_0^- e^{\gamma z}].$$

Equate like terms from this equation:

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

## 2-4 Transmission-Line Solutions

So we get:

$$I_0^+ = \frac{\gamma}{R' + j\omega L'} V_0^+$$

$$I_0^- = -\frac{\gamma}{R' + j\omega L'} V_0^-$$

Remembering Ohm's Law:  $I = V/R$ , write as:

$$I_0^+ = \frac{V_0^+}{Z_0}$$

$$I_0^- = -\frac{V_0^-}{Z_0}$$

## 2-4 Transmission-Line Solutions

Where:

$$Z_0 = \frac{R' + j\omega L'}{\gamma}$$

which is a complex resistance (impedance), in Ohms.  
This is called the **Characteristic Impedance**

## 2-4 Transmission-Line Solutions

Another way to express it is:

$$Z_0 = \frac{R' + j\omega L'}{\gamma}$$

$$Z_0 = \frac{R' + j\omega L'}{\sqrt{(R' + j\omega L')(G' + j\omega C')}}}$$

$$Z_0 = \sqrt{\frac{(R' + j\omega L')(R' + j\omega L')}{(R' + j\omega L')(G' + j\omega C')}}}$$

$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

## 2-4 Transmission-Line Solutions

Using this relationship we get:

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z} \quad (\text{A}).$$

which now has only **2 unknowns**.

## 2-4 Transmission-Line Solutions

Each of these unknowns is complex:

$$V_0^+ = |V_0^+| e^{j\phi^+}$$

$$V_0^- = |V_0^-| e^{j\phi^-}$$

## 2-4 Transmission-Line Solutions

Express the solution, so far, in the time-domain:

$$v(z, t) = \Re \left\{ \tilde{V}(z) e^{j\omega t} \right\}$$

$$v(z, t) = \Re \left\{ (V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}) e^{j\omega t} \right\}$$

$$v(z, t) = \Re \left\{ (|V_0^+| e^{j\phi^+} e^{-\gamma z} + |V_0^-| e^{j\phi^-} e^{+\gamma z}) e^{j\omega t} \right\}$$

$$v(z, t) = \Re \left\{ (|V_0^+| e^{j\phi^+} e^{-(\alpha+j\beta)z} + |V_0^-| e^{j\phi^-} e^{+(\alpha+j\beta)z}) e^{j\omega t} \right\}$$

$$v(z, t) = \Re \left\{ |V_0^+| e^{-\alpha z} e^{j(\phi^+ - \beta z + \omega t)} + |V_0^-| e^{+\alpha z} e^{j(\phi^- + \beta z + \omega t)} \right\}$$

$$v(z, t) = |V_0^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi^+) + |V_0^-| e^{+\alpha z} \cos(\omega t + \beta z + \phi^-)$$


## 2-4 Transmission-Line Solutions

Express the solution, so far, in the time-domain:

$$v(z, t) = |V_0^+|e^{-\alpha z} \cos(\omega t - \beta z + \phi^+) + |V_0^-|e^{+\alpha z} \cos(\omega t + \beta z + \phi^-)$$

This is two travelling waves:

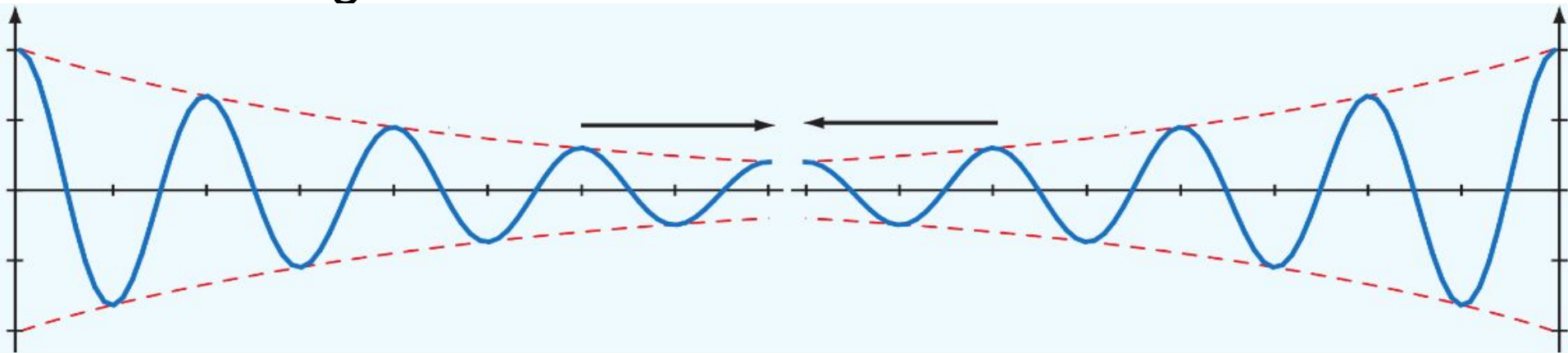one moving in the +z direction      another in the -z direction



## 2-4 Transmission-Line Solutions

For the current, we use:  $Z_0 = |Z_0|e^{j\phi_z}$

$$i(z,t) = \Re(\tilde{I}(z) e^{j\omega t}) = \Re \left[ \frac{|V_0^+|}{|Z_0|} e^{j\phi^+} e^{-j\phi_z} e^{j\omega t} e^{-(\alpha+j\beta)z} - \frac{|V_0^-|}{|Z_0|} e^{j\phi^-} e^{-j\phi_z} e^{j\omega t} e^{(\alpha+j\beta)z} \right],$$

which yields

$$i(z,t) = \frac{|V_0^+|}{|Z_0|} e^{-\alpha z} \cos(\omega t - \beta z + \phi^+ - \phi_z) - \frac{|V_0^-|}{|Z_0|} e^{+\alpha z} \cos(\omega t + \beta z + \phi^- - \phi_z) \quad (2.35)$$

## 2-4 Transmission-Line Solutions

$$v(z,t) = |V_0^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi^+) + |V_0^-| e^{+\alpha z} \cos(\omega t + \beta z + \phi^-) \quad (2.32)$$

$$i(z,t) = \frac{|V_0^+|}{|Z_0|} e^{-\alpha z} \cos(\omega t - \beta z + \phi^+ - \phi_z) - \frac{|V_0^-|}{|Z_0|} e^{+\alpha z} \cos(\omega t + \beta z + \phi^- - \phi_z) \quad (2.35)$$

Current has an extra phase term due to  $Z_0$ ,  
Current magnitudes are basically  $V/R$   
Reflected  $i$  has opposite sign compared with  $v$

# Example 2-1 Air Line

**Given:** Air separates the  
2 conductors, so:


$$G' = 0$$

Conductors are  
very good:  $R' = 0$

$$Z_0 = 50 \Omega,$$

$$\beta = 20 \text{ rad/m},$$

$$f = 700 \text{ MHz}$$

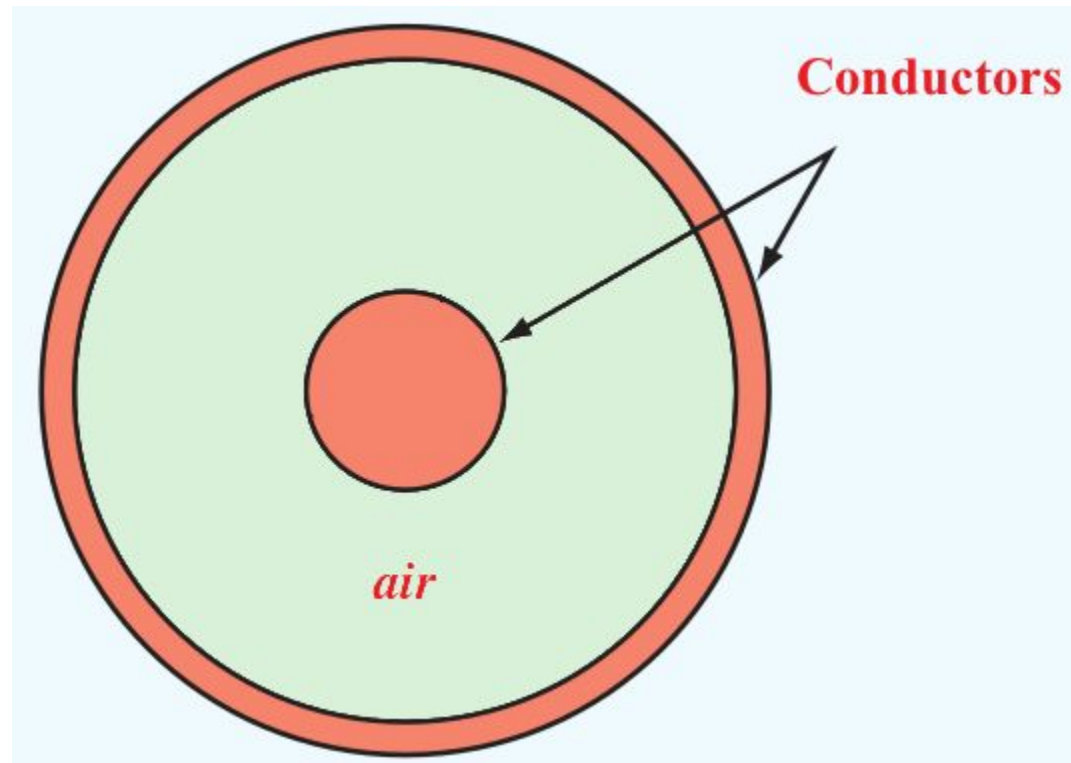

**Find:**  $L'$ ,  $C'$

**Solution:** Since we know  $Z_0$  and  $\beta$ , use those equations

# Example 2-1 Air Line

**Solution:** Since we know  $Z_0$  and  $\beta$ , use those equations

$$\begin{aligned}\beta &= \Im(\gamma) \\ &= \Im\left(\sqrt{(R' + j\omega L')(G' + j\omega C')}\right)\end{aligned}$$

$$\begin{aligned}\beta &= \Im\left[\sqrt{(j\omega L')(j\omega C')}\right] \\ &= \Im\left(j\omega\sqrt{L'C'}\right) \\ &= \omega\sqrt{L'C'}\end{aligned}$$

# Example 2-1 Air Line

**Solution:** Since we know  $Z_0$  and  $\beta$ , use those equations

$$Z_0 = \frac{R' + j\omega L'}{\gamma} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

$$Z_0 = \sqrt{\frac{j\omega L'}{j\omega C'}} = \sqrt{\frac{L'}{C'}}$$

Notice that:  $\beta / Z_0 = \frac{\omega \sqrt{L' C'}}{\sqrt{\frac{L'}{C'}}} = \omega C'$

# Example 2-1 Air Line

**Solution:** So:  $\omega C' = \beta / Z_0$

$$C' = \frac{\beta}{\omega Z_0} = \frac{\beta}{2\pi f Z_0}$$

$$C' = \frac{20 \text{ rad/m}}{2\pi(700 \times 10^6 \text{ Hz})(50 \Omega)}$$

$$C' = 9.09 \times 10^{-11} \text{ F/m}$$

$$C' = 90.9 \text{ pF/m}$$

# Example 2-1 Air Line

**Solution:** Given:  $Z_0 = \sqrt{\frac{L'}{C'}}$

$$L' = Z_0^2 C'$$

$$= (50)^2 \times 90.9 \times 10^{-12} :$$

$$= 2.27 \times 10^{-7} \text{ (H/m)}$$

$$L' = 227 \text{ (nH/m)}$$

# Exercise 2-4 Two-Wire Air Line

**Given:**  $R' = 0.404 \text{ m}\Omega/\text{m}$


$L' = 2.0 \text{ }\mu\text{H}/\text{m}$

$G' = 0$

$C' = 5.56 \text{ pF}/\text{m}$

$f = 5 \text{ kHz}$

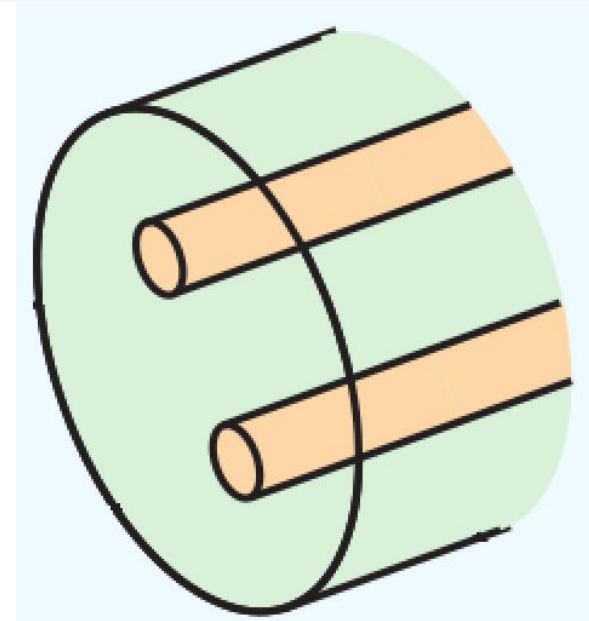**Find:**  $\alpha$ ,  $\beta$ ,  $u_p$ ,  $Z_0$



# Exercise 2-4 Two-Wire Air Line

Solution:

$$\begin{aligned}\alpha &= \Re \left\{ [(R' + j\omega L')(G' + j\omega C')]^{1/2} \right\} \\ &= \Re \left\{ [(0.404 \times 10^{-3} + j2\pi \times 5 \times 10^3 \times 2 \times 10^{-6}) \right. \\ &\quad \left. \cdot (0 + j2\pi \times 5 \times 10^3 \times 5.56 \times 10^{-12})]^{1/2} \right\} \\ &= \Re [3.37 \times 10^{-7} + j1.05 \times 10^{-4}]\end{aligned}$$

$$\alpha = 3.37 \times 10^{-7} \text{ (Np/m).}$$

Note the units!

# Exercise 2-4 Two-Wire Air Line

**Solution:**

from part (a):

$$\beta = \Im \left\{ [(R' + j\omega L')(G' + j\omega C')]^{1/2} \right\}$$

$$\beta = 1.05 \times 10^{-4} \text{ (rad/m).}$$

$$u_p = \frac{\omega}{\beta} = \frac{2\pi f}{\beta} = \frac{2\pi(5 \times 10^3 \text{ Hz})}{1.05 \times 10^{-4} \text{ rad/m}}$$

$$u_p = 3 \times 10^8 \text{ m/sec}$$

# Exercise 2-4 Two-Wire Air Line

Solution:

$$Z_0 = \frac{R' + j\omega L'}{\gamma}$$

$$Z_0 = \frac{R' + j\omega L'}{\alpha + j\beta}$$

$$Z_0 = \frac{R' + j(2\pi f)L'}{\alpha + j\beta}$$

$$Z_0 = \frac{(0.404 \times 10^{-3} \Omega/\text{m} + j2\pi(5 \times 10^3 \text{ Hz})(2 \times 10^{-6} \text{ H/m}))}{3.37 \times 10^{-7} \text{ m}^{-1} + j1.05 \times 10^{-4} \text{ m}^{-1}}$$

# Exercise 2-4 Two-Wire Air Line

**Solution:**

$$Z_0 = \frac{0.404 \times 10^{-3} + j0.062832}{3.37 \times 10^{-7} + j1.05 \times 10^{-4}}$$

$$Z_0 = \frac{\sqrt{(0.404 \times 10^{-3})^2 + (0.062832)^2} e^{j \tan^{-1}(0.062832/0.404 \times 10^{-3})}}{\sqrt{(3.37 \times 10^{-7})^2 + (1.05 \times 10^{-4})^2} e^{j \tan^{-1}(1.05 \times 10^{-4}/3.37 \times 10^{-7})}}$$

$$Z_0 = \frac{\sqrt{1.63216 \times 10^{-7} + 0.0039478} e^{j \tan^{-1}(155.44)}}{\sqrt{1.13569 \times 10^{-13} + 1.1025 \times 10^{-8}} e^{j \tan^{-1}(311.57)}}$$

$$Z_0 = \frac{\sqrt{0.003948} e^{j89.631^\circ}}{\sqrt{1.10251136 \times 10^{-8}} e^{j89.816^\circ}}$$

# Exercise 2-4 Two-Wire Air Line

Solution:

$$Z_0 = \frac{0.06283315}{0.000105} e^{j(89.631^\circ - 89.816^\circ)}$$

$$Z_0 = 598.4 e^{-j0.1846^\circ} \Omega$$

$$Z_0 = 598.4 \cos(-0.1846^\circ) + j598.4 \sin(-0.1846^\circ)$$

$$Z_0 = 598.4 - j1.928 \Omega$$


# 2-5 Lossless Microstrip Line

Designed to be compatible with usual Printed-Circuit Board (PCB) technology:


Narrow metal strip on top

Large ground plane on bottom

Dielectric between

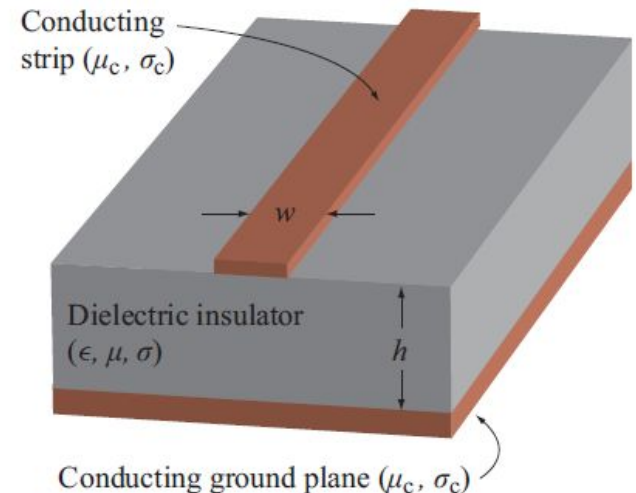

(a) Longitudinal view

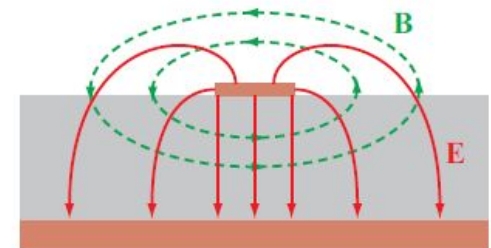

(b) Cross-sectional view with  $E$  and  $B$  field lines

# 2-5 Lossless Microstrip Line

Modeled Transmission-Line Parameters:


$$Z_0 = \frac{60}{\sqrt{\epsilon_{\text{eff}}}} \ln \left\{ \frac{6 + (2\pi - 6)e^{-t}}{s} + \sqrt{1 + \frac{4}{s^2}} \right\},$$

$$t = \left( \frac{30.67}{s} \right)^{0.75} \quad s = \frac{w}{h},$$

$$\epsilon_{\text{eff}} = \frac{\epsilon_r + 1}{2} + \left( \frac{\epsilon_r - 1}{2} \right) \left( 1 + \frac{10}{s} \right)^{-xy},$$

$$x = 0.56 \left[ \frac{\epsilon_r - 0.9}{\epsilon_r + 3} \right]^{0.05},$$
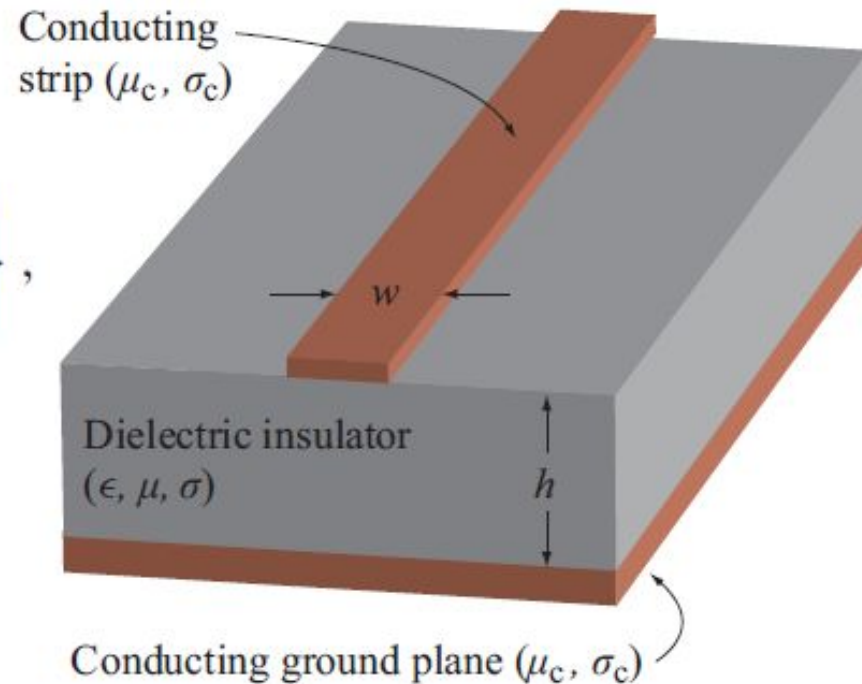
$$y = 1 + 0.02 \ln \left( \frac{s^4 + 3.7 \times 10^{-4} s^2}{s^4 + 0.43} \right) + 0.05 \ln(1 + 1.7 \times 10^{-4} s^3).$$



Largely the result of fitting lots of data using functional forms based on intuition.

# 2-5 Lossless Microstrip Line

Modeled Transmission-Line Parameters:

$$R' = 0 \quad (\text{because } \sigma_c = \infty),$$


$$G' = 0 \quad (\text{because } \sigma = 0),$$

$$C' = \frac{\sqrt{\epsilon_{\text{eff}}}}{Z_0 c},$$


$$L' = Z_0^2 C',$$

$$\alpha = 0 \quad (\text{because } R' = G' = 0),$$

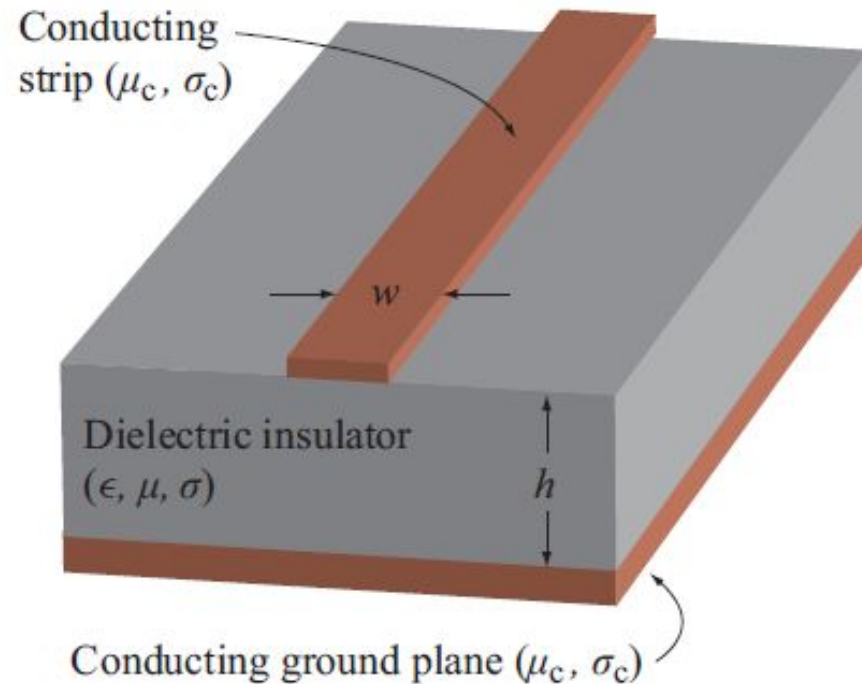
$$\beta = \frac{\omega}{c} \sqrt{\epsilon_{\text{eff}}}.$$



# 2-5 Lossless Microstrip Line

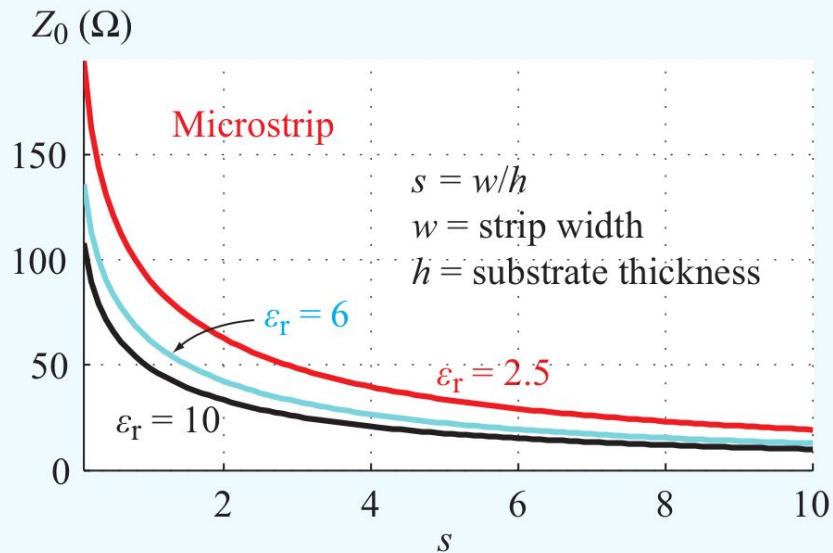

**Figure 2-11** Plots of  $Z_0$  as a function of  $s$  for various types of dielectric materials.

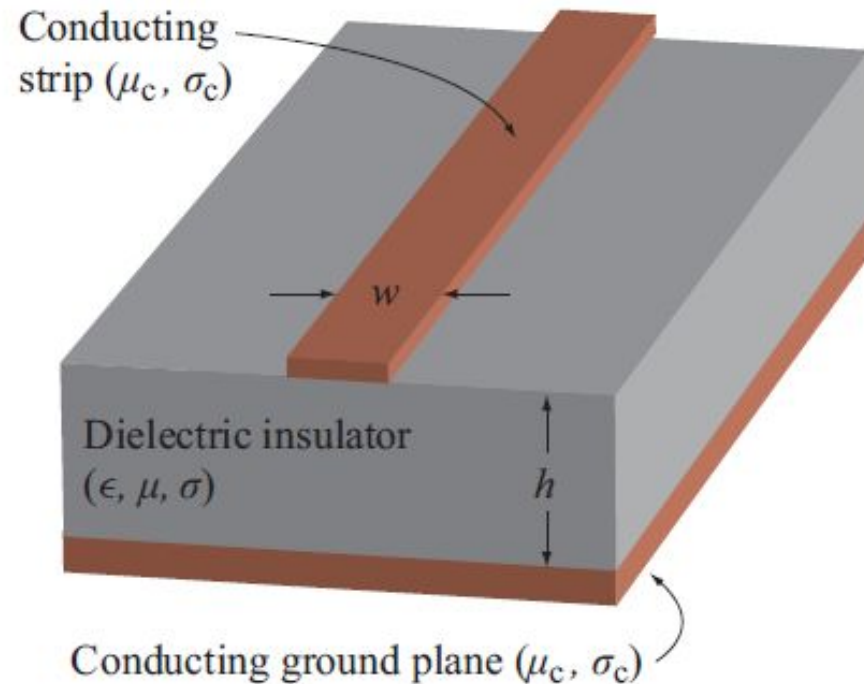

## 2-5 Lossless Microstrip Line

Use a curve-fit of the previous plots in order to solve for  $s$ , given other params.

(a) For  $Z_0 \leq (44 - 2\epsilon_r) \Omega$ ,

$$s = \frac{w}{h} = \frac{2}{\pi} \left\{ (q - 1) - \ln(2q - 1) + \frac{\epsilon_r - 1}{2\epsilon_r} \left[ \ln(q - 1) + 0.29 - \frac{0.52}{\epsilon_r} \right] \right\}$$

with

$$q = \frac{60\pi^2}{Z_0\sqrt{\epsilon_r}},$$

## 2-5 Lossless Microstrip Line

Use a curve-fit of the previous plots in order to solve for  $s$ , given other params.

**(b)** for  $Z_0 \geq (44 - 2\epsilon_r) \Omega$ ,

$$s = \frac{w}{h} = \frac{8e^p}{e^{2p} - 2},$$

with

$$p = \sqrt{\frac{\epsilon_r + 1}{2}} \frac{Z_0}{60} + \left( \frac{\epsilon_r - 1}{\epsilon_r + 1} \right) \left( 0.23 + \frac{0.12}{\epsilon_r} \right)$$

# Example 2-2 Microstrip Line Design

**Given:** Have a substrate:  $h=0.5\text{mm}$  thick,  $\epsilon_r=9$

**Find:** strip width,  $w$ , to get  $Z_0 = 50 \Omega$

**Solution:**  $44 - 2\epsilon_r = 44 - 2(9) = 32$ , so use:

$$s = \frac{w}{h} = \frac{8e^p}{e^{2p} - 2},$$

with

$$p = \sqrt{\frac{\epsilon_r + 1}{2} \frac{Z_0}{60}} + \left( \frac{\epsilon_r - 1}{\epsilon_r + 1} \right) \left( 0.23 + \frac{0.12}{\epsilon_r} \right)$$

# Example 2-2 Microstrip Line Design

Solution:

$$\begin{aligned} p &= \sqrt{\frac{\epsilon_r + 1}{2}} \times \frac{Z_0}{60} + \left( \frac{\epsilon_r - 1}{\epsilon_r + 1} \right) \left( 0.23 + \frac{0.12}{\epsilon_r} \right) \\ &= \sqrt{\frac{9 + 1}{2}} \times \frac{50}{60} + \left( \frac{9 - 1}{9 + 1} \right) \left( 0.23 + \frac{0.12}{9} \right) = 2.06, \end{aligned}$$

$$s = \frac{w}{h} = \frac{8e^p}{e^{2p} - 2} = \frac{8e^{2.06}}{e^{4.12} - 2} = 1.056.$$

# Example 2-2 Microstrip Line Design

Solution:

$$w = sh = 1.056 \times 0.5 \text{ mm} = 0.53 \text{ mm.}$$

Microwave CAD design codes use this for an initial design.

# 2-5 Lossless Microstrip Line


mod2-3 - Google Chrome

Inbox (3,9 x) University x eecs230\_f x Schedule - x EECS230\_ x EECS230\_ x Scientific x mod2-3 x


em8e.eecs.umich.edu/jsmodules/ch2/mod2\_3.html

### Module 2.3 Lossless Microstrip Line

Select: *Permittivity vs. Frequency*

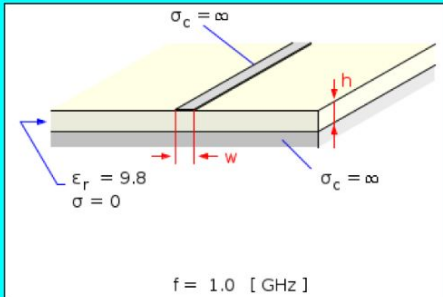

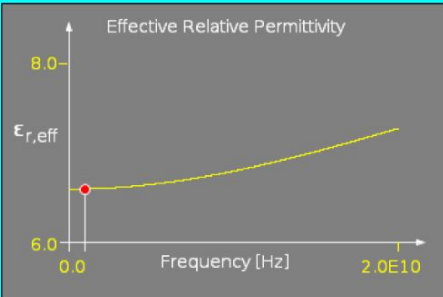$\sigma_c = \infty$   
 $\epsilon_r = 9.8$   
 $\sigma = 0$   
 $f = 1.0$  [GHz]



Effective Relative Permittivity

$\epsilon_{r,eff}$

Frequency [Hz]

#### Input

Instructions

Strip width  $w = 0.6$  [mm]

Substrate thickness  $h = 0.635$  [mm]

Frequency  $f = 1E9$  [Hz]

$\epsilon_r = 9.8$

Update

#### Output

Structure Data

$w = 0.6$  [mm]  
 $h = 0.635$  [mm]     $w/h = 0.944882$

---

$Z_0 = 50.564898$  [ $\Omega$ ]  
 $\epsilon_{r,eff} = 6.591438$   
 $u_p = 1.168507$  [ $10^8$  m/s]  
 $\lambda = 0.116851$  [m]

---

$C' = 169.218917$  [pF/m]  
 $L' = 432.660438$  [nH/m]  
 $R' = 0$  [ $\Omega$ /m]  
 $G' = 0$  [S/m]

---

$\alpha = 0$  [Np/m]  
 $\beta = 53.76231$  [rad/m]

## 2-5 Lossless Microstrip Line

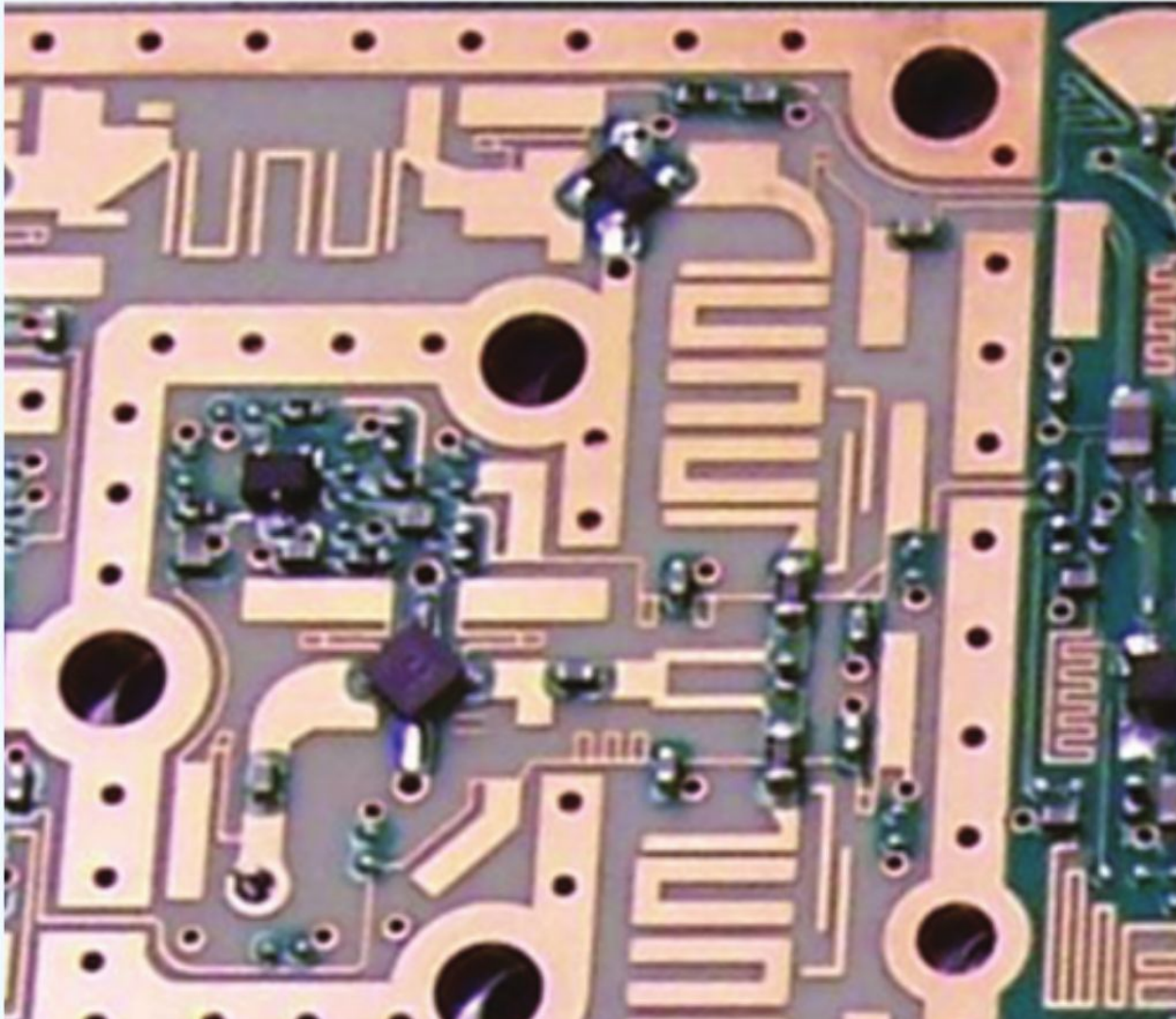


Photo of a microstrip circuit

# Homework

58

**Homework 4 is due tomorrow at midnight.**

**submit to gradescope via the canvas site.**

# Next Time



## **Section 2-6:**

Simplify by assuming lossless line.

Investigate various parameters that characterize the solution.