

EECS 230  
*ENGINEERING ELECTROMAGNETICS*  
*Leland Pierce*

Transmission Lines 4

# Chapter 2 Overview

## What is a transmission line?

Why study transmission lines?

model

diffeq

solve diffeq

wave propagation

lossless transmission line

microstrip lines

reflections

standing waves

impedance




short, open

matching


power flow

smith chart


transients

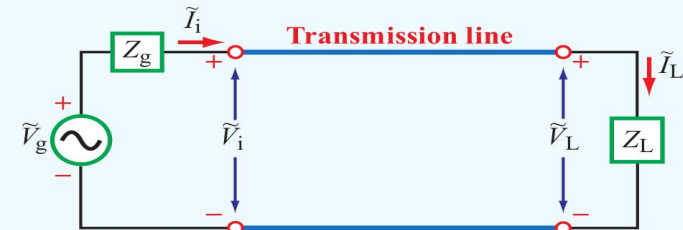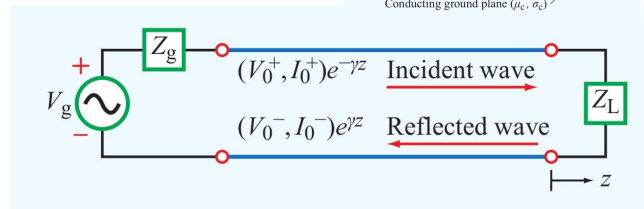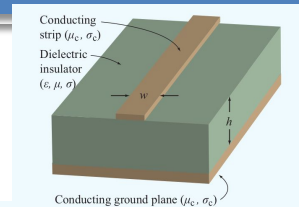



Typical High-Frequency Circuit

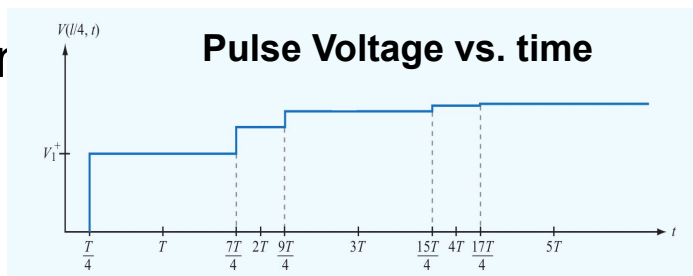

Pulse Voltage vs. time

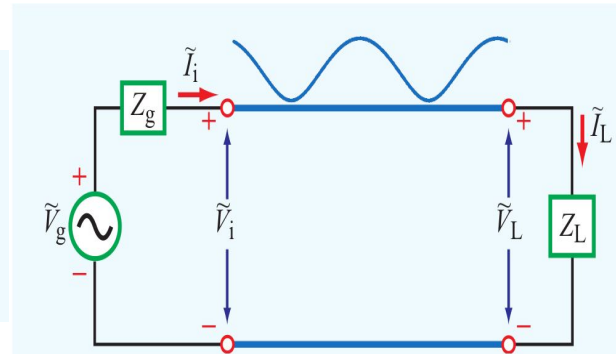

Waves on line: old methods don't work

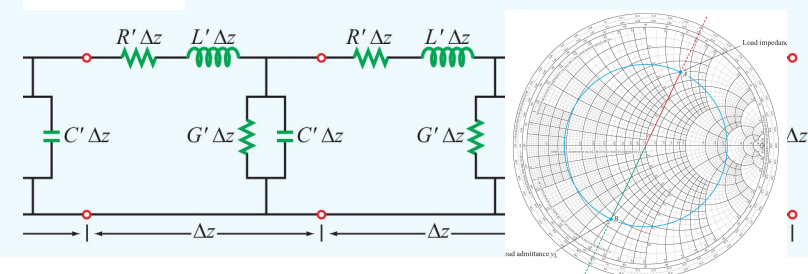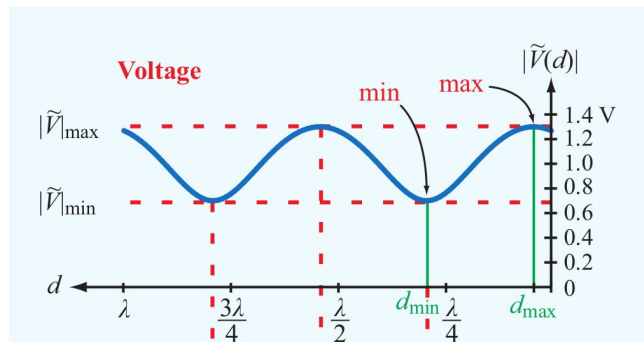

# Today's Lecture Coverage

## **Review Sections 2-1 through 2-6 of the book:**

**2-1:** What is a transmission line?

Why study transmission lines?

**2-2:** Lumped-Element Model

**2-3:** Governing Differential Eqns

**2-4:** Solve the Differential Equations

Properties of the solution: wave propagation

**2-5:** Lossless Microstrip Line

**2-6:** Lossless Transmission Lines

## **Section 2-7 of the book:**

**2-7:** Lossless Transmission Lines: Wave Impedance


# Chapter 2 Review

- A transmission line connects a **generator** to a **load**.


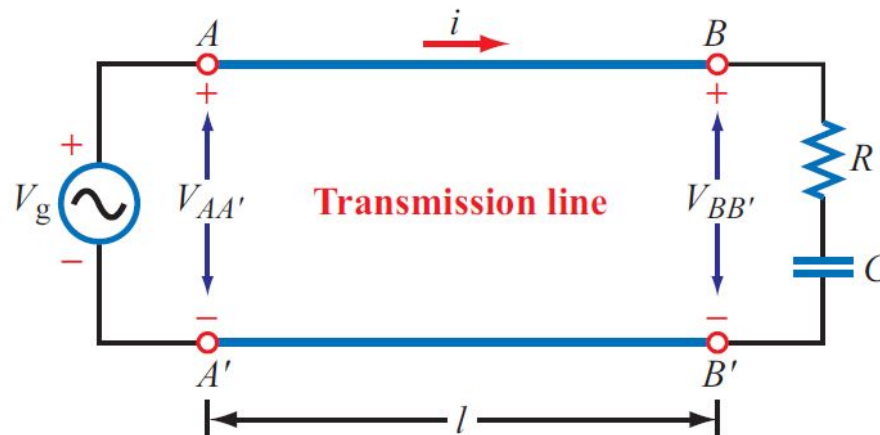
# Chapter 2 Review

Phase Delay due to length of transmission line:




$$\phi_0 = \frac{\omega l}{c} = \frac{2\pi f l}{c} = 2\pi \frac{l}{\lambda} \text{ radians.}$$

$l/\lambda \lesssim 0.01$ : Can ignore transmission-line effects


$l/\lambda \gtrsim 0.01$ : Must deal with phase shift, and other effects...
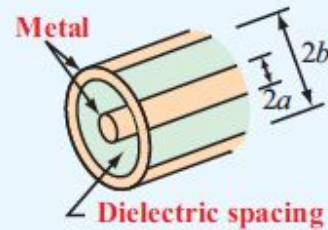
# Chapter 2 Review


Different geometries for transmission lines




(a) Coaxial line

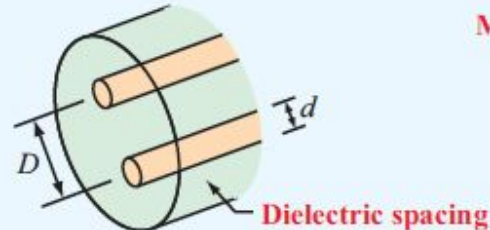


(b) Two-wire line

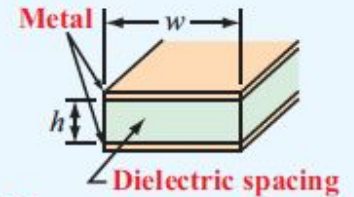


(c) Parallel-plate line

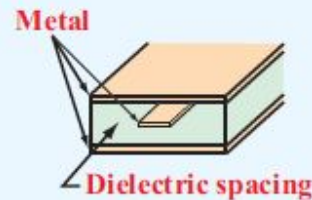

(d) Strip line

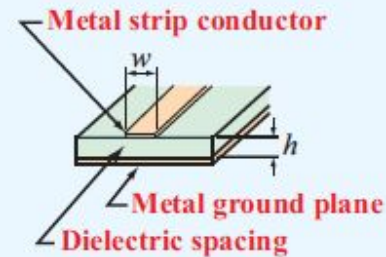


(e) Microstrip line

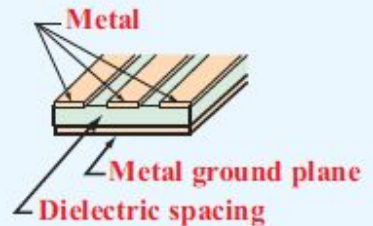


(f) Coplanar waveguide

## TEM Transmission Lines

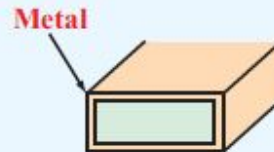

(g) Rectangular waveguide

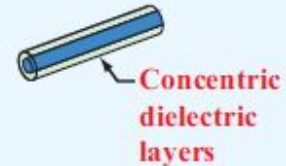


(h) Optical fiber

## Higher-Order Transmission Lines

# Chapter 2 Review

## Lumped-Element Model:

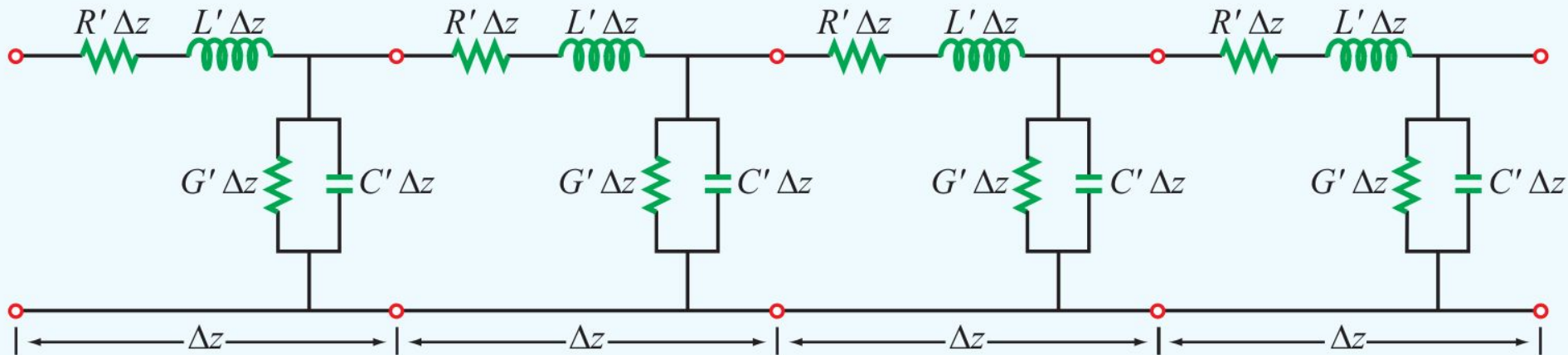

**All parameters are "per unit length":**

**R': Combined Resistance of BOTH conductors:  $\square/m$**

**L': Combined Inductance of BOTH conductors, H/m**

**G': Conductance of insulation**

between inner and outer conductor, S/m

**C': Capacitance**

between inner and outer conductors, F/m

# Chapter 2 Review

## Lumped-Element Values: geometry/materials/freq

**Table 2-1** Transmission-line parameters  $R'$ ,  $L'$ ,  $G'$ , and  $C'$  for three types of lines.

Parameter	Coaxial	Two-Wire	Parallel-Plate	Unit
$R'$	$\frac{R_s}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right)$	$\frac{2R_s}{\pi d}$	$\frac{2R_s}{w}$	$\Omega/\text{m}$
$L'$	$\frac{\mu}{2\pi} \ln(b/a)$	$\frac{\mu}{\pi} \ln \left[ (D/d) + \sqrt{(D/d)^2 - 1} \right]$	$\frac{\mu h}{w}$	$\text{H}/\text{m}$
$G'$	$\frac{2\pi\sigma}{\ln(b/a)}$	$\frac{\pi\sigma}{\ln \left[ (D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\sigma w}{h}$	$\text{S}/\text{m}$
$C'$	$\frac{2\pi\epsilon}{\ln(b/a)}$	$\frac{\pi\epsilon}{\ln \left[ (D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\epsilon w}{h}$	$\text{F}/\text{m}$

$$R_s = \sqrt{\pi f \mu_c / \sigma_c}$$

# Chapter 2 Review

Lumped-Element Values: geometry/materials/freq

$$L' C' = \mu \epsilon$$

$$\frac{G'}{C'} = \frac{\sigma}{\epsilon}$$

This turns out to be true for all the transmission-lines we study.

# Chapter 2 Review

Transmission-line governing Differential Equations

$$-\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L') \tilde{I}(z),$$

$$-\frac{d\tilde{I}(z)}{dz} = (G' + j\omega C') \tilde{V}(z).$$

**(telegrapher's equations in phasor form)**

# Chapter 2 Review

Transmission-line governing Differential Equation for  $V$ :

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0,$$

**(wave equation for  $\tilde{V}(z)$ )**

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}.$$

**(propagation constant)**

# Chapter 2 Review

Complex propagation constant:

$$\gamma = \alpha + j\beta$$

Where:

$\gamma$ : Units of 1/m

$\alpha$ : Attenuation constant, units of Np/m (>0 in this class)

$\beta$ : Phase constant, units of rad/m

Np and radians are both "dimensionless", and are the conventional "units" for these parameters.

# Chapter 2 Review

Form of the solution: traveling waves, going in both directions:

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z} \quad (\text{A}).$$

$$Z_0 = \frac{R' + j\omega L'}{\gamma} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \quad (\Omega),$$

# Chapter 2 Review

Solution in time-domain

$$v(z,t) = |V_0^+|e^{-\alpha z} \cos(\omega t - \beta z + \phi^+) \\ + |V_0^-|e^{+\alpha z} \cos(\omega t + \beta z + \phi^-)$$

Remaining unknowns are determined via specification of source and load.

# Chapter 2 Review

## Microstrip Transmission-Line Parameters:


$$Z_0 = \frac{60}{\sqrt{\epsilon_{\text{eff}}}} \ln \left\{ \frac{6 + (2\pi - 6)e^{-t}}{s} + \sqrt{1 + \frac{4}{s^2}} \right\},$$

$$t = \left( \frac{30.67}{s} \right)^{0.75} \quad s = \frac{w}{h},$$

$$\epsilon_{\text{eff}} = \frac{\epsilon_r + 1}{2} + \left( \frac{\epsilon_r - 1}{2} \right) \left( 1 + \frac{10}{s} \right)^{-xy},$$

$$x = 0.56 \left[ \frac{\epsilon_r - 0.9}{\epsilon_r + 3} \right]^{0.05},$$
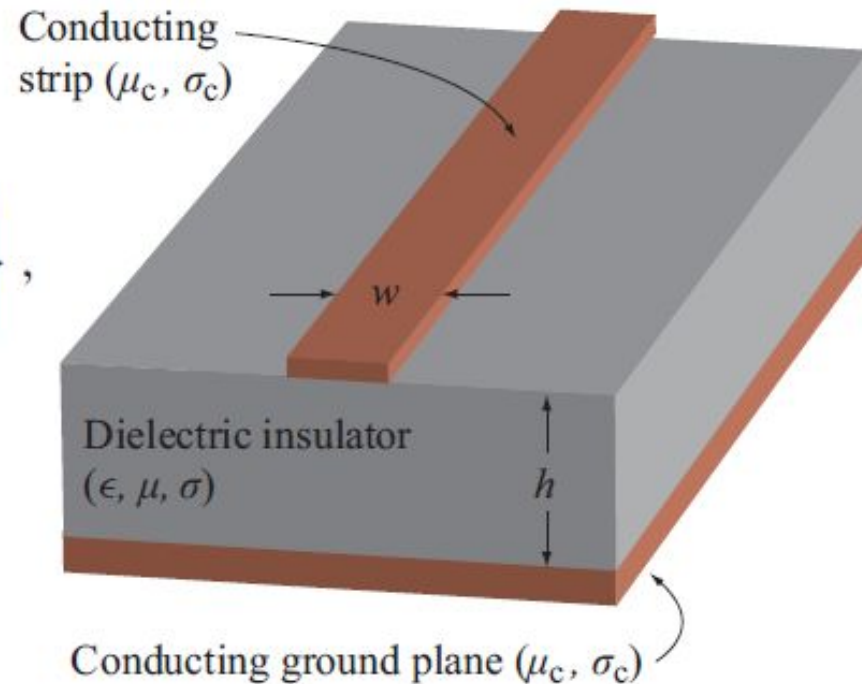
$$y = 1 + 0.02 \ln \left( \frac{s^4 + 3.7 \times 10^{-4} s^2}{s^4 + 0.43} \right) + 0.05 \ln(1 + 1.7 \times 10^{-4} s^3).$$



Largely the result of fitting lots of data using functional forms based on intuition.

# Chapter 2 Review

- The wave equation for a general Transmission Line.

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0, \quad (2.21)$$

- General solution of the wave equation
  - *It involves both incident and reflected waves*

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$

# Chapter 2 Review

- Useful Relations for lossless Transmission Lines:

$$\alpha = 0 \quad (\text{lossless line}),$$
$$\beta = \omega\sqrt{L'C'} \quad (\text{lossless line}). \quad (2.45)$$

$$\beta = \omega\sqrt{\mu\varepsilon} \quad (\text{rad/m}), \quad (2.49)$$

$$u_p = \frac{1}{\sqrt{\mu_0\varepsilon_0}} \frac{1}{\sqrt{\varepsilon_r}} = \frac{c}{\sqrt{\varepsilon_r}}$$

$$\lambda = \frac{u_p}{f} = \frac{c}{f} \frac{1}{\sqrt{\varepsilon_r}} = \frac{\lambda_0}{\sqrt{\varepsilon_r}}$$

$$Z_0 = \sqrt{\frac{L'}{C'}} \quad (\text{lossless line}), \quad (2.46) \quad (\text{REAL})$$

# Chapter 2 Review

- Voltage reflection coefficient due to load:







$$\begin{aligned}\Gamma &= \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \\ &= \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} \\ &= \frac{z_L - 1}{z_L + 1}\end{aligned}$$

- Load impedance in terms of  $\Gamma$ :

$$Z_L = \frac{1 + \Gamma}{1 - \Gamma} Z_0$$

# Chapter 2 Review

**Reflection Coefficient  $\Gamma = |\Gamma|e^{j\theta_r}$**

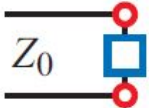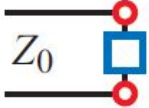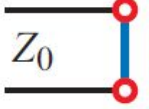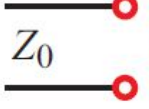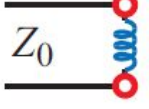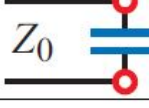Load	$ \Gamma $	$\theta_r$
 $Z_L = (r + jx)Z_0$	$\left[ \frac{(r - 1)^2 + x^2}{(r + 1)^2 + x^2} \right]^{1/2}$	$\tan^{-1} \left( \frac{x}{r - 1} \right) - \tan^{-1} \left( \frac{x}{r + 1} \right)$
 $Z_0$	0 (no reflection)	irrelevant
 (short)	1	$\pm 180^\circ$ (phase opposition)
 (open)	1	0 (in-phase)
 $jX = j\omega L$	1	$\pm 180^\circ - 2 \tan^{-1} x$
 $jX = \frac{-j}{\omega C}$	1	$\pm 180^\circ + 2 \tan^{-1} x$

$$z_L = Z_L/Z_0 = (R + jX)/Z_0 = r + jx$$

# Chapter 2 Review

- Concept of standing wave



$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z}),$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z}).$$

- Voltage (current) magnitudes at any point on line:

$$|\tilde{V}(d)| = |V_0^+| \left[ 1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}. \quad (2.66)$$

# Chapter 2 Review

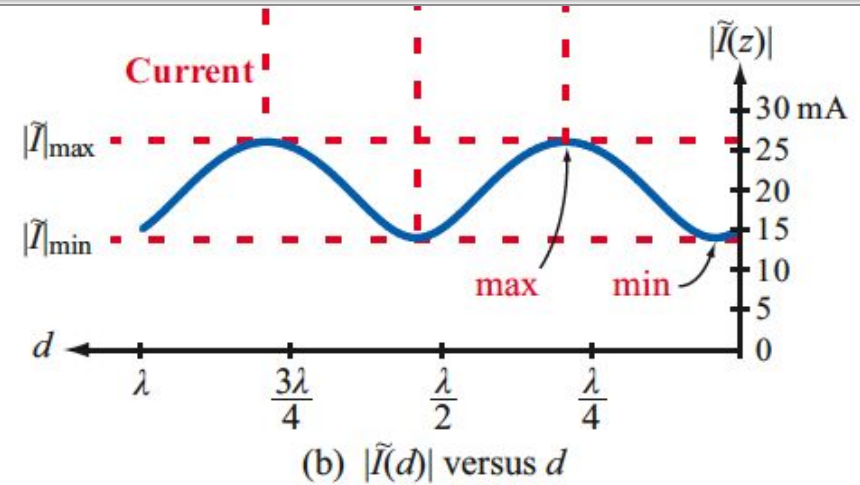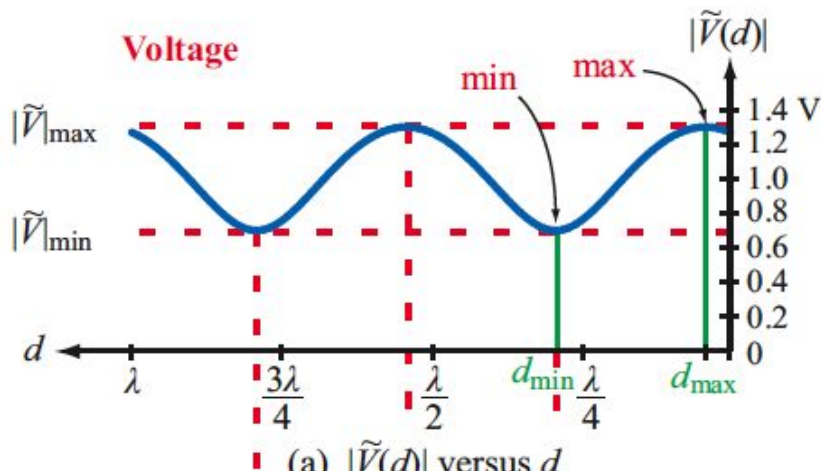



- Location of minima / maxima

$$d_{\max} = \frac{\theta_r + 2n\pi}{2\beta} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2},$$

$$\begin{cases} n = 1, 2, \dots & \text{if } \theta_r < 0, \\ n = 0, 1, 2, \dots & \text{if } \theta_r \geq 0, \end{cases} \quad (2.70)$$

Value of  $V_{\max}$ :  $|\tilde{V}(d)| = |\tilde{V}|_{\max} = |V_0^+| [1 + |\Gamma|],$

# Chapter 2 Review

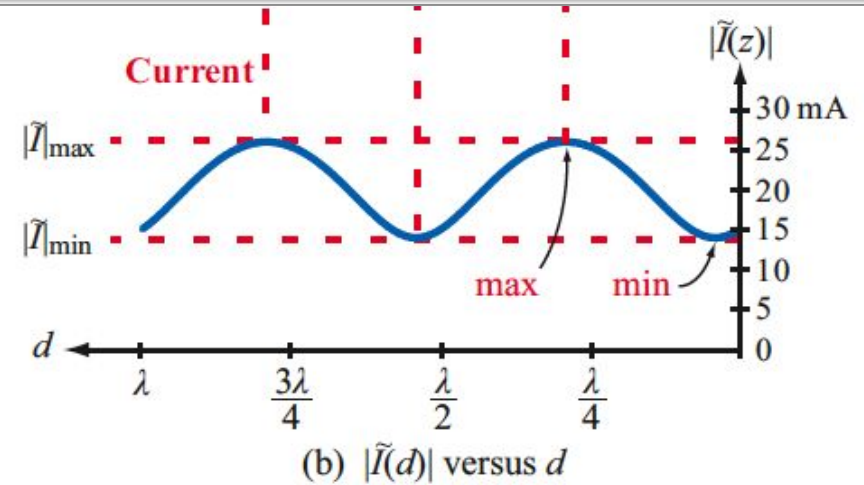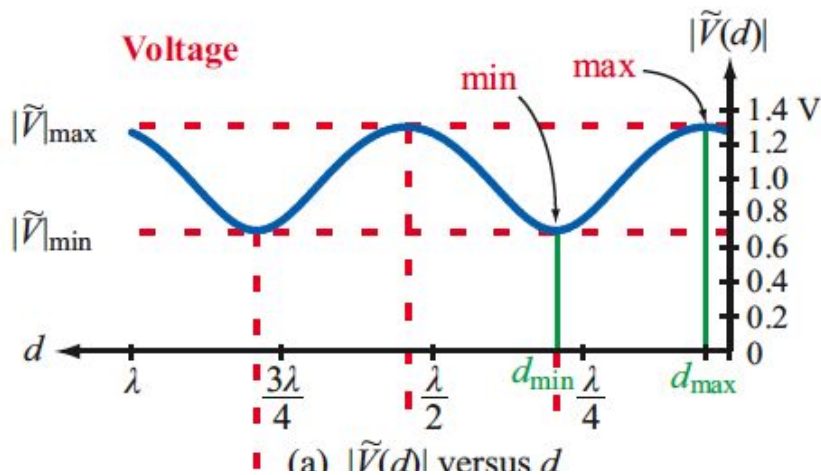


- Spatial period of standing wave:  $\frac{\lambda}{2}$
- Standing wave ratio S:

$$S = \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

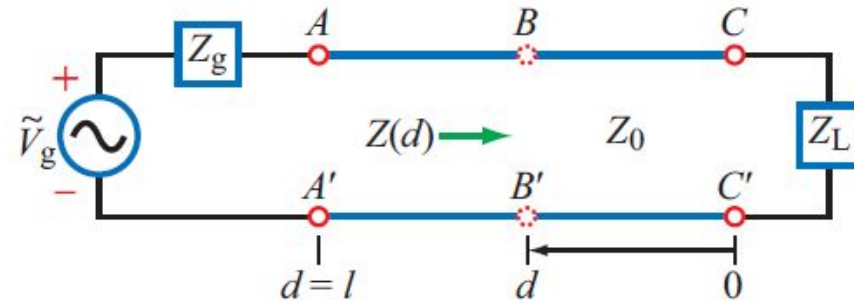
# 2-7 Wave Impedance

At a distance  $d$  from the load:

$$\begin{aligned}
 Z(d) &= \frac{\tilde{V}(d)}{\tilde{I}(d)} \\
 &= \frac{V_0^+ [e^{j\beta d} + \Gamma e^{-j\beta d}]}{V_0^+ [e^{j\beta d} - \Gamma e^{-j\beta d}]} Z_0 \\
 &= Z_0 \left[ \frac{1 + \Gamma e^{-j2\beta d}}{1 - \Gamma e^{-j2\beta d}} \right] \\
 &= Z_0 \left[ \frac{1 + \Gamma_d}{1 - \Gamma_d} \right] \quad (\Omega),
 \end{aligned}$$



(a) Actual circuit

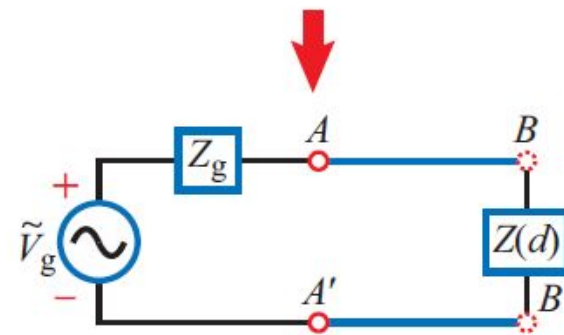

(b) Equivalent circuit

# 2-7 Wave Impedance

Define the phase-shifted voltage reflection coefficient:


$$\Gamma_d = \Gamma e^{-j2\beta d} = |\Gamma| e^{j\theta_r} e^{-j2\beta d}$$

$$= |\Gamma| e^{j(\theta_r - 2\beta d)}$$


$Z(d)$  is different than  $Z_0$ :  
Ratio of **Total** Voltage and Current

Recall:  $Z_0 = \frac{V_0^+}{I_0^+}$

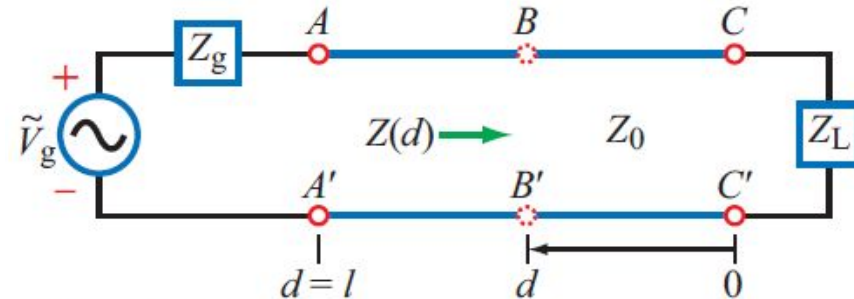The ratio for the forward-going wave only.



(a) Actual circuit

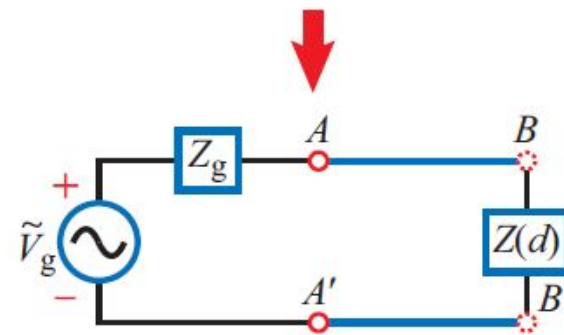

(b) Equivalent circuit


# 2-7 Wave Impedance

Reflection coefficient at  $d=l$ :


$$\Gamma_l = \Gamma e^{-j2\beta l} = |\Gamma| e^{j(\theta_r - 2\beta l)}$$

Impedance at  $z=l$ :
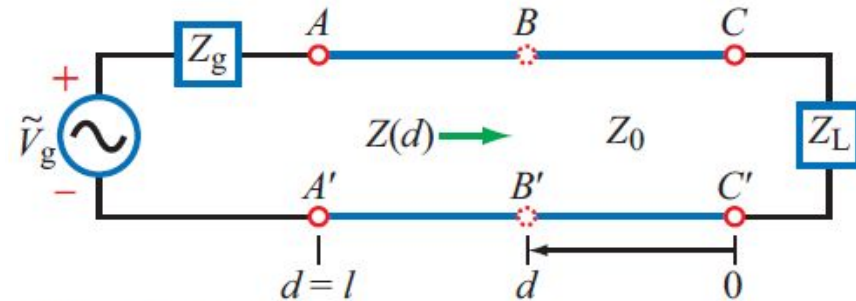
$$Z_{\text{in}} = Z(d=l) = Z_0 \left[ \frac{1 + \Gamma_l}{1 - \Gamma_l} \right]$$




(a) Actual circuit

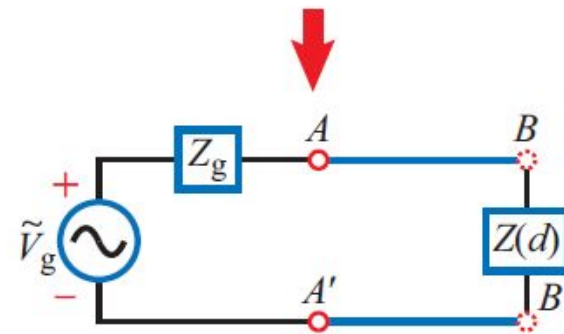

(b) Equivalent circuit

# 2-7 Input Impedance

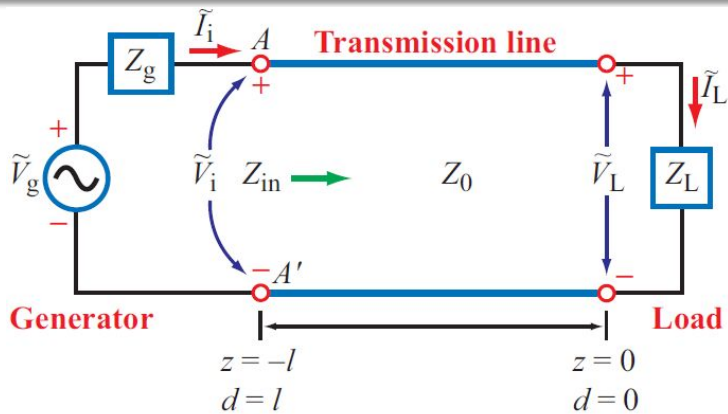


Alternative expression:

Input impedance:

impedance of the transmission line at  $d=l$ :
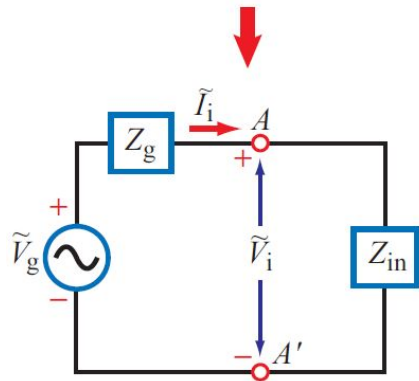
$$Z_{in} = Z(d = l) = \frac{\tilde{V}(d = l)}{\tilde{I}(d = l)}$$




Note that  $Z_{in}$  is different from the Characteristic Impedance, and is different from the Load Impedance:

$$Z_{in} \neq Z_0$$

$$Z_{in} \neq Z_L$$

# 2-7 Input Impedance


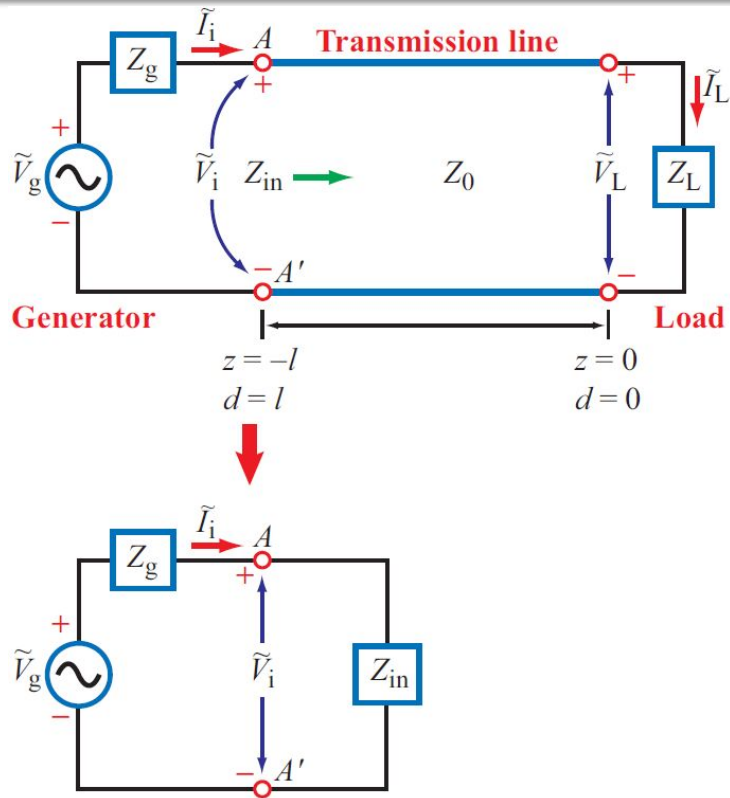


Use voltage and current at  $d=l$ :

$$Z_{in} = \frac{V_0^+ [e^{+j\beta l} + \Gamma_L e^{-j\beta l}]}{\frac{V_0^+}{Z_0} [e^{+j\beta l} - \Gamma_L e^{-j\beta l}]}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$


# 2-7 Input Impedance

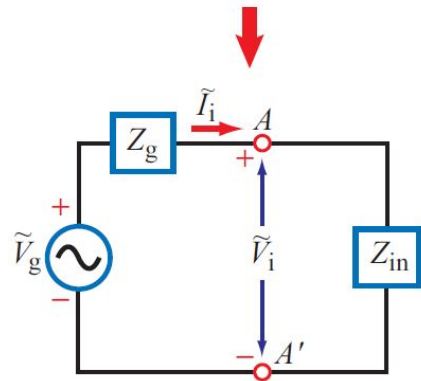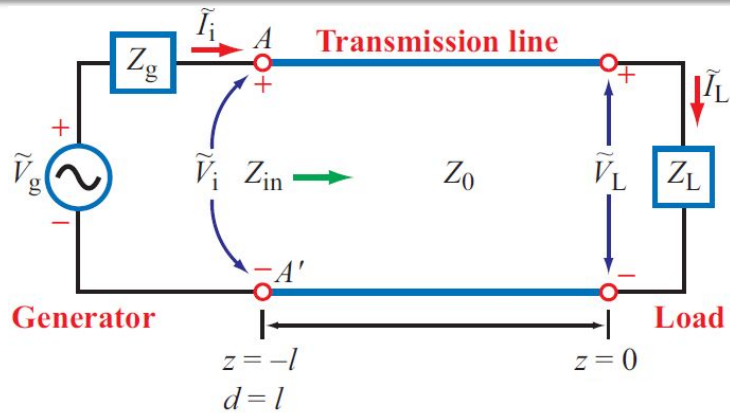

Use expression for  $\Gamma$ :

$$\begin{aligned}
 Z_{in} &= Z_0 \left[ \frac{e^{+j\beta l} + \left( \frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-j\beta l}}{e^{+j\beta l} - \left( \frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-j\beta l}} \right] \\
 &= Z_0 \left[ \frac{(Z_L + Z_0)e^{+j\beta l} + (Z_L - Z_0)e^{-j\beta l}}{(Z_L + Z_0)e^{+j\beta l} - (Z_L - Z_0)e^{-j\beta l}} \right] \\
 &= Z_0 \left[ \frac{Z_L(e^{+j\beta l} + e^{-j\beta l}) + Z_0(e^{+j\beta l} - e^{-j\beta l})}{Z_L(e^{+j\beta l} - e^{-j\beta l}) + Z_0(e^{+j\beta l} + e^{-j\beta l})} \right]
 \end{aligned}$$


# 2-7 Input Impedance

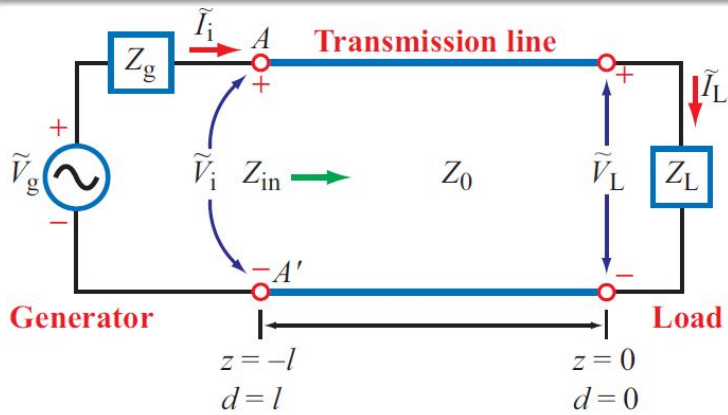

Use expressions for sin and cos:

$$e^{+j\beta l} + e^{-j\beta l} = 2 \cos(\beta l)$$
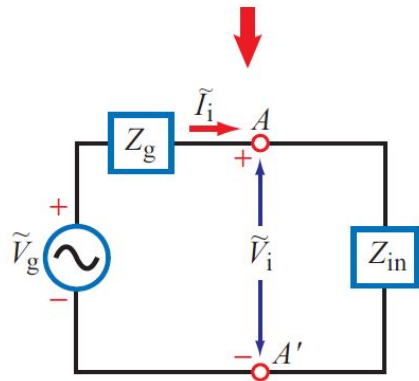
$$e^{+j\beta l} - e^{-j\beta l} = 2j \sin(\beta l)$$




$$Z_{\text{in}} = Z_0 \left[ \frac{Z_L \cos(\beta l) + jZ_0 \sin(\beta l)}{jZ_L \sin(\beta l) + Z_0 \cos(\beta l)} \right]$$

$$= Z_0 \left[ \frac{z_L \cos(\beta l) + j \sin(\beta l)}{\cos(\beta l) + jz_L \sin(\beta l)} \right]$$

$$Z_{\text{in}} = Z_0 \left[ \frac{z_L + j \tan(\beta l)}{1 + jz_L \tan(\beta l)} \right]$$

## 2-7 Voltage Amplitude

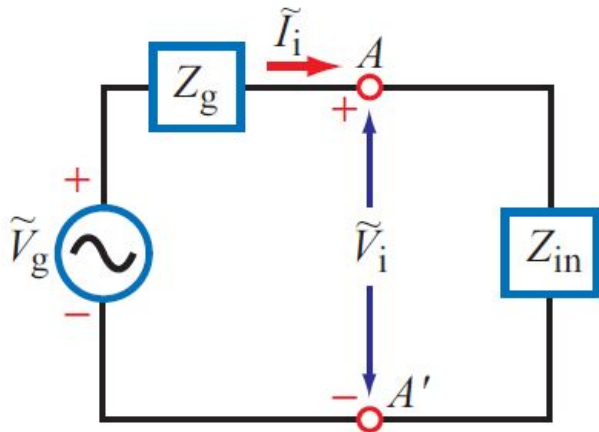

Finally, can solve for the amplitude of the voltage. Voltage division:

$$\tilde{V}_i = \tilde{I}_i Z_{in} = \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}},$$


And from the transmission line solution:

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$$

at  $z=-l$ :

$$\tilde{V}_i = \tilde{V}(-l) = V_0^+ [e^{j\beta l} + \Gamma e^{-j\beta l}].$$

# 2-7 Voltage Amplitude

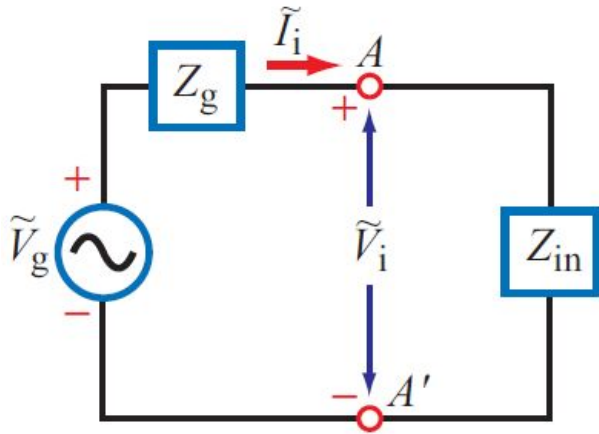


Equate these 2 expressions.  
Solve for the Voltage Amplitude:

$$\frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} = V_0^+ [e^{j\beta l} + \Gamma e^{-j\beta l}]$$

$$\frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} = V_0^+$$

## 2-7 Voltage Amplitude

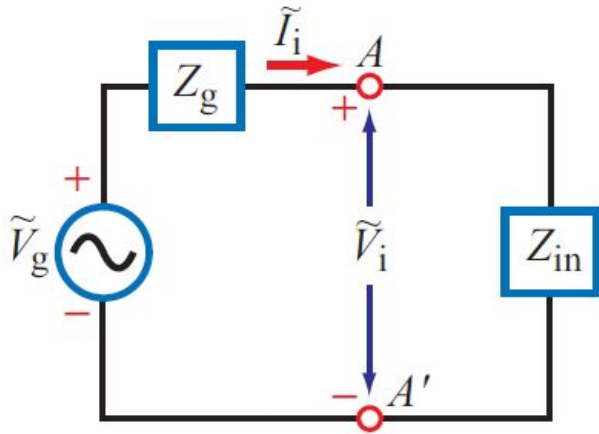

Equate these 2 expressions.  
Solve for the Voltage Amplitude:

$$V_0^+ = \left( \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left( \frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right).$$

We used the boundary conditions ( $Z_L, Z_g, V_g, l$ ) to solve for the 2 remaining unknowns:  $V_0^+, V_0^-$

This completes the solution of the transmission line differential equation.

# Example 2-7

**Given:** Lossless transmission line with:

$$f = 1.05 \text{ GHz}$$

$$Z_g = 10 \ \Omega$$

$$V_g = 10\text{V} \sin(\omega t + 30^\circ)$$

$$Z_L = 100 + j 50 \ \Omega$$


$$Z_0 = 50 \ \Omega$$

$$l = 67 \text{ cm}$$

$$u_p = 0.7c$$

**Find:**  $v(d,t)$ ,  $i(d,t)$  on the line.

# Example 2-7

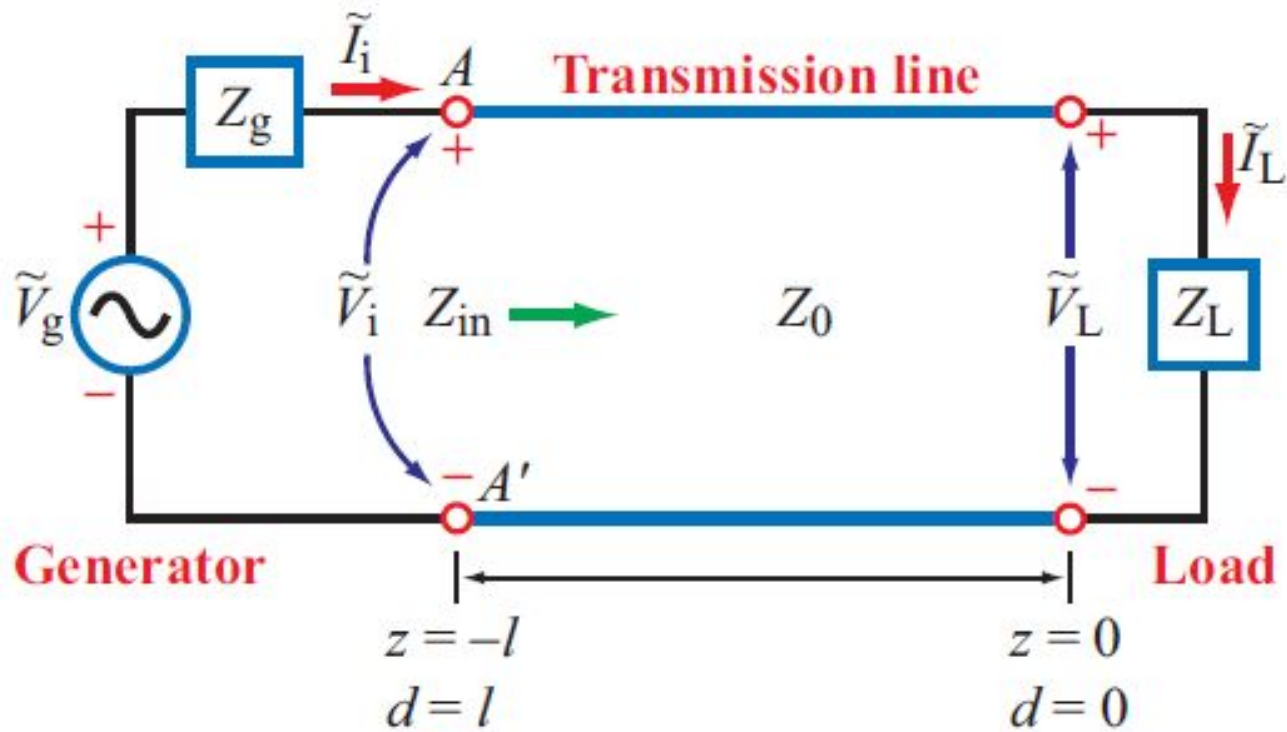

# Example 2-7

Know:

$$\tilde{V}(d) = V_0^+ (e^{j\beta d} + \Gamma e^{-j\beta d})$$

$$\tilde{I}(d) = \frac{V_0^+}{Z_0} (e^{j\beta d} - \Gamma e^{-j\beta d})$$

$$V_0^+ = \left( \frac{\tilde{V}_g Z_{\text{in}}}{Z_g + Z_{\text{in}}} \right) \left( \frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right). \quad (2.82)$$

$$Z_{\text{in}} = Z(l) = Z_0 \left[ \frac{1 + \Gamma_l}{1 - \Gamma_l} \right].$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\beta = \frac{2\pi}{\lambda} \quad u_p = f\lambda \quad \Gamma_l = |\Gamma| e^{j(\theta_r - 2\beta l)}$$

# Example 2-7

Solution:

$$u_p = \lambda f$$

$$\lambda = \frac{u_p}{f}$$

$$\lambda = \frac{(0.7)3 \times 10^8 \text{ m/sec}}{1.05 \times 10^9 \text{ Hz}}$$

$$\lambda = 0.2 \text{ m}$$

# Example 2-7

**Solution:**

$$\beta l = \frac{2\pi}{\lambda} l$$

$$\beta l = \frac{2\pi}{0.2 \text{ m}} (0.67 \text{ m})$$

$$\beta l = 6.7\pi$$

Note that since this is used only in the phase terms, can remove multiples of  $2\pi$

$$\beta l = 0.7\pi = 2.2 \text{ rad} = 126^\circ$$

$$2\beta l = 252^\circ$$

# Example 2-7

Solution:

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma = \frac{100 + j50 - 50}{100 + j50 + 50}$$

$$\Gamma = \frac{50 + j50}{150 + j50}$$

$$\Gamma = \frac{\sqrt{50^2 + 50^2} e^{j \tan^{-1}(1)}}{\sqrt{150^2 + 50^2} e^{j \tan^{-1}(50/150)}}$$

# Example 2-7

Solution:

$$\Gamma = \frac{\sqrt{50^2 + 50^2} e^{j \tan^{-1}(1)}}{\sqrt{150^2 + 50^2} e^{j \tan^{-1}(50/150)}}$$

$$\Gamma = \frac{70.7 e^{j 45^\circ}}{158.1 e^{j 18.4^\circ}}$$

$$\Gamma = 0.447 e^{j(45^\circ - 18.4^\circ)}$$

$$\Gamma = 0.447 e^{j 26.6^\circ}$$

# Example 2-7

**Solution:**

$$Z_{\text{in}} = Z_0 \left( \frac{1 + \Gamma_l}{1 - \Gamma_l} \right)$$

$$\Gamma_l = \Gamma e^{-j2\beta l}$$

$$\Gamma_l = 0.447 e^{j26.6^\circ} e^{-j252^\circ}$$

$$\Gamma_l = 0.447 e^{-j225.4^\circ}$$

$$\Gamma_l = 0.447 \cos(-225.4^\circ) + j0.447 \sin(-225.4^\circ)$$

$$\Gamma_l = -0.314 + j0.318$$

# Example 2-7

Solution:

$$Z_{\text{in}} = Z_0 \left( \frac{1 + \Gamma_l}{1 - \Gamma_l} \right)$$

$$Z_{\text{in}} = (50 \Omega) \left( \frac{1 + (-0.314 + j0.318)}{1 - (-0.314 + j0.318)} \right)$$

$$Z_{\text{in}} = (50 \Omega) \left( \frac{0.686 + j0.318}{1.314 - j0.318} \right)$$

$$Z_{\text{in}} = (50 \Omega) \left( \frac{\sqrt{0.686^2 + 0.318^2} e^{j \tan^{-1}(0.318/0.686)}}{\sqrt{1.314^2 + 0.318^2} e^{j \tan^{-1}(-0.318/1.314)}} \right)$$

## Example 2-7

Solution:

$$Z_{\text{in}} = (50 \Omega) \left( \frac{\sqrt{0.686^2 + 0.318^2} e^{j \tan^{-1}(0.318/0.686)}}{\sqrt{1.314^2 + 0.318^2} e^{j \tan^{-1}(-0.318/1.314)}} \right)$$

$$Z_{\text{in}} = (50 \Omega) \left( \frac{0.756 e^{j24.87^\circ}}{1.352 e^{-j13.6^\circ}} \right)$$

$$Z_{\text{in}} = (50 \Omega) 0.559 e^{j38.47^\circ}$$

$$Z_{\text{in}} = (27.95 \Omega) \cos(38.47^\circ) + j(27.95 \Omega) \sin(38.47^\circ)$$

$$Z_{\text{in}} = 21.88 + j17.39 \Omega$$

# Example 2-7

Solution:

$$v_g(t) = 10 \text{ V} \sin(\omega t + 30^\circ)$$

$$v_g(t) = 10 \text{ V} \cos(90^\circ - (\omega t + 30^\circ))$$

$$v_g(t) = 10 \text{ V} \cos(-\omega t + 60^\circ)$$

$$v_g(t) = 10 \text{ V} \cos(\omega t - 60^\circ)$$

$$\tilde{V}_g = 10e^{-j60^\circ} \text{ V}$$

## Example 2-7

Solution:

$$V_0^+ = \left[ \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right] \left[ \frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right]$$

$$Z_g + Z_{in} = 10 + 21.88 + j17.39$$

$$Z_g + Z_{in} = 31.88 + j17.39$$

$$Z_g + Z_{in} = \sqrt{31.88^2 + 17.39^2} e^{j \tan^{-1}(17.39/31.88)}$$

$$Z_g + Z_{in} = 36.31 e^{j28.6^\circ}$$

# Example 2-7

Solution:

$$\frac{\tilde{V}_g Z_{\text{in}}}{Z_g + Z_{\text{in}}} = \frac{10e^{-j60^\circ} 27.95e^{j38.47^\circ}}{36.31e^{j28.6^\circ}}$$

$$\frac{\tilde{V}_g Z_{\text{in}}}{Z_g + Z_{\text{in}}} = \frac{279.5e^{-j21.53^\circ}}{36.31e^{j28.6^\circ}}$$

$$\frac{\tilde{V}_g Z_{\text{in}}}{Z_g + Z_{\text{in}}} = 7.7e^{-j50.13^\circ}$$

# Example 2-7

## Solution:

$$e^{j\beta l} + \Gamma e^{-j\beta l} = e^{j126^\circ} + 0.447e^{j26.6^\circ} e^{-j126^\circ}$$

$$e^{j\beta l} + \Gamma e^{-j\beta l} = e^{j126^\circ} + 0.447e^{-j99.4^\circ}$$

$$e^{j\beta l} + \Gamma e^{-j\beta l} = \cos(126^\circ) + j \sin(126^\circ) + \\ 0.447 \cos(-99.4^\circ) + j0.447 \sin(-99.4^\circ)$$

$$e^{j\beta l} + \Gamma e^{-j\beta l} = -0.588 + j0.809 + -0.073 - j0.441$$

$$e^{j\beta l} + \Gamma e^{-j\beta l} = -0.661 + j0.368$$

# Example 2-7

**Solution:**

$$e^{j\beta l} + \Gamma e^{-j\beta l} = -0.661 + j0.368$$

$$e^{j\beta l} + \Gamma e^{-j\beta l} = \sqrt{0.661^2 + 0.368^2} e^{j(180^\circ + \tan^{-1}(-0.368/.661))}$$

$$e^{j\beta l} + \Gamma e^{-j\beta l} = 0.757 e^{j(180^\circ - 29.1^\circ)}$$

$$e^{j\beta l} + \Gamma e^{-j\beta l} = 0.757 e^{j150.9^\circ}$$

$$\frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} = 1.32 e^{-j150.9^\circ}$$

# Example 2-7

Solution:

$$V_0^+ = 7.7e^{-j50.13^\circ} + 1.32e^{-j150.93^\circ} \text{ V}$$

$$V_0^+ = 10.17e^{-j201.06^\circ} \text{ V}$$

$$V_0^+ = 10.17e^{j(360^\circ - 201.06^\circ)} \text{ V}$$

$$V_0^+ = 10.17e^{j158.94^\circ} \text{ V}$$

# Example 2-7

**Solution:** combining all this:

$$\tilde{V}(d) = V_0^+ \left( e^{j\beta d} + \Gamma e^{-j\beta d} \right)$$

$$\tilde{V}(d) = 10.17e^{j158.94^\circ} \mathbf{V} \left( e^{j\beta d} + 0.447e^{j26.6^\circ} e^{-j\beta d} \right)$$

$$\tilde{V}(d) = 10.17e^{j158.94^\circ} e^{j\beta d} \mathbf{V} + 4.55e^{j158.94^\circ} e^{j26.6^\circ} e^{-j\beta d}$$

$$\tilde{V}(d) = 10.17e^{j158.94^\circ} e^{j\beta d} + 4.55e^{j185.54^\circ} e^{-j\beta d} \mathbf{V}$$

## Example 2-7

**Solution:** and in the time-domain:

$$v(d, t) = \Re \left\{ \tilde{V}(d) e^{j\omega t} \right\}$$

$$v(d, t) = 10.17 \cos(\omega t + \beta d + 158.94^\circ) \\ + 4.55 \cos(\omega t - \beta d + 185.54^\circ) \text{ V}$$

## Example 2-7

**Solution:** and for the current:

$$\tilde{I}(d) = \frac{V_0^+}{Z_0} \left( e^{j\beta d} - \Gamma e^{-j\beta d} \right)$$

$$\tilde{I}(d) = \frac{10.17e^{j158.94^\circ}}{50} \text{ A} \left( e^{j\beta d} - 0.447e^{j26.6^\circ} e^{-j\beta d} \right)$$

$$\tilde{I}(d) = 0.2e^{j158.94^\circ} e^{j\beta d} - 0.9e^{j185.54^\circ} e^{-j\beta d} \text{ V}$$

$$i(d, t) = \Re \left\{ \tilde{I}(d) e^{j\omega t} \right\}$$

$$i(d, t) = 0.2 \cos(\omega t + \beta d + 158.94^\circ) - 0.9 \cos(\omega t - \beta d + 185.54^\circ) \text{ A}$$

# Example 2-7

**Solution:**

where:

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi}{0.2 \text{ m}} = 31.42 \text{ rad/m}$$

$$\omega = 2\pi f = 2\pi(1.05 \times 10^9 \text{ Hz}) = 6.6 \times 10^9 \text{ rad/sec}$$




# Example 2-7

Module 2.4

Transmission Line Simulator

Options: View Plots (time) ▾

d =

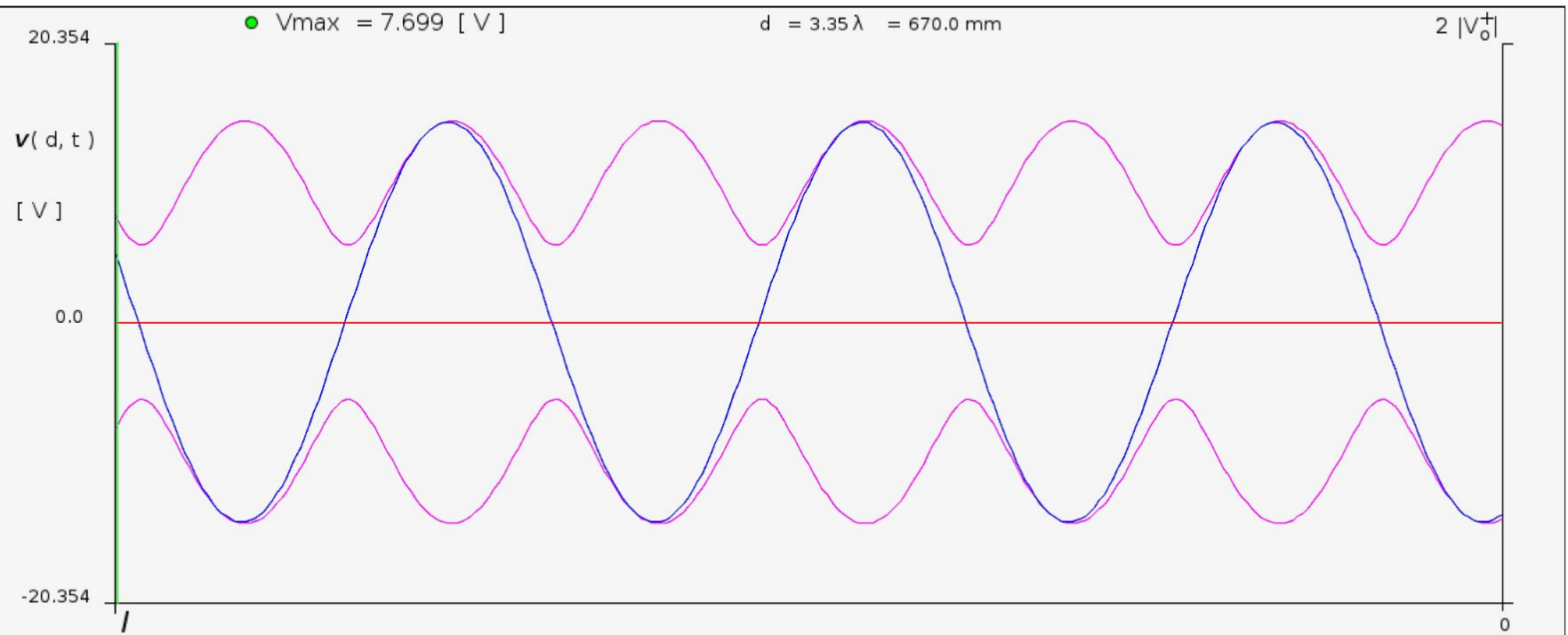

Time Dependent Voltage ▾

Incident  
Reflected  
Total

START STOP

Trace ON  Envelope ON

slower faster


# Example 2-7

Module 2.4

Transmission Line Simulator

Options: View Plots (time) ▾

d =

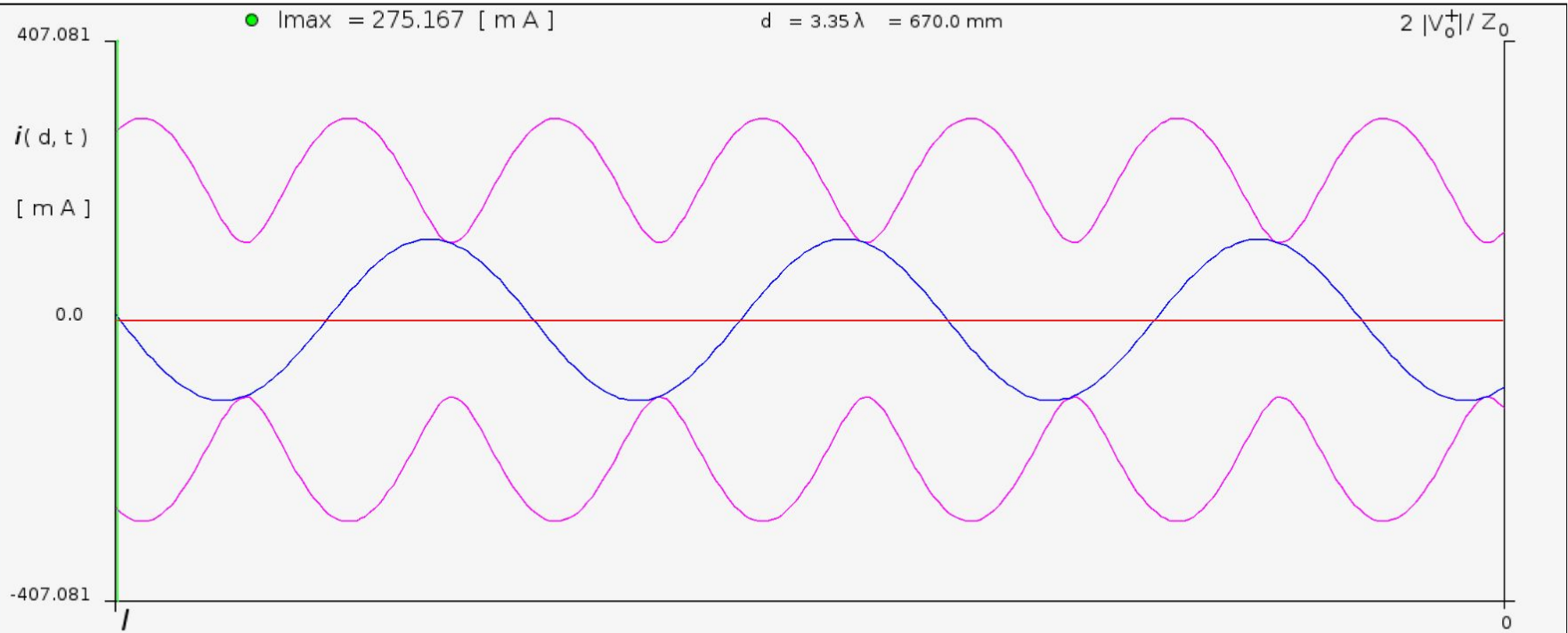

Time Dependent Current ▾


Incident

Reflected

Total

START

STOP

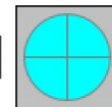

Trace ON

Envelope ON

← slower

faster →

**Module 2.5 Wave and Input Impedance** The wave impedance,  $Z(d) = \tilde{V}(d)/\tilde{I}(d)$ , exhibits a cyclical pattern as a function of position along the line. This module displays plots of the real and imaginary parts of  $Z(d)$ , specifies the locations of the voltage maximum and minimum nearest to the load, and provides other related information.

**Module 2.5 Wave and Input Impedance**

**Options:**  Display Plots & Output Data

$z =$    $\lambda$

$d = 0.0 \lambda$

$Z(d) = 25.0 - j 50.0 \ \Omega$

$d = 3.333333 \lambda = 500.0 \text{ mm}$

$Z_L = 25.0 - j 50.0 \ \Omega$

$Z_0 = 50.0 \ \Omega$

$\epsilon_r = 1.0$

$f = 2.0 \text{ GHz}$

Instructions

### Impedance λ

Re{ Z ( d ) } [ Ω ]

Im{ Z ( d ) } [ Ω ]

### Output

<b>Cursor</b>	$d = 0$ [ λ ]	
	$= 0.0$ [ m ]	
<b>Impedance</b>	$Z(d) = 25 - j 50$	
[ Ω ]	$= 55.902 \angle -1.1071 \text{ rad}$	
<b>Admittance</b>	$Y(d) = 0.008 + j 0.016$	
[ S ]	$= 0.018 \angle 1.1071 \text{ rad}$	
<b>Reflection Coefficient</b>	$\Gamma_d = 0.076 - j 0.615$	
	$= 0.62 \angle -1.446 \text{ rad}$	
	$= 0.62 \angle -82.875^\circ$	
<b>Voltage Standing Wave Ratio</b>	SWR = 4.266	
<b>Location of First Voltage Maximum &amp; Minimum</b>		
	$d(\text{max}) = 0.385 \lambda = 57.734$ [ mm ]	
	$d(\text{min}) = 0.135 \lambda = 20.234$ [ mm ]	
<b>Wavelength</b>	$\lambda = 150$ [ mm ]	


# Example 2

**Given:** Lossless transmission-line

$$Z_0 = 50 \Omega, l = 0.4 \lambda$$

$$Z_L = 30 + j60 \Omega$$

**Find:**  $\Gamma$ ,  $S$ ,  $Z_{in}$

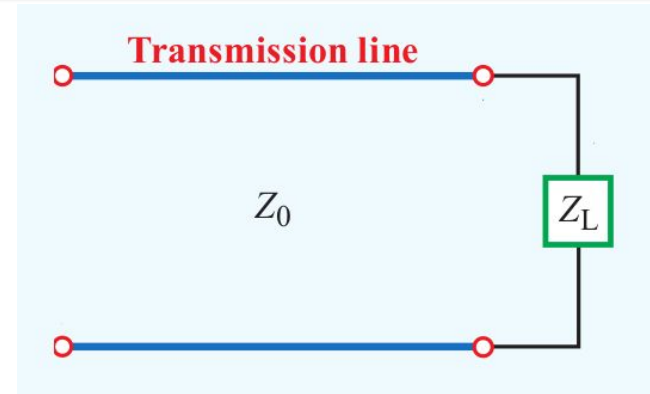

# Example 2

**Solution:**


$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma = \frac{30 + j60 - 50}{30 + j60 + 50}$$

$$\Gamma = \frac{-20 + j60}{80 + j60}$$

$$\Gamma = \frac{\sqrt{20^2 + 60^2} e^{j(180^\circ + \tan^{-1}(-60/20))}}{\sqrt{80^2 + 60^2} e^{j \tan^{-1}(60/80)}}$$
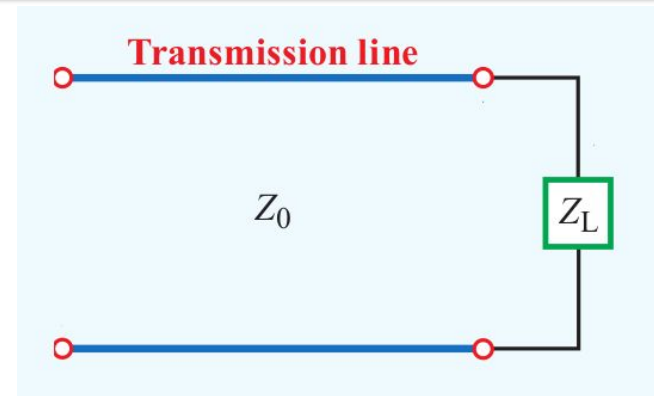
$$\Gamma = \frac{63.25 e^{j(180^\circ - 71.6^\circ)}}{100 e^{j36.9}}$$




# Example 2

Solution:

$$\Gamma = \frac{63.25e^{j(180^\circ - 71.6^\circ)}}{100e^{j36.9^\circ}}$$

$$\Gamma = 0.6325e^{j(180^\circ - 71.6^\circ - 36.9^\circ)}$$

$$\Gamma = 0.63e^{j71.5^\circ}$$

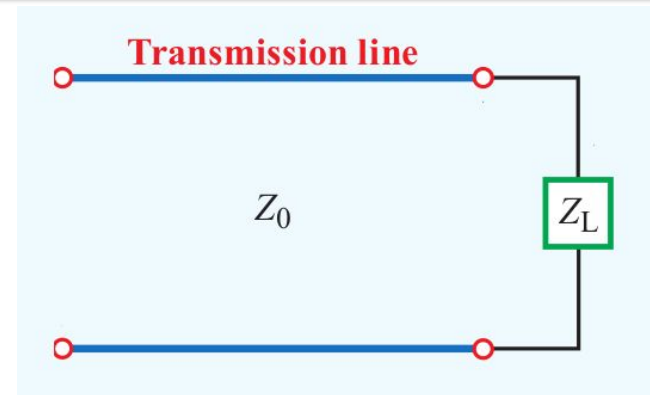


# Example 2

Solution:

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$S = \frac{1 + 0.63}{1 - 0.63}$$

$$S = 4.4$$

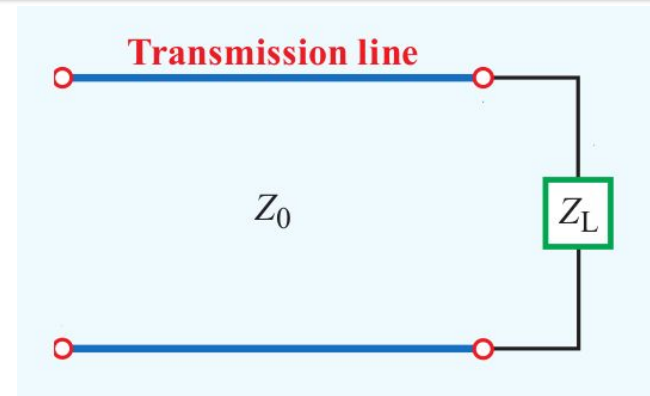

# Example 2

**Solution:**


$$Z_{\text{in}} = Z_0 \left( \frac{1 + \Gamma_l}{1 - \Gamma_l} \right)$$

$$\Gamma_l = \Gamma e^{-j2\beta l}$$

$$\beta l = 2\pi l / \lambda$$

$$\beta l = 2\pi(0.4)$$

$$\beta l = 2.5 \text{ rad}$$

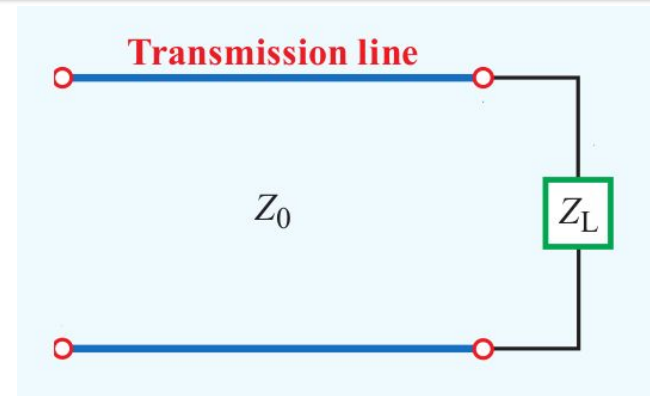

# Example 2

**Solution:**

$$\Gamma_l = \Gamma e^{-j2\beta l}$$

$$\Gamma_l = 0.63e^{j71.5^\circ} e^{-j2(2.5 \text{ rad})}$$


$$\Gamma_l = 0.63e^{j(71.5^\circ - 5 \text{ rad})}$$

$$\Gamma_l = 0.63e^{j(71.5^\circ - 286.5^\circ)}$$

$$\Gamma_l = 0.63e^{-j215.5^\circ}$$

$$\Gamma_l = 0.63 \cos(-215^\circ) + 0.63 \sin(-215^\circ)$$

$$\Gamma_l = -0.516 + j0.36$$

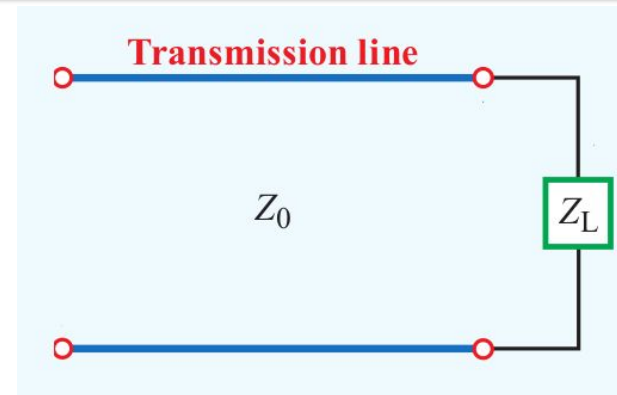

# Example 2


**Solution:**

$$Z_{\text{in}} = Z_0 \left( \frac{1 + \Gamma_l}{1 - \Gamma_l} \right)$$

$$Z_{\text{in}} = (50 \Omega) \left( \frac{1 + (-0.516 + j0.36)}{1 - (-0.516 + j0.36)} \right)$$


$$Z_{\text{in}} = (50 \Omega) \left( \frac{0.484 + j0.36}{1.516 - j0.36} \right)$$
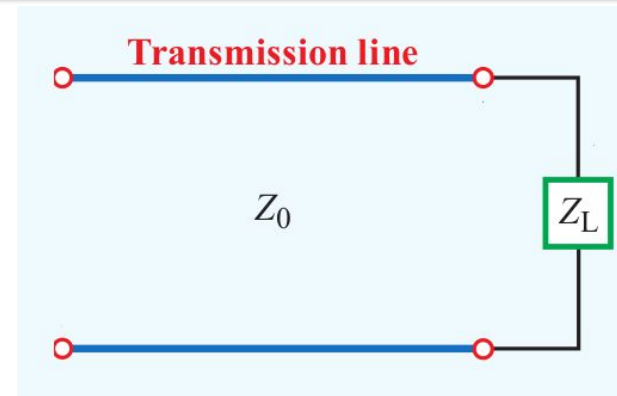
$$Z_{\text{in}} = (50 \Omega) \left( \frac{\sqrt{0.484^2 + 0.36^2} e^{j \tan^{-1}(0.36/0.484)}}{\sqrt{1.516^2 + 0.36^2} e^{j \tan^{-1}(-0.36/1.516)}} \right)$$



# Example 2

Solution:

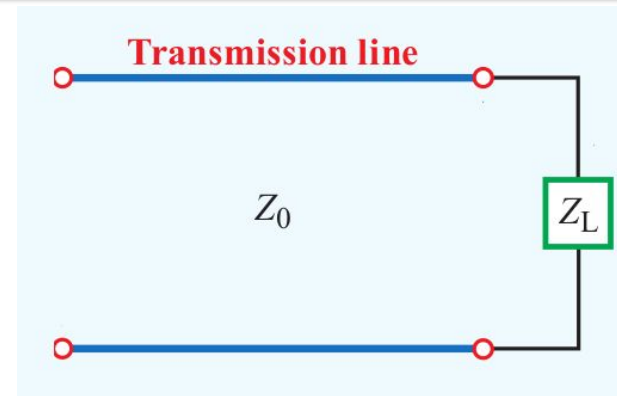

$$Z_{\text{in}} = (50 \Omega) \left( \frac{\sqrt{0.484^2 + 0.36^2} e^{j \tan^{-1}(0.36/0.484)}}{\sqrt{1.516^2 + 0.36^2} e^{j \tan^{-1}(-0.36/1.516)}} \right)$$

$$Z_{\text{in}} = (50 \Omega) \left( \frac{0.6 e^{j36.6^\circ}}{1.56 e^{-j13.4^\circ}} \right)$$

$$Z_{\text{in}} = (50 \Omega) 0.4 e^{j(36.6^\circ + 13.4^\circ)}$$

$$Z_{\text{in}} = 20 e^{j50^\circ} \Omega$$

# Example 3

**Given:** Lossless transmission-line

$$V_g = 10V \cos(\omega t)$$

$$\omega = 1 \times 10^9 \text{ rad/sec}$$

$$Z_g = 50 \Omega$$

$$Z_0 = 50 \Omega$$


$$\epsilon_r = 3$$

$$l = 10 \text{ cm}$$

$$Z_L = 50 + j 150 \Omega$$

**Find:**  $\Gamma$ ,  $Z_{in}$ ,  $\tilde{V}_i$

# Example 3

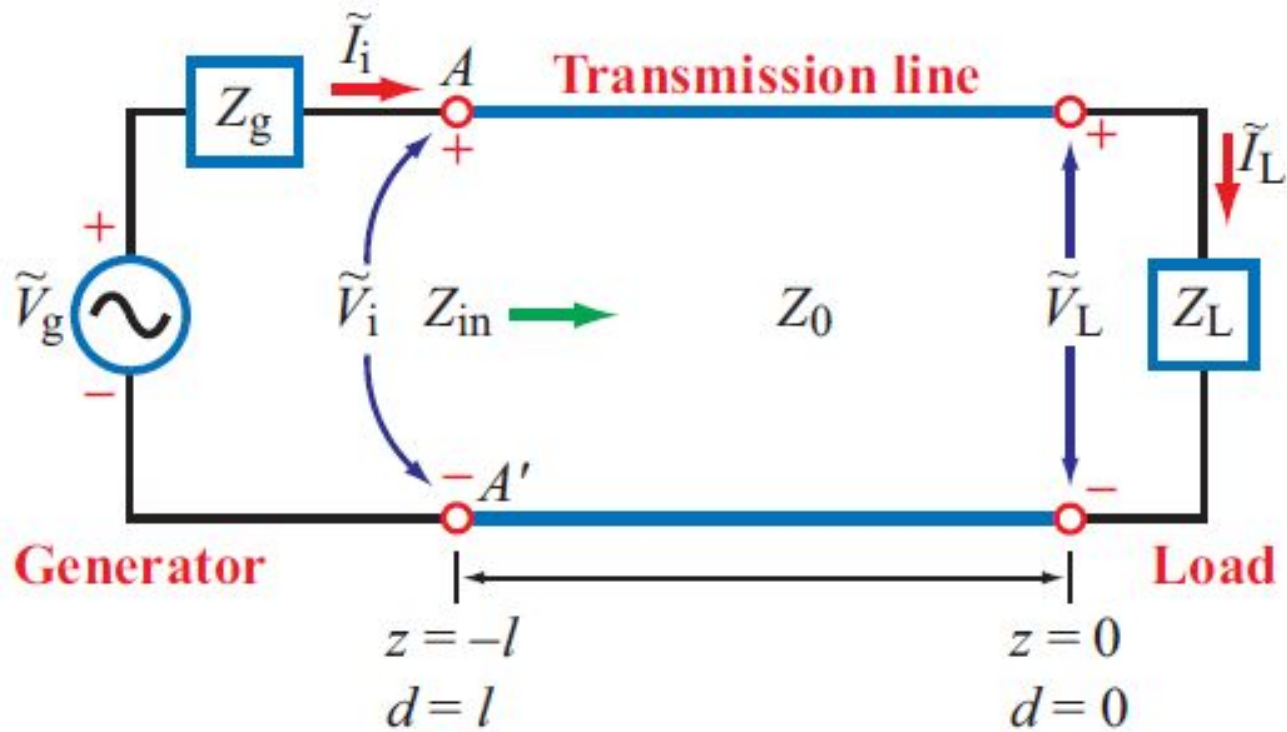

# Example 3

Know:

$$\tilde{V}_i = \left( \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right)$$

$$Z_{in} = Z(l) = Z_0 \left[ \frac{1 + \Gamma_l}{1 - \Gamma_l} \right].$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\lambda = \frac{u_p}{f} = \frac{c}{f} \frac{1}{\sqrt{\epsilon_r}} = \frac{\lambda_0}{\sqrt{\epsilon_r}}$$

$$\beta = \frac{2\pi}{\lambda} \quad u_p = f\lambda \quad \Gamma_l = |\Gamma| e^{j(\theta_r - 2\beta l)}$$

# Example 3

Solution:

$$\lambda = \frac{c}{f} \frac{1}{\sqrt{\epsilon_r}}$$

$$\lambda = \frac{c}{\omega/(2\pi)} \frac{1}{\sqrt{\epsilon_r}}$$

$$\lambda = \frac{3 \times 10^8 \text{ m/sec}}{1 \times 10^9 \text{ rad/sec}/(2\pi)} \frac{1}{\sqrt{3}}$$

$$\lambda = 1.09 \text{ m}$$

# Example 3

Solution:

$$\beta l = \frac{2\pi}{\lambda} l$$

$$\beta l = \frac{2\pi}{1.09 \text{ m}} 0.1 \text{ m}$$

$$\beta l = 0.58 \text{ rad} = 33.23^\circ$$

$$2\beta l = 1.16 \text{ rad} = 66.46^\circ$$

# Example 3

Solution:

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma = \frac{50 + j150 - 50}{50 + j150 + 50}$$

$$\Gamma = \frac{j150}{100 + j150}$$

$$\Gamma = \frac{150e^{j90^\circ}}{\sqrt{100^2 + 150^2}e^{j \tan^{-1}(150/100)}}$$

$$\Gamma = \frac{150e^{j90^\circ}}{180.3e^{j56.3^\circ}}$$

# Example 3

Solution:

$$\Gamma = \frac{150e^{j90^\circ}}{180.3e^{j56.3^\circ}}$$

$$\Gamma = 0.83e^{j(90^\circ - 56.3^\circ)}$$

$$\Gamma = 0.83e^{j33.7^\circ}$$

# Example 3

Solution:

$$Z_{\text{in}} = Z_0 \left( \frac{1 + \Gamma_l}{1 - \Gamma_l} \right)$$

$$\Gamma_l = \Gamma e^{-j2\beta l}$$

$$\Gamma_l = 0.83 e^{j33.7^\circ} e^{-j66.46^\circ}$$

$$\Gamma_l = 0.83 e^{-j32.76^\circ}$$

$$\Gamma_l = 0.83 \cos(-32.76^\circ) + j0.83 \sin(-32.76^\circ)$$

$$\Gamma_l = 0.7 - j0.45$$

# Example 3

Solution:

$$Z_{\text{in}} = (50 \Omega) \left( \frac{1 + (0.7 - j0.45)}{1 - (0.7 - j0.45)} \right)$$

$$Z_{\text{in}} = (50 \Omega) \left( \frac{1.7 - j0.45}{0.3 + j0.45} \right)$$

$$Z_{\text{in}} = (50 \Omega) \left( \frac{\sqrt{1.7^2 + 0.45^2} e^{j \tan^{-1}(-0.45/1.7)}}{\sqrt{0.3^2 + 0.45^2} e^{j \tan^{-1}(0.45/0.3)}} \right)$$

$$Z_{\text{in}} = (50 \Omega) \left( \frac{1.76 e^{-j14.8^\circ}}{0.54 e^{j56.3^\circ}} \right)$$

# Example 3

Solution:

$$Z_{\text{in}} = (50 \Omega) \left( \frac{1.76e^{-j14.8^\circ}}{0.54e^{j56.3^\circ}} \right)$$

$$Z_{\text{in}} = (50 \Omega) 3.26e^{j(-14.8^\circ - 56.3^\circ)}$$

$$Z_{\text{in}} = (163 \Omega)e^{-j71.1^\circ}$$

$$Z_{\text{in}} = (163 \Omega) \cos(-71.1^\circ) + j(163 \Omega) \sin(-71.1^\circ)$$

$$Z_{\text{in}} = 52.8 - j154 \Omega$$

# Example 3

Solution:

$$v_g(t) = 10 \text{ V} \cos(\omega t)$$

$$\tilde{V}_g = 10 \text{ V}$$

# Example 3

**Solution:**

$$\tilde{V}_i = \frac{\tilde{V}_g Z_{\text{in}}}{Z_g + Z_{\text{in}}}$$

$$\tilde{V}_i = \frac{(10 \text{ V})(163 \Omega e^{-j71.1^\circ})}{50. + 52.8 - j154 \Omega}$$

$$Z_g + Z_{\text{in}} = 50. + 52.8 - j154 \Omega$$

$$Z_g + Z_{\text{in}} = 102.8 - j154 \Omega$$

$$Z_g + Z_{\text{in}} = \sqrt{102.8^2 + 154^2} e^{j \tan^{-1}(-154/102.8)} \Omega$$

$$Z_g + Z_{\text{in}} = 185.2 e^{-j56.3^\circ} \Omega$$

# Example 3

Solution:

$$\tilde{V}_i = \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}}$$

$$\tilde{V}_i = \frac{(10 \text{ V})(163 \Omega e^{-j71.1^\circ})}{185.2 e^{-j56.3^\circ} \Omega}$$

$$\tilde{V}_i = 8.8 e^{j(-71.1^\circ + 56.3^\circ)} \text{ V}$$

$$\tilde{V}_i = 8.8 e^{-j14.8^\circ} \text{ V}$$

# Example 4

**Given:** Lossless transmission-line

$$V_g = 5V \cos(\omega t - 50^\circ)$$

$$\omega = 3 \times 10^7 \text{ rad/sec}$$

$$Z_g = 150 \Omega$$

$$Z_0 = 75 \Omega$$


$$\epsilon_r = 4$$

$$l = 12 \text{ m}$$

$$Z_L = 50 + j 100 \Omega$$

**Find:**  $\Gamma$ ,  $Z_{in}$ ,  $\tilde{V}_i$

# Example 4

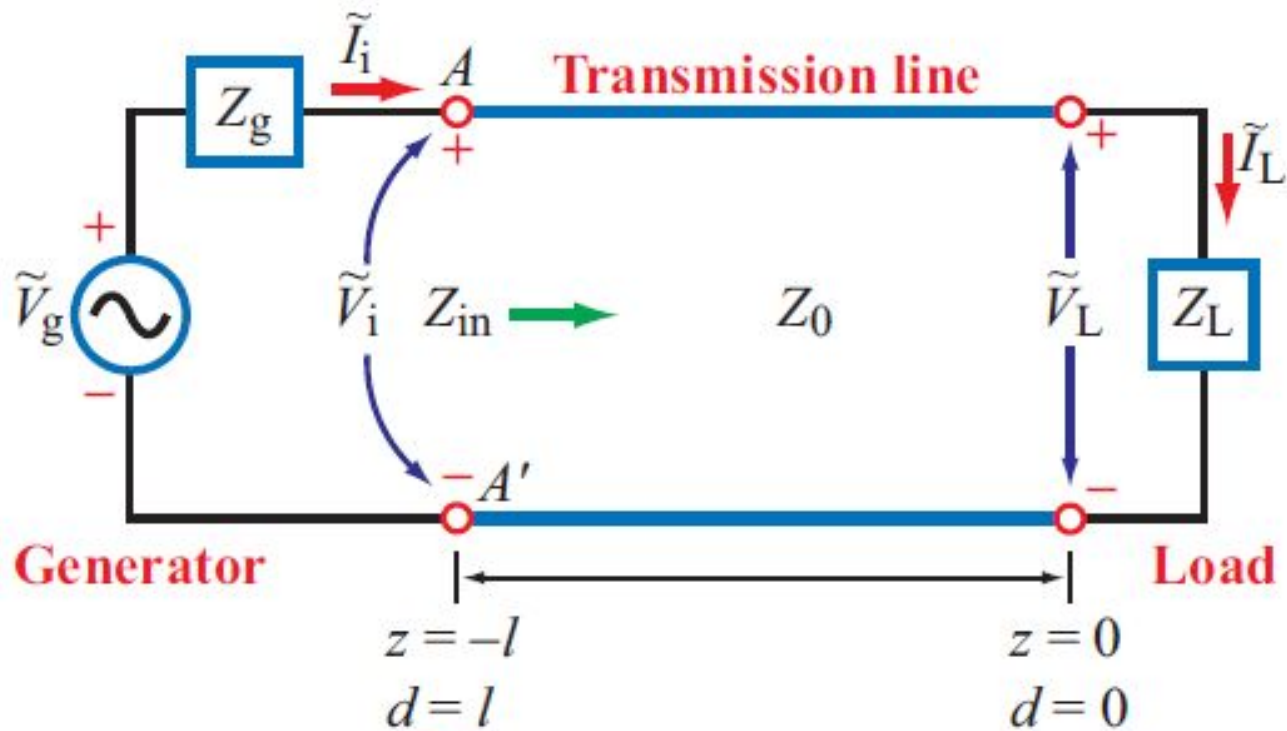

# Example 4

Know:

$$\tilde{V}_i = \left( \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right)$$

$$Z_{in} = Z(l) = Z_0 \left[ \frac{1 + \Gamma_l}{1 - \Gamma_l} \right].$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\lambda = \frac{u_p}{f} = \frac{c}{f} \frac{1}{\sqrt{\epsilon_r}} = \frac{\lambda_0}{\sqrt{\epsilon_r}}$$

$$\beta = \frac{2\pi}{\lambda} \quad u_p = f\lambda \quad \Gamma_l = |\Gamma| e^{j(\theta_r - 2\beta l)}$$

# Example 4

Solution:

$$\lambda = \frac{c}{f} \frac{1}{\sqrt{\epsilon_r}}$$

$$\lambda = \frac{c}{\omega/(2\pi)} \frac{1}{\sqrt{\epsilon_r}}$$

$$\lambda = \frac{3 \times 10^8 \text{ m/sec}}{3 \times 10^7 \text{ rad/sec}/(2\pi)} \frac{1}{\sqrt{4}}$$

$$\lambda = 31.4 \text{ m}$$

# Example 4

Solution:

$$\beta l = \frac{2\pi}{\lambda} l$$

$$\beta l = \frac{2\pi}{31.4 \text{ m}} 12 \text{ m}$$

$$\beta l = 2.4 \text{ rad} = 137.6^\circ$$

$$2\beta l = 4.8 \text{ rad} = 275.2^\circ$$

# Example 4

Solution:

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma = \frac{50 + j100 - 75}{50 + j100 + 75}$$

$$\Gamma = \frac{-25 + j100}{125 + j100}$$

$$\Gamma = \frac{\sqrt{25^2 + 100^2} e^{j(180^\circ + \tan^{-1}(-100/25))}}{\sqrt{125^2 + 100^2} e^{j \tan^{-1}(100/125)}}$$

$$\Gamma = \frac{103.1 e^{j104^\circ}}{160.1 e^{j38.7^\circ}}$$

# Example 4

Solution:

$$\Gamma = \frac{103.1e^{j104^\circ}}{160.1e^{j38.7^\circ}}$$

$$\Gamma = 0.64e^{j(104^\circ - 38.7^\circ)}$$

$$\Gamma = 0.64e^{j65.3^\circ}$$

# Example 4

Solution:

$$Z_{\text{in}} = Z_0 \left( \frac{1 + \Gamma_l}{1 - \Gamma_l} \right)$$

$$\Gamma_l = \Gamma e^{-j2\beta l}$$

$$\Gamma_l = 0.64e^{j65.3^\circ} e^{-j275.2^\circ}$$

$$\Gamma_l = 0.64e^{-j210^\circ}$$

$$\Gamma_l = 0.64 \cos(-210^\circ) + j0.64 \sin(-210^\circ)$$

$$\Gamma_l = -0.55 + j0.32$$

# Example 4

**Solution:**

$$Z_{\text{in}} = (75 \Omega) \left( \frac{1 + (-0.55 + j0.32)}{1 - (-0.55 + j0.32)} \right)$$

$$Z_{\text{in}} = (75 \Omega) \left( \frac{0.45 + j0.32}{1.55 - j0.32} \right)$$

$$Z_{\text{in}} = (75 \Omega) \left( \frac{\sqrt{0.45^2 + 0.32^2} e^{j \tan^{-1}(0.32/0.45)}}{\sqrt{1.55^2 + 0.32^2} e^{j \tan^{-1}(-0.32/1.55)}} \right)$$

$$Z_{\text{in}} = (75 \Omega) \left( \frac{0.55 e^{j35.4^\circ}}{1.58 e^{-j11.7^\circ}} \right)$$

$$Z_{\text{in}} = (75 \Omega) 0.348 e^{j(35.4^\circ + 11.7^\circ)}$$

# Example 4

**Solution:**

$$Z_{\text{in}} = (75 \Omega) 0.348 e^{j(35.4^\circ + 11.7^\circ)}$$

$$Z_{\text{in}} = (26.1 \Omega) e^{j47.1^\circ}$$

$$Z_{\text{in}} = (26.1 \Omega) \cos(47.1^\circ) + j(26.1 \Omega) \sin(47.1^\circ)$$

$$Z_{\text{in}} = 17.8 + j19.1 \Omega$$

# Example 4

Solution:

$$v_g(t) = 5 \text{ V} \cos(\omega t - 50^\circ)$$

$$\tilde{V}_g = 5e^{-j50^\circ} \text{ V}$$

# Example 4

Solution:

$$\tilde{V}_i = \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}}$$

$$\tilde{V}_i = \frac{(5e^{-j50^\circ} \text{ V})(26.1 \Omega e^{j47.1^\circ})}{150. + 17.8 + j19.1 \Omega}$$

# Example 4

Solution:

$$Z_g + Z_{in} = 150. + 17.8 + j19.1 \Omega$$

$$Z_g + Z_{in} = 167.8 + j19.1 \Omega$$

$$Z_g + Z_{in} = \sqrt{167.8^2 + 19.1^2} e^{j \tan^{-1}(19.1/167.8)} \Omega$$

$$Z_g + Z_{in} = 169 e^{j6.5^\circ} \Omega$$

# Example 4

Solution:

$$\tilde{V}_i = \frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}}$$

$$\tilde{V}_i = \frac{(5e^{-j50^\circ} \text{ V})(26.1 \Omega e^{j47.1^\circ})}{169e^{j6.5^\circ} \Omega}$$

$$\tilde{V}_i = 0.77e^{j(-50^\circ + 47.1^\circ - 6.5^\circ)} \text{ V}$$

$$\tilde{V}_i = 0.77e^{-j9.4^\circ} \text{ V}$$

# Homework

92

**Homework 6 is due tomorrow at midnight.**

**submit to gradescope via the canvas site.**

# Next Time



## **Sections 2-8, 2-9:**

Lossless Line: Special Cases

Lossless Line: Power Flow