

EECS 230
ENGINEERING ELECTROMAGNETICS
Leland Pierce

Transmission Lines 5

Chapter 2 Overview

What is a transmission line?

Why study transmission lines?

model

diffeq

solve diffeq

wave propagation

lossless transmission line

microstrip lines

reflections

standing waves

impedance




short, open

matching


power flow

smith chart


transients

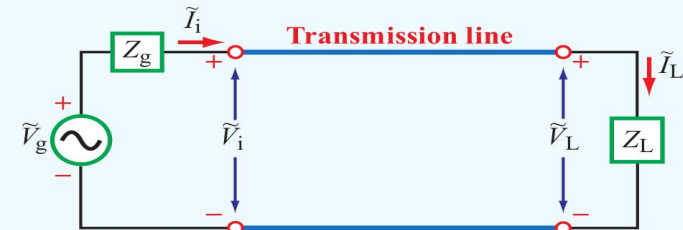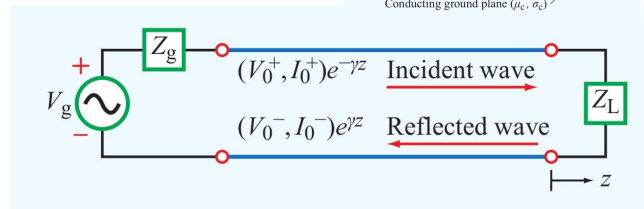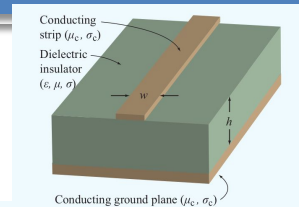



Typical High-Frequency Circuit

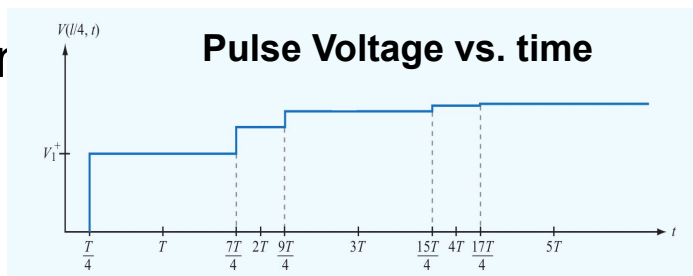

Pulse Voltage vs. time

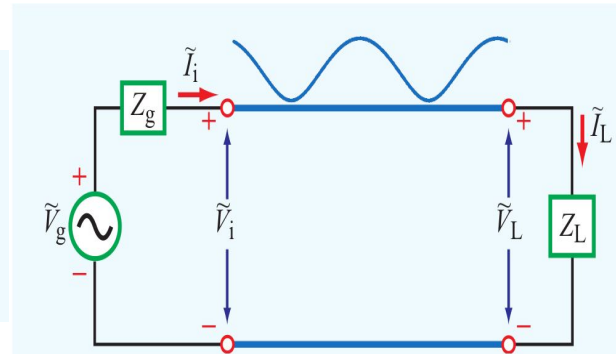

Waves on line: old methods don't work

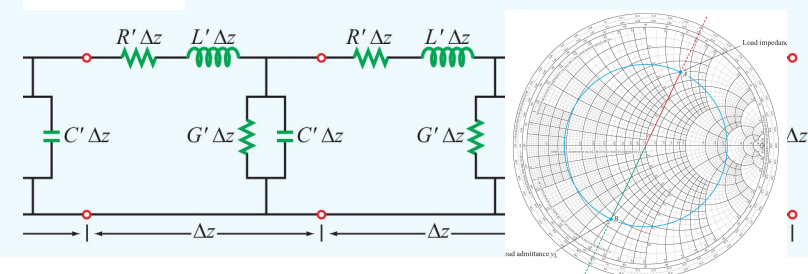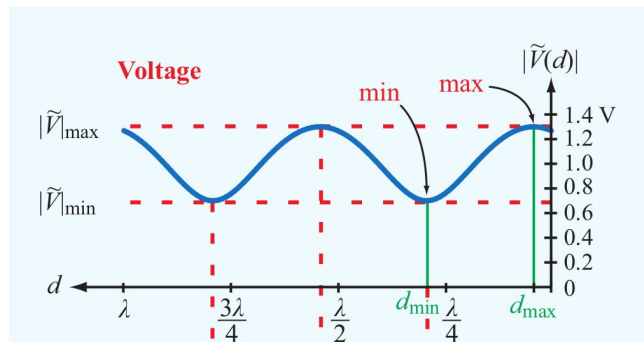

Today's Lecture Coverage

Review Sections 2-1 through 2-5 of the book:

2-1: What is a transmission line?

Why study transmission lines?

2-2: Lumped-Element Model

2-3: Governing Differential Eqns

2-4: Solve the Differential Equations

Properties of the solution: wave propagation

2-5: Lossless Microstrip Line

2-6: Lossless Transmission Lines

2-7: Lossless Transmission Lines: Wave Impedance

Sections 2-8, 2-9 of the book:

2-8: Lossless Transmission Lines: Special Cases

2-9: Lossless Transmission Lines: Power Flow


Chapter 2 Review

- A transmission line connects a generator to a load.



Chapter 2 Review

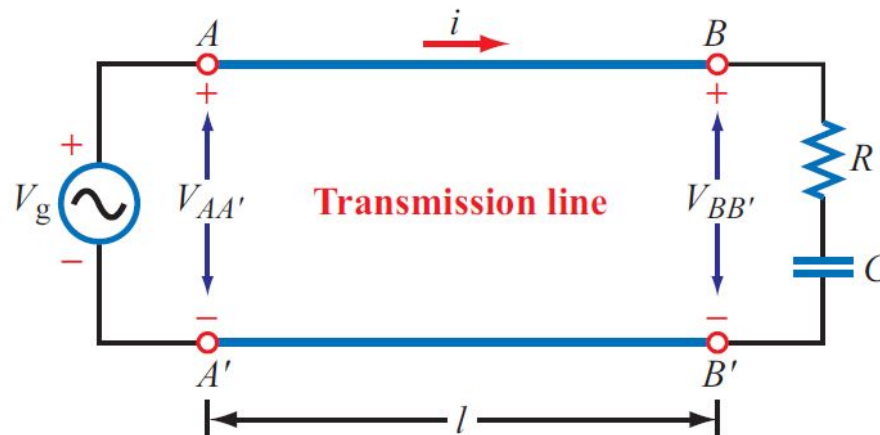Phase Delay due to length of transmission line:




$$\phi_0 = \frac{\omega l}{c} = \frac{2\pi f l}{c} = 2\pi \frac{l}{\lambda} \text{ radians.}$$

$l/\lambda \lesssim 0.01$: Can ignore transmission-line effects


$l/\lambda \gtrsim 0.01$: Must deal with phase shift, and other effects...

Chapter 2 Review

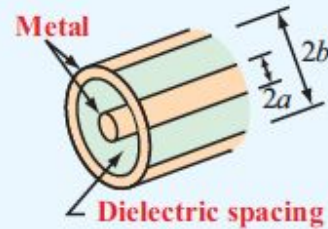
Different geometries for transmission lines




(a) Coaxial line

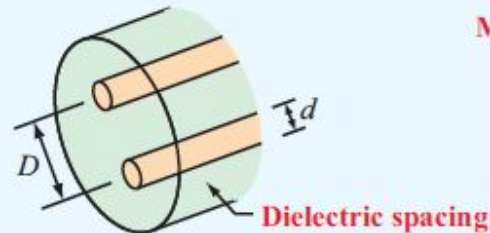


(b) Two-wire line

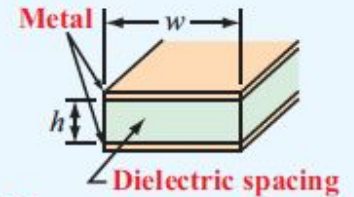


(c) Parallel-plate line

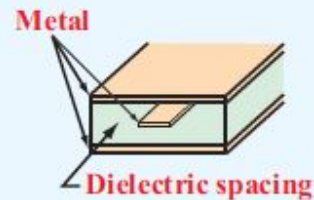

(d) Strip line

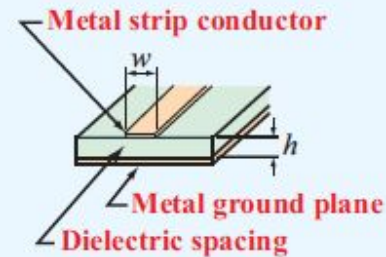


(e) Microstrip line

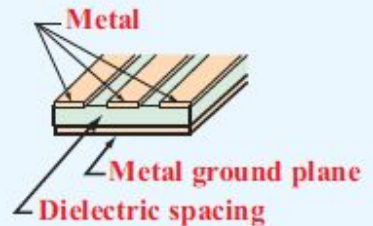


(f) Coplanar waveguide

TEM Transmission Lines

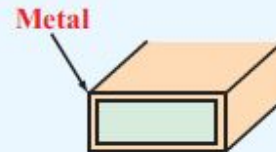

(g) Rectangular waveguide

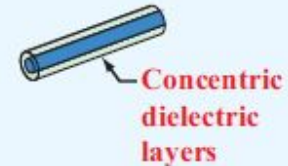


(h) Optical fiber

Higher-Order Transmission Lines

Chapter 2 Review

Lumped-Element Model:

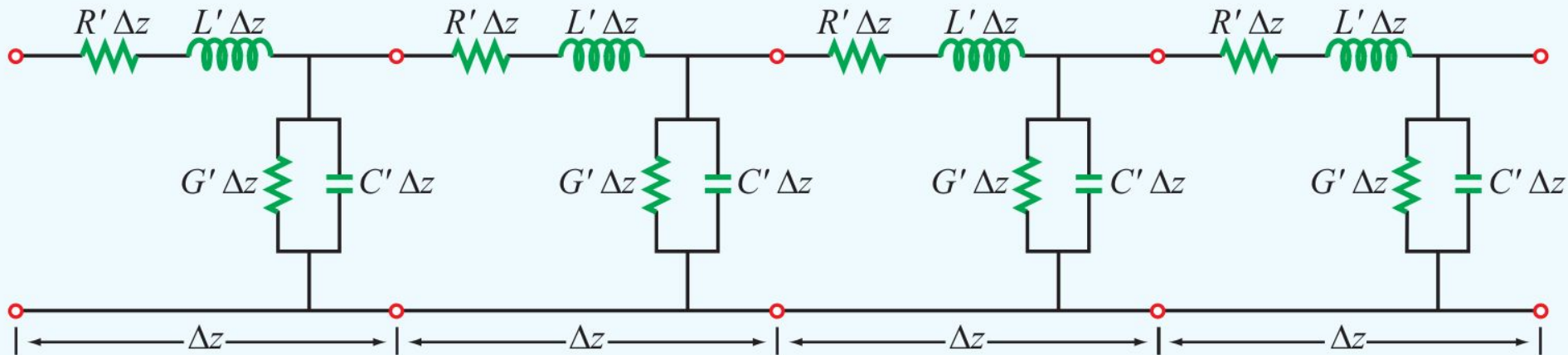

All parameters are "per unit length":

R': Combined Resistance of BOTH conductors: \square/m

L': Combined Inductance of BOTH conductors, H/m

G': Conductance of insulation

between inner and outer conductor, S/m

C': Capacitance

between inner and outer conductors, F/m

Chapter 2 Review

Lumped-Element Values: geometry/materials/freq

Table 2-1 Transmission-line parameters R' , L' , G' , and C' for three types of lines.

Parameter	Coaxial	Two-Wire	Parallel-Plate	Unit
R'	$\frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$	$\frac{2R_s}{\pi d}$	$\frac{2R_s}{w}$	Ω/m
L'	$\frac{\mu}{2\pi} \ln(b/a)$	$\frac{\mu}{\pi} \ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]$	$\frac{\mu h}{w}$	H/m
G'	$\frac{2\pi\sigma}{\ln(b/a)}$	$\frac{\pi\sigma}{\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\sigma w}{h}$	S/m
C'	$\frac{2\pi\epsilon}{\ln(b/a)}$	$\frac{\pi\epsilon}{\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\epsilon w}{h}$	F/m

$$R_s = \sqrt{\pi f \mu_c / \sigma_c}$$

Chapter 2 Review

Transmission-line governing Differential Equations

$$-\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L') \tilde{I}(z),$$
$$-\frac{d\tilde{I}(z)}{dz} = (G' + j\omega C') \tilde{V}(z).$$

(telegrapher's equations in phasor form)

Chapter 2 Review

Transmission-line governing Differential Equation for V :

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0,$$

(wave equation for $\tilde{V}(z)$)

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}.$$

(propagation constant)

Chapter 2 Review

Complex propagation constant:

$$\gamma = \alpha + j\beta$$

Where:

γ : Units of 1/m

α : Attenuation constant, units of Np/m (>0 in this class)

β : Phase constant, units of rad/m

Np and radians are both "dimensionless", and are the conventional "units" for these parameters.

Chapter 2 Review

Form of the solution: traveling waves, going in both directions:

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z} \quad (\text{A}).$$

$$Z_0 = \frac{R' + j\omega L'}{\gamma} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \quad (\Omega),$$

Chapter 2 Review

Solution in time-domain

$$v(z, t) = |V_0^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi^+) \\ + |V_0^-| e^{+\alpha z} \cos(\omega t + \beta z + \phi^-)$$

Remaining unknowns are determined via specification of source and load.

Chapter 2 Review

- The wave equation for a general Transmission Line.

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0, \quad (2.21)$$

- General solution of the wave equation
 - *It involves both incident and reflected waves*

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$

Chapter 2 Review

- Useful Relations for lossless Transmission Lines:

$$\alpha = 0 \quad (\text{lossless line}),$$
$$\beta = \omega\sqrt{L'C'} \quad (\text{lossless line}). \quad (2.45)$$

$$\beta = \omega\sqrt{\mu\varepsilon} \quad (\text{rad/m}), \quad (2.49)$$

$$u_p = \frac{1}{\sqrt{\mu_0\varepsilon_0}} \frac{1}{\sqrt{\varepsilon_r}} = \frac{c}{\sqrt{\varepsilon_r}}$$

$$\lambda = \frac{u_p}{f} = \frac{c}{f} \frac{1}{\sqrt{\varepsilon_r}} = \frac{\lambda_0}{\sqrt{\varepsilon_r}}$$

$$Z_0 = \sqrt{\frac{L'}{C'}} \quad (\text{lossless line}), \quad (2.46) \quad (\text{REAL})$$

Chapter 2 Review

- Voltage reflection coefficient due to load:







$$\begin{aligned}\Gamma &= \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \\ &= \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} \\ &= \frac{z_L - 1}{z_L + 1}\end{aligned}$$

- Load impedance in terms of Γ :

$$Z_L = \frac{1 + \Gamma}{1 - \Gamma} Z_0$$

Chapter 2 Review

Reflection Coefficient $\Gamma = |\Gamma|e^{j\theta_r}$

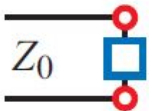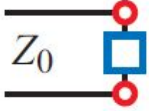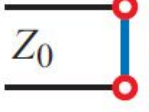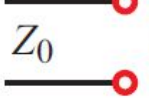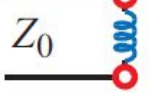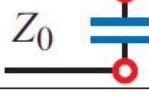Load	$ \Gamma $	θ_r
 $Z_L = (r + jx)Z_0$	$\left[\frac{(r - 1)^2 + x^2}{(r + 1)^2 + x^2} \right]^{1/2}$	$\tan^{-1} \left(\frac{x}{r - 1} \right) - \tan^{-1} \left(\frac{x}{r + 1} \right)$
 Z_0	0 (no reflection)	irrelevant
 (short)	1	$\pm 180^\circ$ (phase opposition)
 (open)	1	0 (in-phase)
 $jX = j\omega L$	1	$\pm 180^\circ - 2 \tan^{-1} x$
 $jX = \frac{-j}{\omega C}$	1	$\pm 180^\circ + 2 \tan^{-1} x$

$$z_L = Z_L/Z_0 = (R + jX)/Z_0 = r + jx$$

Chapter 2 Review

- Concept of standing wave



$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z}),$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z}).$$

- Voltage magnitudes at any point on line:

$$|\tilde{V}(d)| = |V_0^+| \left[1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}. \quad (2.66)$$

Chapter 2 Review

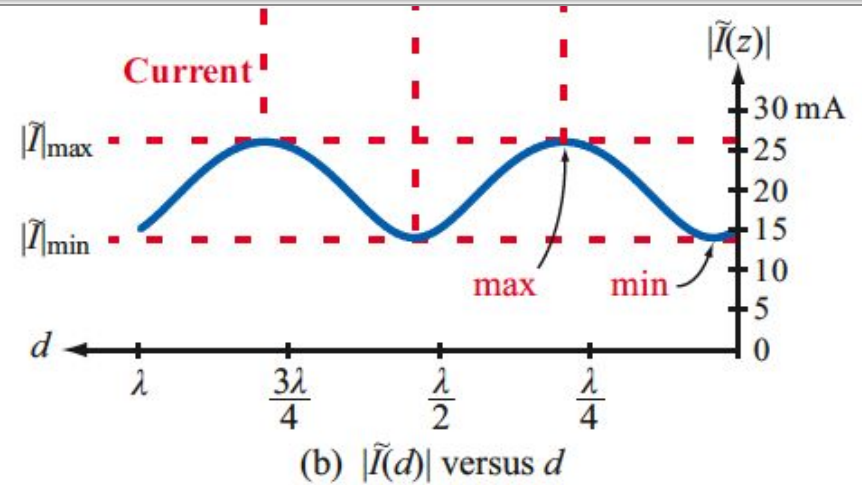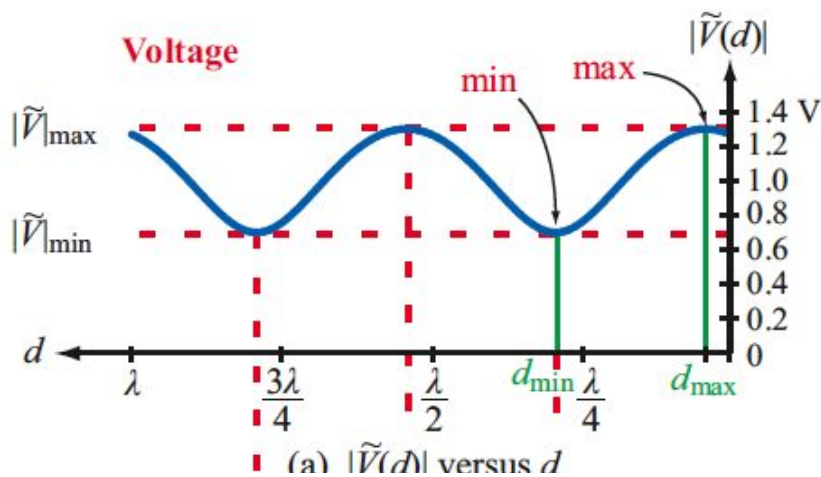



- Location of minima / maxima

$$d_{\max} = \frac{\theta_r + 2n\pi}{2\beta} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2},$$

$$\begin{cases} n = 1, 2, \dots & \text{if } \theta_r < 0, \\ n = 0, 1, 2, \dots & \text{if } \theta_r \geq 0, \end{cases} \quad (2.70)$$

Value of V_{\max} : $|\tilde{V}(d)| = |\tilde{V}|_{\max} = |V_0^+| [1 + |\Gamma|],$

Chapter 2 Review

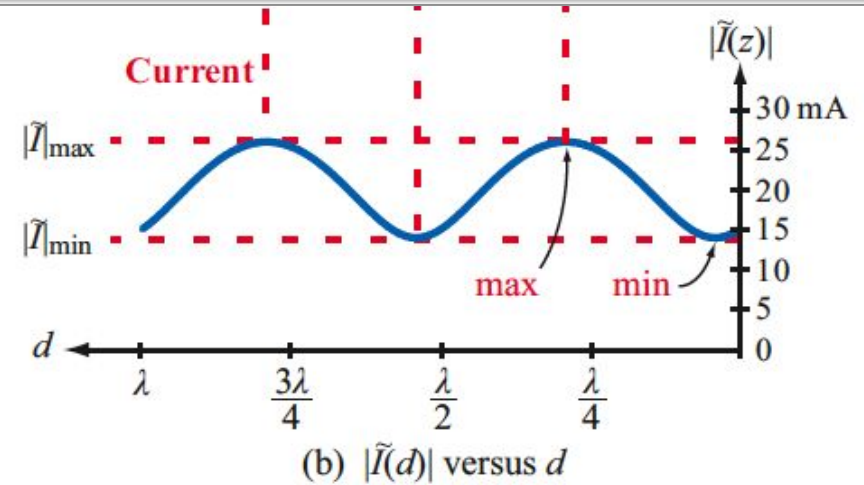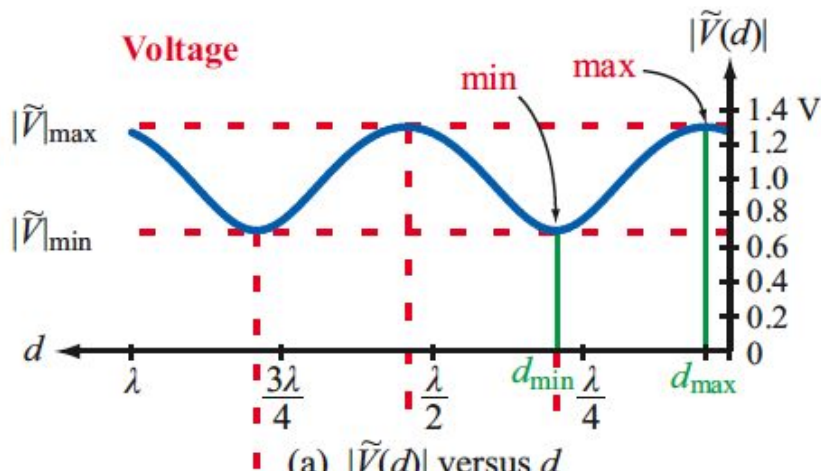


- Spatial period of standing wave: $\frac{\lambda}{2}$
- Standing wave ratio S:

$$S = \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$


Chapter 2 Review

Wave Impedance:
At a distance d from the load:
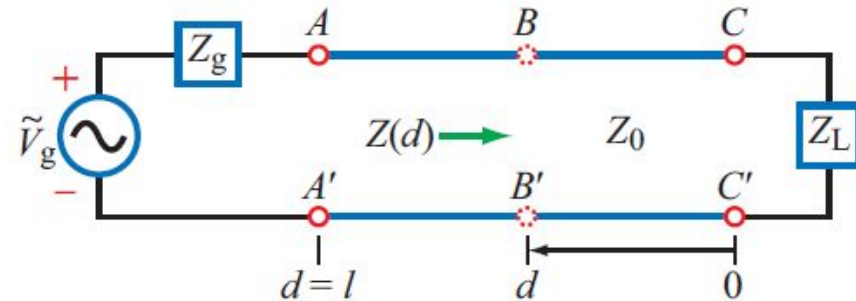
$$\begin{aligned}
 Z(d) &= \frac{\tilde{V}(d)}{\tilde{I}(d)} \\
 &= \frac{V_0^+ [e^{j\beta d} + \Gamma e^{-j\beta d}]}{V_0^+ [e^{j\beta d} - \Gamma e^{-j\beta d}]} Z_0 \\
 &= Z_0 \left[\frac{1 + \Gamma e^{-j2\beta d}}{1 - \Gamma e^{-j2\beta d}} \right] \\
 &= Z_0 \left[\frac{1 + \Gamma_d}{1 - \Gamma_d} \right] \quad (\Omega),
 \end{aligned}$$



(a) Actual circuit

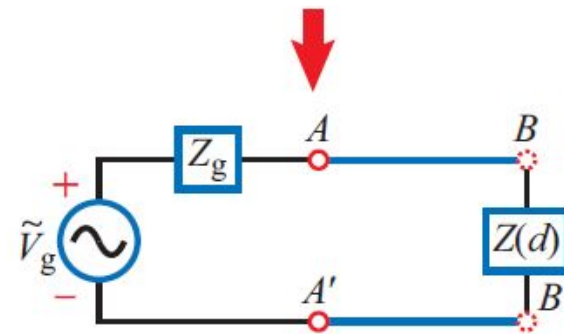

(b) Equivalent circuit


Chapter 2 Review

Define the phase-shifted voltage reflection coefficient:


$$\begin{aligned}\Gamma_d &= \Gamma e^{-j2\beta d} = |\Gamma| e^{j\theta_r} e^{-j2\beta d} \\ &= |\Gamma| e^{j(\theta_r - 2\beta d)}\end{aligned}$$

$Z(d)$ is different than Z_0 :
Ratio of **Total** Voltage and
Current

Recall: $Z_0 = \frac{V_0^+}{I_0^+}$

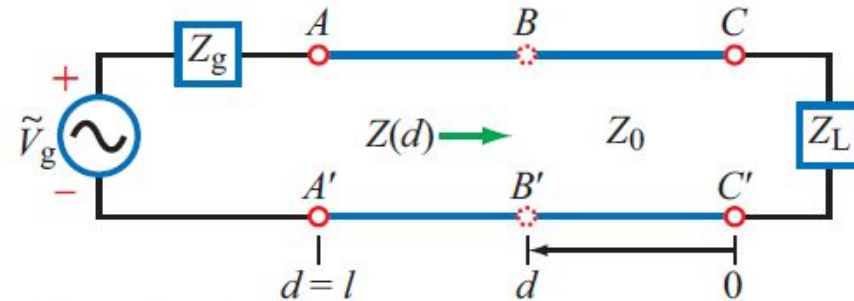


(a) Actual circuit

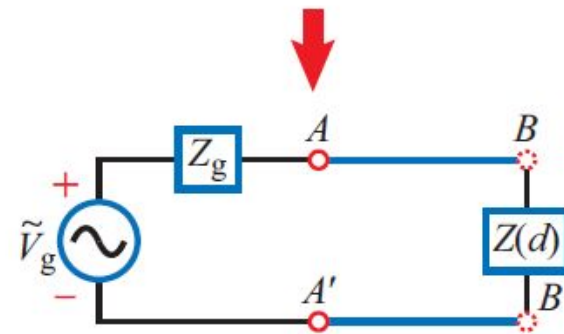


(b) Equivalent circuit

Chapter 2 Review

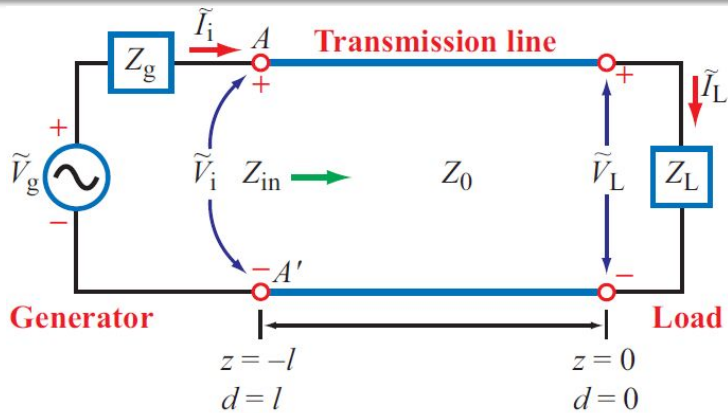

Input impedance:
impedance of the transmission
line at $d=l$:
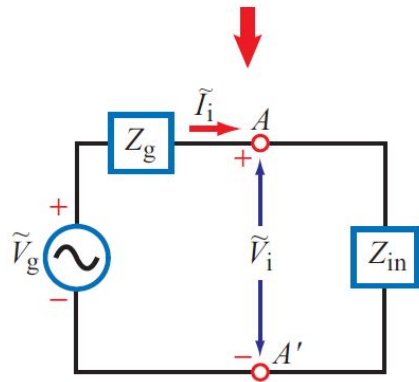
$$Z_{in} = Z(d=l) = \frac{\tilde{V}(d=l)}{\tilde{I}(d=l)}$$




Note that Z_{in} is different from the
Characteristic Impedance, and is different
from the Load Impedance:

$$Z_{in} \neq Z_0$$

$$Z_{in} \neq Z_L$$

Chapter 2 Review

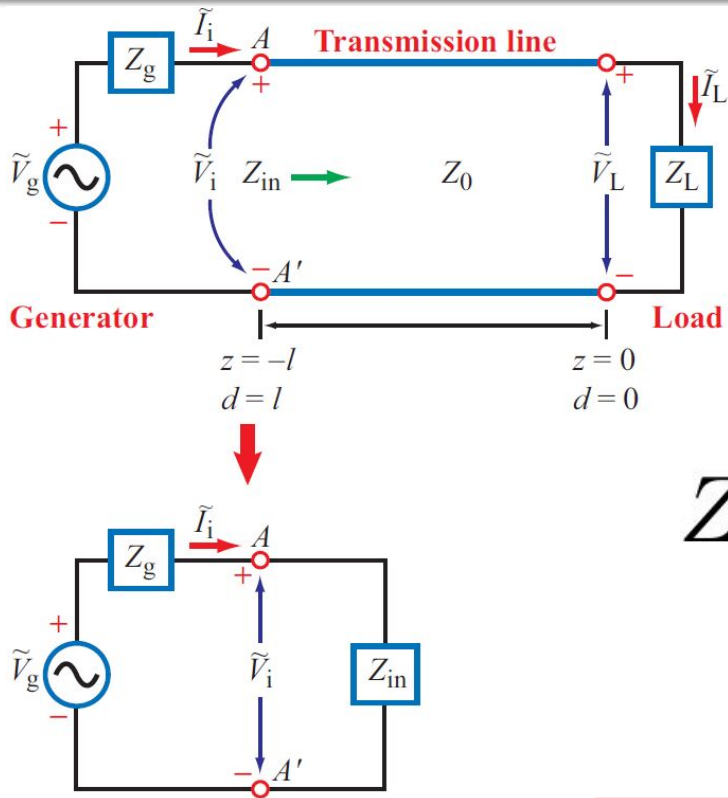


Input impedance:
impedance of the transmission
line at $d=l$:

$$Z_{in} = Z(d = l) = \frac{\tilde{V}(d = l)}{\tilde{I}(d = l)}$$

$$Z_{in} = Z_0 \left[\frac{z_L + j \tan(\beta l)}{1 + j z_L \tan(\beta l)} \right]$$

Chapter 2 Review

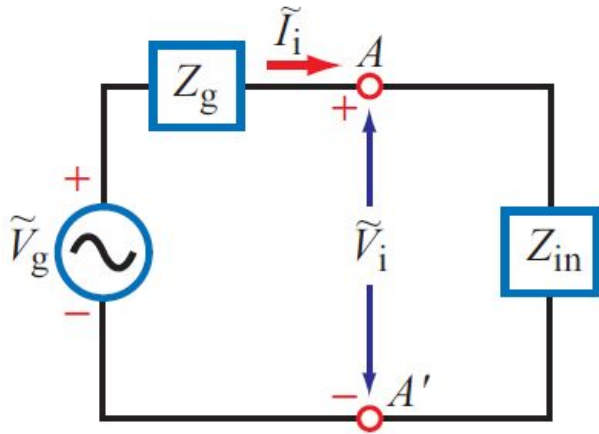


Voltage Amplitude:

$$V_0^+ = \left(\frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left(\frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right).$$

We used the boundary conditions (Z_L , Z_g , V_g , l) to solve for the 2 unknowns.

This completes the solution of the transmission line differential equation.

2-8 Short-Circuited Line

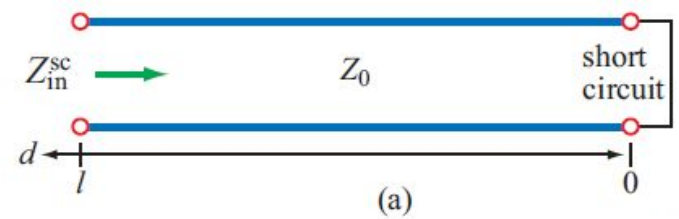

$$\tilde{V}(d) = V_0^+ (e^{j\beta d} + \Gamma e^{-j\beta d})$$

$$\tilde{I}(d) = \frac{V_0^+}{Z_0} (e^{j\beta d} - \Gamma e^{-j\beta d})$$


For the short-circuited line:

$$\Gamma = -1$$


$$\tilde{V}_{sc}(d) = V_0^+ [e^{j\beta d} - e^{-j\beta d}]$$

$$= 2jV_0^+ \sin \beta d,$$
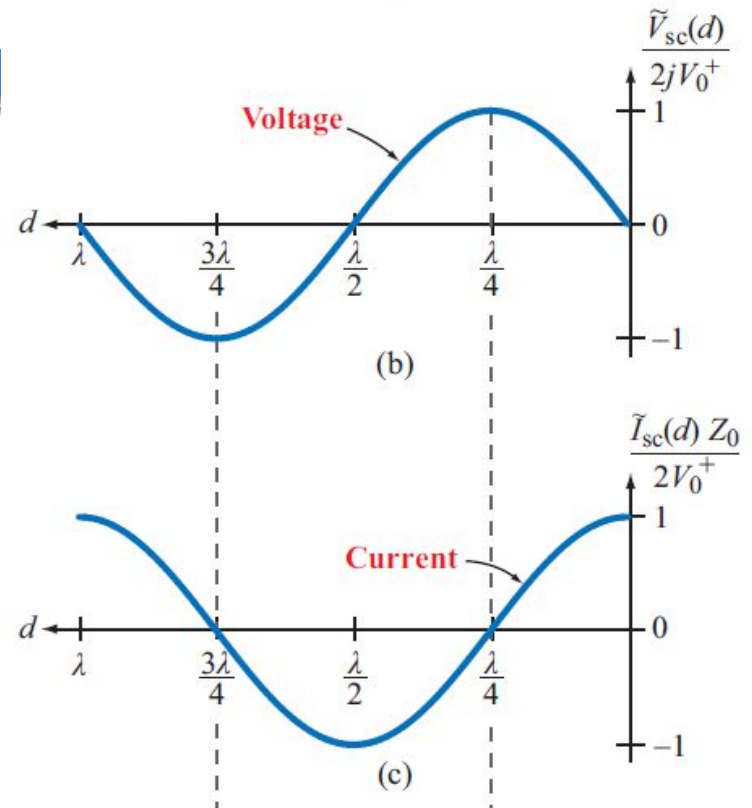
$$\tilde{I}_{sc}(d) = \frac{2V_0^+}{Z_0} \cos \beta d,$$



2-8 Short-Circuited Line

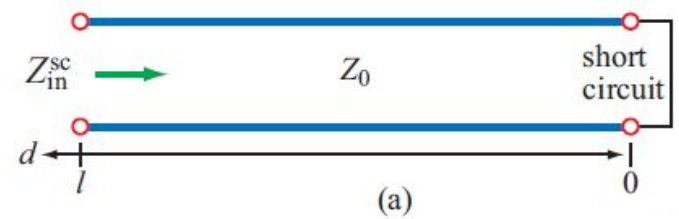

For the short-circuited line:


$$\Gamma = -1$$

$$\tilde{V}_{sc}(d) = 2jV_0^+ \sin \beta d,$$


$$\tilde{I}_{sc}(d) = \frac{2V_0^+}{Z_0} \cos \beta d,$$

$$Z_{sc}(d) = \frac{\tilde{V}_{sc}(d)}{\tilde{I}_{sc}(d)} = jZ_0 \tan \beta d.$$

repeats every $\lambda/2$ (or: π rad)

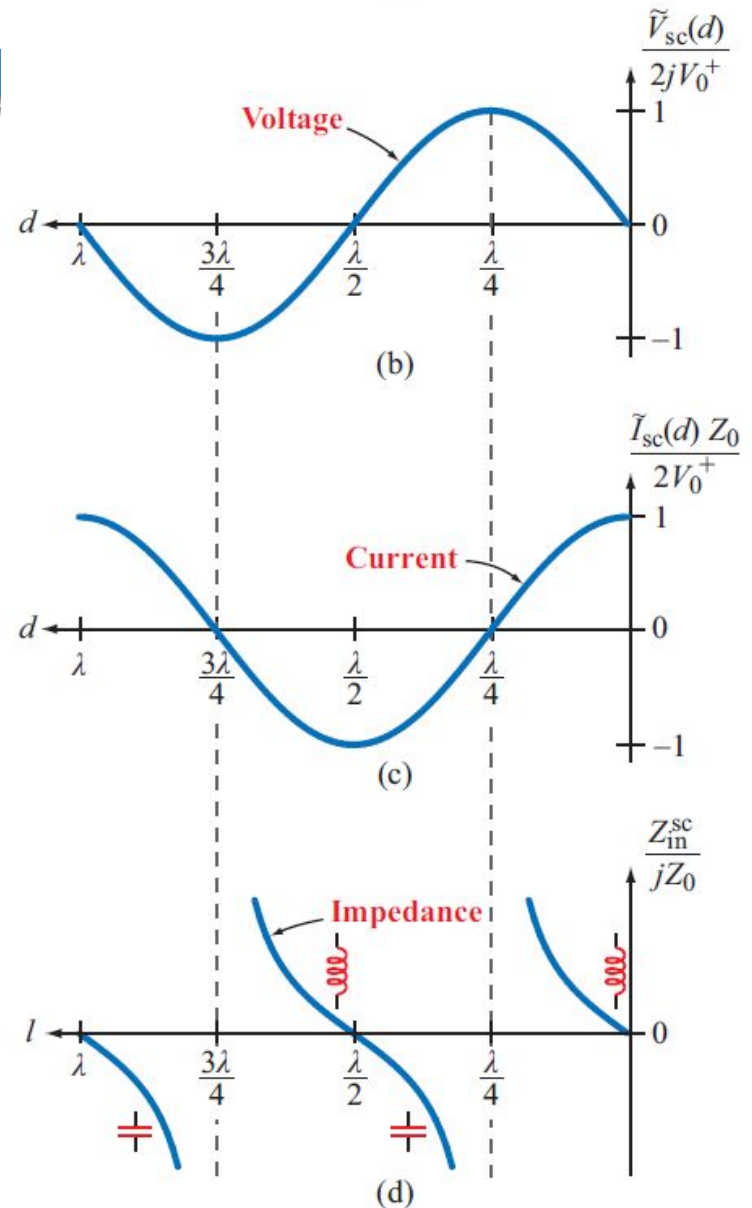

2-8 Short-Circuited Line

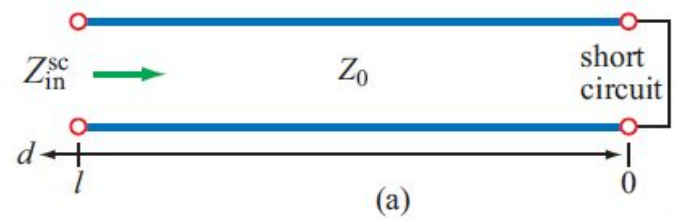

At its input, the line appears like an inductor or a capacitor depending on the sign of


$$\tan \beta d$$

$$j\omega L_{eq} = jZ_0 \tan \beta l, \quad \text{if } \tan \beta l \geq 0$$

$$\text{if } \tan \beta l \geq 0$$

$$\frac{1}{j\omega C_{eq}} = jZ_0 \tan \beta l, \quad \text{if } \tan \beta l \leq 0$$

$$\text{if } \tan \beta l \leq 0$$

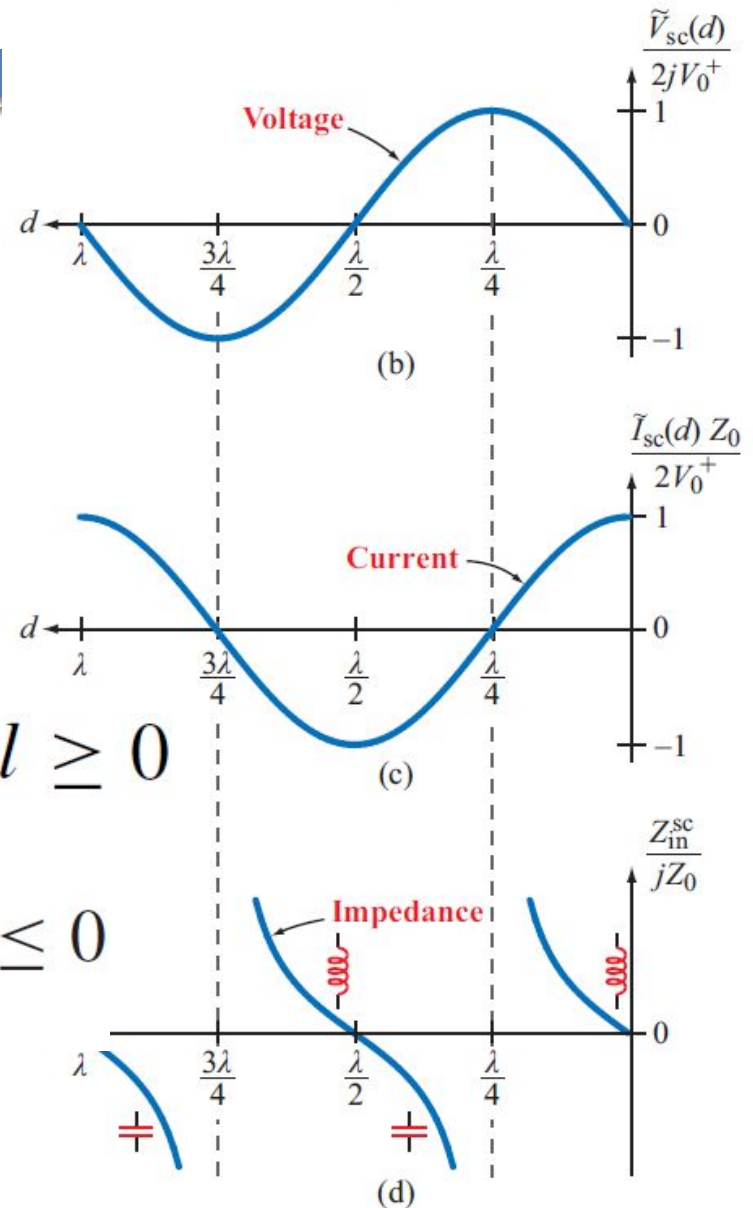


Example 2-8

Given: short-circuited transmission line,

$$Z_0 = 50\Omega, f = 2.25 \text{ GHz}, u_p = 0.75c$$

Find: length, l , so that input impedance is the same as a capacitor with value 4pF.

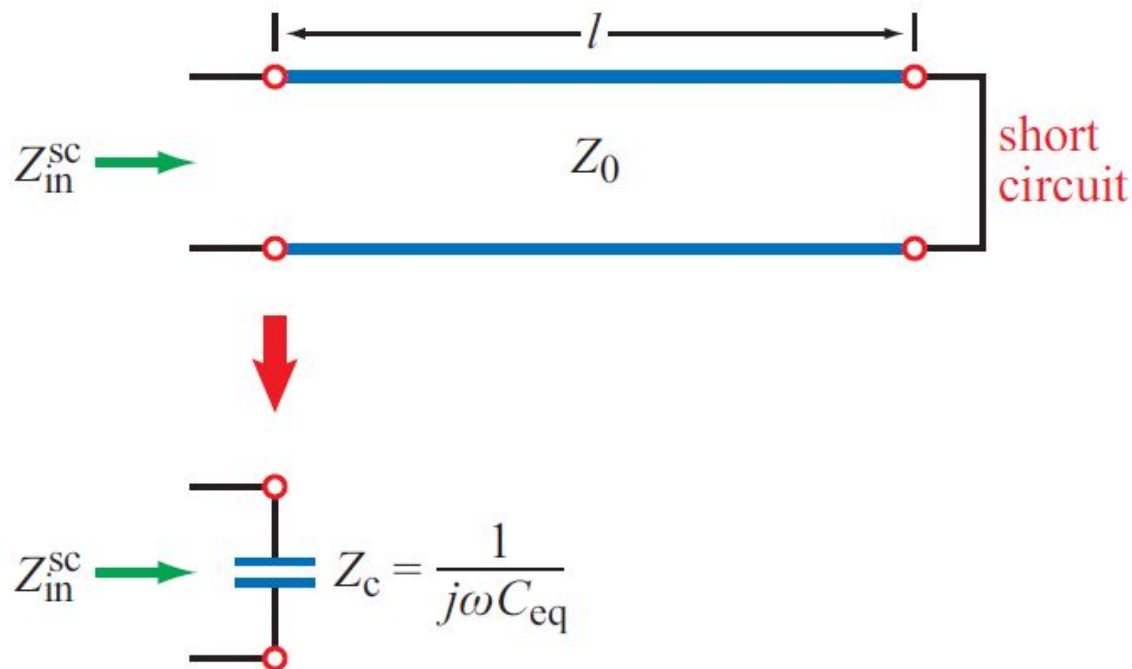

Example 2-8

Solution: Given:

$$u_p = 0.75c = (0.75)3 \times 10^8 \text{ m/sec} = 2.25 \times 10^8 \text{ m/sec}$$

$$Z_0 = 50 \Omega$$

$$f = 2.25 \text{ GHz} = 2.25 \times 10^9 \text{ Hz}$$

$$C_{\text{eq}} = 4 \text{ pF} = 4 \times 10^{-12} \text{ F}$$

Example 2-8

Solution:

we know that: $Z_{\text{in}} = jZ_0 \tan \beta l = \frac{1}{j\omega C_{\text{eq}}}$

so:

$$\tan \beta l = \frac{1}{jZ_0 j\omega C_{\text{eq}}}$$

$$\tan \beta l = -\frac{1}{Z_0 \omega C_{\text{eq}}}$$

$$\beta l = \tan^{-1} \left(-\frac{1}{Z_0 \omega C_{\text{eq}}} \right)$$

$$l = \frac{1}{\beta} \tan^{-1} \left(-\frac{1}{Z_0 \omega C_{\text{eq}}} \right)$$

Example 2-8

Solution:

$$\omega = 2\pi f = (2\pi)2.25 \times 10^9 \text{ Hz} = 14.14 \times 10^9 \text{ rad/sec}$$

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi f}{u_p} = \frac{\omega}{u_p}$$

$$\beta = \frac{14.14 \times 10^9 \text{ rad/sec}}{2.25 \times 10^8 \text{ m/sec}}$$

$$\beta = 62.83 \text{ rad/m}$$

Example 2-8

Solution:

$$l = \frac{1}{\beta} \tan^{-1} \left(-\frac{1}{Z_0 \omega C_{\text{eq}}} \right)$$

$$l = \frac{1}{62.83 \text{ rad/m}} \tan^{-1} \left(-\frac{1}{(50\Omega)(14.14 \times 10^9 \text{ rad/sec})(4 \times 10^{-12} \text{ F})} \right)$$

$$l = 0.015915 \text{ m/rad} \tan^{-1} \left(-\frac{1}{2.828} \right)$$

$$l = 0.015915 \text{ m/rad} \tan^{-1}(-0.3536)$$

$$l = 0.015915 \text{ m/rad}(-0.34 \text{ rad})$$

But the length can't be negative !

Example 2-8

Solution:

$$l = 0.015915 \text{ m/rad}(-0.34 \text{ rad} + \pi)$$

$$l = 0.015915 \text{ m/rad}(2.8 \text{ rad})$$

$$l = 0.0446 \text{ m}$$

and since it repeats every $\lambda/2$:

$$l = 0.0446 + n\lambda/2 \text{ m}$$

Example 2-8

Solution:

with:


$$\lambda = \frac{u_p}{f} = \frac{2.25 \times 10^8 \text{ m/sec}}{2.25 \times 10^9 \text{ Hz}}$$

$$\lambda = 0.1 \text{ m}$$

so:

$$l = 0.0446 + n(0.05) \text{ m}$$

2-8 Open-Circuited Line

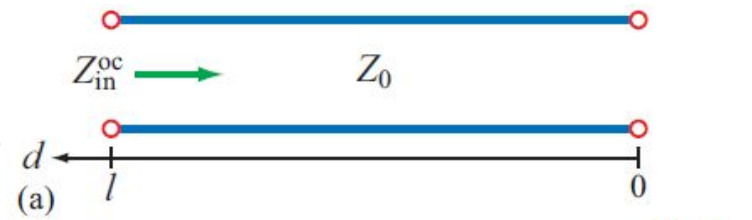


$$\Gamma = 1$$

$$\tilde{V}_{oc}(d) = V_0^+ [e^{j\beta d} + e^{-j\beta d}] = 2V_0^+ \cos \beta d,$$

$$\tilde{I}_{oc}(d) = \frac{V_0^+}{Z_0} [e^{j\beta d} - e^{-j\beta d}] = \frac{2jV_0^+}{Z_0} \sin \beta d,$$

$$Z_{in}^{oc} = \frac{\tilde{V}_{oc}(l)}{\tilde{I}_{oc}(l)} = -jZ_0 \cot \beta l. \quad (2.93)$$

repeats every $\lambda/2$ (or: π rad)

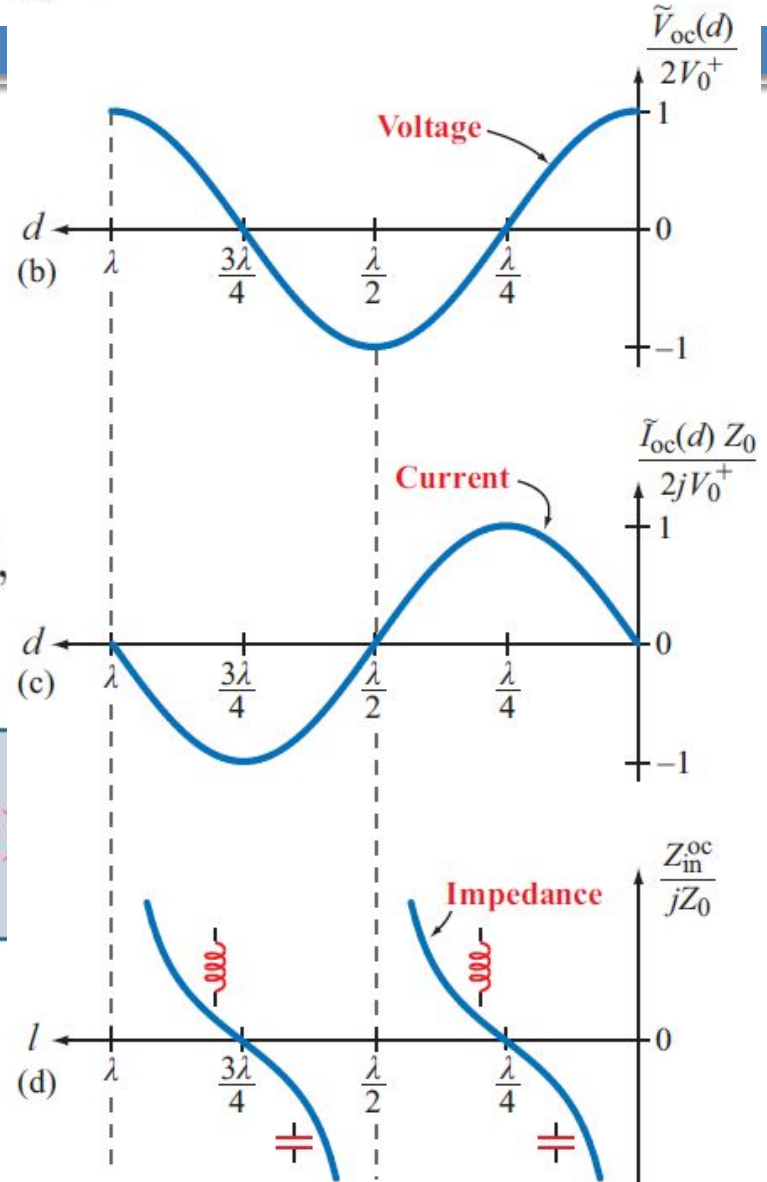


Example 2-8a

Given: open-circuited transmission line,

$$Z_0 = 50\Omega, f = 2.25 \text{ GHz}, u_p = 0.75c$$

Find: length, l , so that input impedance is the same as a capacitor with value 4pF.

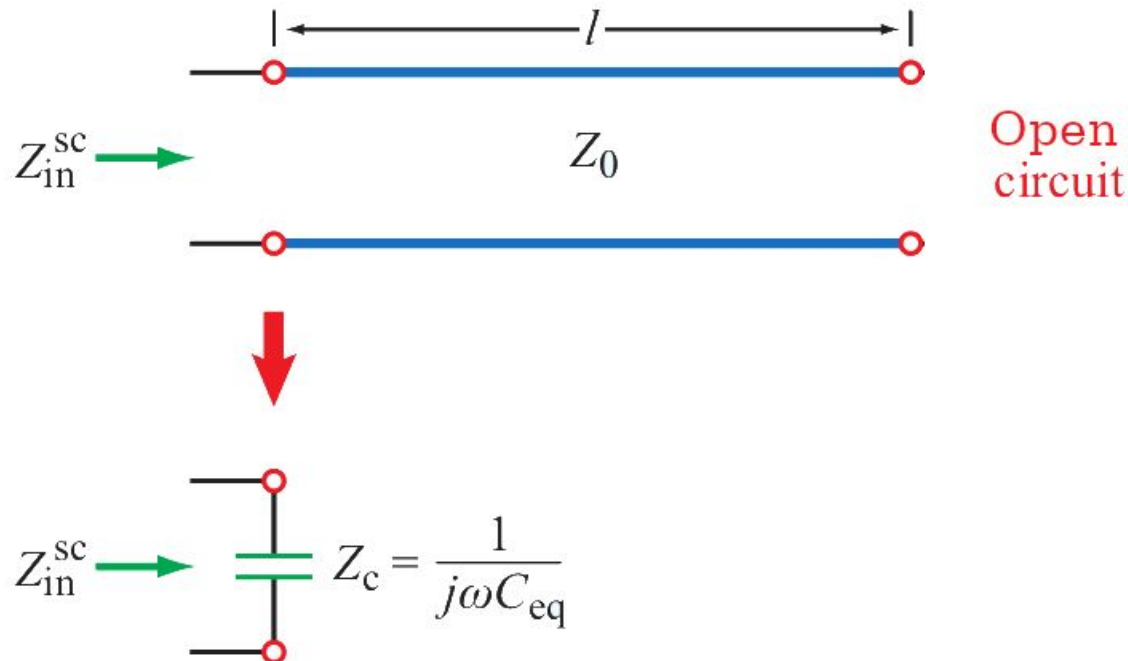

Example 2-8a

Solution: Given:

$$u_p = 0.75c = (0.75)3 \times 10^8 \text{ m/sec} = 2.25 \times 10^8 \text{ m/sec}$$

$$Z_0 = 50 \Omega$$

$$f = 2.25 \text{ GHz} = 2.25 \times 10^9 \text{ Hz}$$

$$C_{\text{eq}} = 4 \text{ pF} = 4 \times 10^{-12} \text{ F}$$

Example 2-8a

Solution:

we know that: $Z_{\text{in}} = -jZ_0 \cot \beta l = \frac{1}{j\omega C_{\text{eq}}}$

so:

$$\cot \beta l = -\frac{1}{jZ_0 j\omega C_{\text{eq}}}$$

$$\cot \beta l = \frac{1}{Z_0 \omega C_{\text{eq}}}$$

$$\tan \beta l = Z_0 \omega C_{\text{eq}}$$

$$\beta l = \tan^{-1} (Z_0 \omega C_{\text{eq}})$$

$$l = \frac{1}{\beta} \tan^{-1} (Z_0 \omega C_{\text{eq}})$$

Example 2-8a

Solution:

$$\omega = 2\pi f = (2\pi)2.25 \times 10^9 \text{ Hz} = 14.14 \times 10^9 \text{ rad/sec}$$

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi f}{u_p} = \frac{\omega}{u_p}$$

$$\beta = \frac{14.14 \times 10^9 \text{ rad/sec}}{2.25 \times 10^8 \text{ m/sec}}$$

$$\beta = 62.83 \text{ rad/m}$$

Example 2-8a

Solution:

$$l = \frac{1}{\beta} \tan^{-1} (Z_0 \omega C_{\text{eq}})$$

$$l = \frac{1}{62.83 \text{ rad/m}} \tan^{-1} ((50 \Omega)(14.14 \times 10^9 \text{ rad/sec})(4 \times 10^{-12} \text{ F}))$$

$$l = 0.015915 \text{ m/rad} \tan^{-1} (2.828)$$

$$l = 0.015915 \text{ m/rad} (1.231 \text{ rad})$$

$$l = 0.0196 \text{ m}$$

and since it repeats every $\lambda/2$:

$$l = 0.0196 + n\lambda/2 \text{ m}$$

Example 2-8a

Solution:

with:

$$\lambda = \frac{u_p}{f} = \frac{2.25 \times 10^8 \text{ m/sec}}{2.25 \times 10^9 \text{ Hz}}$$

$$\lambda = 0.1 \text{ m}$$

so:

$$l = 0.0196 + n(0.05) \text{ m}$$

2-8 Short-Circuit/Open-Circuit Method

Starting with:

$$Z_{\text{in}}^{\text{SC}} = jZ_0 \tan \beta l$$

$$Z_{\text{in}}^{\text{OC}} = -jZ_0 \cot \beta l$$

multiply the 2 equations together:

$$Z_{\text{in}}^{\text{SC}} Z_{\text{in}}^{\text{OC}} = [jZ_0 \tan \beta l] [-jZ_0 \cot \beta l]$$

$$Z_{\text{in}}^{\text{SC}} Z_{\text{in}}^{\text{OC}} = Z_0^2$$

so:

$$Z_0 = \sqrt{Z_{\text{in}}^{\text{SC}} Z_{\text{in}}^{\text{OC}}}$$

2-8 Short-Circuit/Open-Circuit Method

- Measure Z_{in} twice:
 - when terminated in a short
 - when terminated in an open

Use both: get Z_0 :

$$Z_0 = \sqrt{Z_{in}^{SC} Z_{in}^{OC}}$$

Example 2-9a

Given: lossless transmission line

$$Z_{\text{in}}^{\text{SC}} = j40.42 \, \Omega, \quad Z_{\text{in}}^{\text{OC}} = -j121.24 \, \Omega$$

Find: Z_0

Solution:

$$Z_0 = \sqrt{Z_{\text{in}}^{\text{SC}} Z_{\text{in}}^{\text{OC}}}$$
$$Z_0 = \sqrt{(j40.42 \, \Omega)(-j121.24 \, \Omega)}$$
$$Z_0 = \sqrt{4900 \, \Omega^2}$$
$$Z_0 = 70 \, \Omega$$

2-8 Special Case: $\lambda/2$

Recall the input impedance of a lossless line:

$$Z_{\text{in}} = Z_0 \left(\frac{z_L + j \tan(\beta l)}{1 + j z_L \tan(\beta l)} \right)$$

If the length is constrained to be a multiple of $\lambda/2$:

$$\beta l = (2\pi/\lambda) (n\lambda/2) = n\pi$$

so:

$$\tan \beta l = \tan n\pi = 0$$

Hence:

$$Z_{\text{in}} = Z_0 z_L = Z_0 z_L / Z_0$$

$$Z_{\text{in}} = Z_L$$

2-8 Special Case: $\lambda/2$

Recall the input impedance of a lossless line:

$$Z_{\text{in}} = Z_0 \left(\frac{z_L + j \tan(\beta l)}{1 + j z_L \tan(\beta l)} \right)$$

If $l = n\lambda/2$, then $\tan(\beta l) = \tan(n\pi) = 0$.
So for a line of length $n\lambda/2$, $Z_{\text{in}} = Z_L$!

Hence:

$$Z_{\text{in}} = Z_0 z_L = Z_0 z_L / Z_0$$

$$Z_{\text{in}} = Z_L$$

2-8 Special Case: $\lambda/4$

$$Z_{\text{in}} = Z_0 \left(\frac{z_L + j \tan(\beta l)}{1 + j z_L \tan(\beta l)} \right)$$


For $l = \lambda/4$, $\beta l = (2\pi/\lambda)(\lambda/4) = \pi/2$

So, as $\beta l \rightarrow \pi/2$, $\tan(\beta l) \rightarrow \infty$

$$\lim_{\beta l \rightarrow \pi/2} Z_{\text{in}} = Z_0 \left(\frac{j \tan(\beta l)}{j z_L \tan(\beta l)} \right) = \frac{Z_0^2}{Z_L}$$

$$Z_{\text{in}} = \frac{Z_0^2}{Z_L}, \quad \text{for } l = \lambda/4 + n\lambda/2.$$

Example 2-10

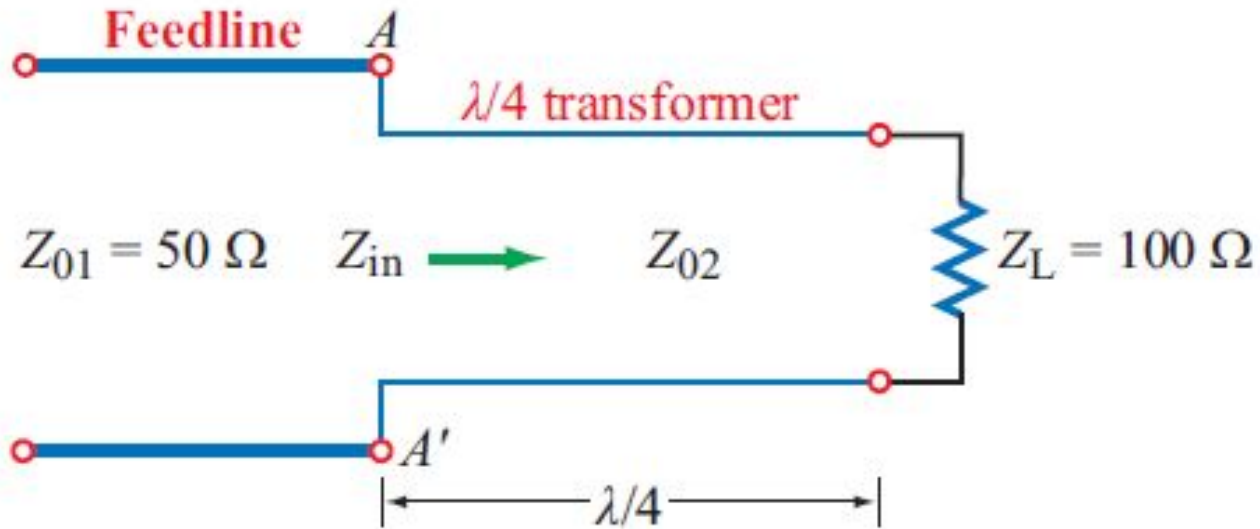

Given: lossless transmission line above.

$$Z_{01} = 50 \Omega, Z_L = 100 \Omega$$

Find: Z_{02} to make $Z_{in} = 50 \Omega$ (Matched Line)

Example 2-10

Solution: We know:

$$Z_{\text{in}} = \frac{Z_{02}^2}{Z_L}$$

so:

$$Z_{02} = \sqrt{Z_{\text{in}} Z_L} :$$

Plug in known values:

$$Z_{02} = \sqrt{50 \times 100} :$$

$$Z_{02} = 70.7 \, \Omega.$$

2-9 Instantaneous Power Flow

From EECS 215:

Power anywhere on the line, at any time t is:

$$\begin{aligned} P(d, t) &= v(d, t) i(d, t) \\ &= |V_0^+| [\cos(\omega t + \beta d + \phi^+) \\ &\quad + |\Gamma| \cos(\omega t - \beta d + \phi^+ + \theta_r)] \\ &\quad \times \frac{|V_0^+|}{Z_0} [\cos(\omega t + \beta d + \phi^+) \\ &\quad - |\Gamma| \cos(\omega t - \beta d + \phi^+ + \theta_r)] \end{aligned}$$

2-9 Instantaneous Power Flow

From EECS 215:

This looks like:

$$P = C (a+b)(a-b)$$

$$P = C (a^2 + ab - ab - b^2)$$

$$P = C (a^2 - b^2)$$

2-9 Instantaneous Power Flow

$$P(d, t) = v(d, t) i(d, t)$$

$$= \frac{|V_0^+|^2}{Z_0} [\cos^2(\omega t + \beta d + \phi^+) - |\Gamma|^2 \cos^2(\omega t - \beta d + \phi^+ + \theta_r)]$$

2-9 Instantaneous Power Flow

$$P(d, t) = P^i(d, t) + P^r(d, t)$$

The 2 terms are the **Incident** and **Reflected power**:

$$P^i(d, t) = \frac{|V_0^+|^2}{Z_0} \cos^2(\omega t + \beta d + \phi^+) \quad (\text{W}),$$

$$P^r(d, t) = -|\Gamma|^2 \frac{|V_0^+|^2}{Z_0} \cos^2(\omega t - \beta d + \phi^+ + \theta_r)$$

2-9 Instantaneous Power Flow

Using the trigonometric identity

$$\cos^2 x = \frac{1}{2}(1 + \cos 2x),$$

$$P^i(d, t) = \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t + 2\beta d + 2\phi^+)],$$

$$P^r(d, t) = -|\Gamma|^2 \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t - 2\beta d + 2\phi^+ + 2\theta_r)].$$


2-9 Instantaneous Power Flow

P oscillates at **twice** the frequency of V and I :

$$P^i(d, t) = \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t + 2\beta d + 2\phi^+)],$$

$$P^r(d, t) = -|\Gamma|^2 \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t - 2\beta d + 2\phi^+ + 2\theta_r)].$$

2-9 Instantaneous Voltage

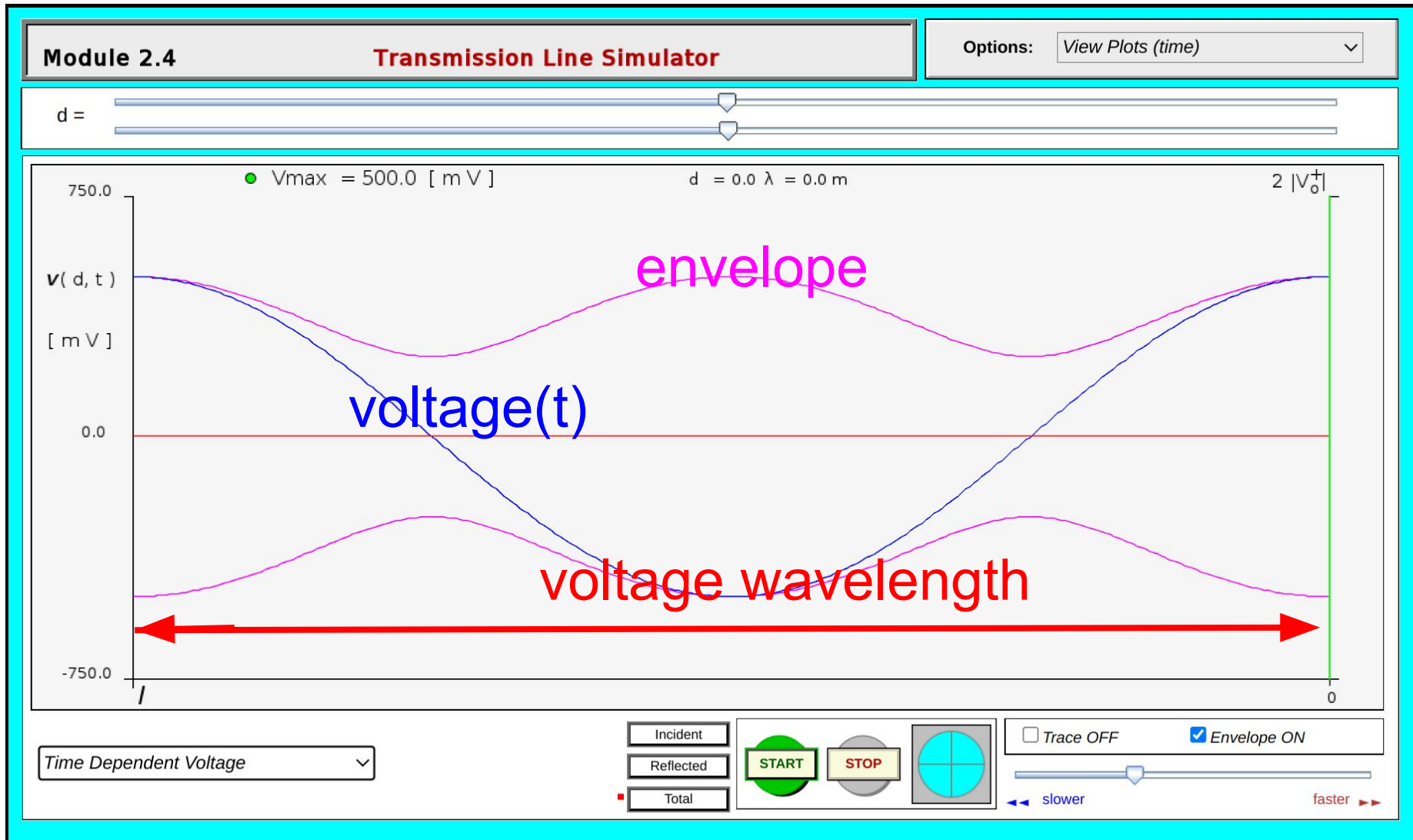


2-9 Instantaneous Power

Module 2.4

Transmission Line Simulator

Options: View Plots (time)

d =

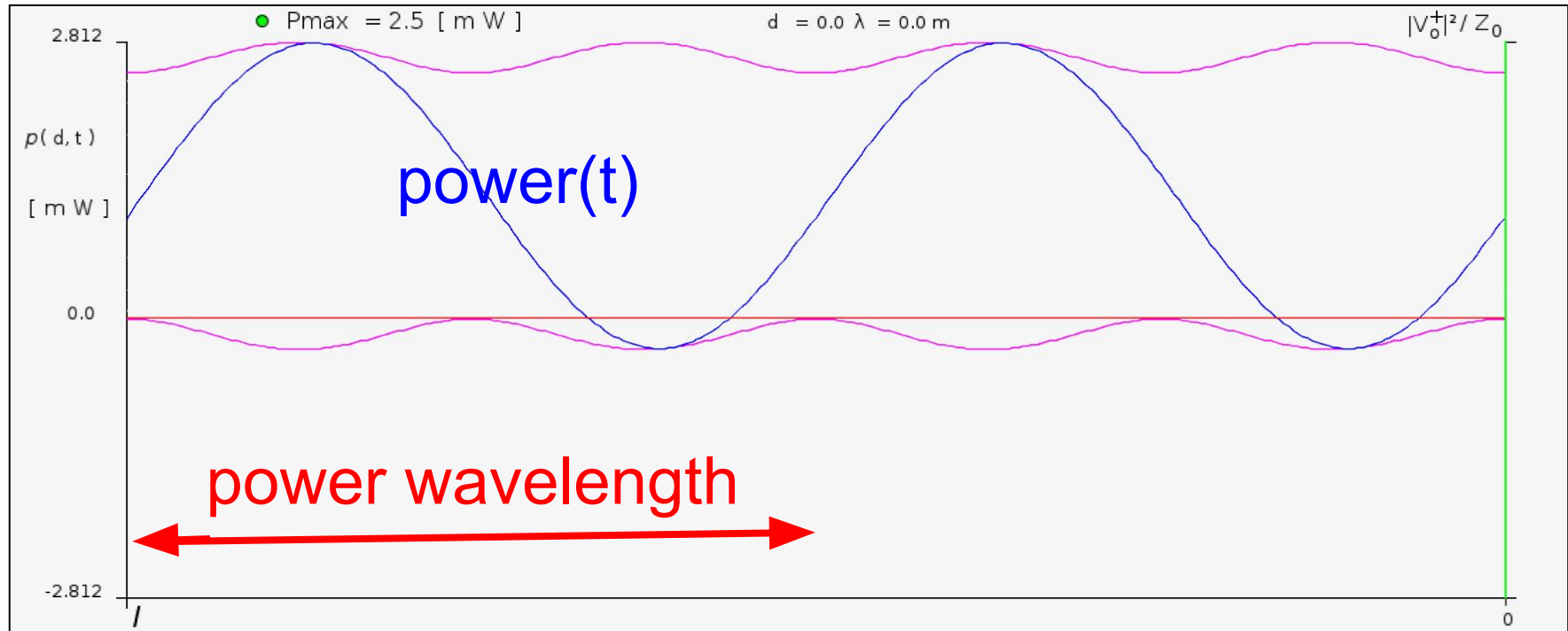

Time Dependent Power

Incident

Reflected

Total

START

STOP

Trace OFF

Envelope ON


slower

faster

Average a Signal

To find the average of a signal over a time period:

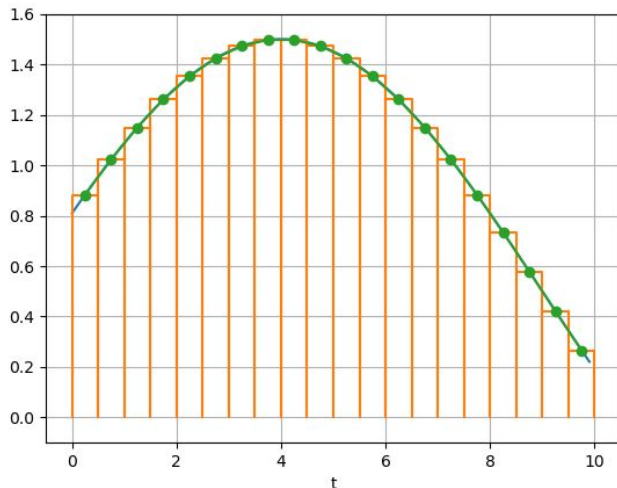
1. Divide up time period into small bins
2. for each bin get the center value
3. add up all the areas: center value X dt
4. divide by the total time
5. take the limit as dt goes to zero



$$\text{average} = \frac{\sum_0^N y(i) dt}{T}$$

$$\text{average} = \frac{1}{T} \int_0^T y(t) dt$$

2-9 Average Power Flow

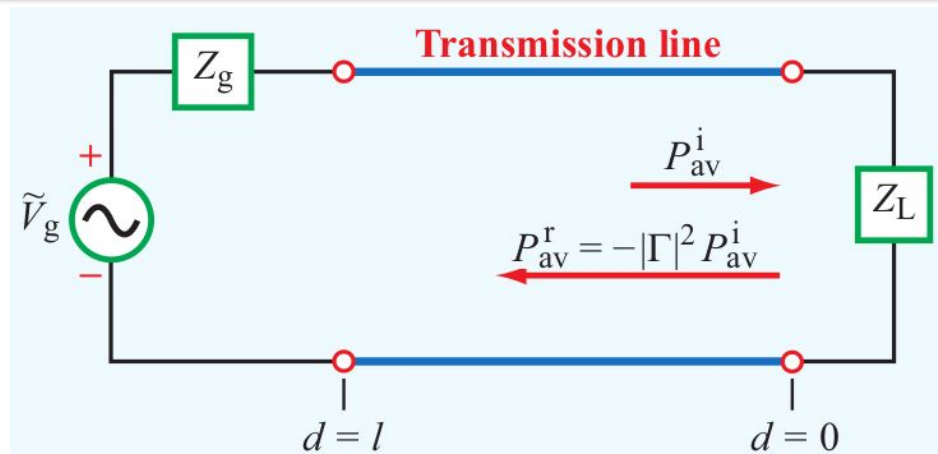


For the incident power, average over one period:

$$P_{avg}^i = \frac{\omega}{2\pi} \int_0^{\frac{2\pi}{\omega}} \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t + 2\beta d + 2\phi^+)] dt$$

$$\omega = \frac{2\pi}{T}, \quad \text{hence} \quad T = \frac{2\pi}{\omega}$$


2-9 Average Power Flow

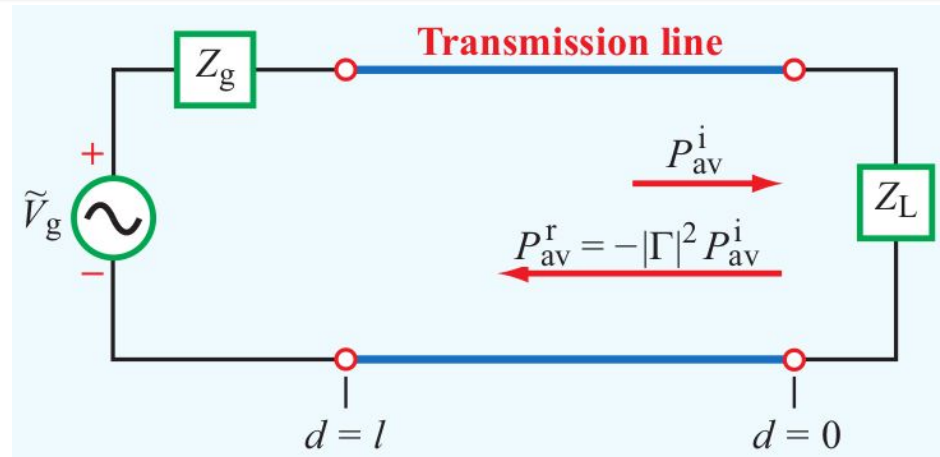

$$P_{avg}^i = \frac{\omega}{2\pi} \int_0^{\frac{2\pi}{\omega}} \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t + 2\beta d + 2\phi^+)] dt$$

$$P_{avg}^i = \frac{\omega}{2\pi} \frac{|V_0^+|^2}{2Z_0} \left[t + \frac{1}{2\omega} \sin(2\omega t + 2\beta d + 2\phi^+) \right]_0^{\frac{2\pi}{\omega}}$$


2-9 Average Power Flow

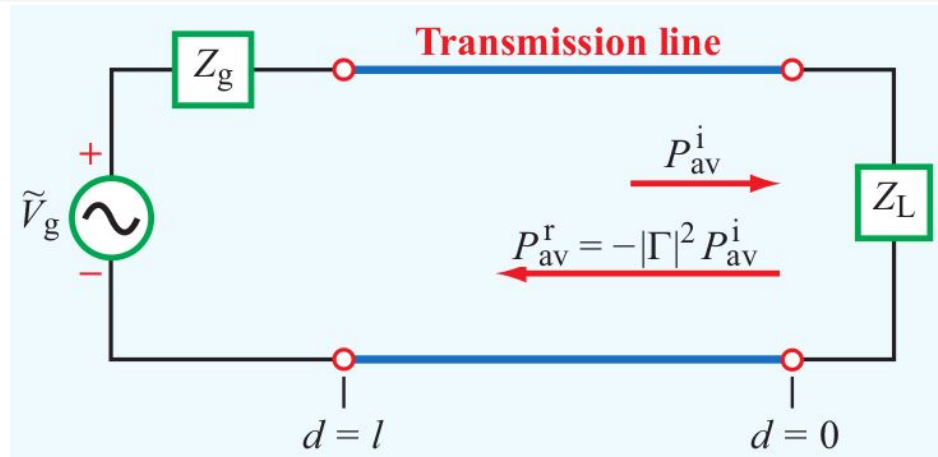

$$P_{\text{avg}}^i = \frac{\omega}{2\pi} \frac{|V_0^+|^2}{2Z_0} \left[t + \frac{1}{2\omega} \sin(2\omega t + 2\beta d + 2\phi^+) \right]_0^{\frac{2\pi}{\omega}}$$

$$P_{\text{avg}}^i = \frac{\omega}{2\pi} \frac{|V_0^+|^2}{2Z_0} \left\{ \left[\frac{2\pi}{\omega} + \frac{1}{2\omega} \sin(4\pi + 2\beta d + 2\phi^+) \right] - \left[0 + \frac{1}{2\omega} \sin(0 + 2\beta d + 2\phi^+) \right] \right\}$$

2-9 Average Power Flow

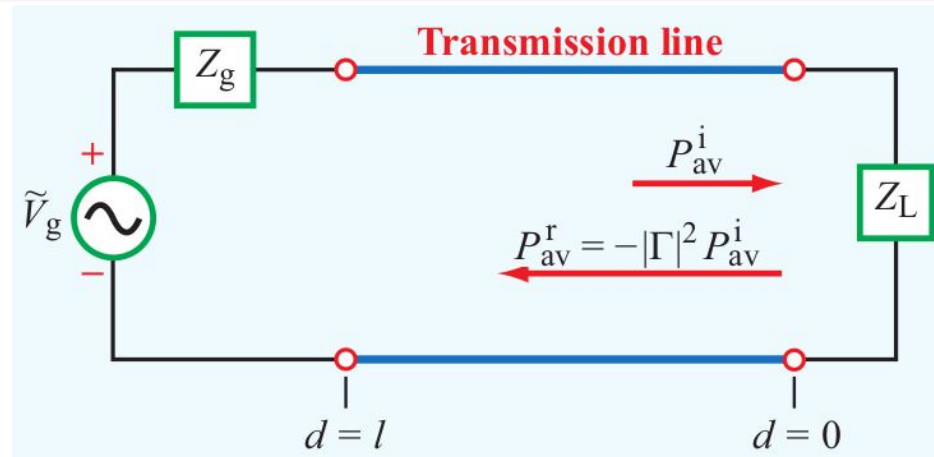


$$P_{\text{avg}}^i = \frac{\omega}{2\pi} \frac{|V_0^+|^2}{2Z_0} \left\{ \left[\frac{2\pi}{\omega} + \frac{1}{2\omega} \sin(4\pi + 2\beta d + 2\phi^+) \right] - \left[0 + \frac{1}{2\omega} \sin(0 + 2\beta d + 2\phi^+) \right] \right\}$$

$$P_{\text{avg}}^i = \frac{\omega}{2\pi} \frac{|V_0^+|^2}{2Z_0} \left[\frac{2\pi}{\omega} \right]$$

$$P_{\text{avg}}^i = \frac{|V_0^+|^2}{2Z_0}$$


2-9 Average Power Flow

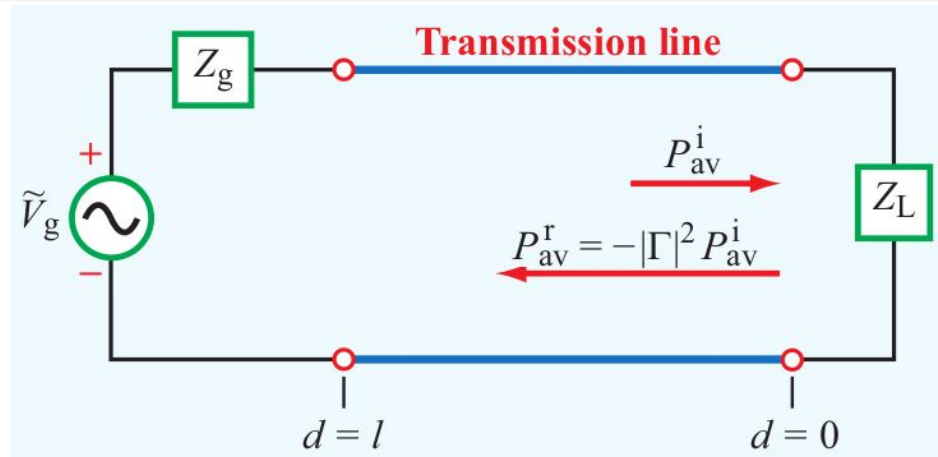

Similarly for the reflected power:

$$P_{avg}^r = -|\Gamma|^2 \frac{|V_0^+|^2}{2Z_0}$$

2-9 Average Power Flow

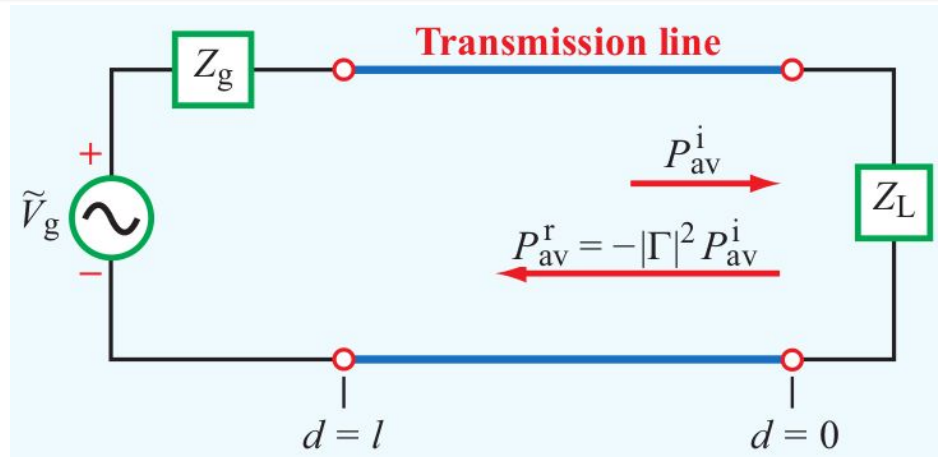

$$P_{avg}^i = \frac{|V_0^+|^2}{2Z_0}$$

$$P_{avg}^r = -|\Gamma|^2 P_{avg}^i$$


$$P_{av} = P_{av}^i + P_{av}^r = \frac{|V_0^+|^2}{2Z_0} [1 - |\Gamma|^2]$$

The average power absorbed by the load.

Exercise 2-17

Given: $Z_0 = 50\Omega$, $Z_L = 100 + j 50 \Omega$

Find: fraction of the avg incident power that is reflected from the load

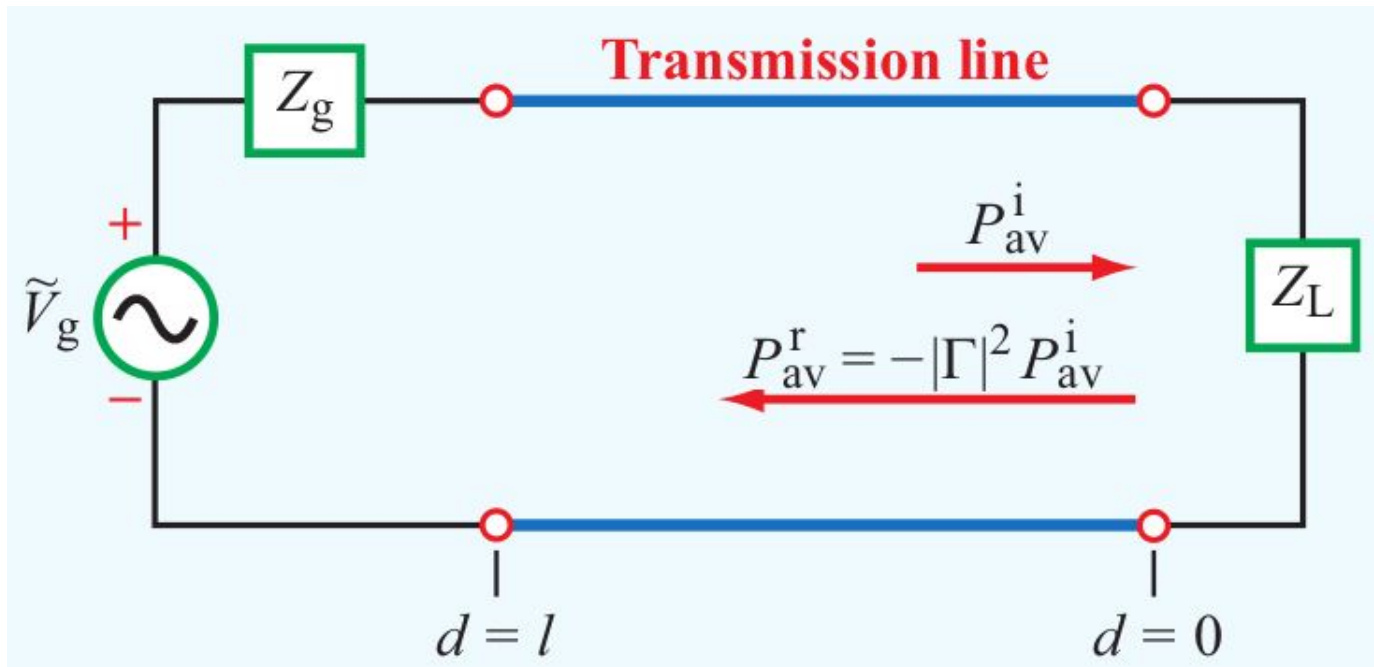

Exercise 2-17

Solution: the "fraction of the avg incident power that is reflected from the load" is just: $|\Gamma|^2$, so:

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\Gamma = \frac{100 + j50 - 50}{100 + j50 + 50}$$

$$\Gamma = \frac{50 + j50}{150 + j50}$$

$$\Gamma = \frac{\sqrt{50^2 + 50^2} e^{j \tan^{-1}(50/50)}}{\sqrt{150^2 + 50^2} e^{j \tan^{-1}(50/150)}}$$

Exercise 2-17

Solution:

$$\Gamma = \frac{\sqrt{50^2 + 50^2} e^{j \tan^{-1}(50/50)}}{\sqrt{150^2 + 50^2} e^{j \tan^{-1}(50/150)}}$$

$$\Gamma = \frac{70.7 e^{j45^\circ}}{158.1 e^{j18.4^\circ}}$$

$$\Gamma = 0.447 e^{j26.6^\circ}$$

hence:

$$|\Gamma|^2 = 0.447^2$$

$$|\Gamma|^2 = 0.2$$

Homework

69

Homework 7 is due tomorrow at midnight.

submit to gradescope via the canvas site.

Next Time



Section 2-10:

The Smith Chart

(A graphical method to solve transmission line problems.)