

EECS 230
ENGINEERING ELECTROMAGNETICS
Leland Pierce

Transmission Lines 7

Chapter 2 Overview

What is a transmission line?

Why study transmission lines?

model

diffeq

solve diffeq

wave propagation

lossless transmission line

microstrip lines

reflections

standing waves

impedance




short, open

matching





power flow

smith chart

transients

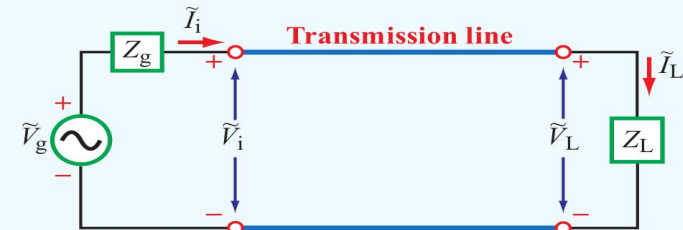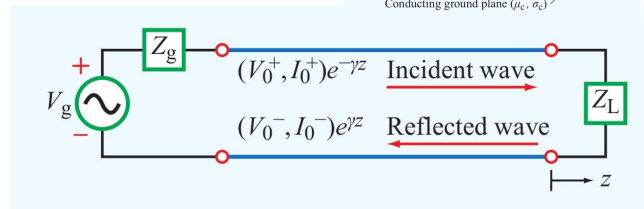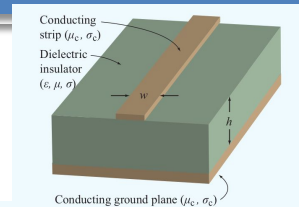

Typical High-Frequency Circuit

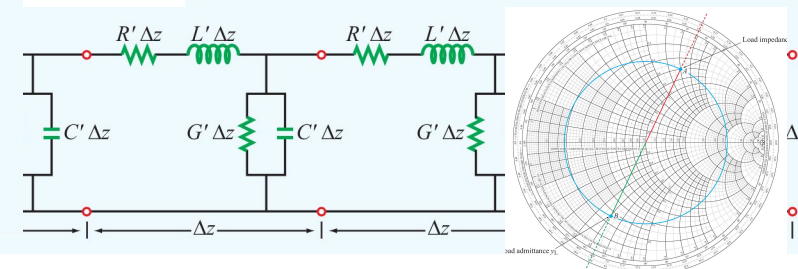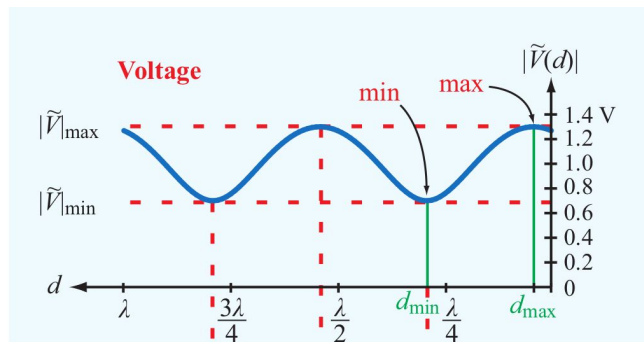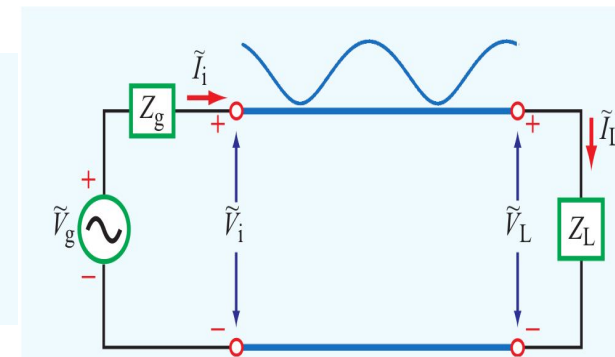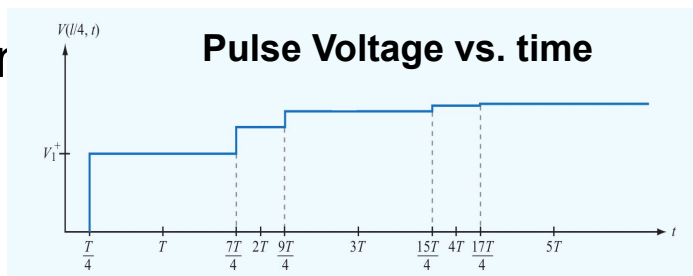

Today's Lecture Coverage

Review Sections 2-1 through 2-10 of the book:

2-1: What is a transmission line? Why study transmission lines?

2-2: Lumped-Element Model

2-3: Governing Differential Eqns

2-4: Solve the Differential Equations

Properties of the solution: wave propagation

2-5: Lossless Microstrip Line

2-6: Lossless Transmission Lines

2-7: Lossless Transmission Lines: Wave Impedance

2-8: Lossless Transmission Lines: Special Cases

2-9: Lossless Transmission Lines: Power Flow

2-10: The Smith Chart

Section 2-11 of the book:

2-11: Matching using the Smith Chart


Chapter 2 Review

- A transmission line connects a **generator** to a **load**.



Chapter 2 Review

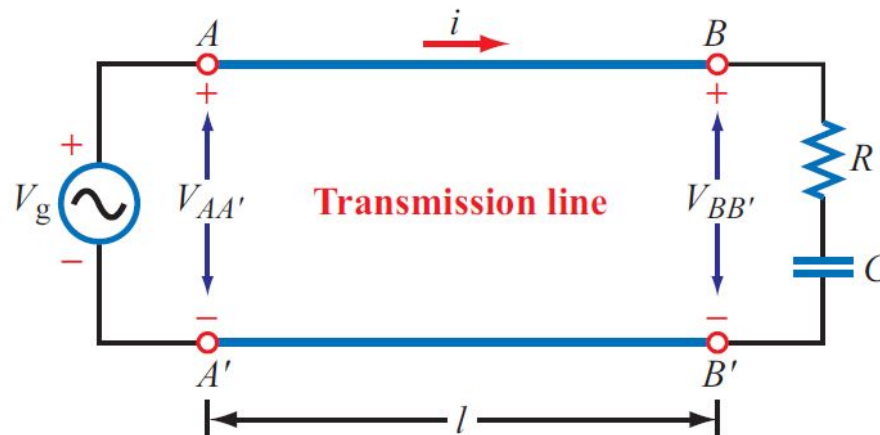Phase Delay due to length of transmission line:




$$\phi_0 = \frac{\omega l}{c} = \frac{2\pi f l}{c} = 2\pi \frac{l}{\lambda} \text{ radians.}$$

$l/\lambda \lesssim 0.01$: Can ignore transmission-line effects


$l/\lambda \gtrsim 0.01$: Must deal with phase shift, and other effects...

Chapter 2 Review

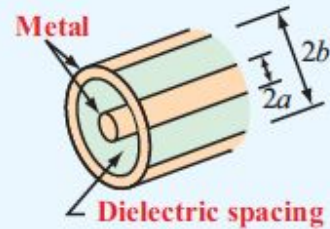
Different geometries for transmission lines




(a) Coaxial line

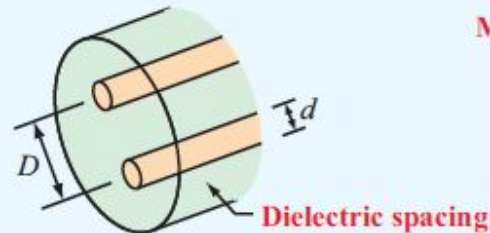


(b) Two-wire line

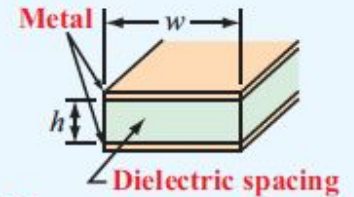


(c) Parallel-plate line

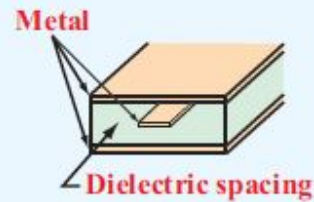

(d) Strip line

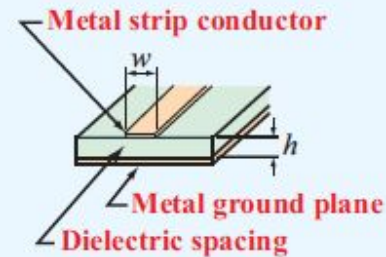


(e) Microstrip line

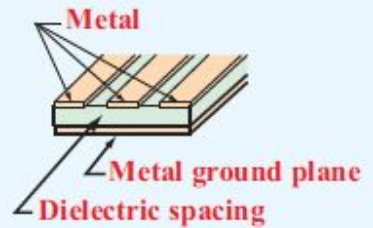


(f) Coplanar waveguide

TEM Transmission Lines

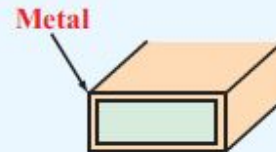

(g) Rectangular waveguide

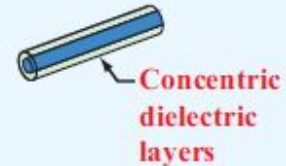


(h) Optical fiber

Higher-Order Transmission Lines

Chapter 2 Review

Lumped-Element Model:

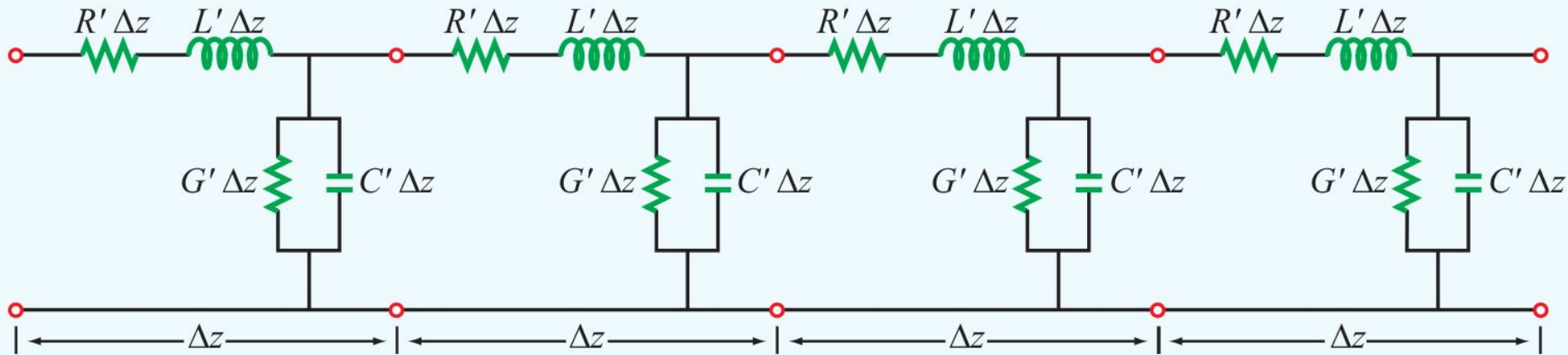

All parameters are "per unit length":

R': Combined Resistance of BOTH conductors: \square/m

L': Combined Inductance of BOTH conductors, H/m

G': Conductance of insulation

between inner and outer conductor, S/m

C': Capacitance

between inner and outer conductors, F/m

Chapter 2 Review

Lumped-Element Values: geometry/materials/freq

Table 2-1 Transmission-line parameters R' , L' , G' , and C' for three types of lines.

| Parameter | Coaxial | Two-Wire | Parallel-Plate | Unit |
|-----------|---|---|------------------------|---------------------|
| R' | $\frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$ | $\frac{2R_s}{\pi d}$ | $\frac{2R_s}{w}$ | Ω/m |
| L' | $\frac{\mu}{2\pi} \ln(b/a)$ | $\frac{\mu}{\pi} \ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]$ | $\frac{\mu h}{w}$ | H/m |
| G' | $\frac{2\pi\sigma}{\ln(b/a)}$ | $\frac{\pi\sigma}{\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]}$ | $\frac{\sigma w}{h}$ | S/m |
| C' | $\frac{2\pi\epsilon}{\ln(b/a)}$ | $\frac{\pi\epsilon}{\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]}$ | $\frac{\epsilon w}{h}$ | F/m |

$$R_s = \sqrt{\pi f \mu_c / \sigma_c}$$

Chapter 2 Review

Transmission-line governing Differential Equations

$$-\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L') \tilde{I}(z),$$
$$-\frac{d\tilde{I}(z)}{dz} = (G' + j\omega C') \tilde{V}(z).$$

(telegrapher's equations in phasor form)

Chapter 2 Review

Transmission-line governing Differential Equation for V :

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0,$$

(wave equation for $\tilde{V}(z)$)

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}.$$

(propagation constant)

Chapter 2 Review

Complex propagation constant:

$$\gamma = \alpha + j\beta$$

Where:

γ : Units of 1/m

α : Attenuation constant, units of Np/m (>0 in this class)

β : Phase constant, units of rad/m

Np and radians are both "dimensionless", and are the conventional "units" for these parameters.

Chapter 2 Review

Form of the solution: traveling waves, going in both directions:

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{\gamma z} \quad (\text{A}).$$

$$Z_0 = \frac{R' + j\omega L'}{\gamma} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \quad (\Omega),$$

Chapter 2 Review

Solution in time-domain

$$v(z, t) = |V_0^+| e^{-\alpha z} \cos(\omega t - \beta z + \phi^+) \\ + |V_0^-| e^{+\alpha z} \cos(\omega t + \beta z + \phi^-)$$

Remaining unknowns are determined via specification of source and load.

Chapter 2 Review

- The wave equation for a general Transmission Line.

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0, \quad (2.21)$$

- General solution of the wave equation
 - *It involves both incident and reflected waves*

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$

Chapter 2 Review

- Useful Relations for lossless Transmission Lines:

$$\alpha = 0 \quad (\text{lossless line}),$$
$$\beta = \omega\sqrt{L'C'} \quad (\text{lossless line}). \quad (2.45)$$

$$\beta = \omega\sqrt{\mu\varepsilon} \quad (\text{rad/m}), \quad (2.49)$$

$$u_p = \frac{1}{\sqrt{\mu_0\varepsilon_0}} \frac{1}{\sqrt{\varepsilon_r}} = \frac{c}{\sqrt{\varepsilon_r}}$$

$$\lambda = \frac{u_p}{f} = \frac{c}{f} \frac{1}{\sqrt{\varepsilon_r}} = \frac{\lambda_0}{\sqrt{\varepsilon_r}}$$

$$Z_0 = \sqrt{\frac{L'}{C'}} \quad (\text{lossless line}), \quad (2.46) \quad (\text{REAL})$$

Chapter 2 Review

- Voltage reflection coefficient due to load:

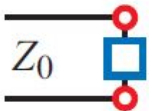

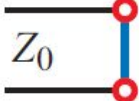
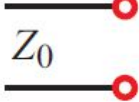
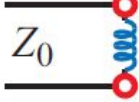
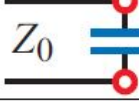
$$\begin{aligned}\Gamma &= \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \\ &= \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} \\ &= \frac{z_L - 1}{z_L + 1}\end{aligned}$$

- Load impedance in terms of Γ :

$$Z_L = \frac{1 + \Gamma}{1 - \Gamma} Z_0$$

Chapter 2 Review

Reflection Coefficient $\Gamma = |\Gamma|e^{j\theta_r}$

| Load | $ \Gamma $ | θ_r |
|--|--|---|
|  $Z_L = (r + jx)Z_0$ | $\left[\frac{(r - 1)^2 + x^2}{(r + 1)^2 + x^2} \right]^{1/2}$ | $\tan^{-1} \left(\frac{x}{r - 1} \right) - \tan^{-1} \left(\frac{x}{r + 1} \right)$ |
|  Z_0 | 0 (no reflection) | irrelevant |
|  (short) | 1 | $\pm 180^\circ$ (phase opposition) |
|  (open) | 1 | 0 (in-phase) |
|  $jX = j\omega L$ | 1 | $\pm 180^\circ - 2 \tan^{-1} x$ |
|  $jX = \frac{-j}{\omega C}$ | 1 | $\pm 180^\circ + 2 \tan^{-1} x$ |

$$z_L = Z_L/Z_0 = (R + jX)/Z_0 = r + jx$$

Chapter 2 Review

- Concept of standing wave



$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z}),$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z}).$$

- Voltage (current) magnitudes at any point on line:

$$|\tilde{V}(d)| = |V_0^+| \left[1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}. \quad (2.66)$$

Chapter 2 Review

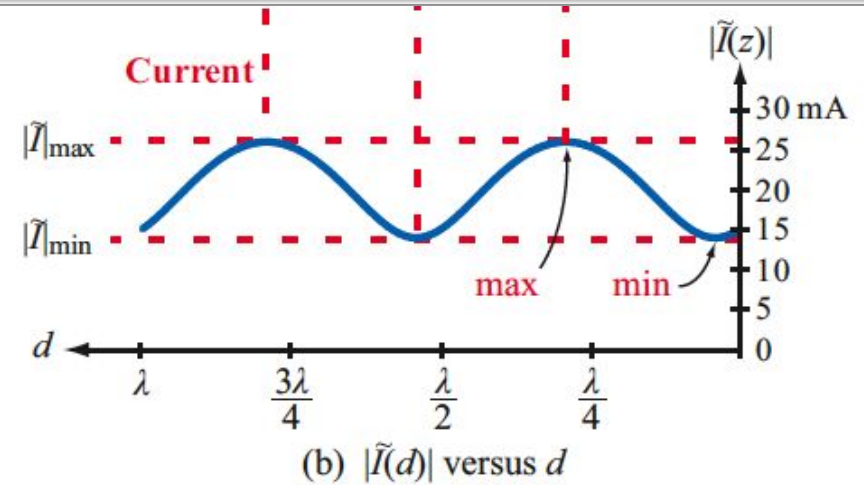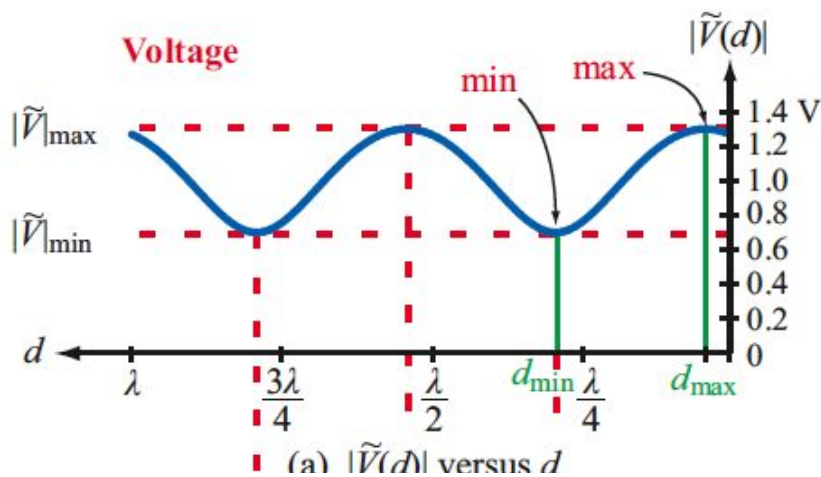



- Location of minima / maxima

$$d_{\max} = \frac{\theta_r + 2n\pi}{2\beta} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2},$$

$$\begin{cases} n = 1, 2, \dots & \text{if } \theta_r < 0, \\ n = 0, 1, 2, \dots & \text{if } \theta_r \geq 0, \end{cases} \quad (2.70)$$

Value of V_{\max} : $|\tilde{V}(d)| = |\tilde{V}|_{\max} = |V_0^+| [1 + |\Gamma|],$

Chapter 2 Review

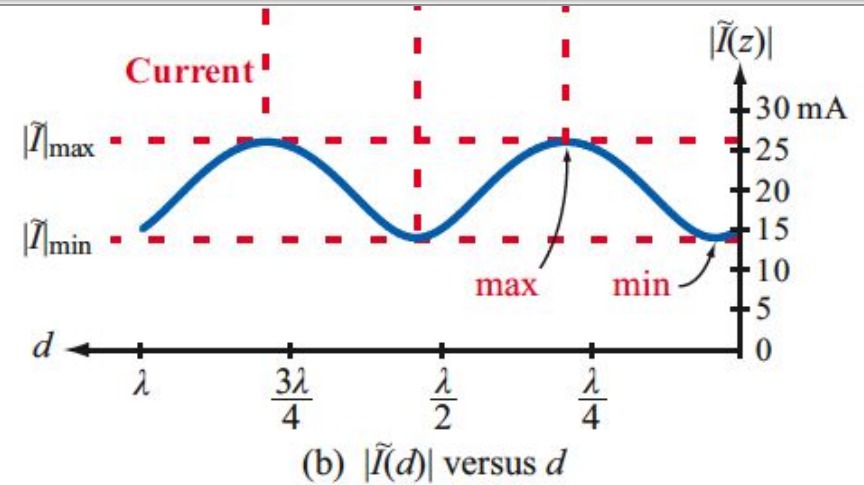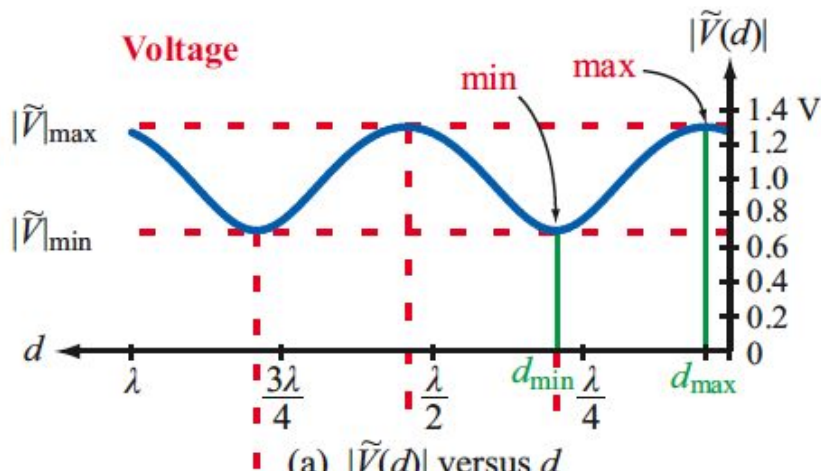


- Spatial period of standing wave: $\frac{\lambda}{2}$
- Standing wave ratio S:

$$S = \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$


Chapter 2 Review

Wave Impedance:
At a distance d from the load:
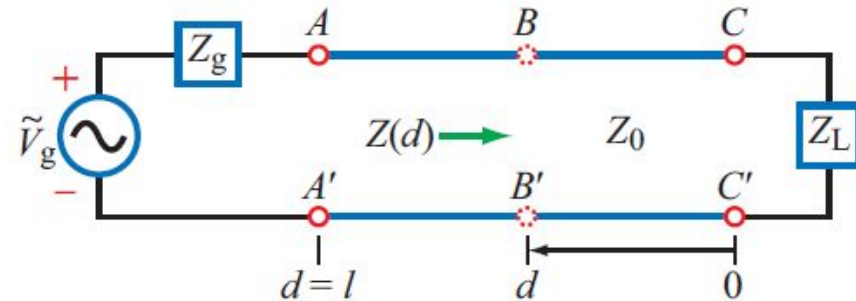
$$\begin{aligned}
 Z(d) &= \frac{\tilde{V}(d)}{\tilde{I}(d)} \\
 &= \frac{V_0^+ [e^{j\beta d} + \Gamma e^{-j\beta d}]}{V_0^+ [e^{j\beta d} - \Gamma e^{-j\beta d}]} Z_0 \\
 &= Z_0 \left[\frac{1 + \Gamma e^{-j2\beta d}}{1 - \Gamma e^{-j2\beta d}} \right] \\
 &= Z_0 \left[\frac{1 + \Gamma_d}{1 - \Gamma_d} \right] \quad (\Omega),
 \end{aligned}$$



(a) Actual circuit

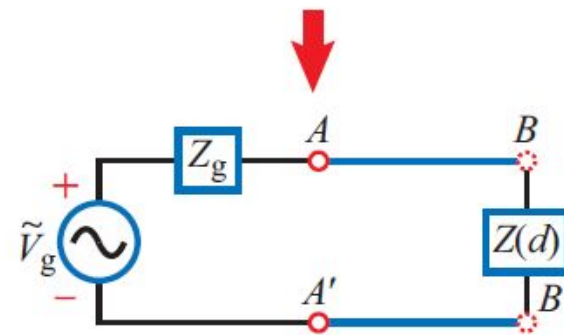

(b) Equivalent circuit

Chapter 2 Review


Define the phase-shifted voltage reflection coefficient:

$$\Gamma_d = \Gamma e^{-j2\beta d} = |\Gamma| e^{j\theta_r} e^{-j2\beta d}$$


$$= |\Gamma| e^{j(\theta_r - 2\beta d)}$$

$Z(d)$ is different than Z_0 :
Ratio of **Total** Voltage and
Current

Recall: $Z_0 = \frac{V_0^+}{I_0^+}$

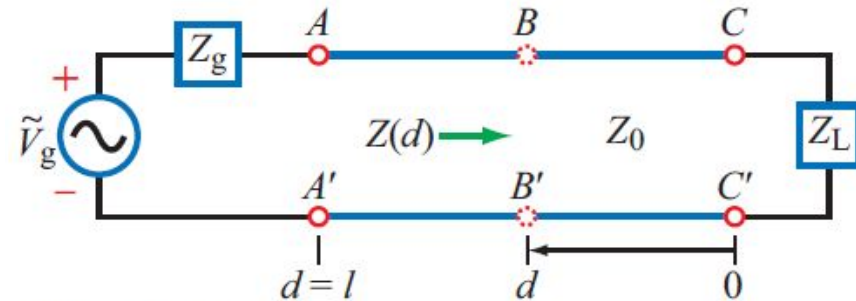


(a) Actual circuit

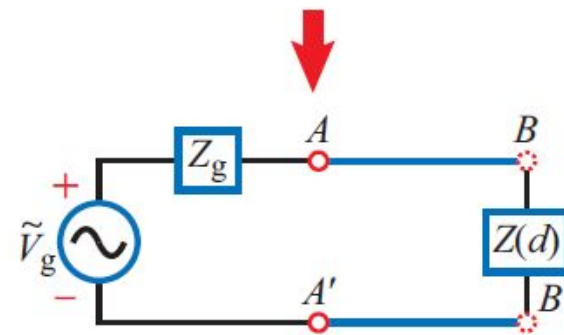


(b) Equivalent circuit

Chapter 2 Review

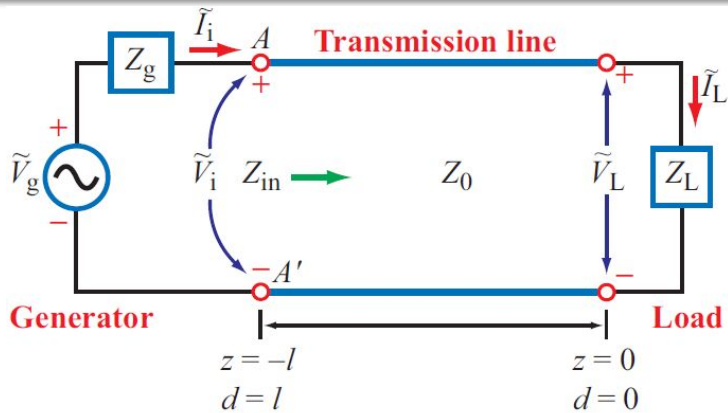

Input impedance:
impedance of the transmission
line at $d=l$:
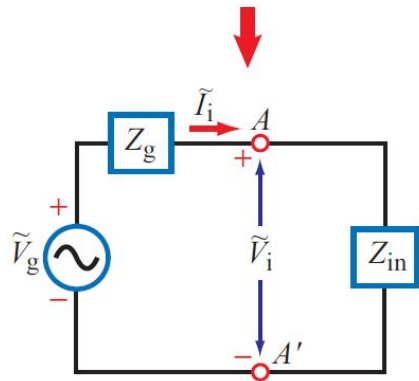
$$Z_{\text{in}} = Z(d = l) = \frac{\tilde{V}(d = l)}{\tilde{I}(d = l)}$$




Note that Z_{in} is different from the
Characteristic Impedance, and is different
from the Load Impedance:

$$Z_{\text{in}} \neq Z_0$$

$$Z_{\text{in}} \neq Z_L$$

Chapter 2 Review

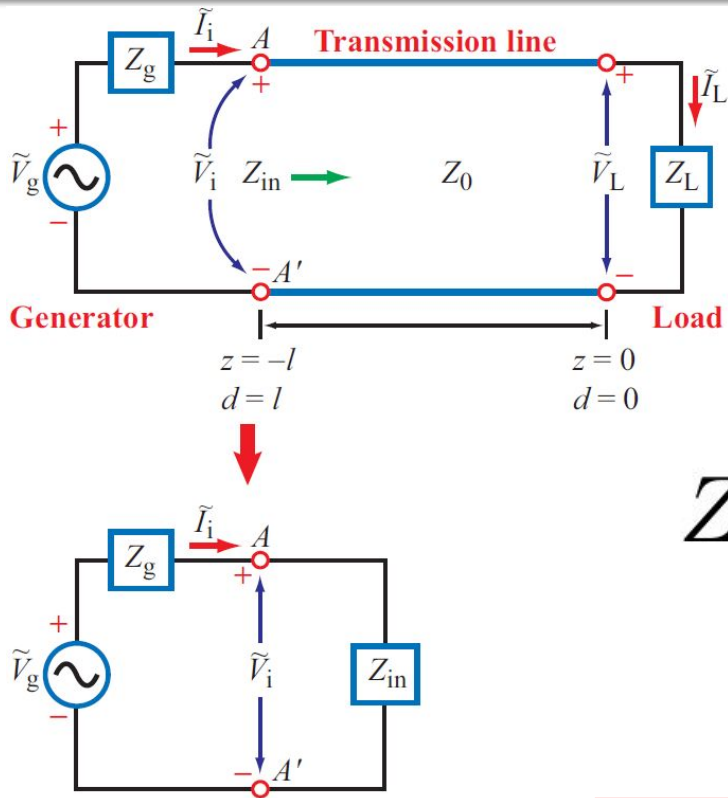


Input impedance:
impedance of the transmission line at $d=l$:

$$Z_{in} = Z(d = l) = \frac{\tilde{V}(d = l)}{\tilde{I}(d = l)}$$

$$Z_{in} = Z_0 \left[\frac{z_L + j \tan(\beta l)}{1 + j z_L \tan(\beta l)} \right]$$

Chapter 2 Review

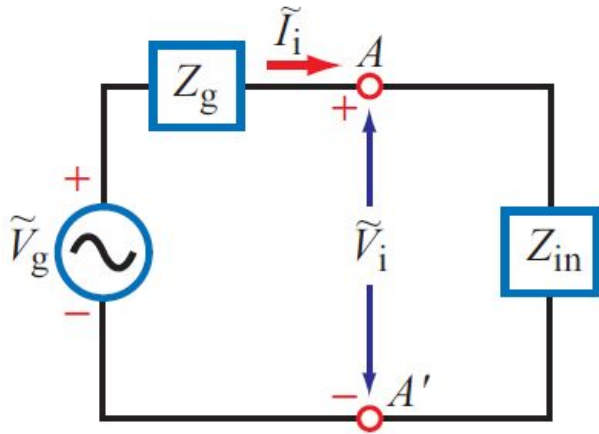


Voltage Amplitude:

$$V_0^+ = \left(\frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left(\frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right).$$

We used the boundary conditions (Z_L , Z_g , V_g , I) to solve for the 2 unknowns.

This completes the solution of the transmission line differential equation.

Chapter 2 Review

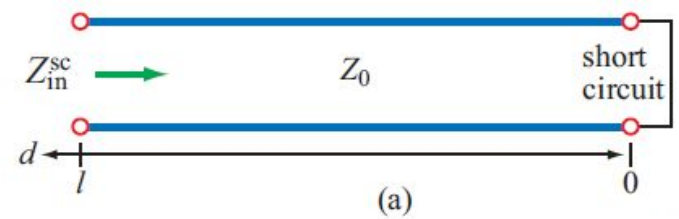


For the short-circuited line:

$$\Gamma = -1$$

$$\tilde{V}_{sc}(d) = 2jV_0^+ \sin \beta d,$$

$$\tilde{I}_{sc}(d) = \frac{2V_0^+}{Z_0} \cos \beta d,$$
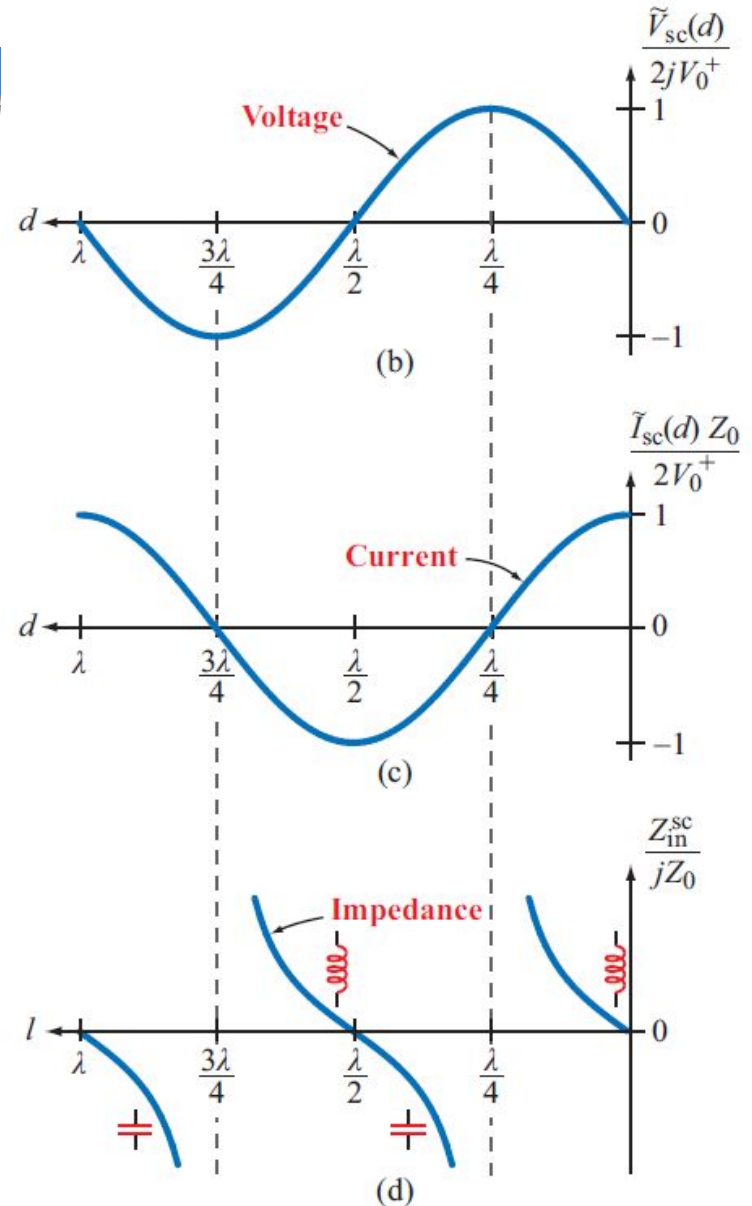
$$Z_{sc}(d) = \frac{\tilde{V}_{sc}(d)}{\tilde{I}_{sc}(d)} = jZ_0 \tan \beta d.$$







Chapter 2 Review

At its input, the short-circuited line appears like an inductor or a capacitor depending on the sign of

$$\tan \beta d$$

$$j\omega L_{\text{eq}} = jZ_0 \tan \beta l, \quad \text{if } \tan \beta l \geq 0$$
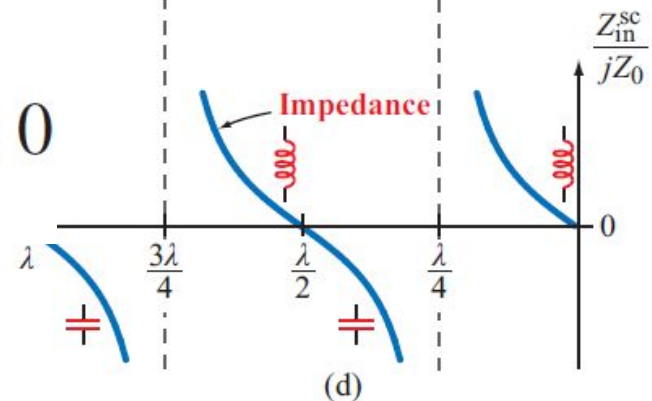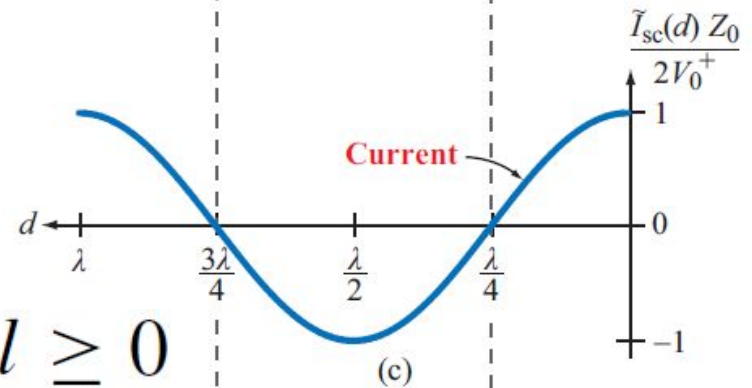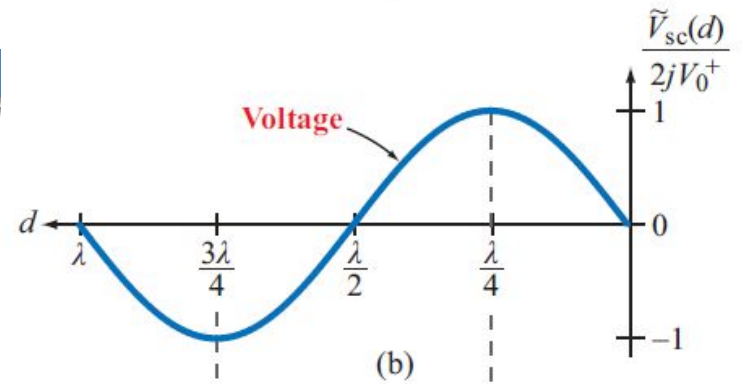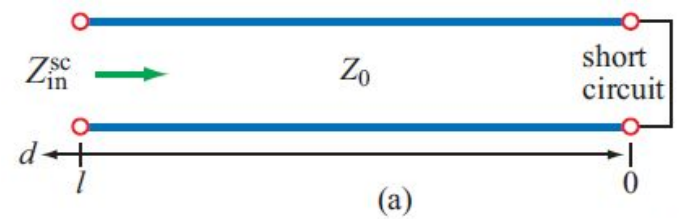
$$\frac{1}{j\omega C_{\text{eq}}} = jZ_0 \tan \beta l, \quad \text{if } \tan \beta l \leq 0$$



Chapter 2 Review


Open-circuited Line:

$$\Gamma = 1$$

$$\tilde{V}_{oc}(d) = V_0^+ [e^{j\beta d} + e^{-j\beta d}] = 2V_0^+ \cos \beta d,$$

$$\tilde{I}_{oc}(d) = \frac{V_0^+}{Z_0} [e^{j\beta d} - e^{-j\beta d}] = \frac{2jV_0^+}{Z_0} \sin \beta d,$$
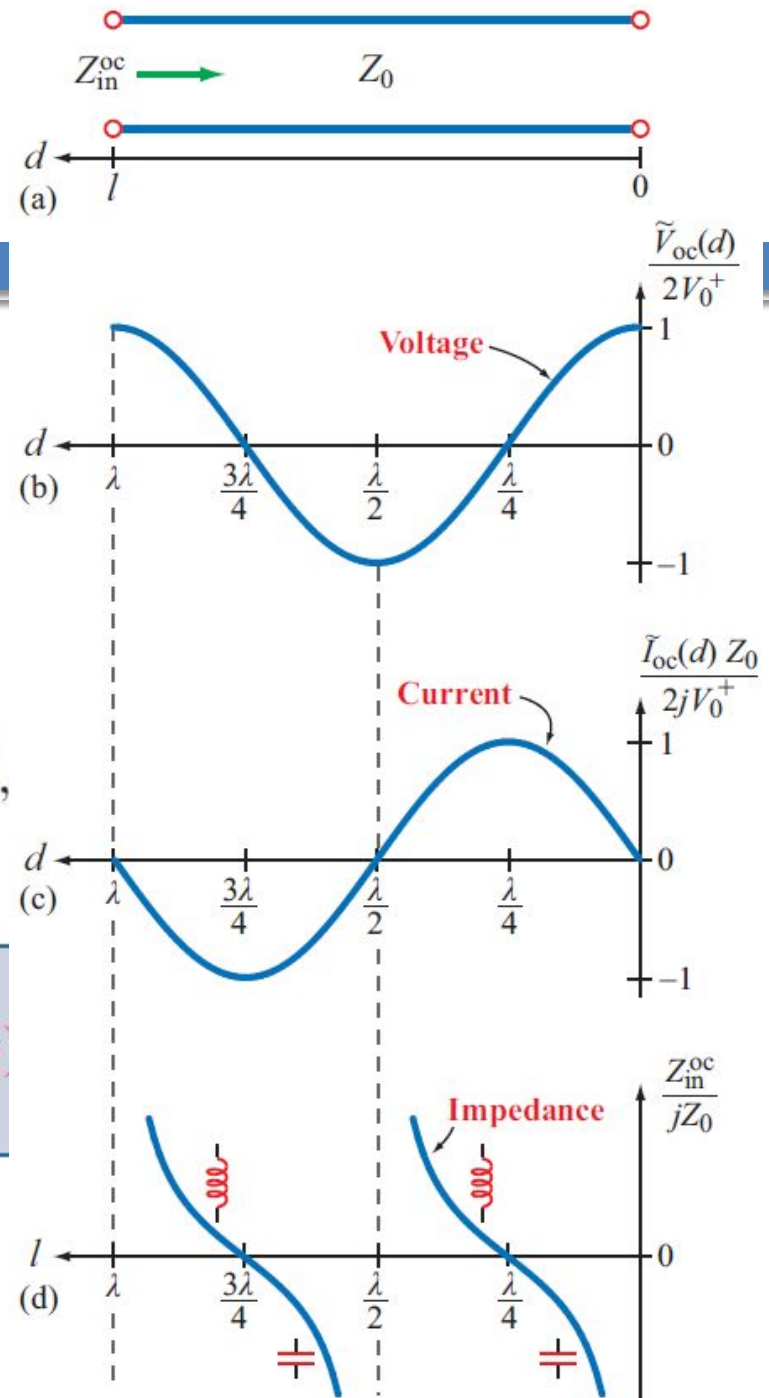
$$Z_{in}^{oc} = \frac{\tilde{V}_{oc}(l)}{\tilde{I}_{oc}(l)} = -jZ_0 \cot \beta l. \quad (2.93)$$



Chapter 2 Review

Short-Circuit/Open-Circuit Method:

- Given length l
- Measure Z_{in} twice:
 - when terminated in a short
 - when terminated in an open

Use both: get Z_0, β :

$$Z_{in}^{sc} = \frac{\tilde{V}_{sc}(l)}{\tilde{I}_{sc}(l)} = jZ_0 \tan \beta l.$$

$$Z_{in}^{oc} = \frac{\tilde{V}_{oc}(l)}{\tilde{I}_{oc}(l)} = -jZ_0 \cot \beta l.$$



$$Z_0 = \sqrt{Z_{in}^{sc} Z_{in}^{oc}},$$

$$\tan \beta l = \sqrt{\frac{-Z_{in}^{sc}}{Z_{in}^{oc}}}.$$

Chapter 2 Review

Half-Wavelength Line:

$$Z_{\text{in}} = Z_0 \left(\frac{z_L + j \tan(\beta l)}{1 + j z_L \tan(\beta l)} \right)$$

If $l = n\lambda/2$, where n is an integer,

$$\tan \beta l = \tan [(2\pi/\lambda) (n\lambda/2)] = \tan n\pi = 0.$$

Consequently, Eq. (2.79) reduces to

$$Z_{\text{in}} = Z_L, \quad \text{for } l = n\lambda/2, \quad (2.96)$$

which means that a half-wavelength line (or any integer multiple of $\lambda/2$) does not modify the load impedance.

Chapter 2 Review

Quarter-Wavelength Line:

$$Z_{\text{in}} = Z_0 \left(\frac{z_L + j \tan(\beta l)}{1 + j z_L \tan(\beta l)} \right)$$

For $l = \lambda/4$, $\beta l = (2\pi/\lambda)(\lambda/4) = \pi/2$

So, as $\beta l \rightarrow \pi/2$, $\tan(\beta l) \rightarrow \infty$

$$\lim_{\beta l \rightarrow \pi/2} Z_{\text{in}} = Z_0 \left(\frac{j \tan(\beta l)}{j z_L \tan(\beta l)} \right) = \frac{Z_0^2}{Z_L}$$

$$Z_{\text{in}} = \frac{Z_0^2}{Z_L}, \quad \text{for } l = \lambda/4 + n\lambda/2.$$

Chapter 2 Review

Instantaneous Power Flow:

$$P(d, t) = P^i(d, t) + P^r(d, t)$$

The 2 terms are the **Incident** and **Reflected power**:


$$P^i(d, t) = \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t + 2\beta d + 2\phi^+)],$$

$$P^r(d, t) = -|\Gamma|^2 \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t - 2\beta d + 2\phi^+ + 2\theta_r)].$$

oscillating at **TWICE** the frequency of V or I

Chapter 2 Review

Average Power Flow:

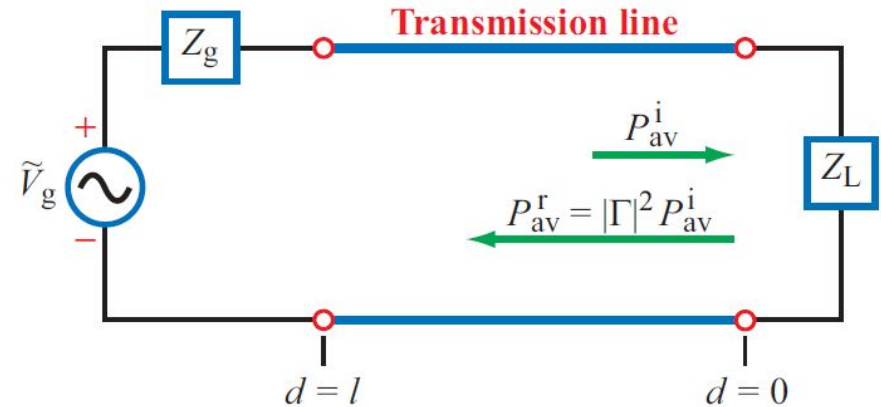


For the **incident** power, average over one period:

$$P_{\text{avg}}^i = \frac{\omega}{2\pi} \int_0^{\frac{2\pi}{\omega}} \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t + 2\beta d + 2\phi^+)] dt$$

$$\omega = \frac{2\pi}{T}, \quad \text{hence} \quad T = \frac{2\pi}{\omega}$$

Chapter 2 Review

Average Power Flow:

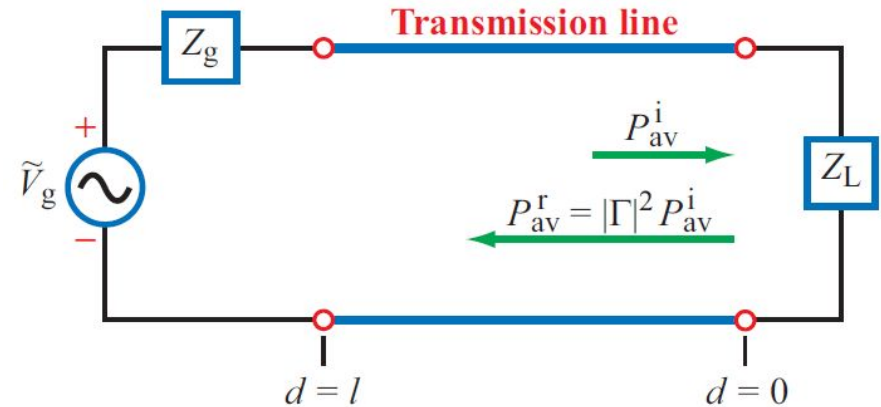


$$P_{avg}^i = \frac{|V_0^+|^2}{2Z_0}$$

$$P_{avg}^r = -|\Gamma|^2 P_{avg}^i$$

Chapter 2 Review

$$\Gamma = |\Gamma|e^{j\theta_r} = \Gamma_r + j\Gamma_i$$

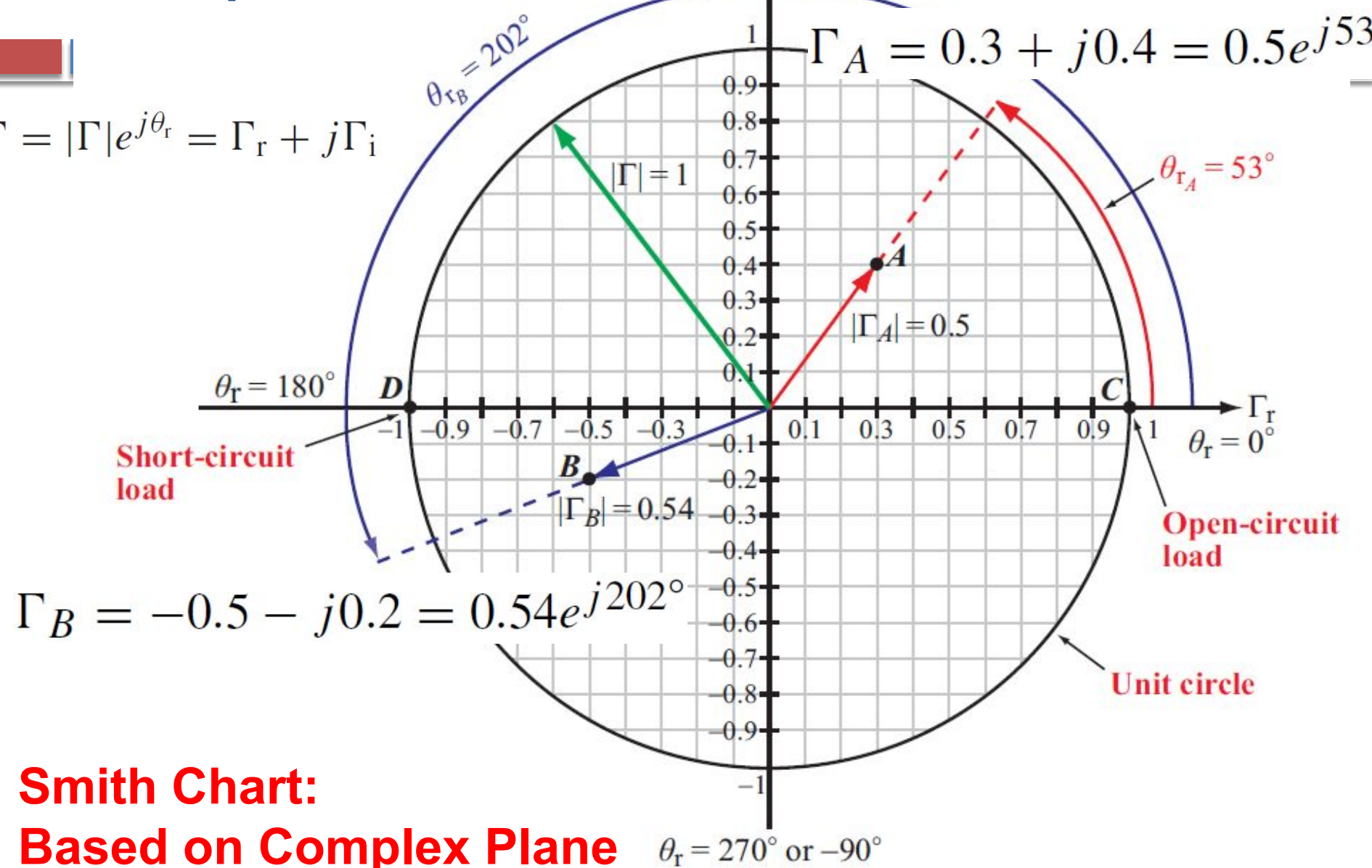


**Smith Chart:
Based on Complex Plane**

Chapter 2 Review

If plotted z_L :
Obtain values for Γ_L
from the angle scale
and magnitude
scale:

0.41, 94°

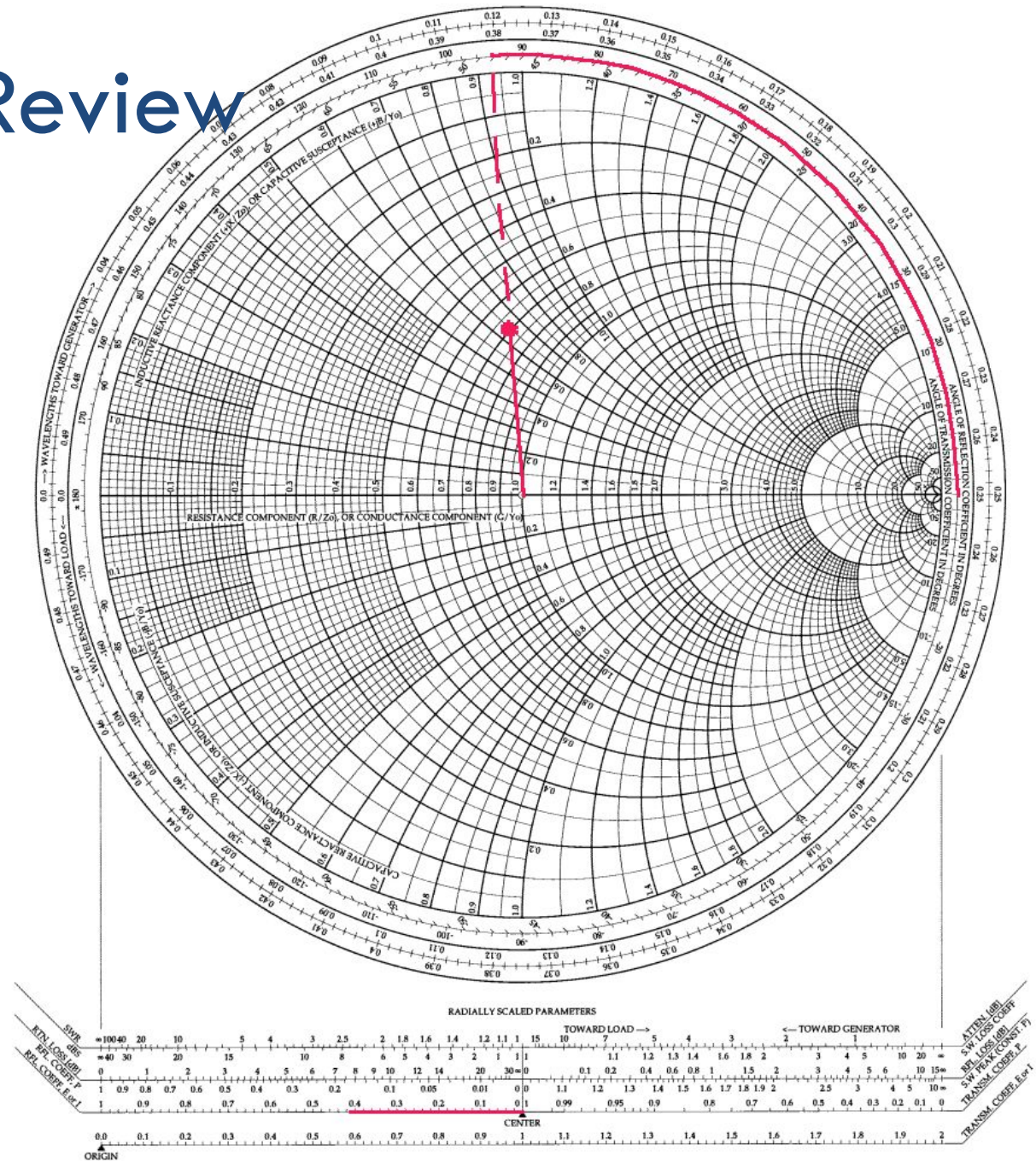


Chapter 2 Review


If plotted Γ_L :
Obtain values for
 r_L , x_L from the
nearest circles:

$$z_L = (0.7, 0.65)$$

To get Z_L :
Multiply z_L by Z_0

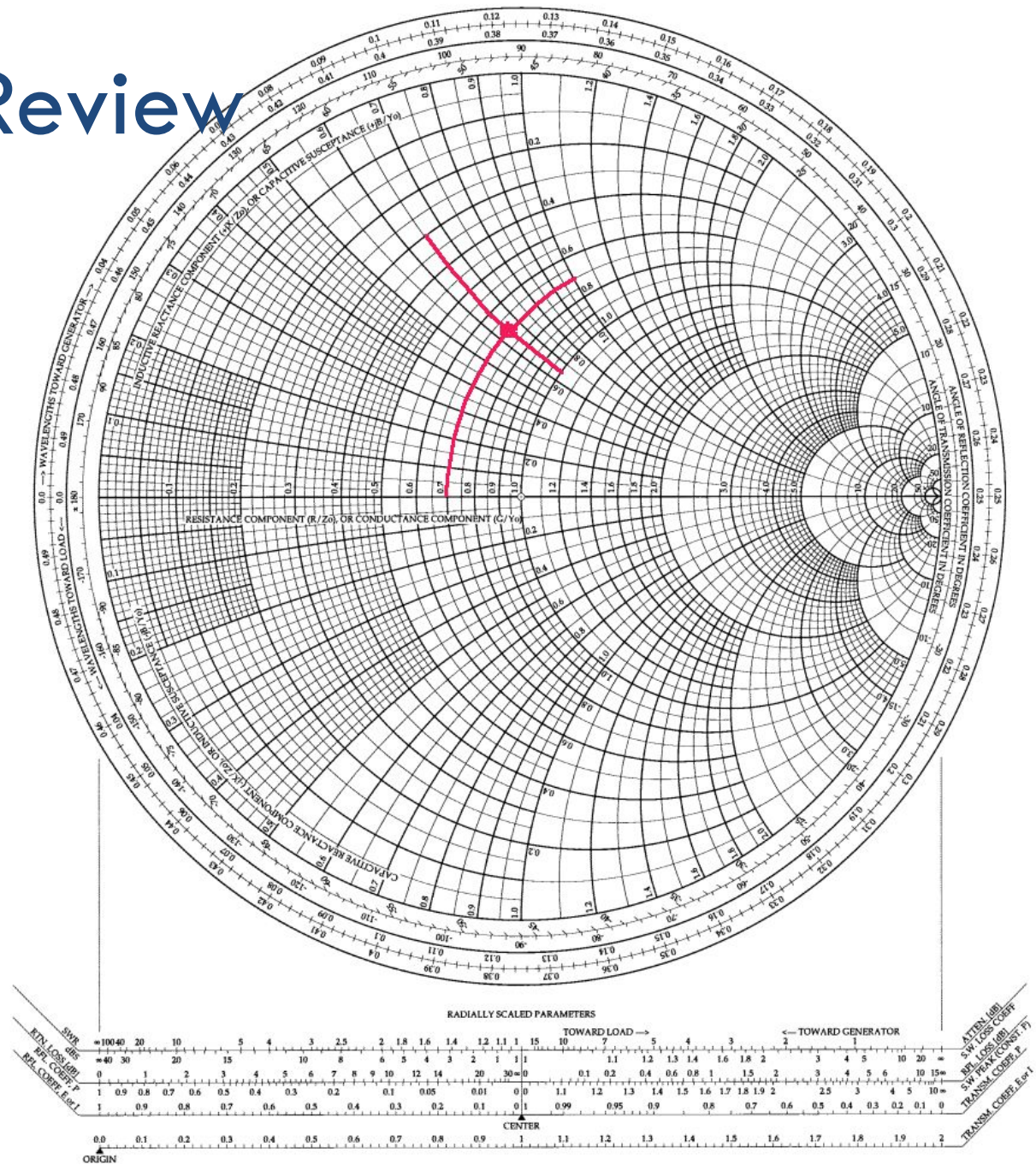

Chapter 2 Review

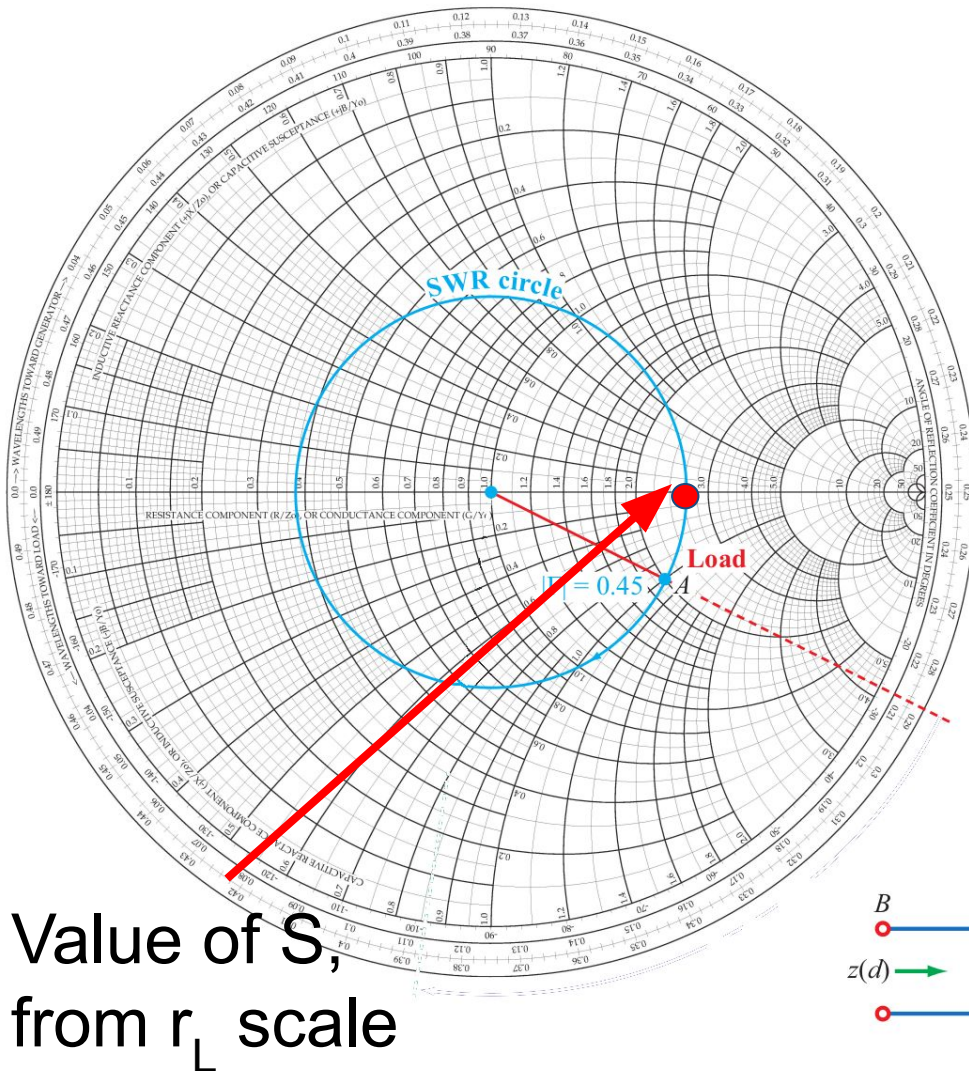


All points on a circle centered at the origin have the same $|\Gamma|$.


Since

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

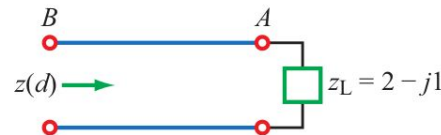this is also a circle of constant S (VSWR).




Chapter 2 Review

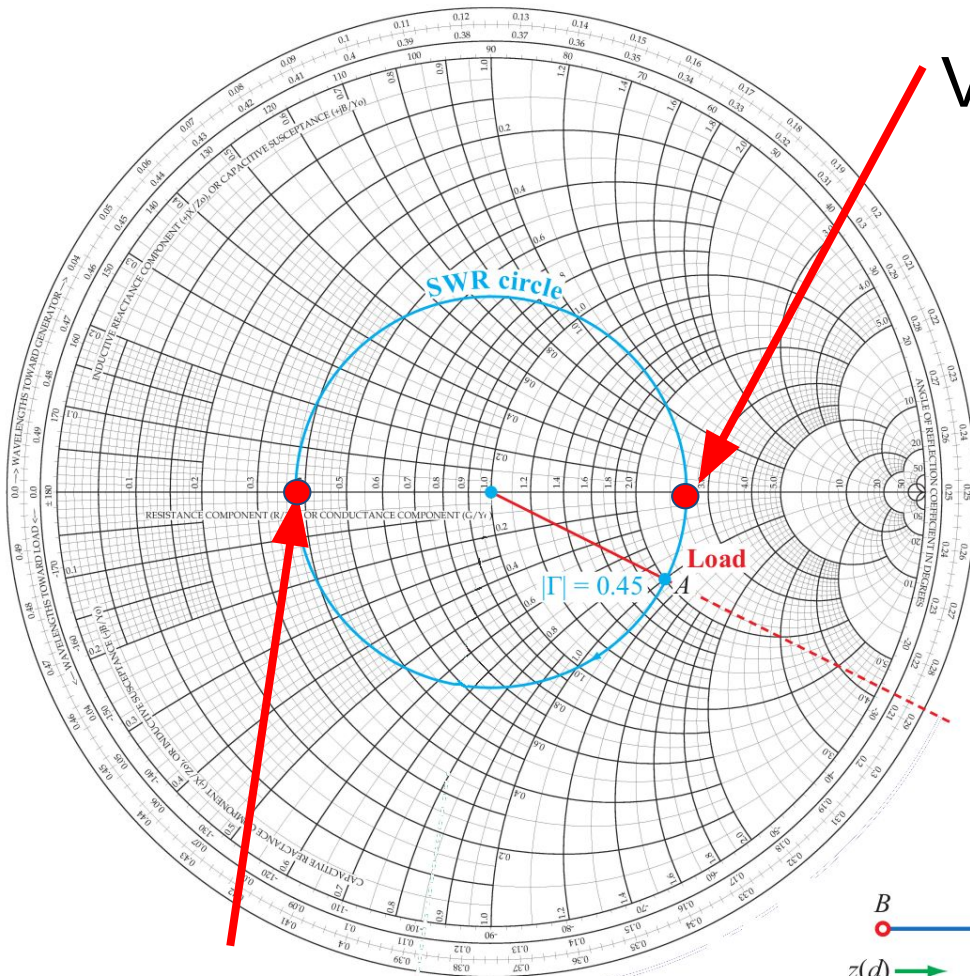


Voltage Maxima position

Voltage Minima position

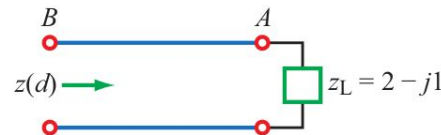

Chapter 2 Review

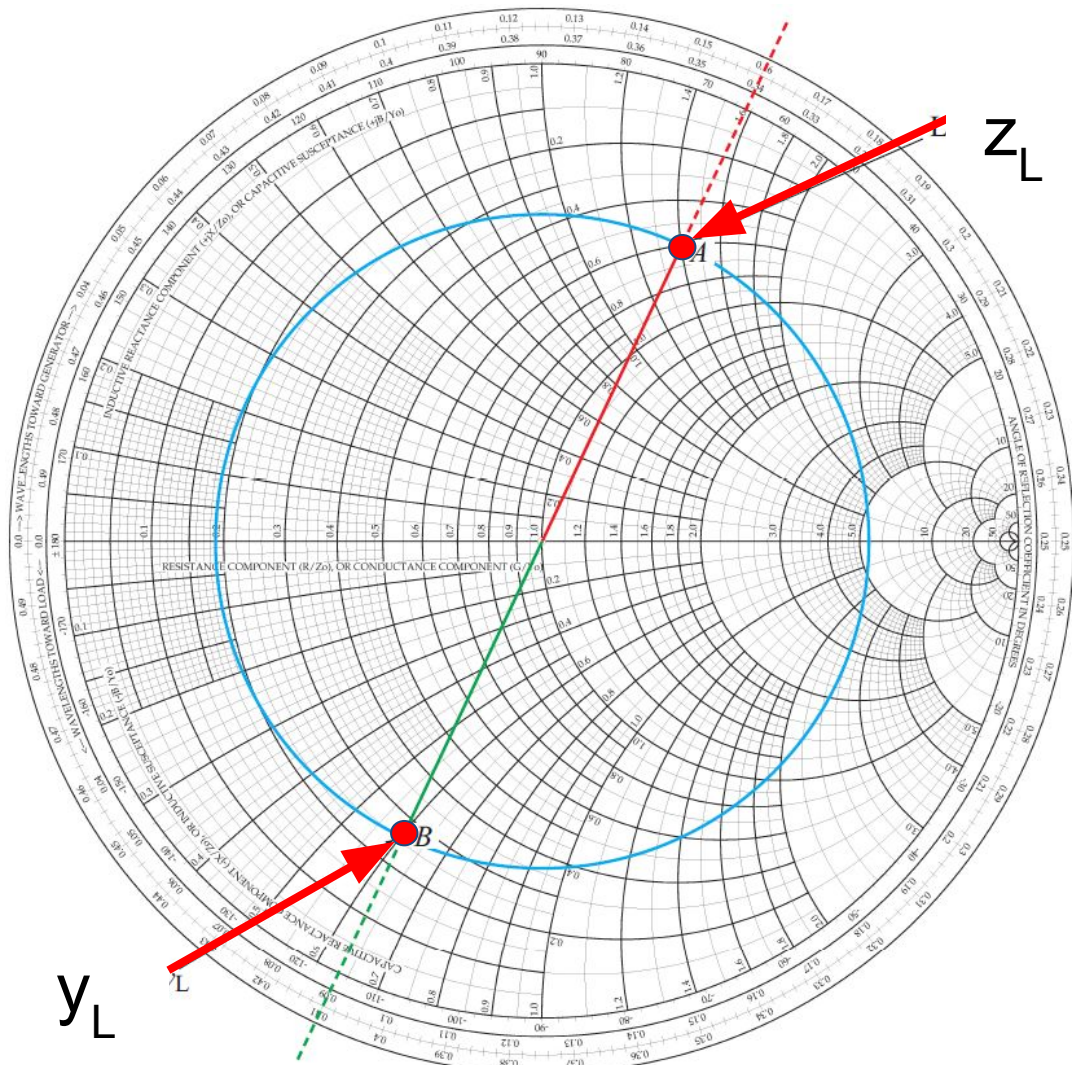

y_L and z_L are inverses of each other.

Occur $\lambda/4$ apart on the Smith Chart.

2-11 Impedance Matching

Often, one wants to maximize the power delivered to a load.

In EECS 215 you learned to have the load resistor equal to the source resistance.

In this class it's similar:

For a lossless transmission-line:

The load resistance should be equal to the transmission-line characteristic impedance:

$$Z_L = Z_0$$

2-1 1 Impedance Matching

Consequences:

$$\Gamma = (Z_L - Z_0) / (Z_L + Z_0) = 0$$

no reflected wave

$$P_{av_inc} = |V_0^+|^2 / (2 Z_0)$$
$$P_{av_refl} = -|\Gamma|^2 P_{av_inc} = 0$$

So, often the load is complex, and so matching it to the transmission-line is important.

2-1 1 Impedance Matching

Common Scenario:

The load was optimized with other issues in mind


The load is not matched to the transmission-line

We need to match it... somehow.


Can add something in series or parallel to modify the *equivalent impedance* to be $= Z_0$

2-1 1 Impedance Matching

Example Matching Networks

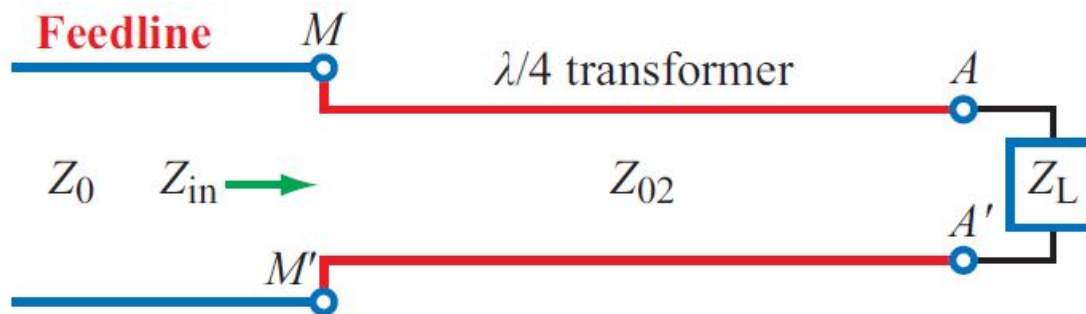

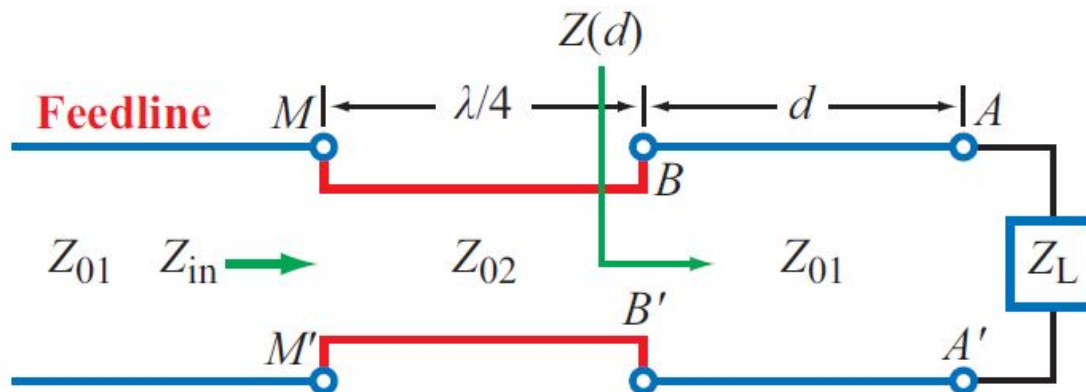
(a) In-series $\lambda/4$ transformer inserted at AA'




(b) In-series $\lambda/4$ transformer inserted at $d = d_{\max}$ or $d = d_{\min}$

2-1 1 Impedance Matching

Example Matching Networks

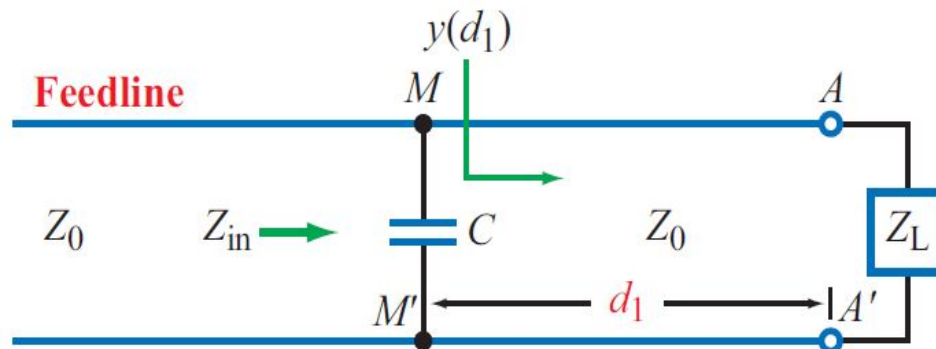

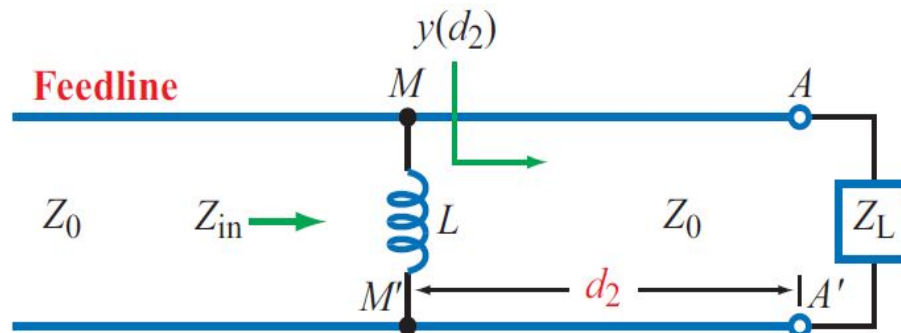
(c) In-parallel insertion of capacitor at distance d_1



(d) In-parallel insertion of inductor at distance d_2

2-1 1 Impedance Matching

Example Matching Networks

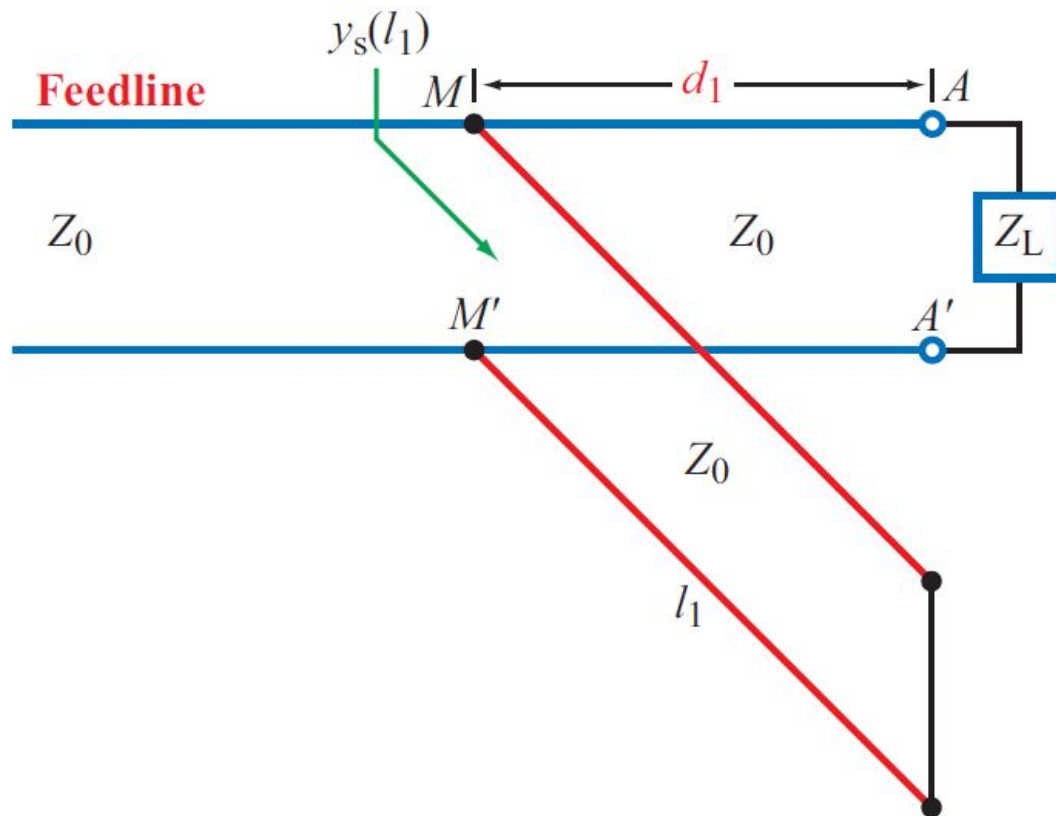

(e) In-parallel insertion of a short-circuited stub

In General:


Matching Networks may consist of:

- * lumped elements, or:
- * TL sections,

Placed in

- * series or
- * parallel.

2-11 Impedance Matching

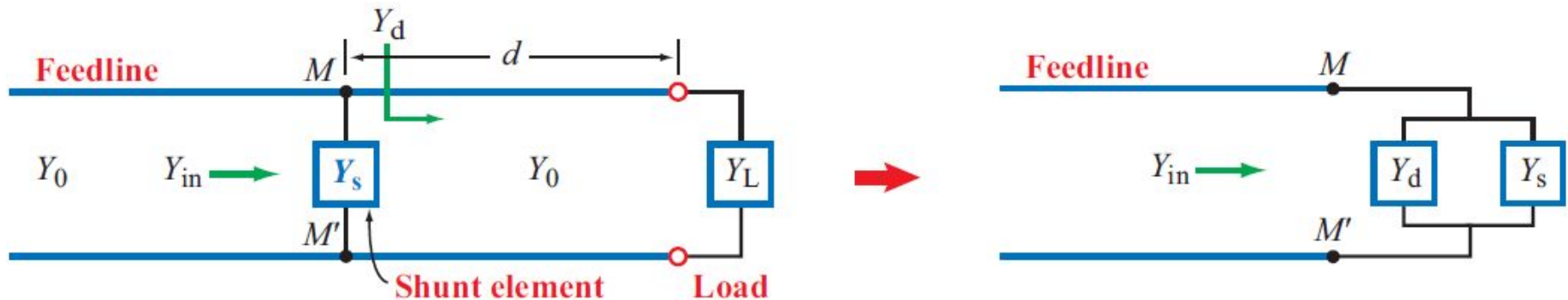

Lumped-Element matching using admittance ($Y=1/Z$)


Y_L transformed to Y_d by the length of transmission line

$$Y_{in} = Y_d + Y_s$$

$$Y_{in} = (G_d + jB_d) + jB_s$$
$$= G_d + j(B_d + B_s).$$

Y_s only needs to be reactive, to cancel the reactive part of Y_d

2-11 Impedance Matching

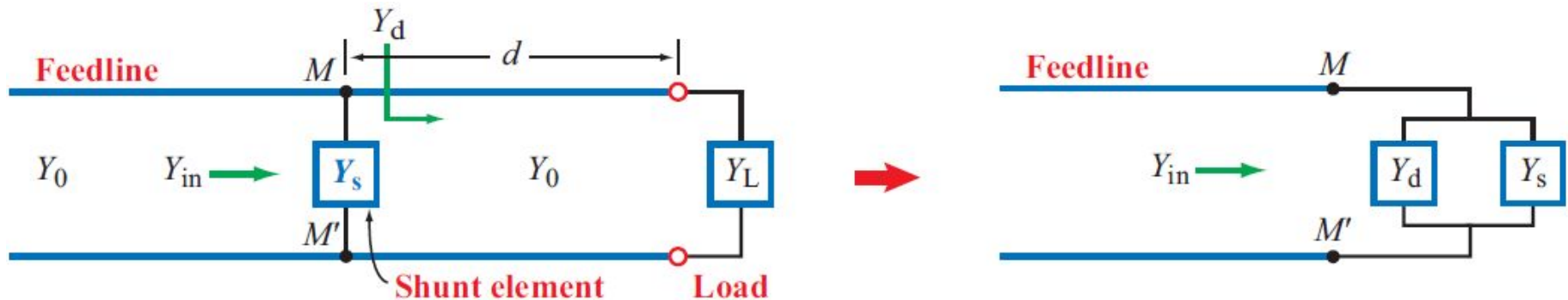

Lumped-Element matching using admittance


Normalized:

$$y_{in} = g_d + j(b_d + b_s).$$

$$g_d = 1 \quad (\text{real-part condition}),$$

$$b_s = -b_d \quad (\text{imaginary-part condition}).$$

2-11 Impedance Matching

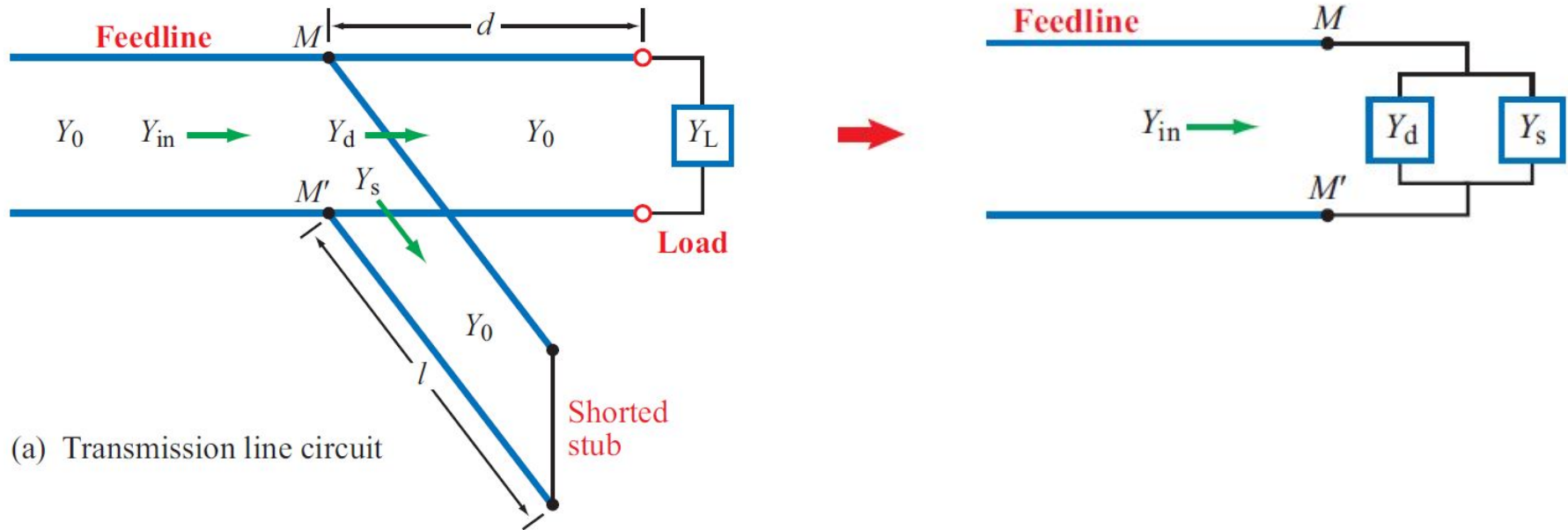


Single-stub Matching:

Can use the same process as we did for lumped-element matching.

Except: transform y_s to a length of shorted transmission line instead of a lumped element.

Example 2-13 Lumped-Element Matching

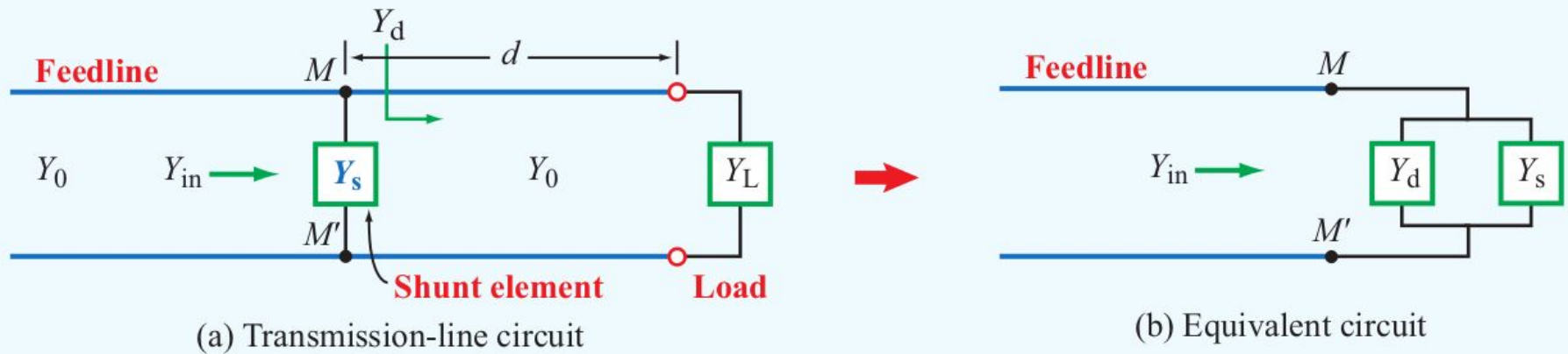


Given: Lossless transmission line, $Z_0 = 50 \Omega$

Load: $Z_L = 25 - j 50 \Omega$, $f = 100 \text{ MHz}$

Find: Element *type* and *value* and d to match the load.


Example 2-13 Lumped-Element Matching

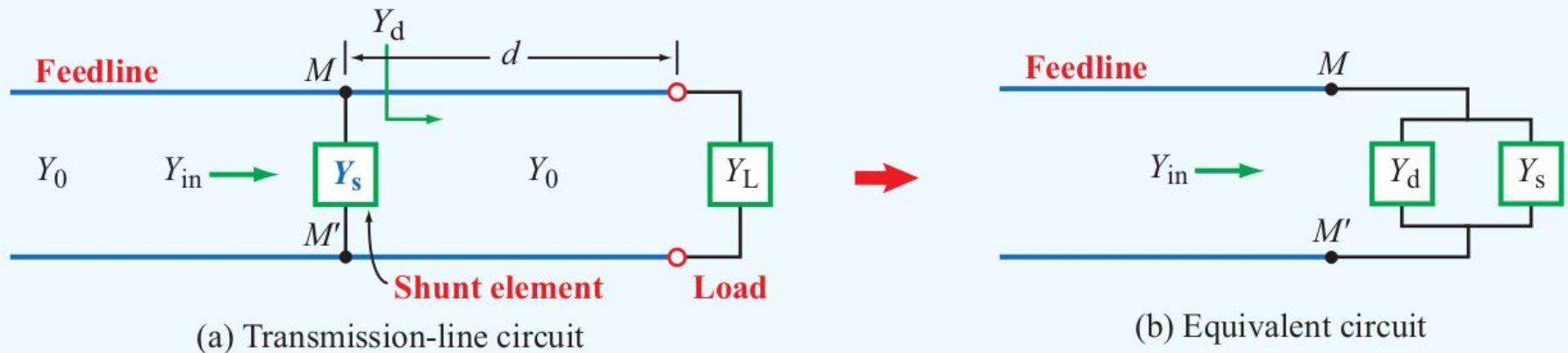

Strategy:

1. choose d to get real-part of $Z_{\text{equiv}} = 50 \Omega$.
will still have non-zero imag-part
2. then choose element to cancel that imag-part.
will be an inductor or a capacitor

Example 2-13 Lumped-Element Matching

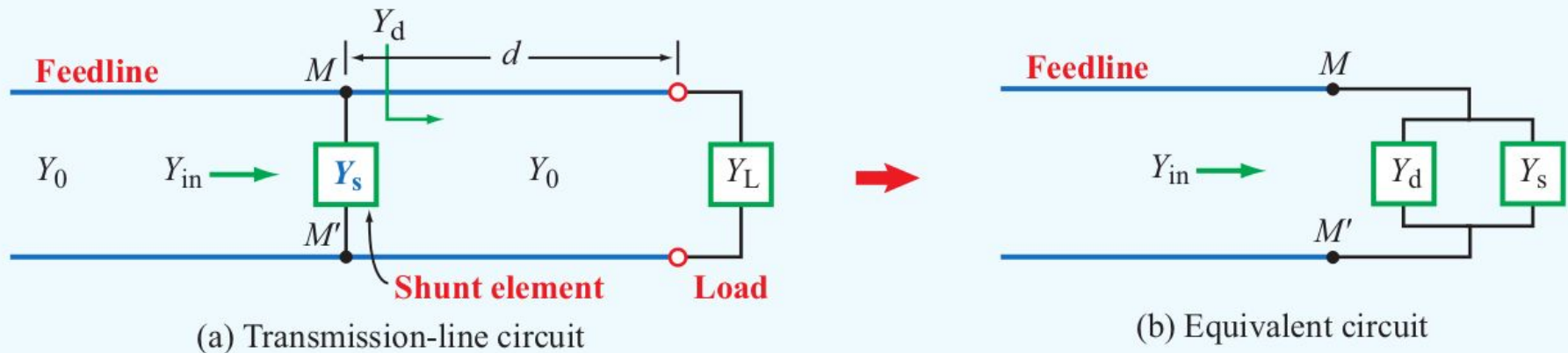


Solution:

step1: normalize the load and plot on Smith Chart

$$z_L = Z_L / Z_0 = (25 - j 50) / 50 = 0.5 - j1$$


step2: draw the VSWR circle thru z_L

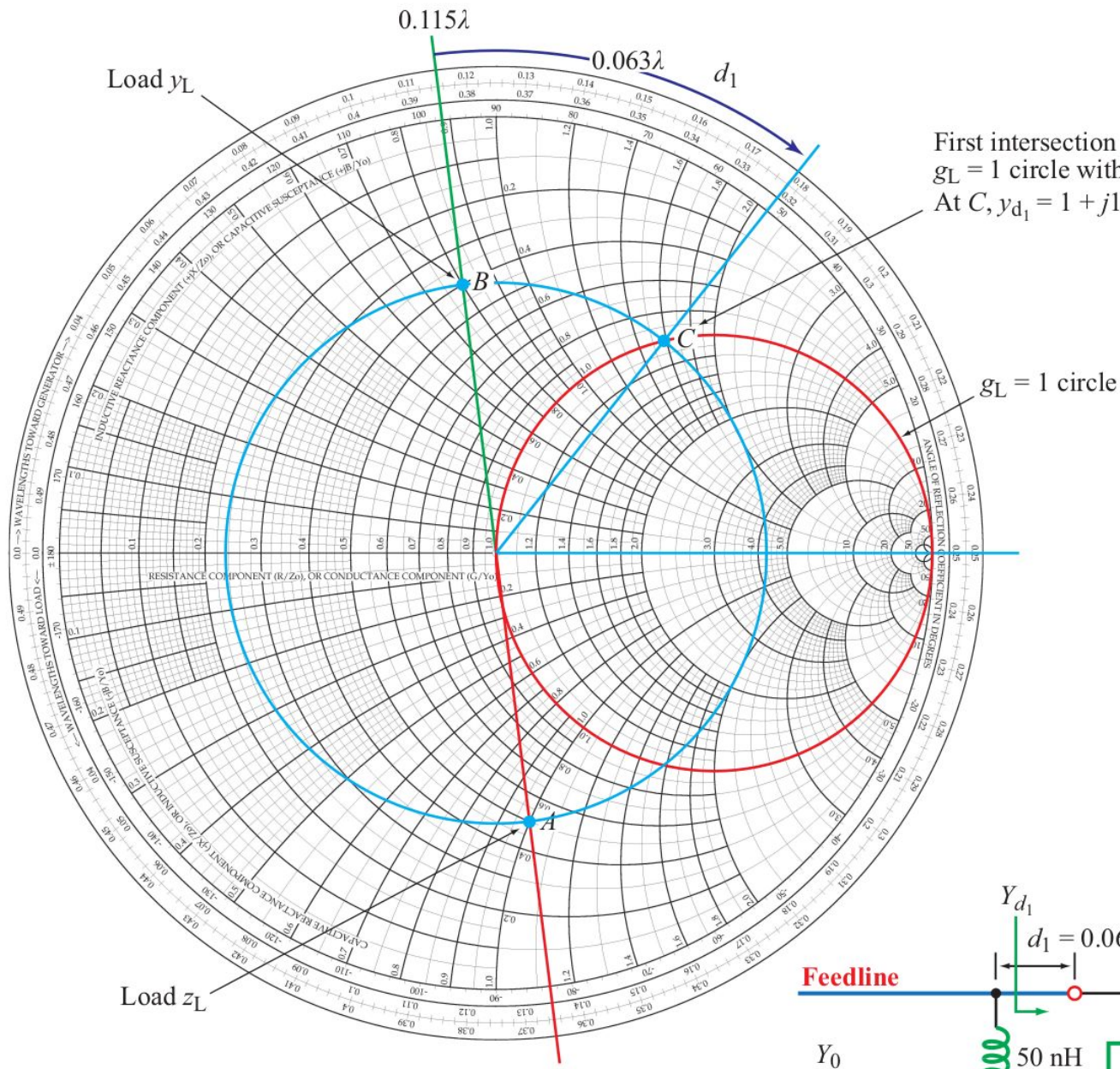step3: locate y_L across the circle from z_L




First intersection of $g_L = 1$ circle with SWR circle. At C, $y_{d1} = 1 + j1.58$.

$g_L = 1$ circle

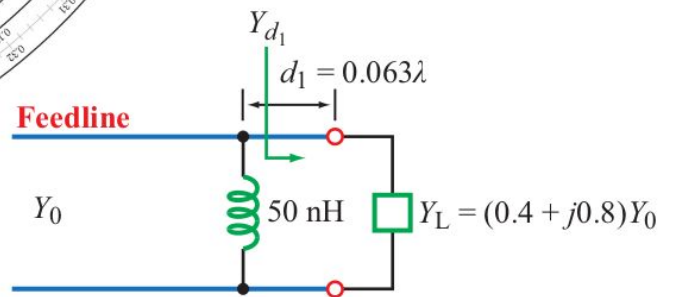

First solution

Example 2-13 Lumped-Element Matching

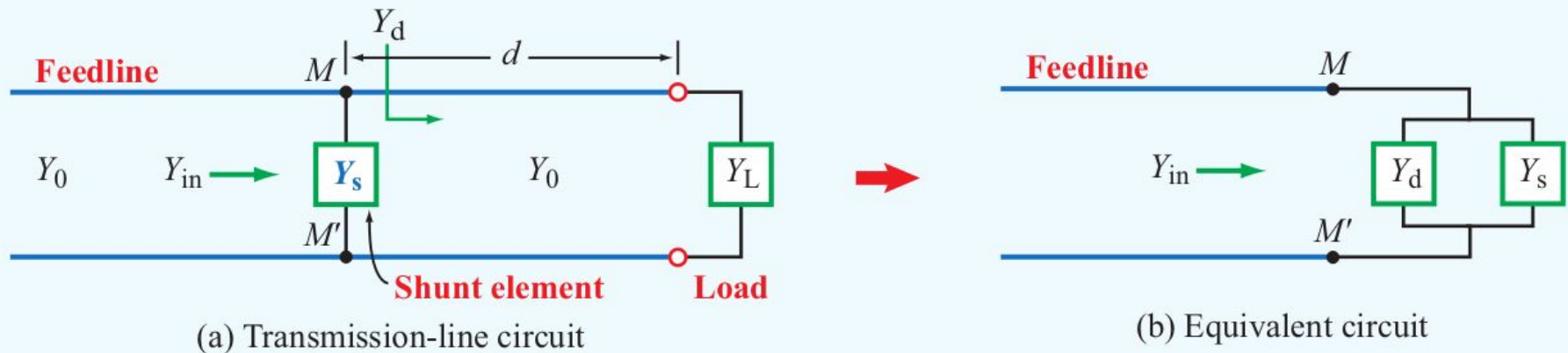


Solution:

step4: read the value of y_L from the chart:


$$y_L = 0.4 + j0.8$$

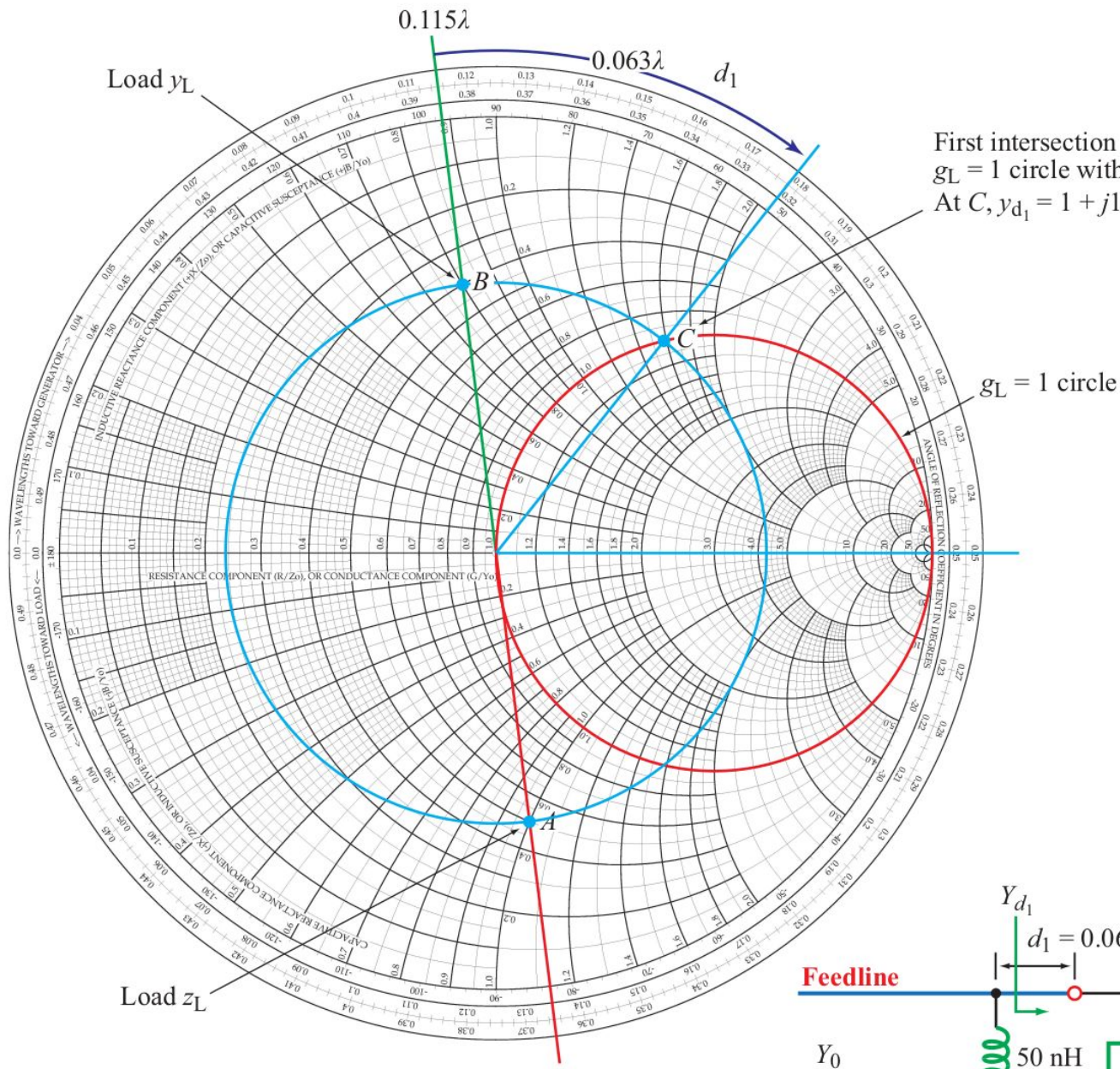step5: draw radial line thru y_L , read off WTG: 0.115λ




First intersection of $g_L = 1$ circle with SWR circle. At C, $y_{d1} = 1 + j1.58$.

$g_L = 1$ circle

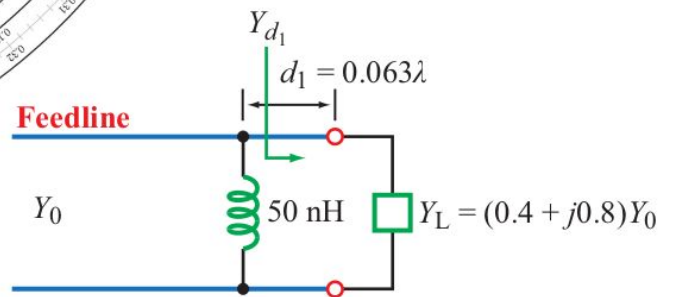

First solution



Example 2-13 Lumped-Element Matching

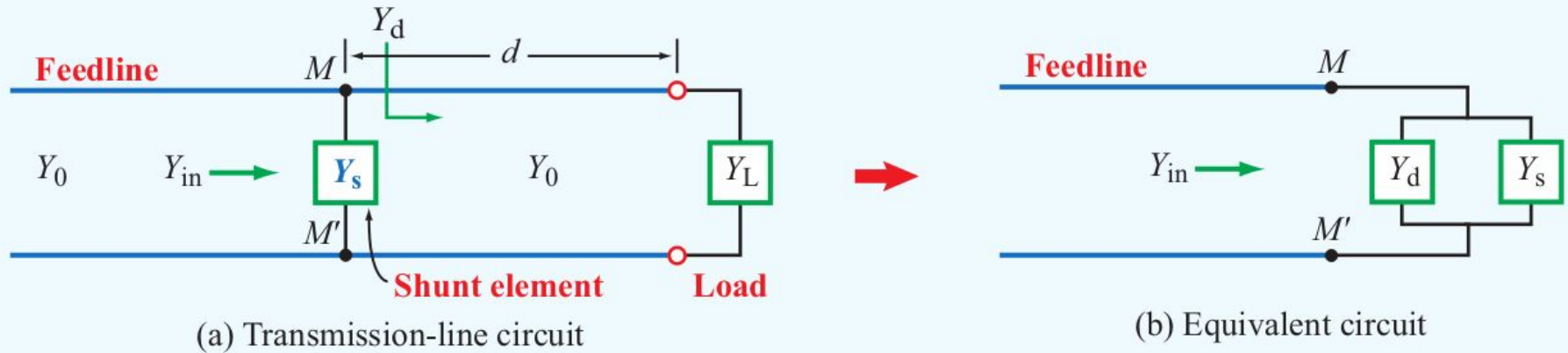

Solution:


step6: move toward generator until $\text{Re}.y_d = 1$

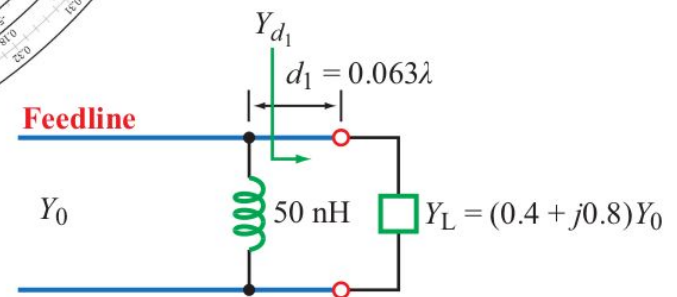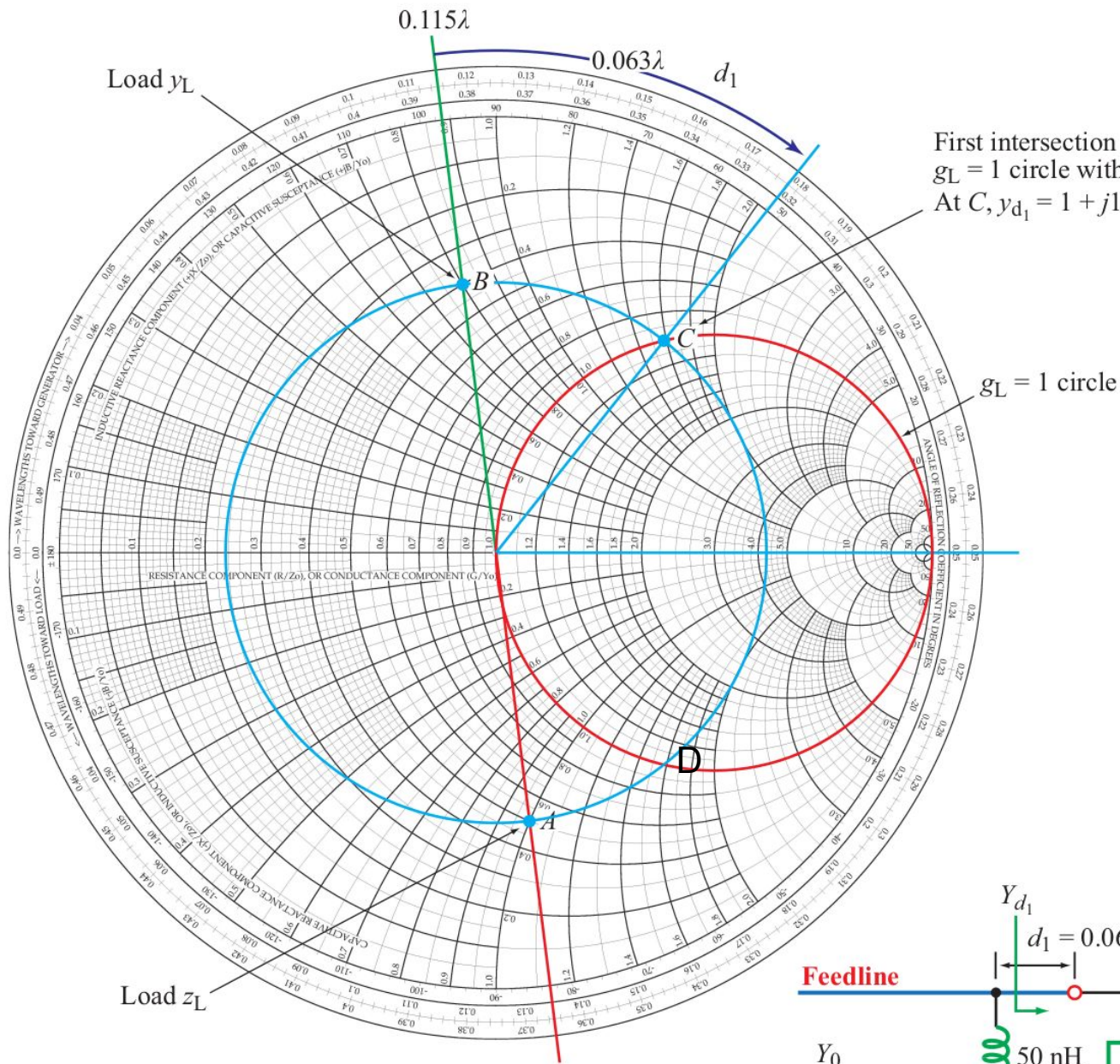note: there are 2 values of d where this is true: C, D



First solution

Example 2-13 Lumped-Element Matching

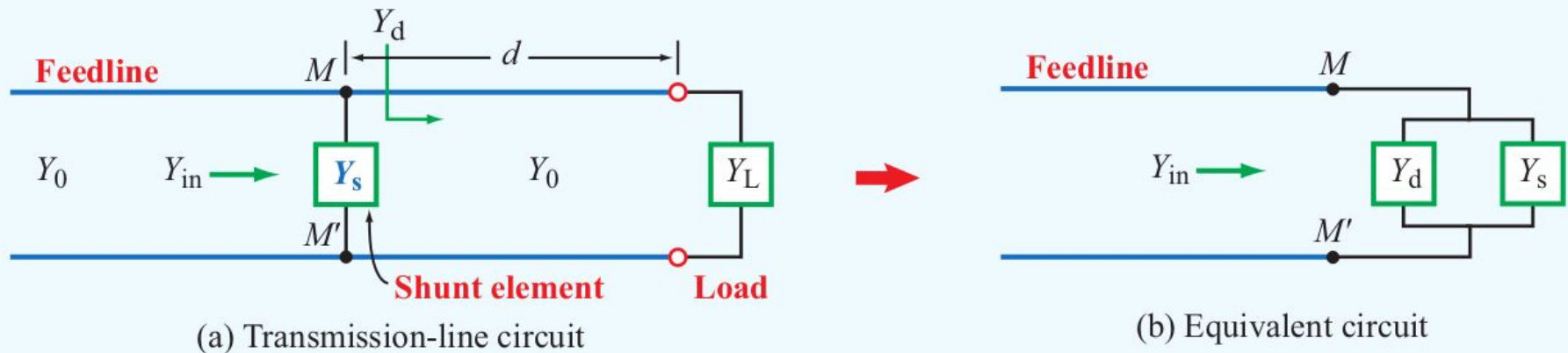

Solution:


step7: For point C, read off value of y_d :

$$y_d = 1 + j 1.58$$


step8: draw radial line thru y_d : WTG=0.178 λ

so distance moved is 0.178 λ - 0.115 λ

$$d = 0.063\lambda$$

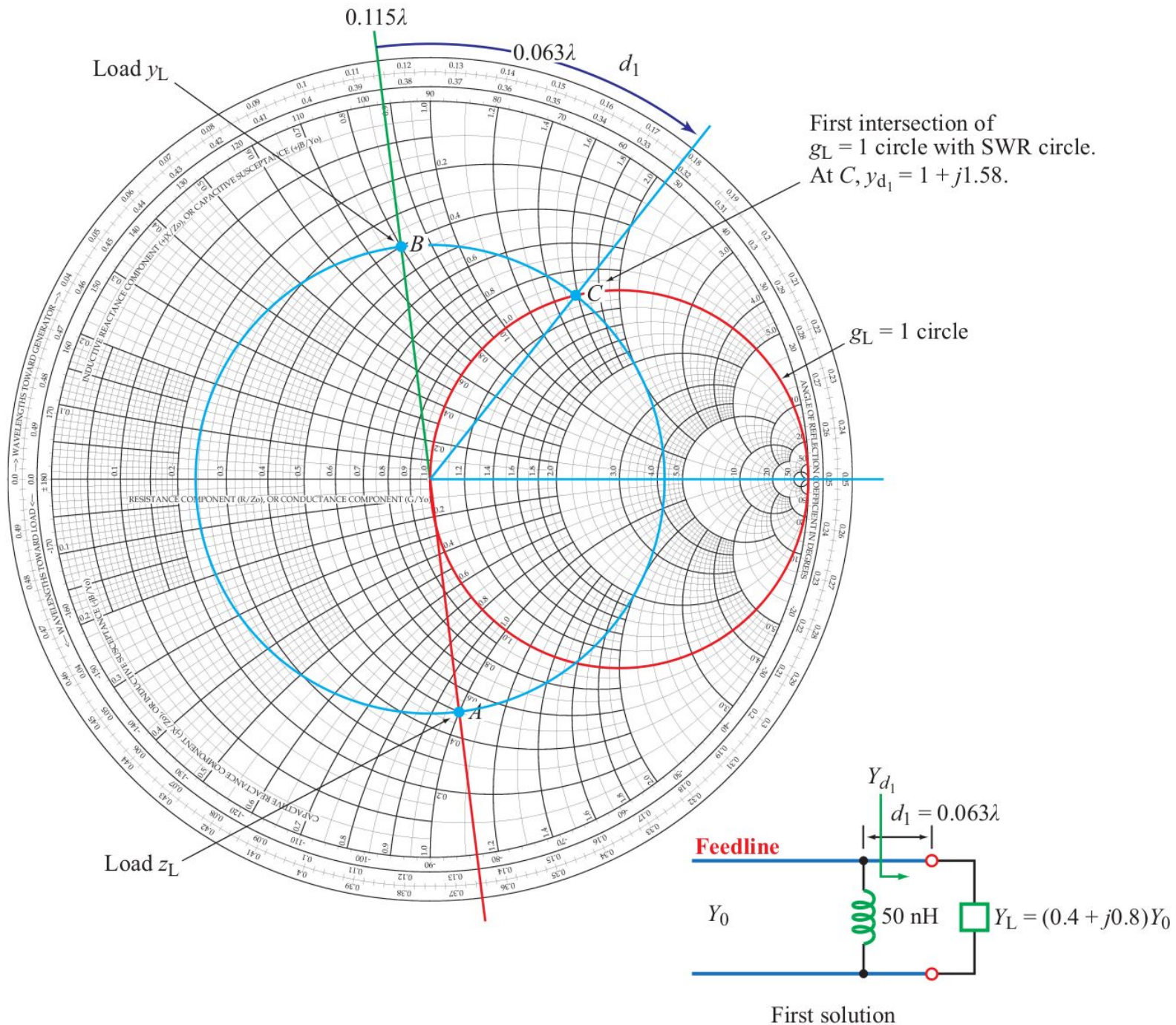

Example 2-13 Lumped-Element Matching

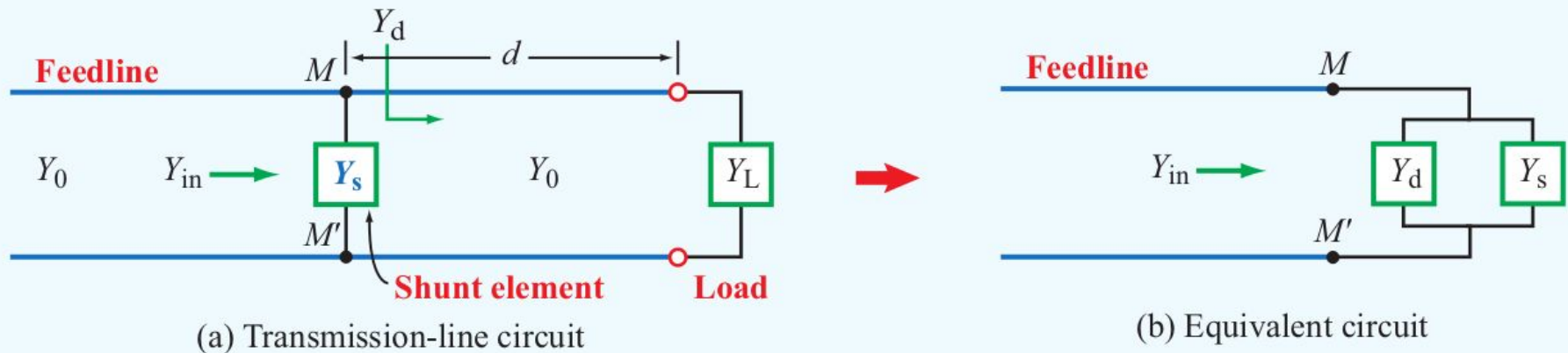

Solution:


step9: Since the line "sees" the parallel combination of the d -offset load and the lumped element:

$$y_{in} = y_d + y_s$$

we want:

$$1 = 1 + j 1.58 + y_s \quad \text{or:} \quad y_s = -j 1.58$$

Example 2-13 Lumped-Element Matching

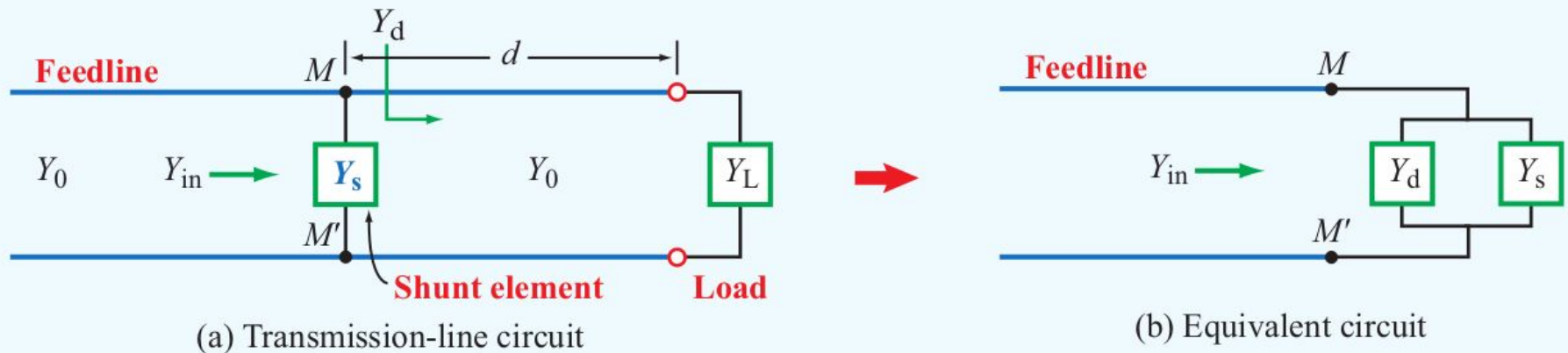

Solution:


step10: Normalized impedance of lumped element is therefore:

$$z_s = 1 / y_s = 1 / -j 1.58 = j / 1.58 = j 0.633$$

so:

$$Z_s = z_s Z_0 = (j 0.633) 50 \Omega = j 31.65 \Omega$$

Example 2-13 Lumped-Element Matching

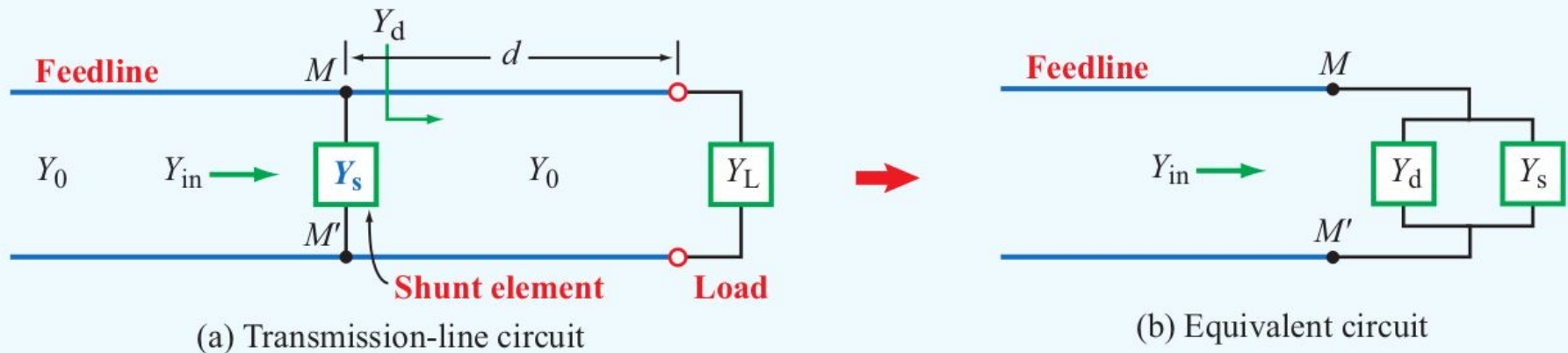


Solution:

step11: Both inductors and capacitors have imaginary impedances. How to choose?

Since: $Z_C = 1/(j\omega C) = -j/(\omega C)$ and $Z_L = j\omega L$

We must choose an inductor since we need a positive imaginary part.

Example 2-13 Lumped-Element Matching

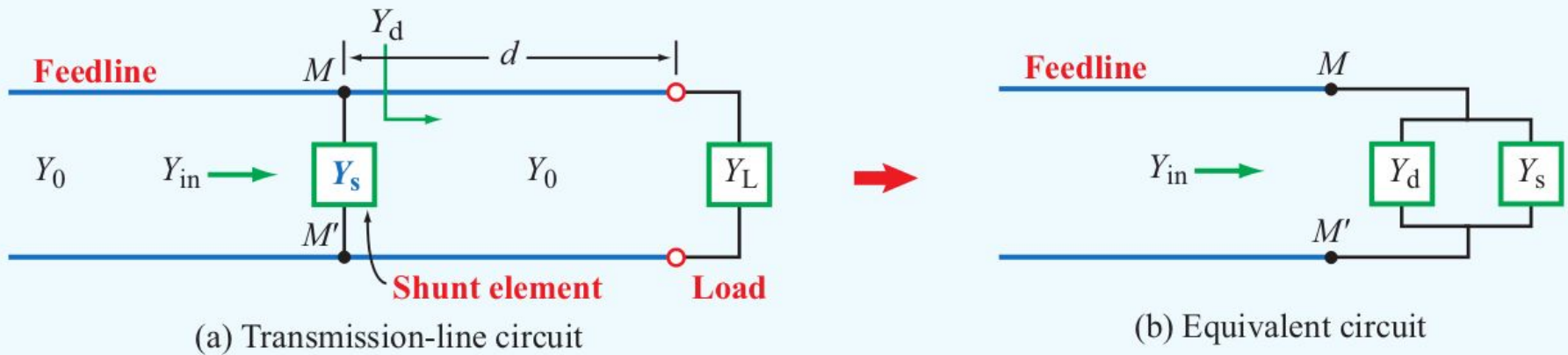

Solution:


step 11: Choose an inductor: $Z_L = j\omega L$

$$Z_S = j 31.65 \Omega = j\omega L$$

so:

$$L = 31.65 \Omega / \omega = 31.65 \Omega / (2\pi f)$$

Example 2-13 Lumped-Element Matching

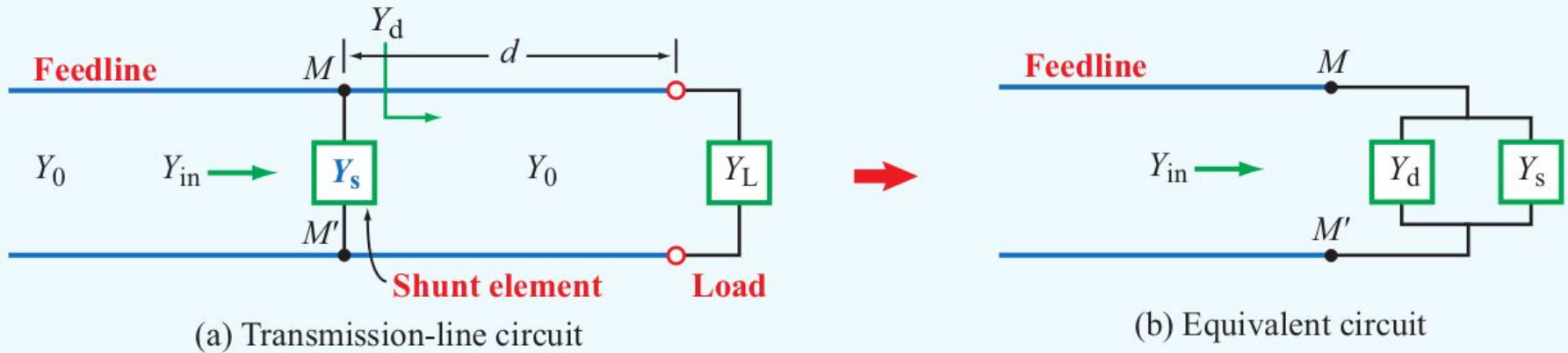

Solution:


step11: $L = 31.65\Omega / (2\pi f)$

$$L = 31.65\Omega / (2\pi (100 \times 10^6 \text{ Hz}))$$

$$L = 5 \times 10^{-8} \text{ H}$$

$$L = 50 \text{ nH}$$

Example 2-13 Lumped-Element Matching

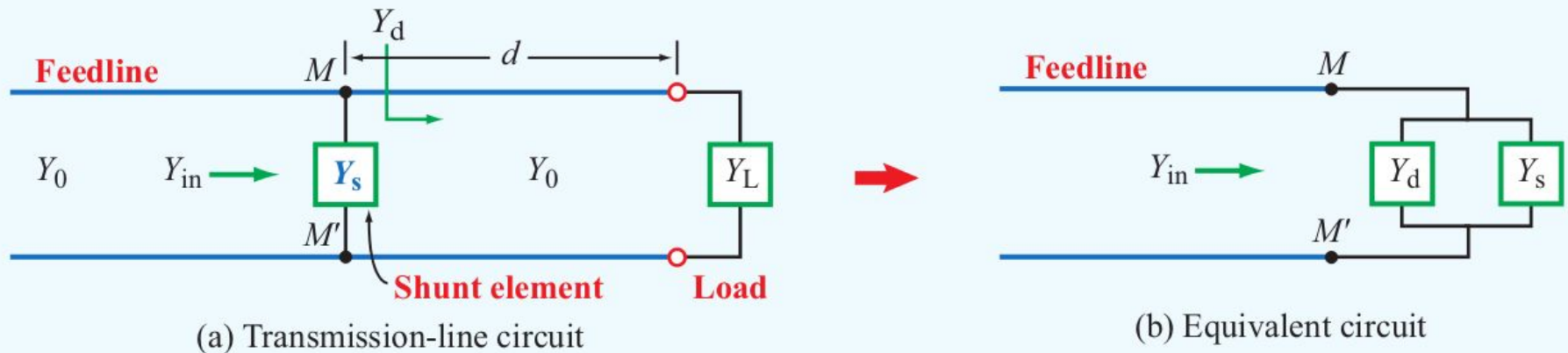

Solution: Do again, choosing point D:


step7: For point D, read off value of y_d :

$$y_d = 1 - j 1.58$$


step8: draw radial line thru y_d : WTG=0.322 λ

so distance moved is 0.322 λ - 0.115 λ


$$d = 0.207\lambda$$

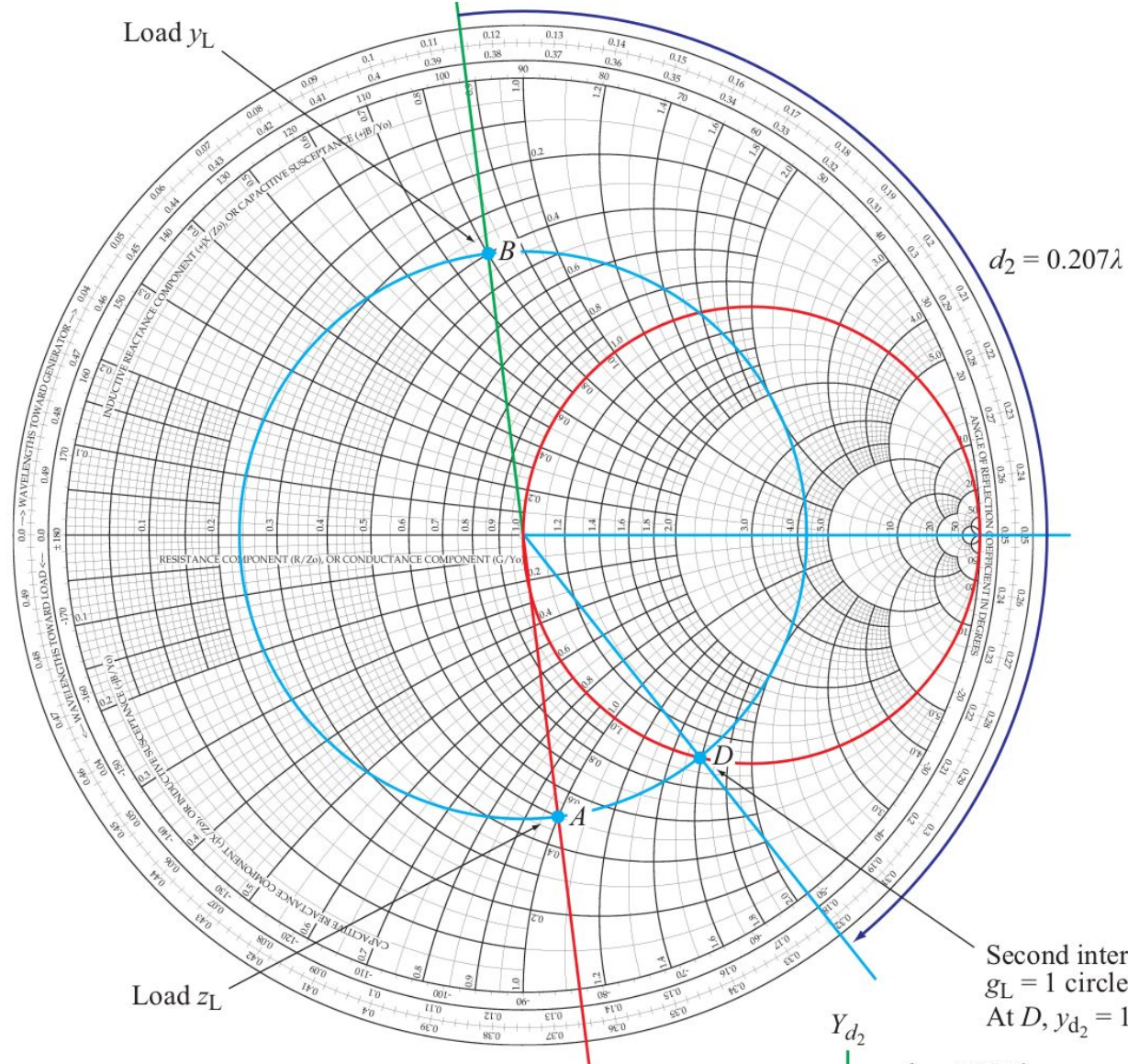

Second intersection of $g_L = 1$ circle with SWR circle.
At D , $y_{d_2} = 1 - j1.58$.

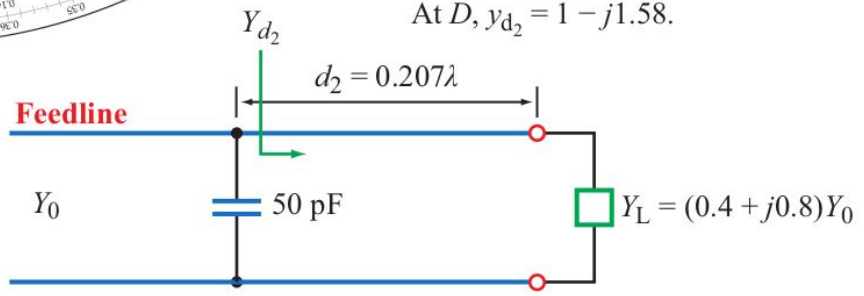

Example 2-13 Lumped-Element Matching

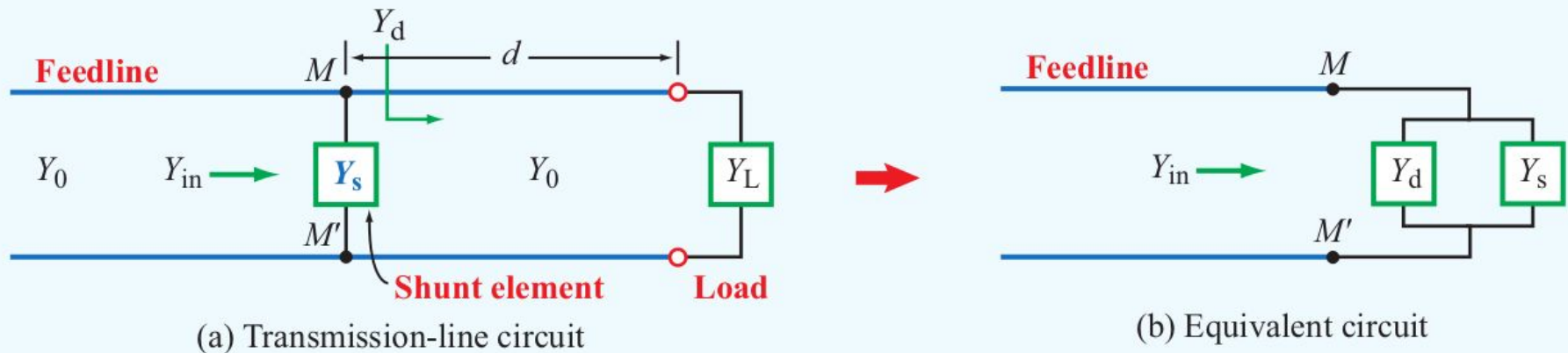

Solution:


step9: Since the line sees the parallel combination of the d -offset load and the lumped element:

$$y_{in} = y_d + y_s$$

we want:

$$1 = 1 - j 1.58 + y_s \quad \text{or:} \quad y_s = +j 1.58$$

Example 2-13 Lumped-Element Matching

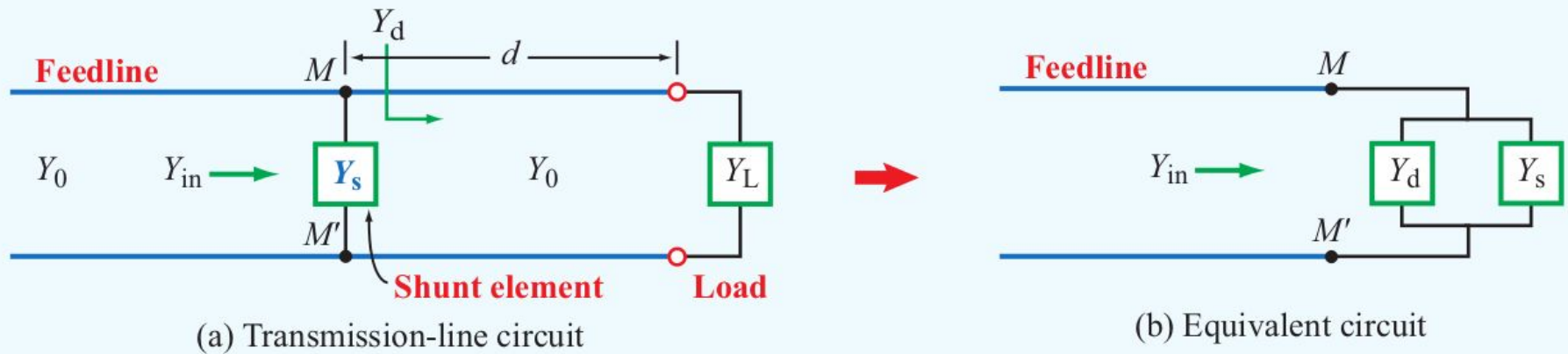

Solution:


step10: Normalized impedance of lumped element is therefore:

$$z_s = 1 / y_s = 1 / j 1.58 = j / 1.58 = -j 0.633$$

so:

$$Z_s = z_s Z_0 = (-j 0.633) 50 \Omega = -j 31.65 \Omega$$

Example 2-13 Lumped-Element Matching

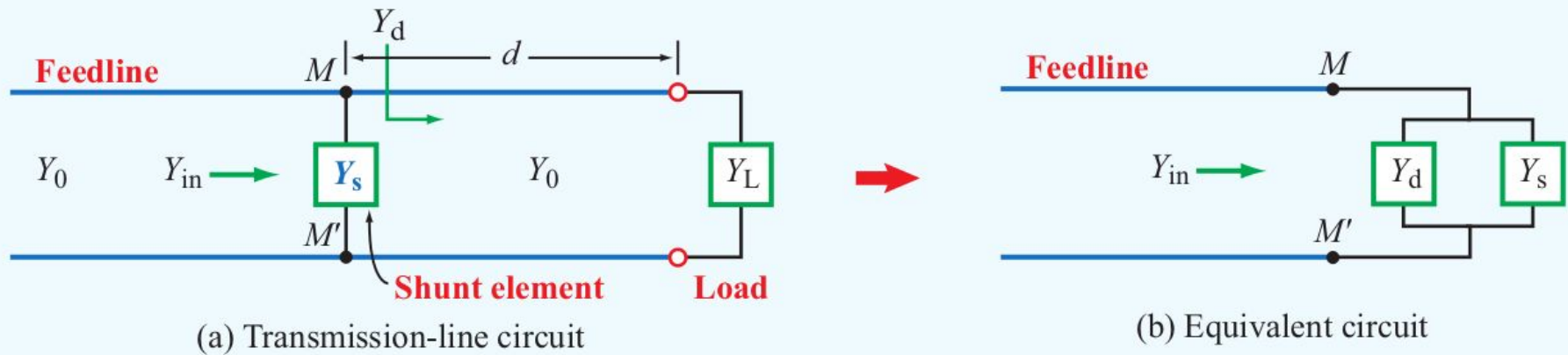


Solution:

step11: Both inductors and capacitors have imaginary impedances. How to choose?

Since: $Z_C = 1 / (j\omega C) = -j / (\omega C)$ and $Z_L = j\omega L$

We must choose an capacitor since we need a negative imaginary part.

Example 2-13 Lumped-Element Matching

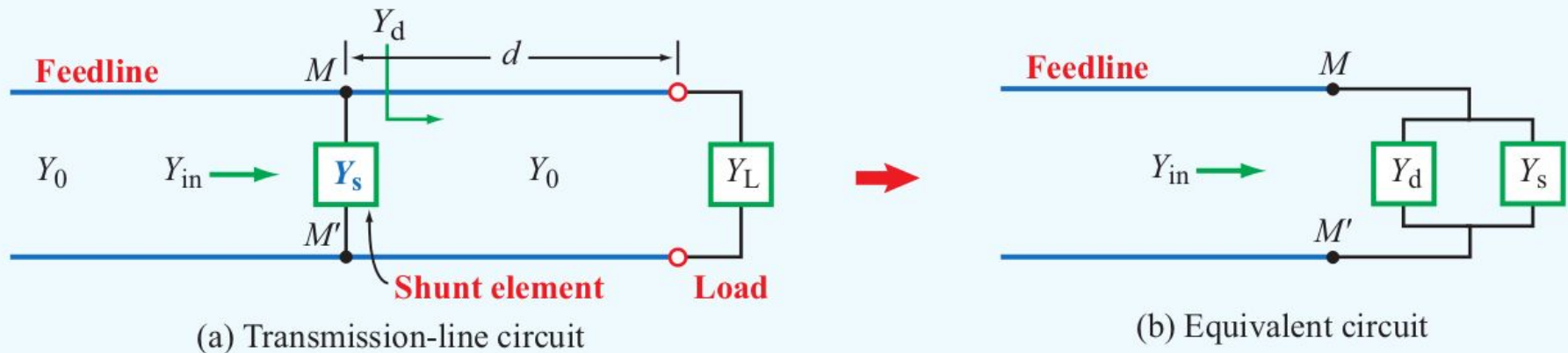

Solution:

step11: Choose a capacitor: $Z_C = -j / (\omega C)$


$$Z_S = -j 31.65 \Omega = -j / \omega C$$

so:

$$C = 1 / (\omega 31.65 \Omega)$$

$$= 1 / (2\pi (100 \times 10^6 \text{ Hz}) (31.65 \Omega))$$

Example 2-13 Lumped-Element Matching

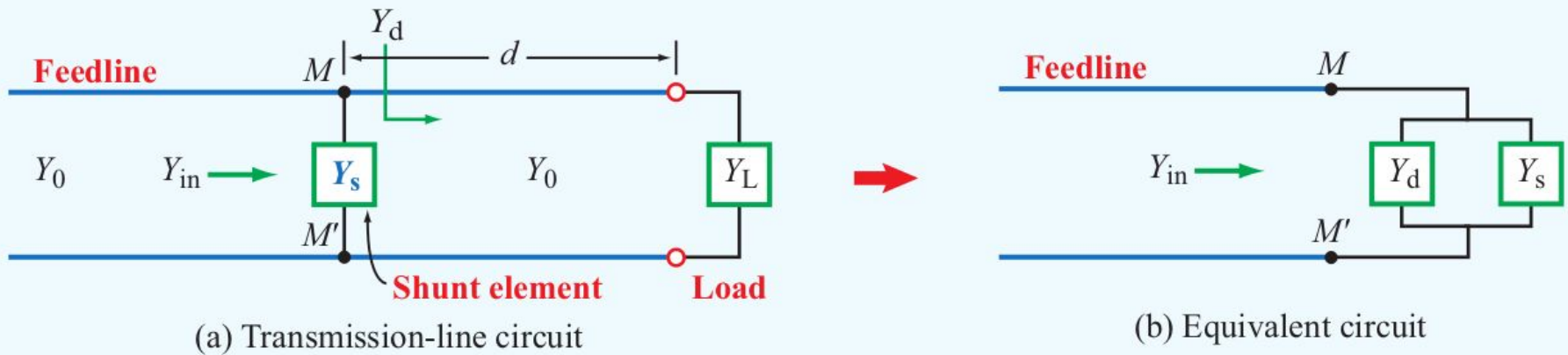


Solution:

step11: $C = 1 / (2\pi (100 \times 10^6 \text{ Hz}) (31.65 \Omega))$


$$C = 50 \times 10^{-12} \text{ F}$$

$$C = 50 \text{ pF}$$

Example 2-13 Lumped-Element Matching

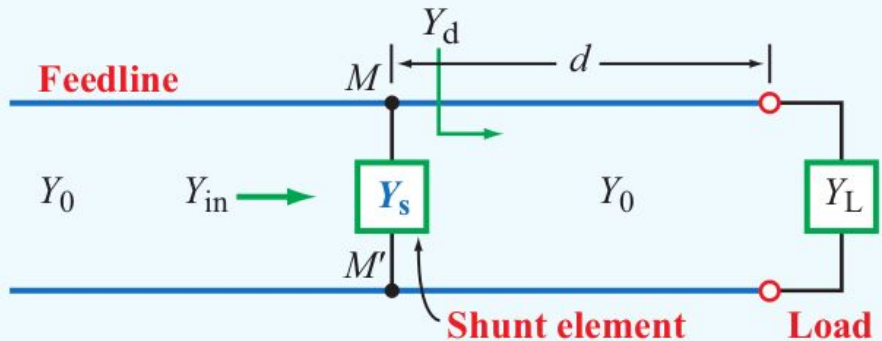

(a) Transmission-line circuit

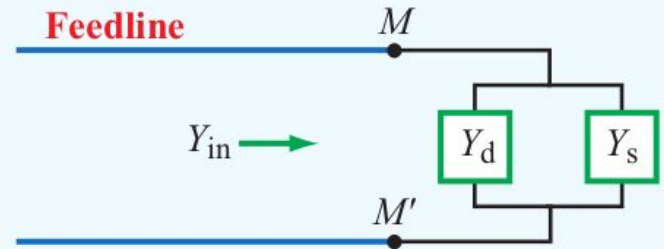

(b) Equivalent circuit

Summary:

at a distance from load of:

$$d = 0.207\lambda$$

place a capacitor in parallel with value:

$$C = 50 \text{ pF}$$

OR:

at a distance from load of:

$$d = 0.063\lambda$$

place an inductor in parallel, with value:

$$L = 50 \text{ nH}$$

2-1 1 Impedance Matching

Recall from before that a shorted transmission line can look like an inductor or a capacitor by just changing its length.

Chapter 2 Review

At its input, the short-circuited line appears like an inductor or a capacitor depending on the sign of





$$\tan \beta d$$

$$j\omega L_{\text{eq}} = jZ_0 \tan \beta l, \quad \text{if } \tan \beta l \geq 0$$

$$\text{if } \tan \beta l \geq 0$$

$$\frac{1}{j\omega C_{\text{eq}}} = jZ_0 \tan \beta l, \quad \text{if } \tan \beta l \leq 0$$

$$\text{if } \tan \beta l \leq 0$$

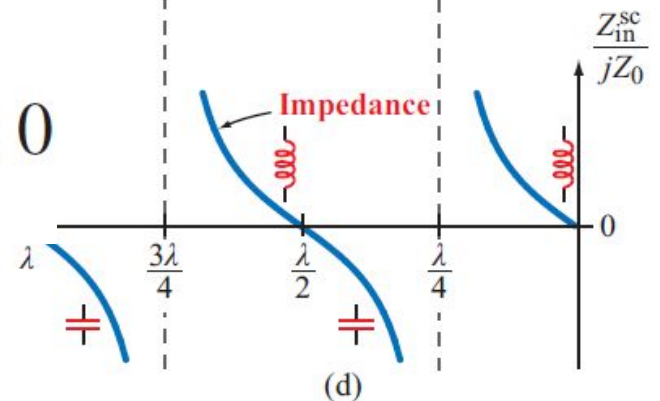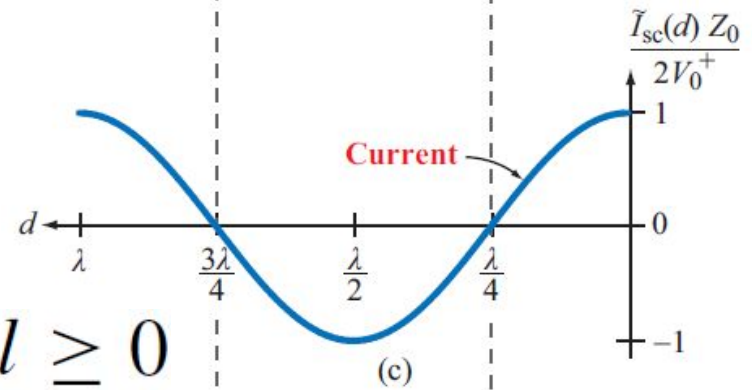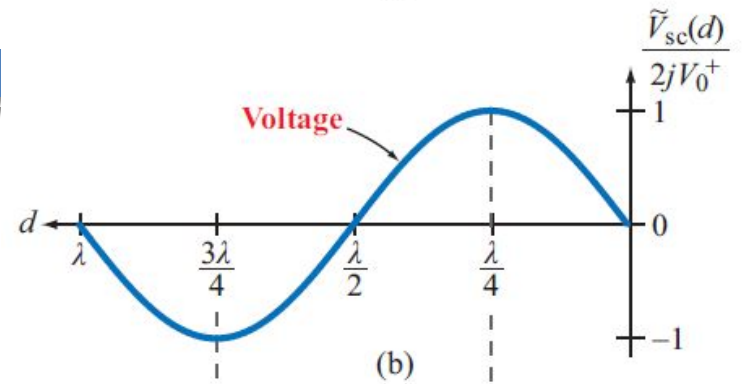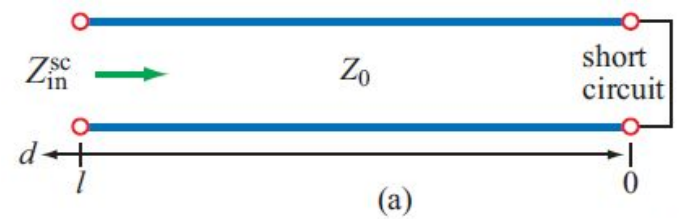


2-1 1 Impedance Matching



So let's re-do the matching problem from before, but use a shorted transmission-line piece instead of lumped-element.

This is called "Single-Stub Matching"


Example 2-14 Single-Stub Matching

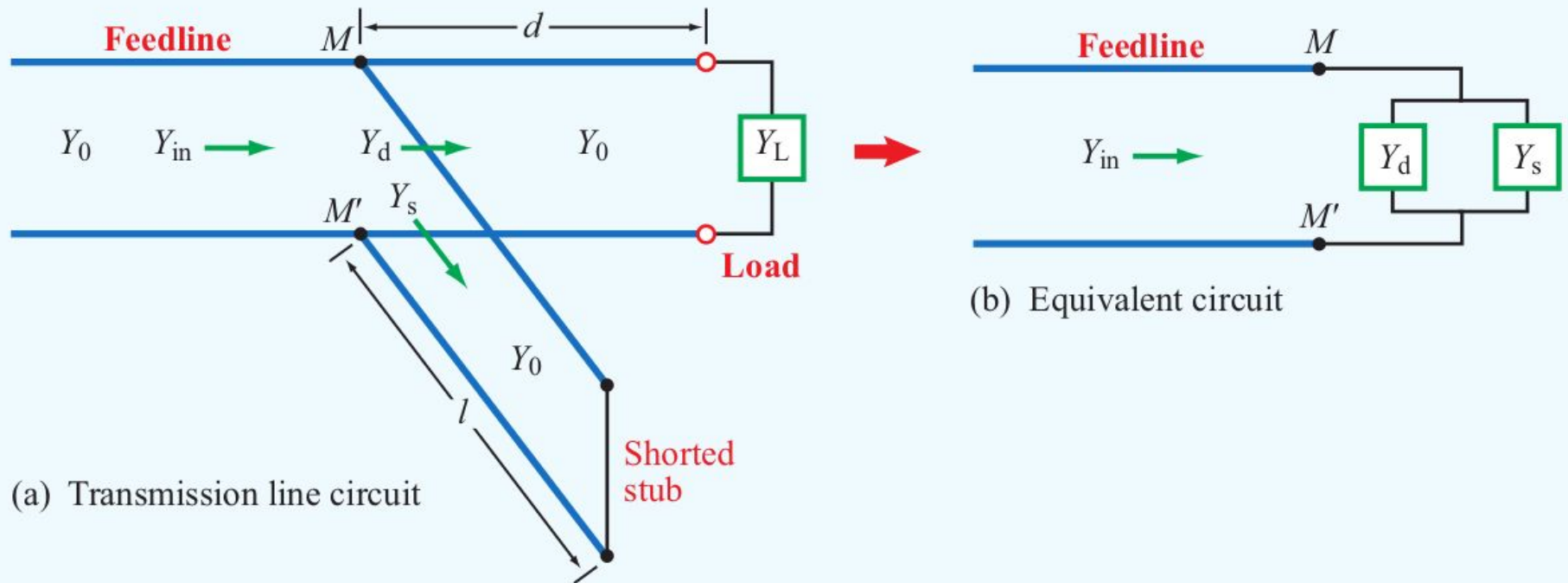

From Example 2-13 we had 2 solutions:


1. $d_1 = 0.063\lambda$, and $y_{s_1} = jb_{s_1} = -j1.58$,
2. $d_2 = 0.207\lambda$, and $y_{s_2} = jb_{s_2} = j1.58$.

Example 2-14 Single-Stub Matching

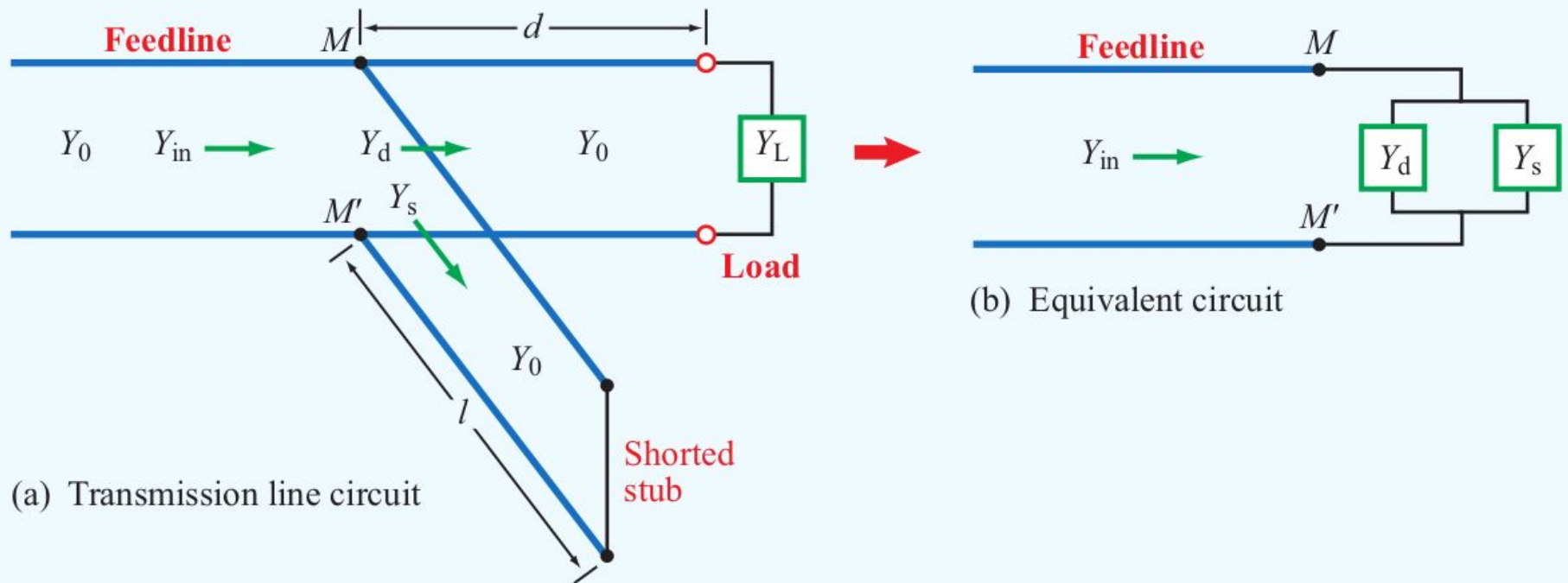



Need to create a stub of some length, such that it has whatever admittance we need.
Using the Smith Chart.

Example 2-14 Single-Stub Matching

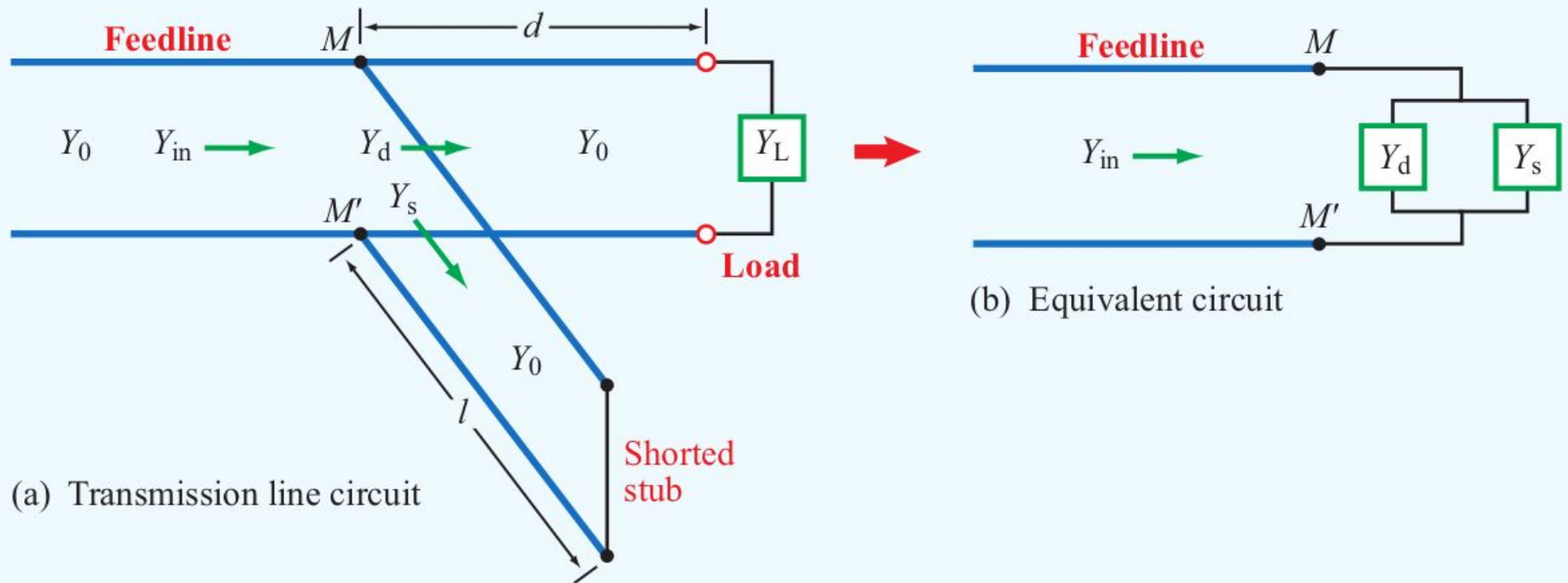


step1: stub load impedance is 0
hence stub load admittance is ∞
locate these on the Smith Chart:
0 impedance is real, far to the left

Example 2-14 Single-Stub Matching

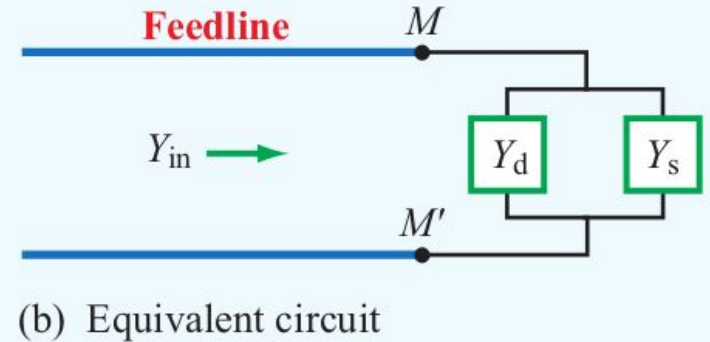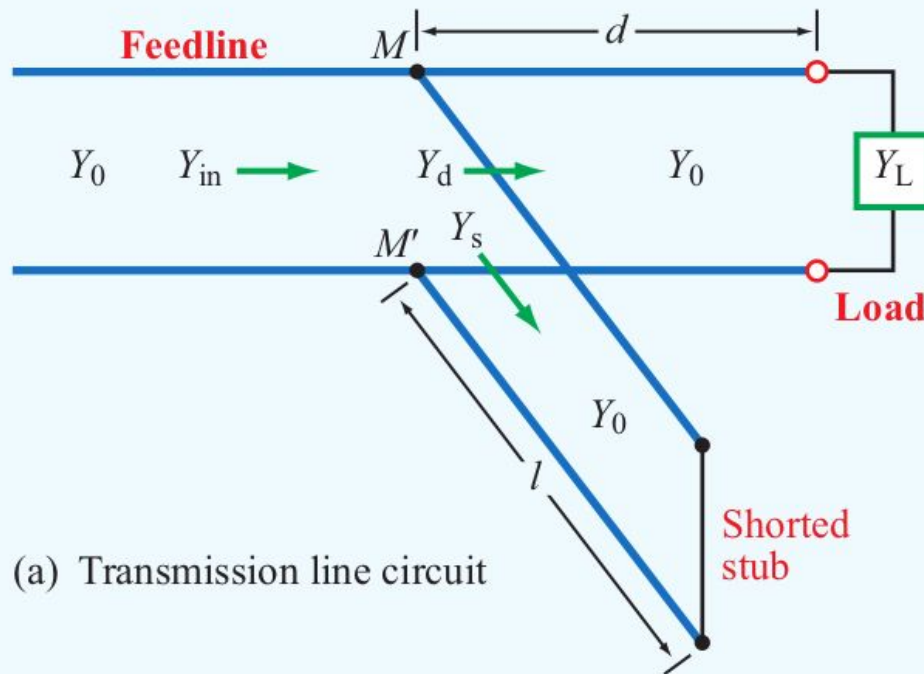

step2: ∞ admittance is real, all the way to the right.

Example 2-14 Single-Stub Matching


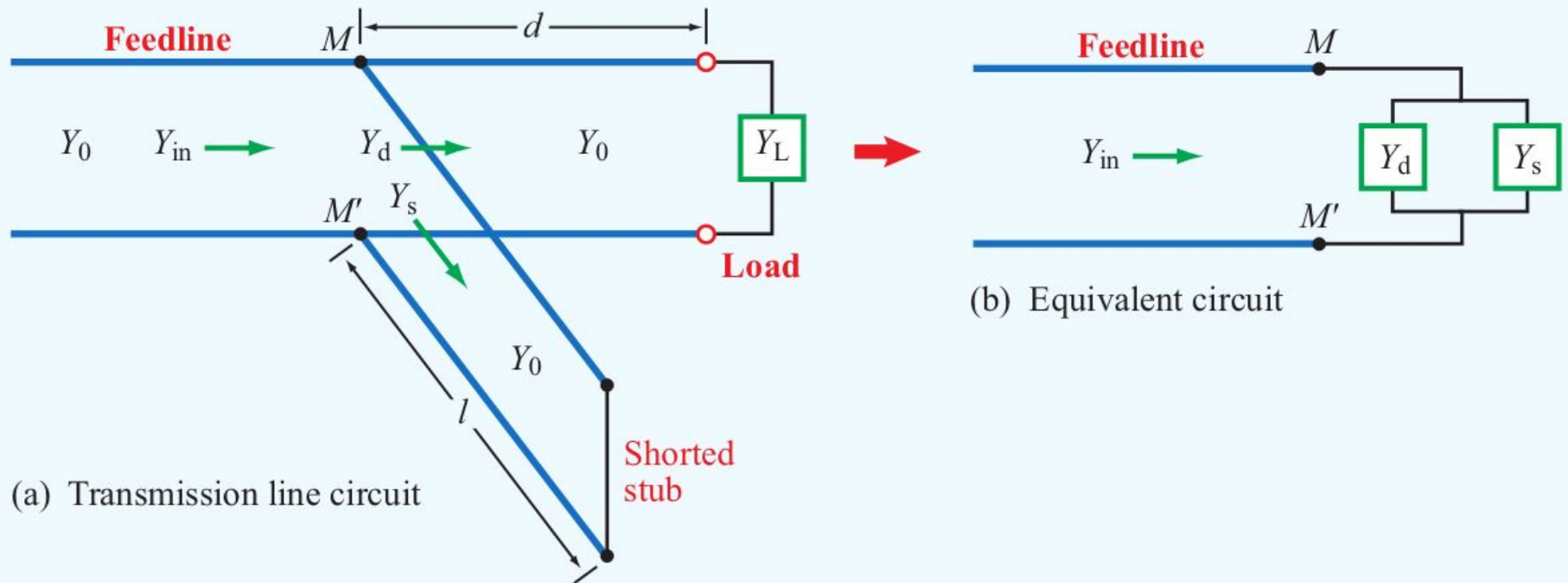


step3: find stub length: rotate toward generator until get desired admittance of $-j1.58$

step4: draw radial line to get WTG: 0.34λ



Impedance of short-circuit stub

Admittance of short-circuit stub

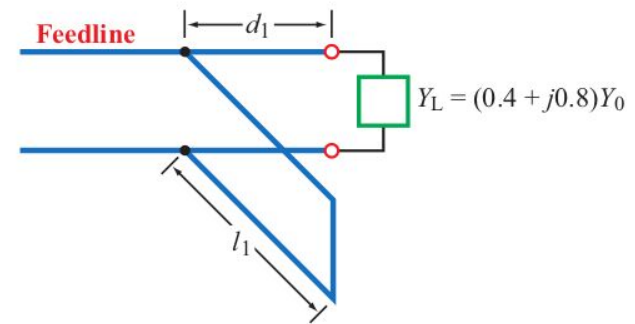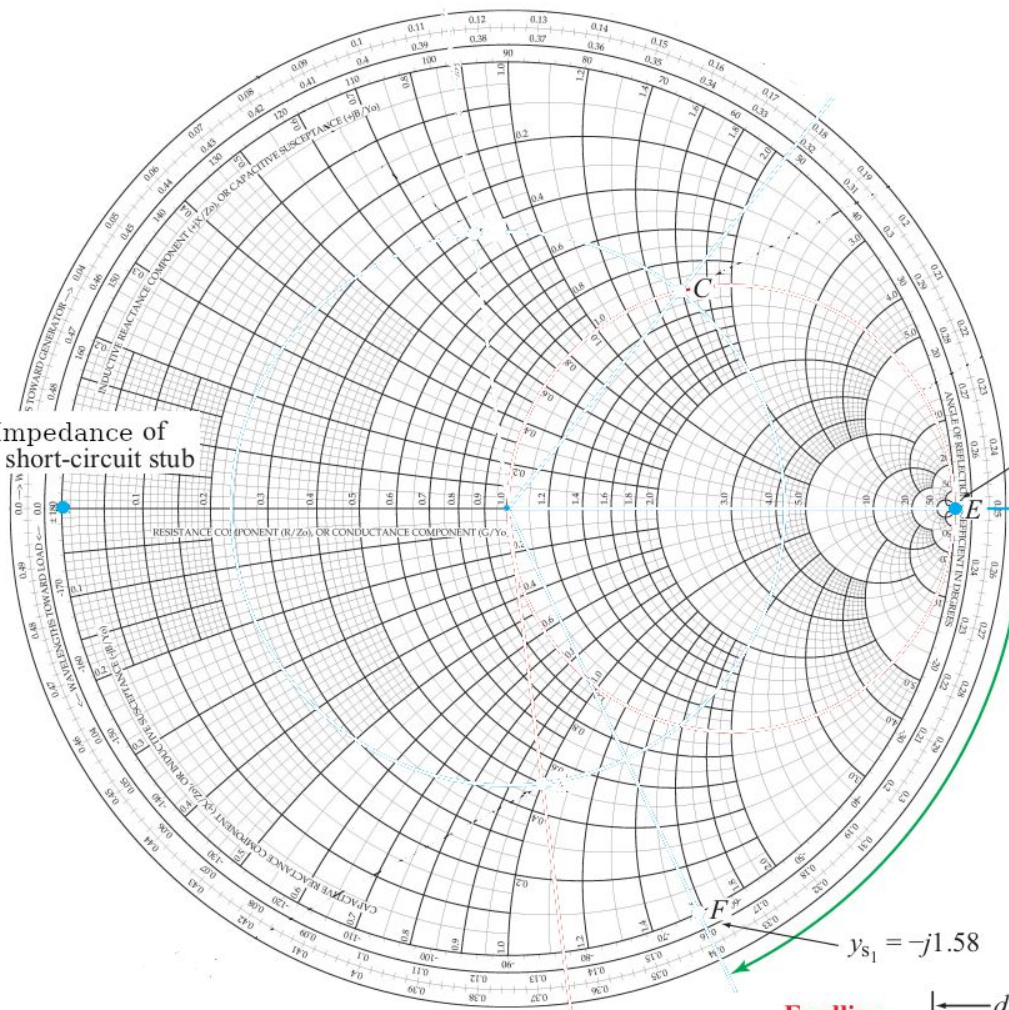


Impedance of short-circuit stub

Admittance of short-circuit stub

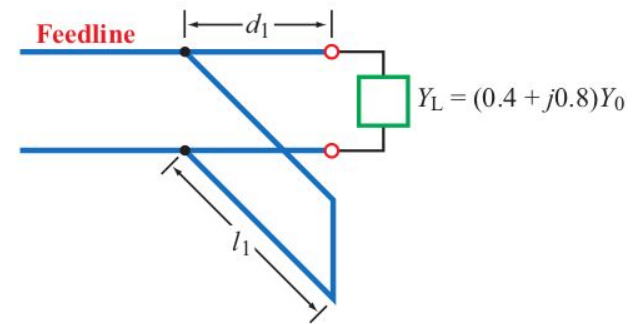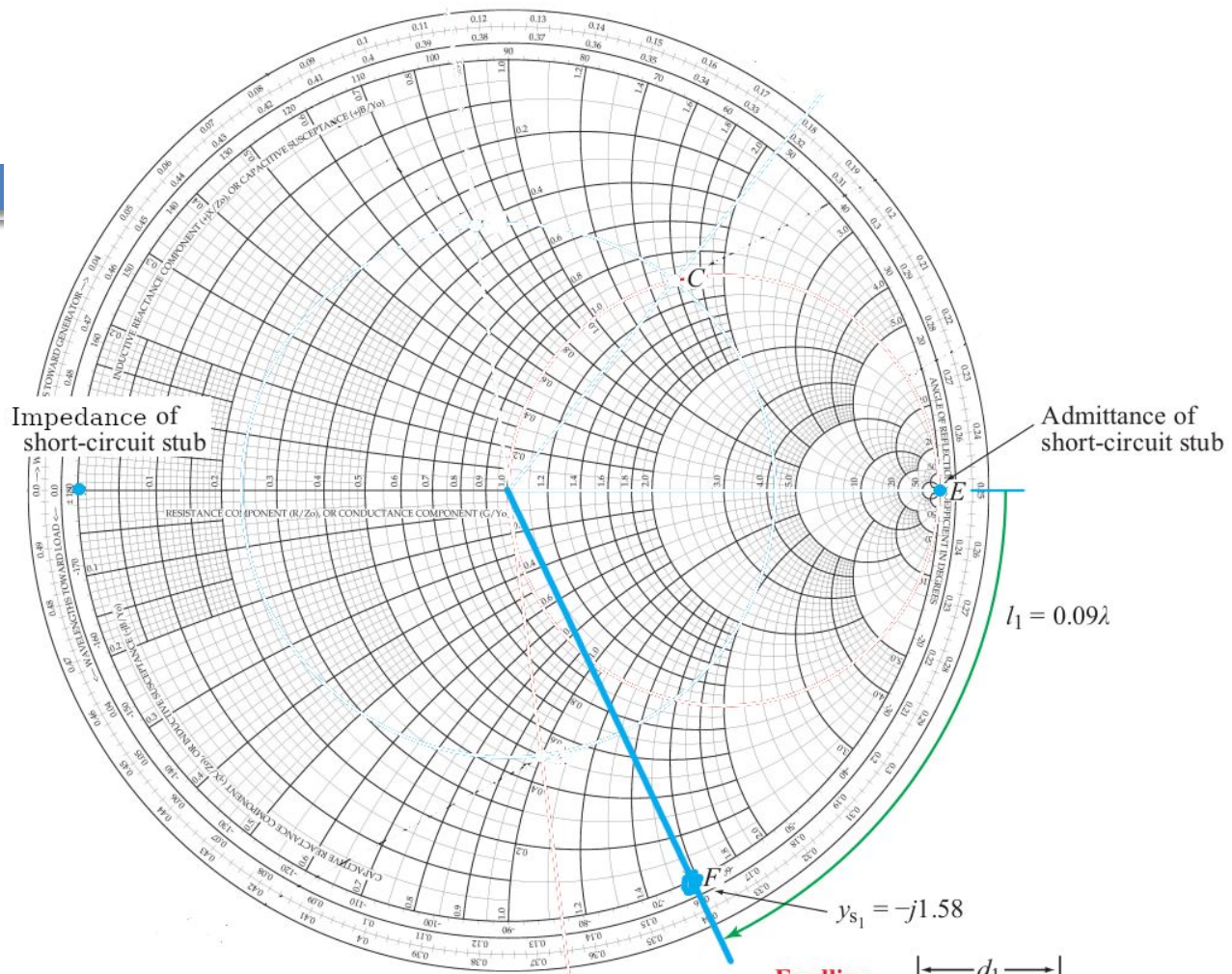


Example 2-14 Single-Stub Matching

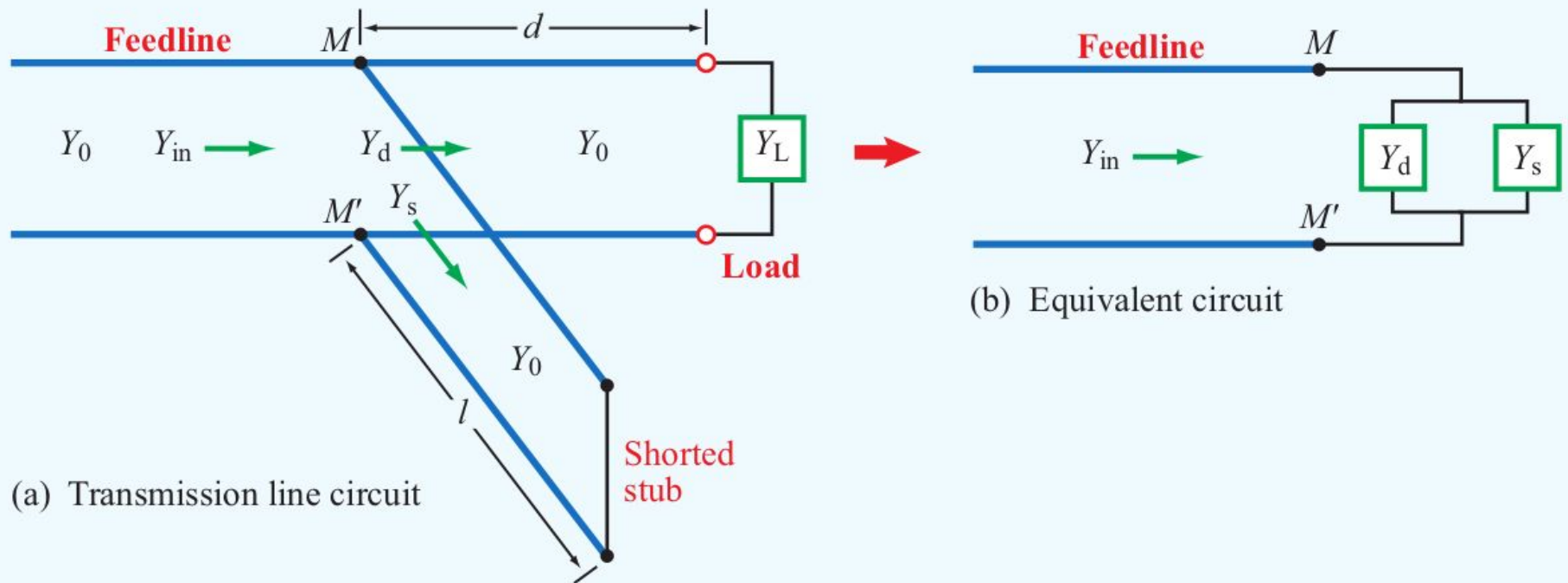

step5: find stub length: $0.34\lambda - 0.25\lambda = 0.09\lambda$



done for when use point C.
NEXT: point D

Example 2-14 Single-Stub Matching

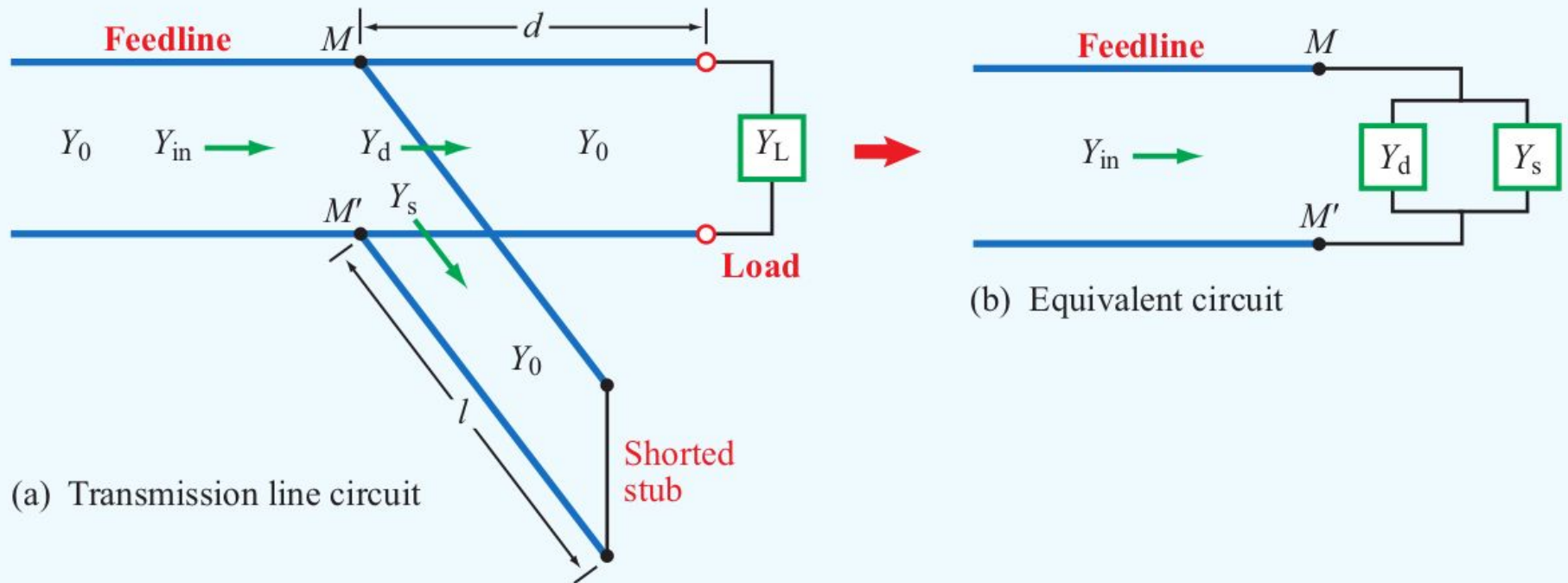


step1: stub load impedance is 0
hence stub load admittance is ∞
locate these on the Smith Chart:
0 impedance is real, far to the left

Example 2-14 Single-Stub Matching

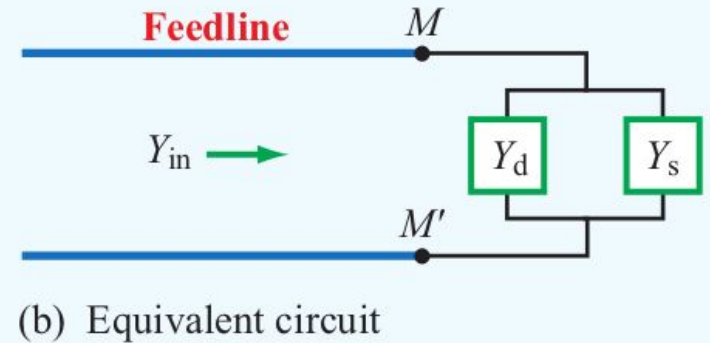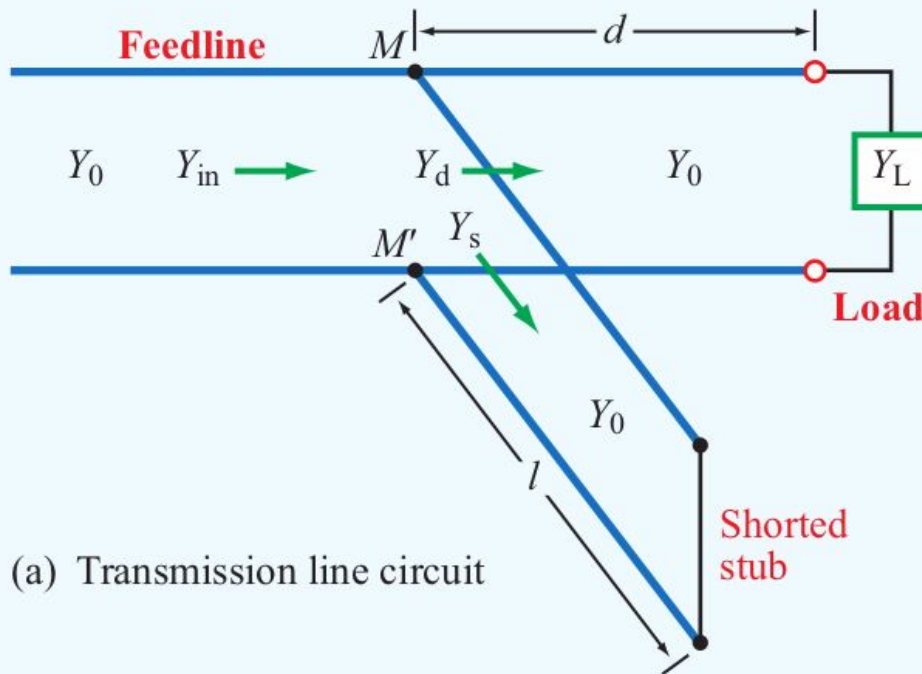

step2: ∞ admittance is real, all the way to the right.


Example 2-14 Single-Stub Matching

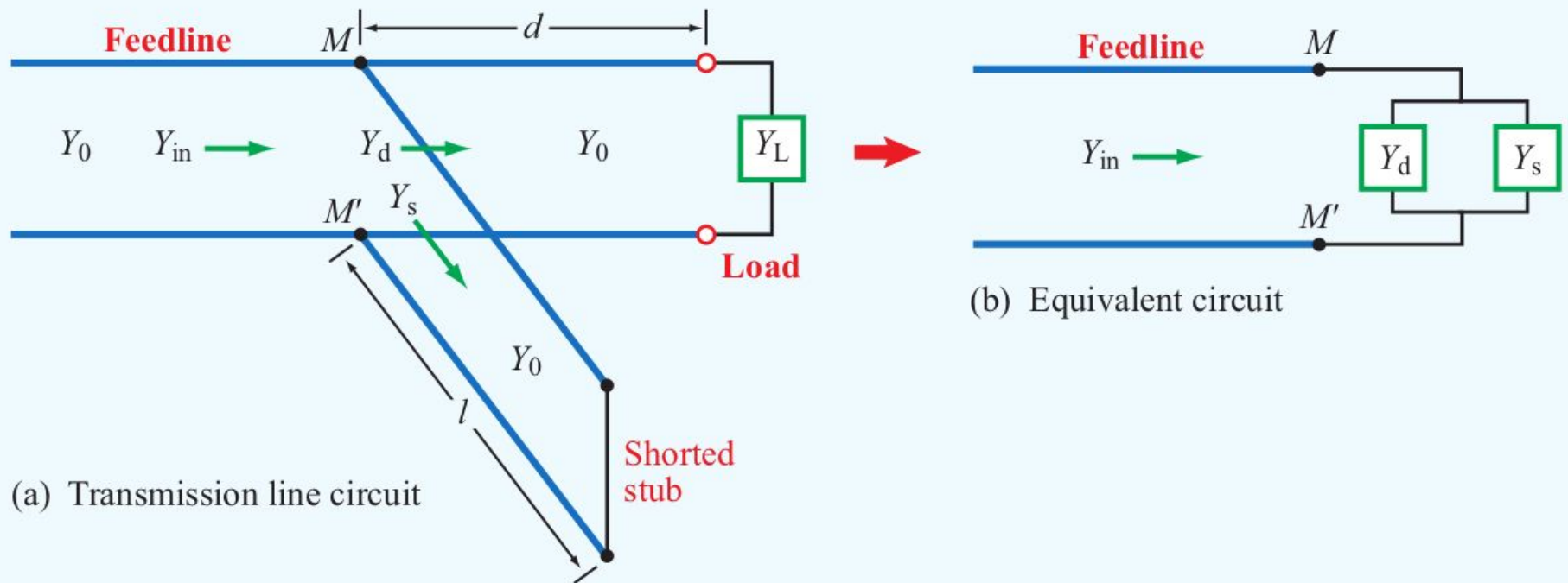


step3: find stub length: rotate toward generator until get desired admittance of $+j1.58$

step4: draw radial line to get WTG: 0.16λ

Example 2-14 Single-Stub Matching

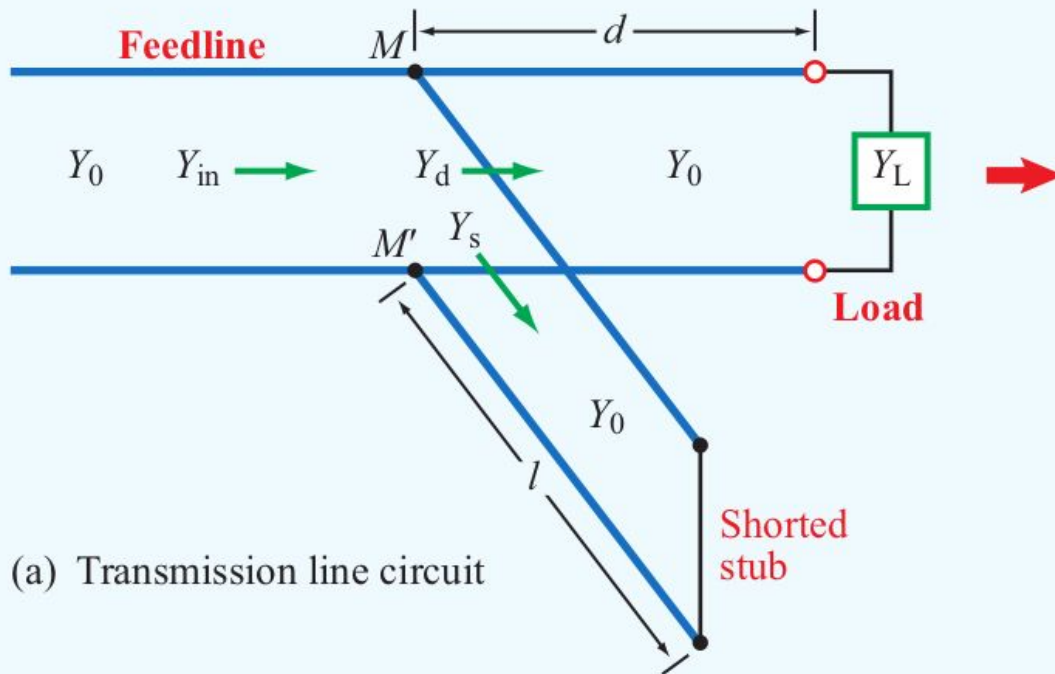

(a) Transmission line circuit

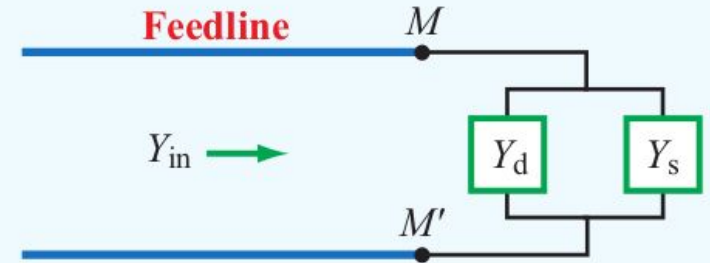


(b) Equivalent circuit

step5: find stub length: $0.16\lambda + 0.25\lambda = 0.41\lambda$

Done matching at point D.


Example 2-15 $\lambda/4$ Matching

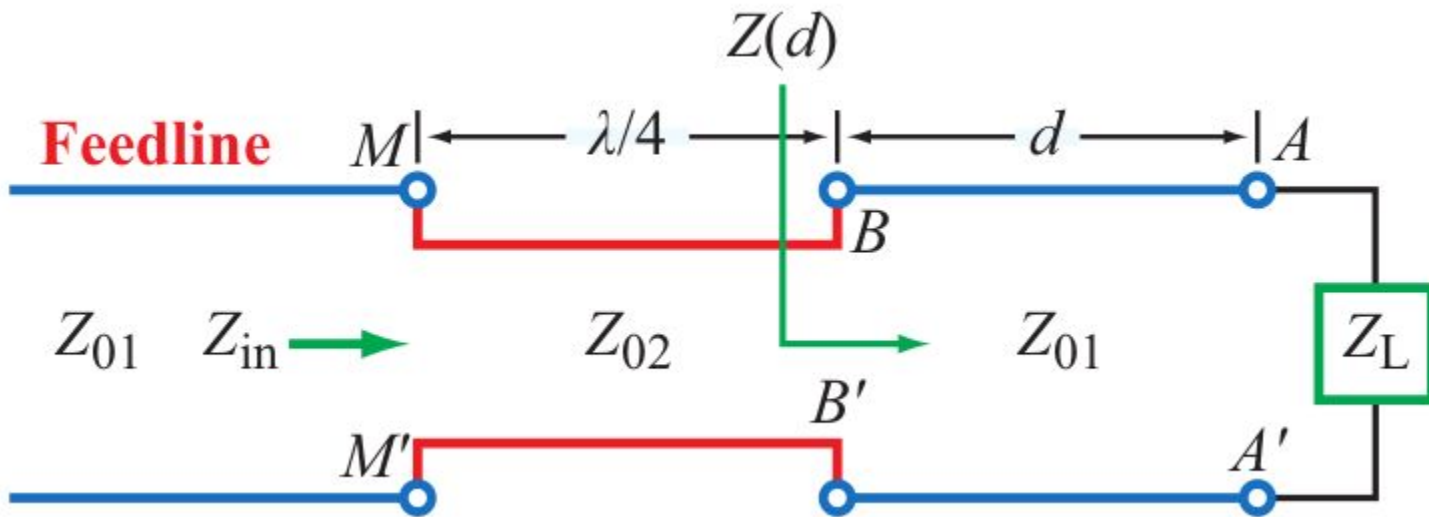

Given: A lossless transmission line with $Z_{01} = 50\Omega$
 $Z_L = 100 + j100 \Omega$

Find: distance, d , and characteristic impedance, Z_{02} , of a lossless $\lambda/4$ -line to match the load.

Example 2-15 $\lambda/4$ Matching

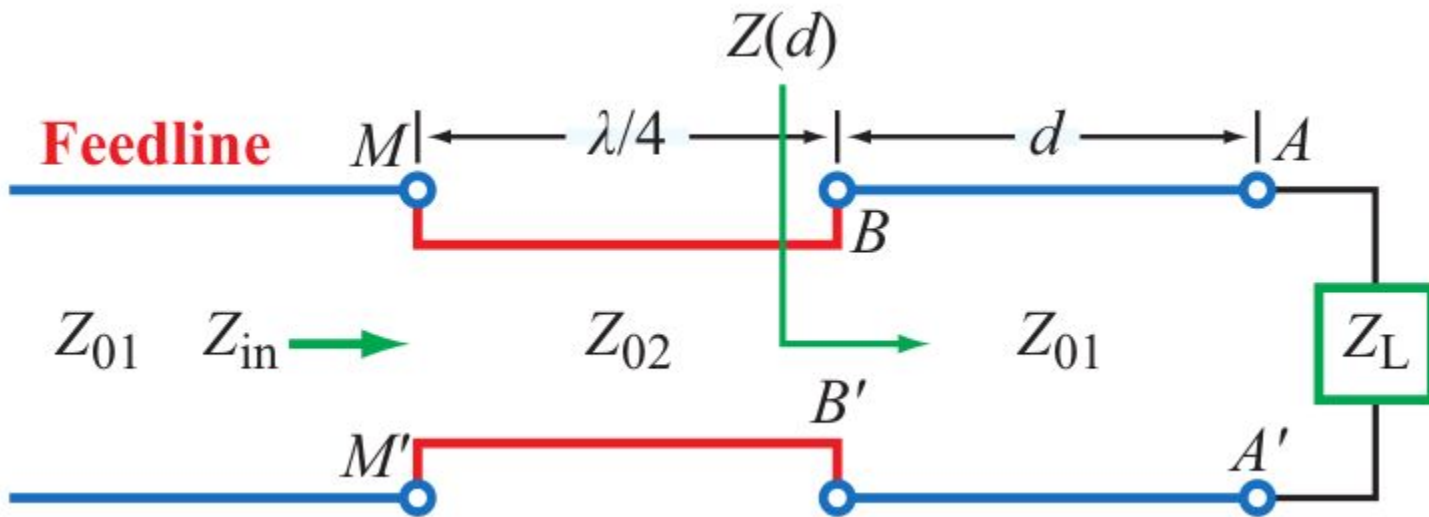

Solution: Recall that for a $\lambda/4$ -line:


$$Z_{in} Z(d) = (Z_{02})^2$$

in our case:

$$Z_{in} = 50 \Omega \quad (\text{for matching})$$


so $Z(d)$ must be real.

Example 2-15 $\lambda/4$ Matching

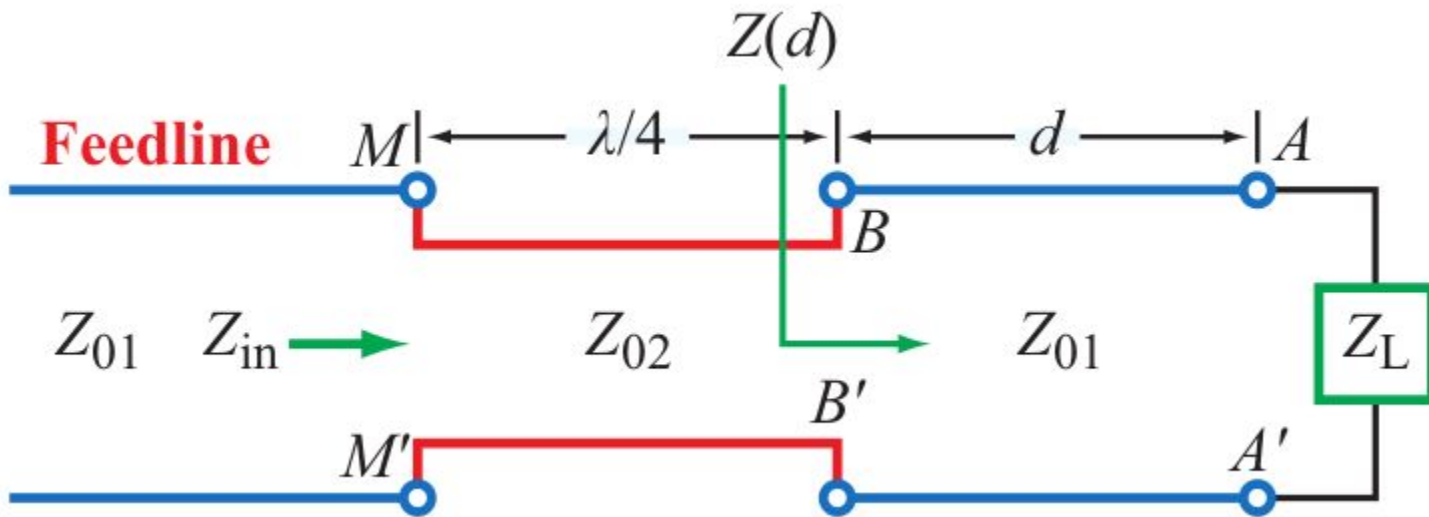

Process: 1. Figure out distance d to get $Z(d)$ real,
2. Use equation to get Z_{02} .

Example 2-15 $\lambda/4$ Matching

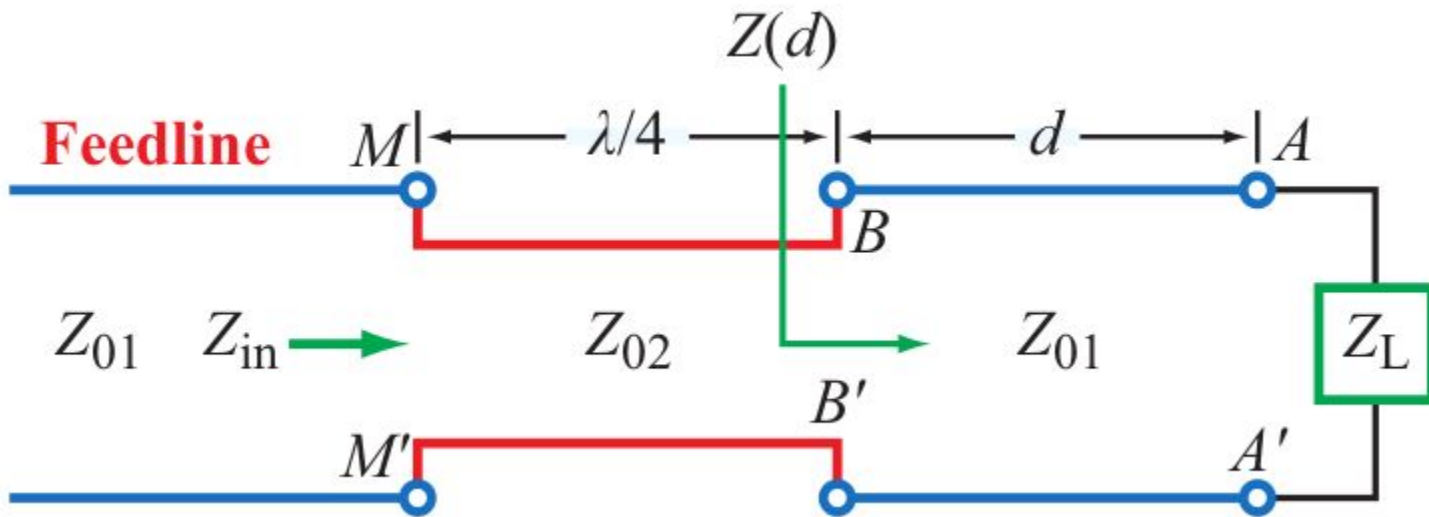


Solution:

step1: calculate z_L and plot on Smith Chart:


$$z_L = (100 + j100 \Omega) / 50 \Omega$$

$$z_L = 2 + j2$$

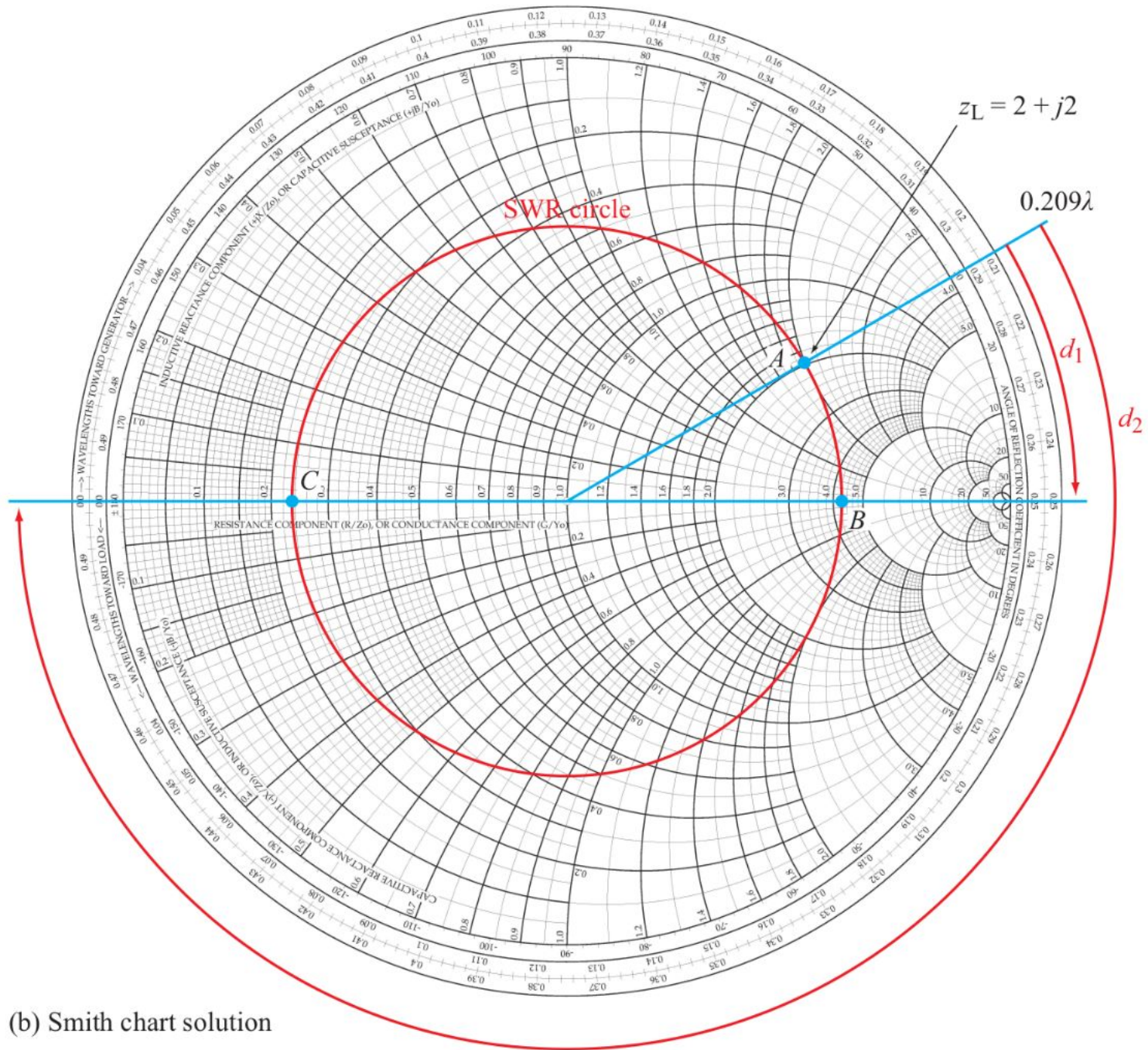

(b) Smith chart solution


Example 2-15 $\lambda/4$ Matching

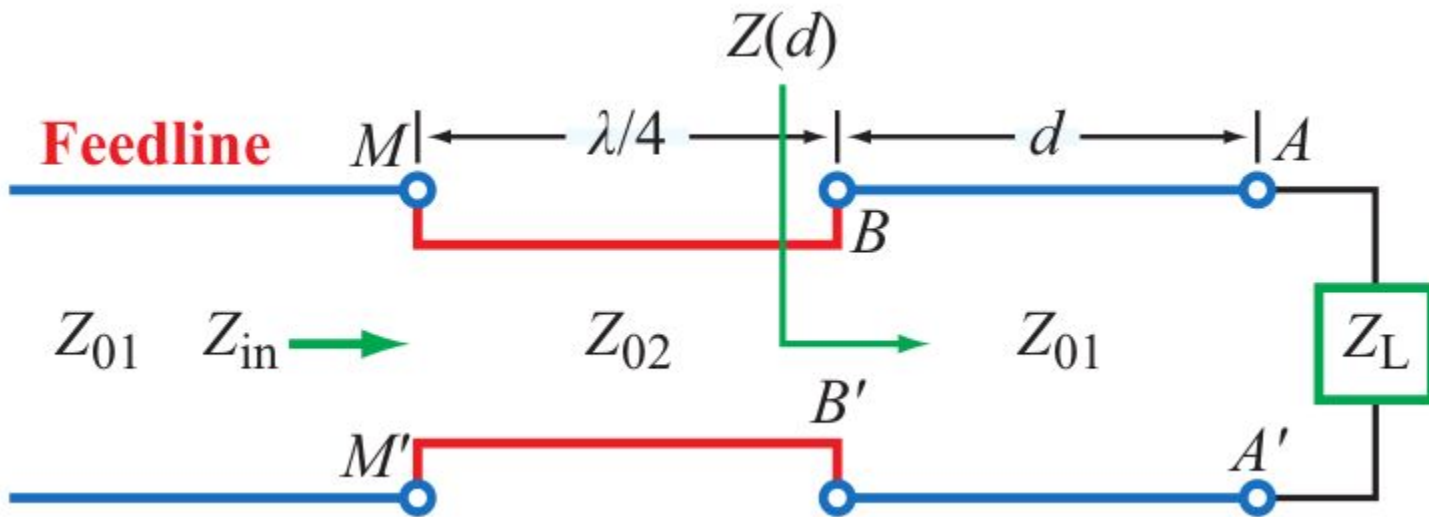

Solution:


step2: draw vswr circle through this point.

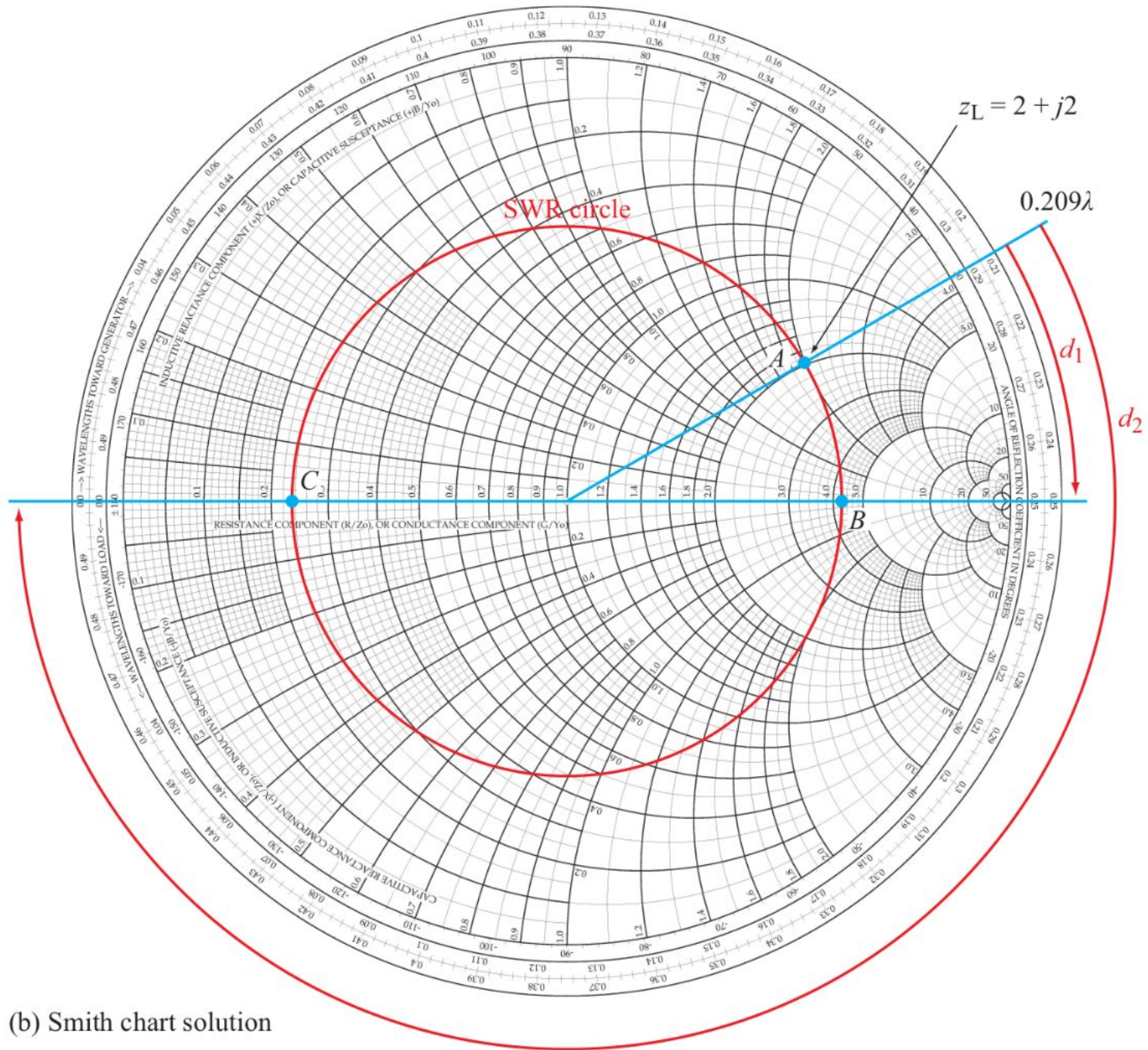step3: draw radial line, read off WTG: 0.209λ



(b) Smith chart solution


Example 2-15 $\lambda/4$ Matching

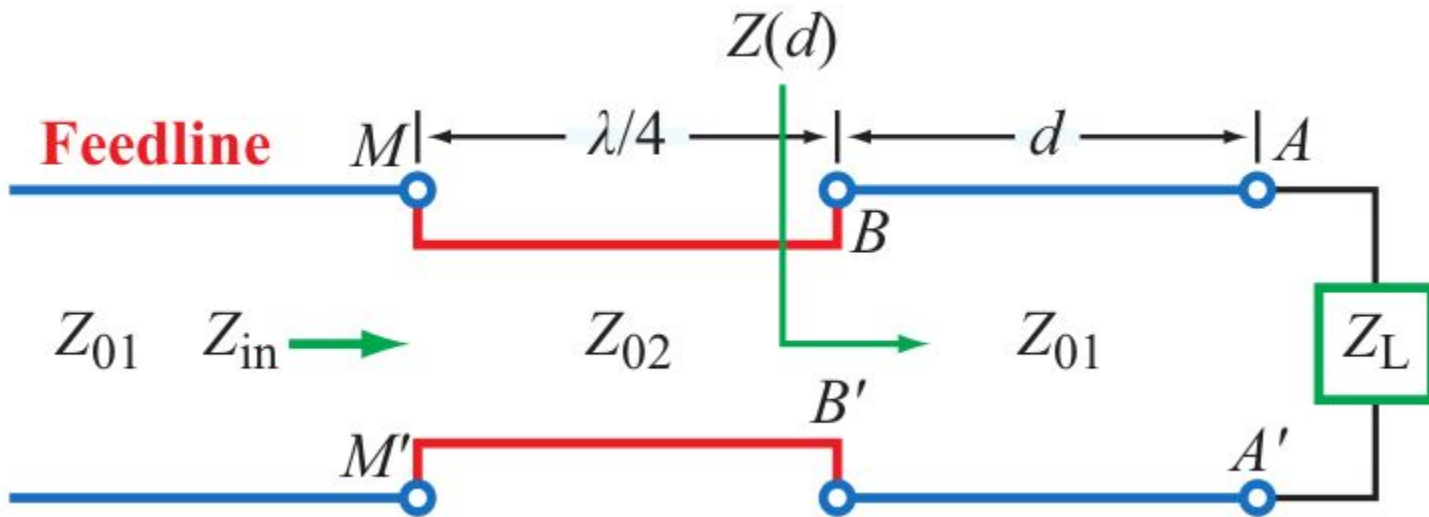

Solution:


step4: move towards generator until get a real impedance:

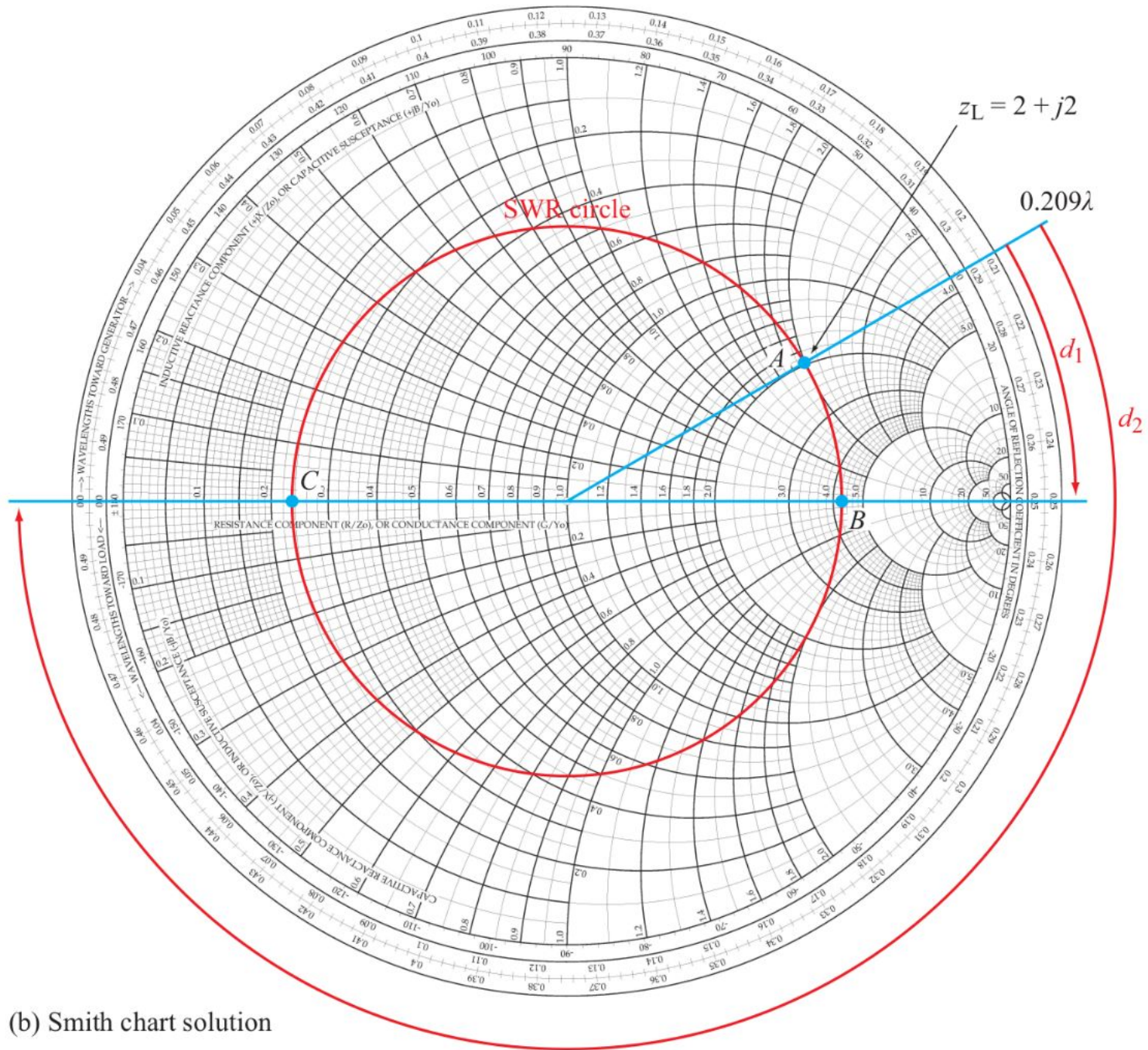1. first point is on positive real axis
2. second point is on negative real axis



(b) Smith chart solution

Example 2-15 $\lambda/4$ Matching

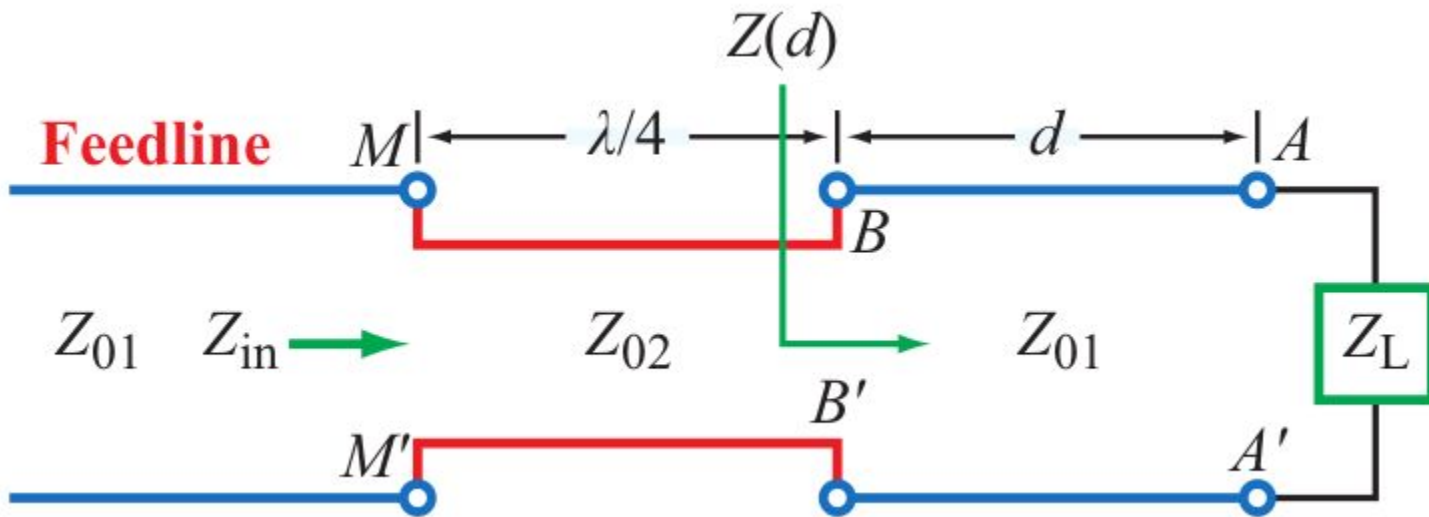

Solution:


step5: For first point:

$$d = 0.25\lambda - 0.209\lambda$$

so: $d = 0.041\lambda$

step6: read off $z(d) = 4.27$


Example 2-15 $\lambda/4$ Matching

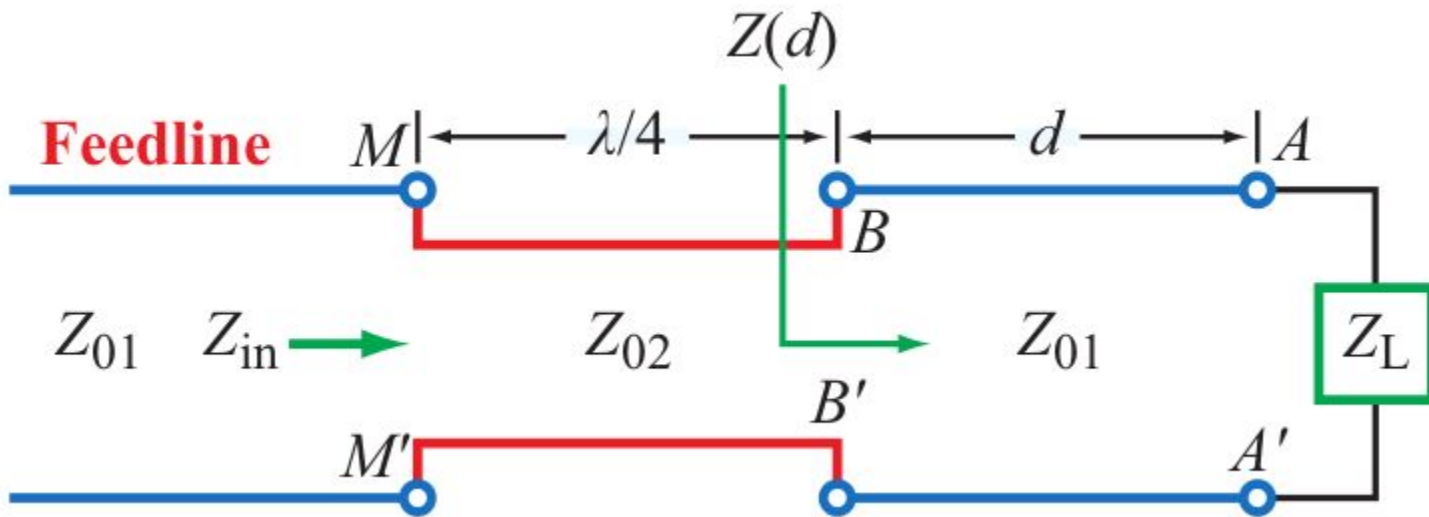

Solution:

$$\text{step 7: } Z(d) = Z_0 z(d) = (50 \Omega) 4.27 = 213.5 \Omega$$

Example 2-15 $\lambda/4$ Matching

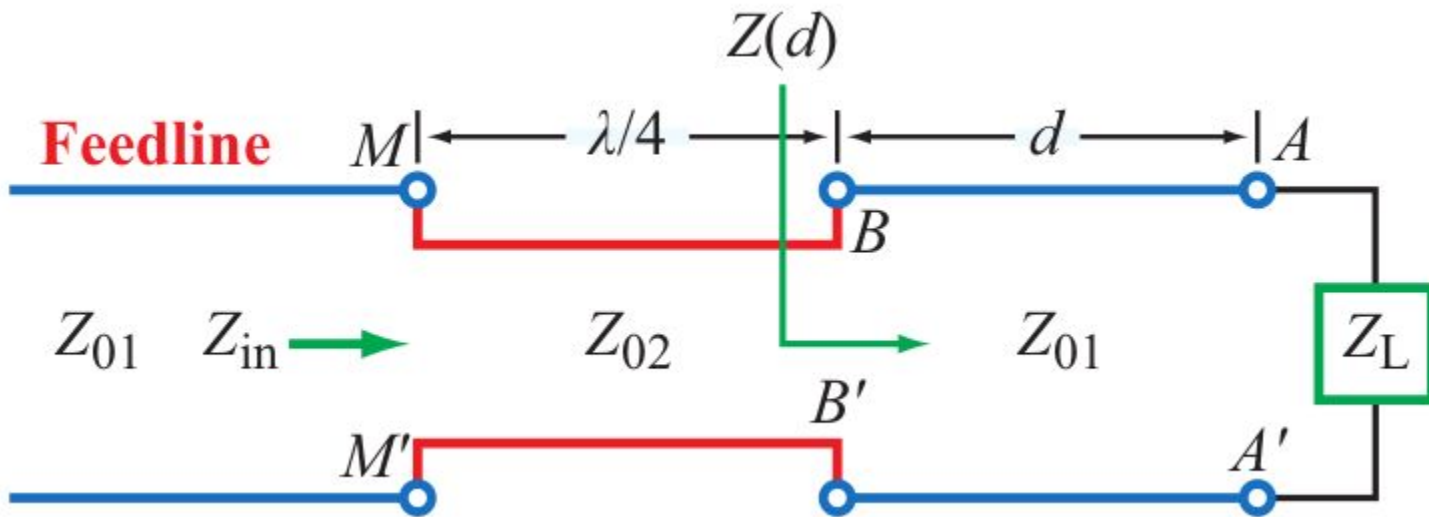


Solution:

step 8: calculate Z_{02} : $Z_{02} = \sqrt{Z(d)Z_{01}}$

$$Z_{02} = \sqrt{(213.5 \Omega)(50 \Omega)}$$

$$Z_{02} = 103.3 \Omega$$

Example 2-15 $\lambda/4$ Matching

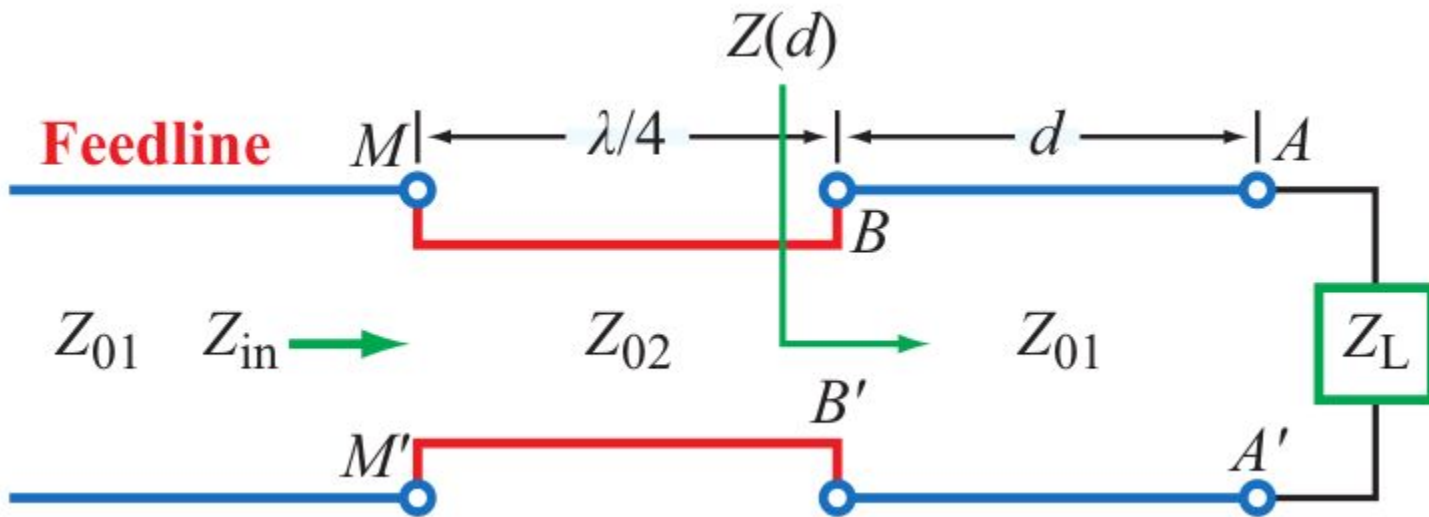


Solution:

step5: For second point:


$$d = 0.25\lambda + (0.25\lambda - 0.209\lambda) \quad \text{so: } d = 0.291\lambda$$

step6: read off $z(d) = 0.23$

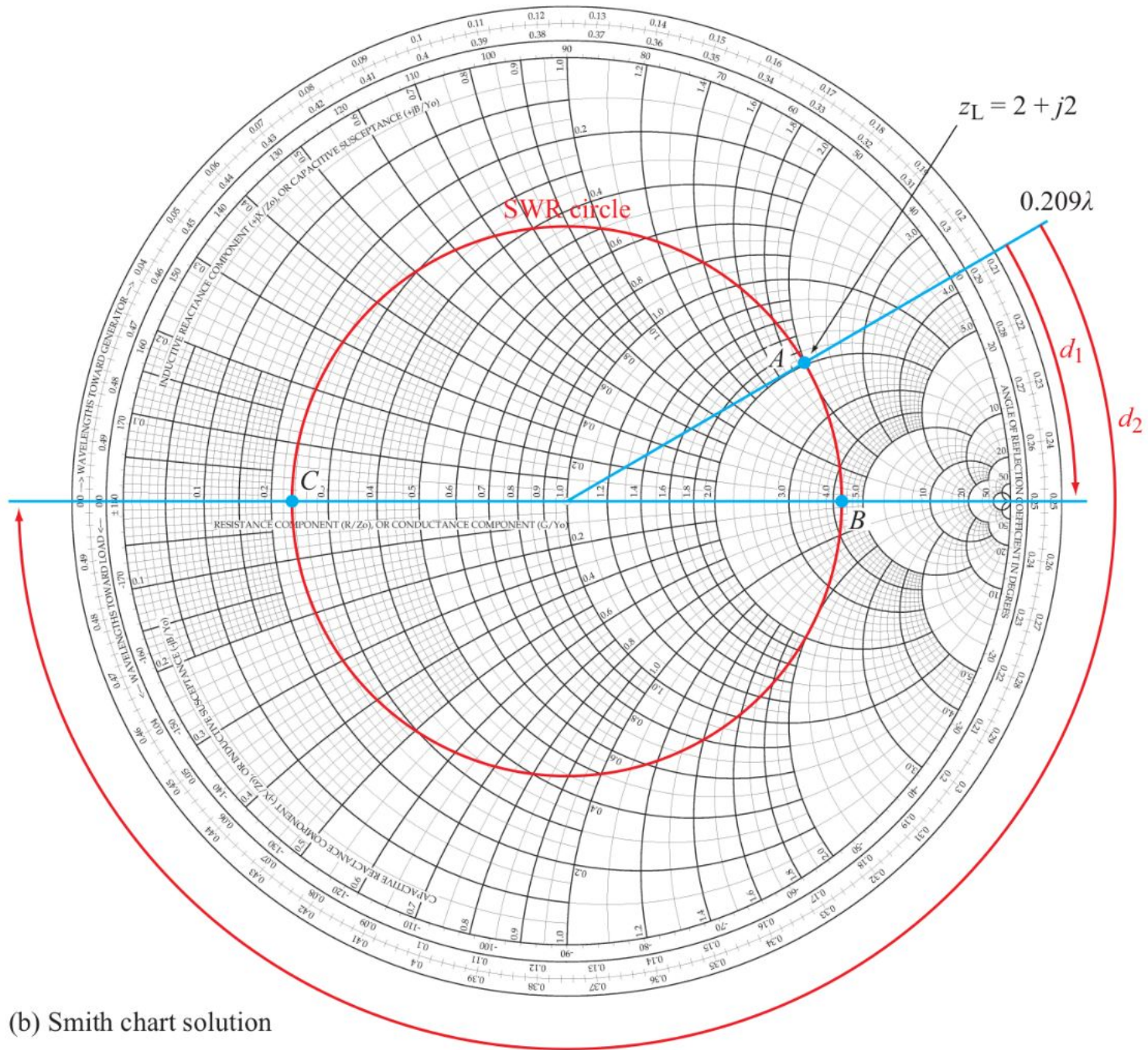

(b) Smith chart solution


Example 2-15 $\lambda/4$ Matching

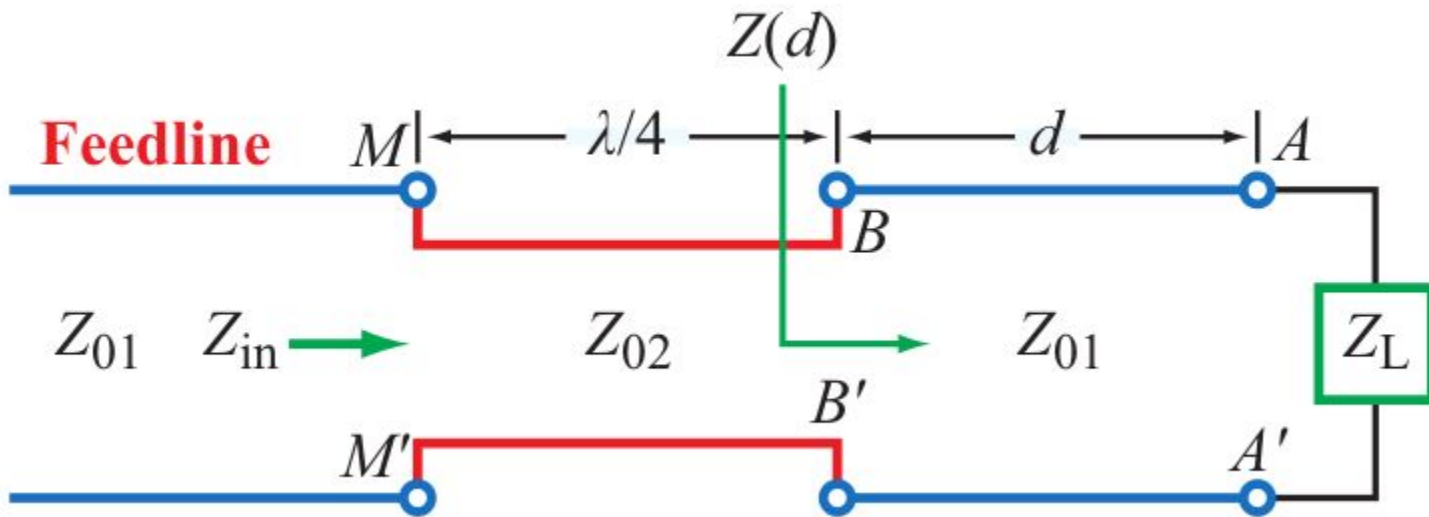

Solution:

$$\text{step 7: } Z(d) = Z_0 z(d) = (50 \Omega) 0.23 = 11.5 \Omega$$

Example 2-15 $\lambda/4$ Matching

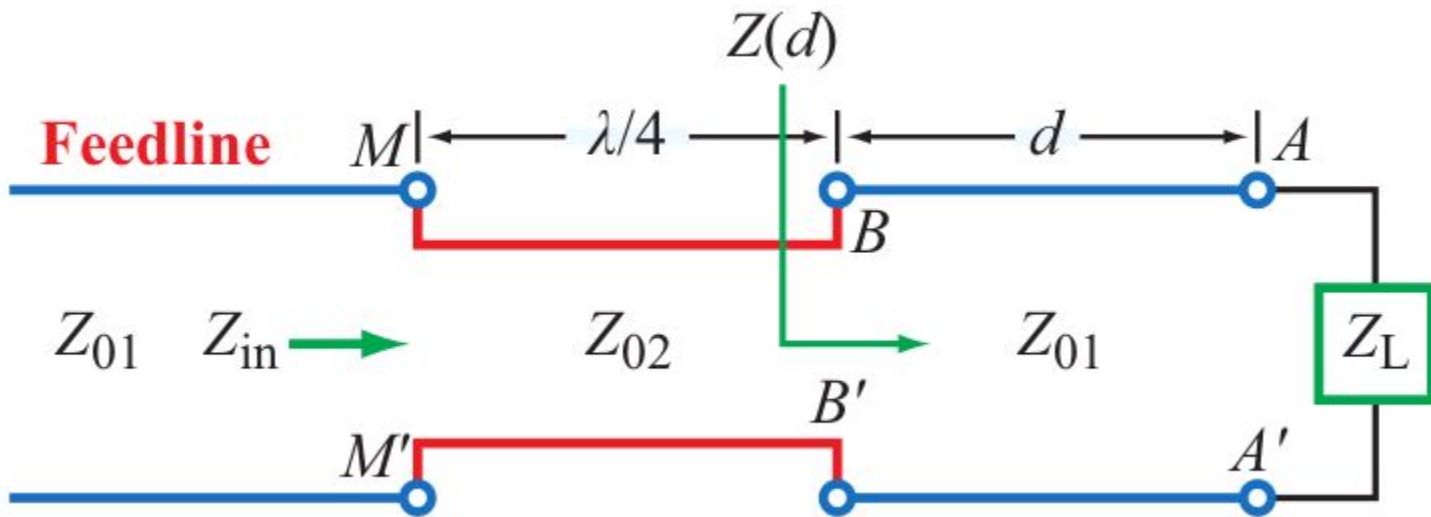

Solution:

step 8: calculate Z_{02} : $Z_{02} = \sqrt{Z(d) Z_{01}}$

$$Z_{02} = \sqrt{(11.5 \Omega) (50 \Omega)}$$

$$Z_{02} = 24.2 \Omega$$

Homework

109

Homework 9 is due tomorrow at midnight.

submit to gradescope via the canvas site.

Next Time



Sections 2-11, 2-12:

The Smith Chart: Impedance Matching

Transients on Transmission Lines